 


Chapter 11. Arithmetic Building Blocks


A Generic Digital Processor



Building Blocks for Digital Architectures


- ❑ **Arithmetic unit**
 - ✓ Bit-sliced datapath (adder, multiplier, shifter, comparator, etc.)
- ❑ **Memory**
 - ✓ RAM, ROM, Buffers, Shift registers
- ❑ **Control**
 - ✓ Finite state machine (PLA, random logic.)
 - ✓ Counters
- ❑ **Interconnect**
 - ✓ Switches
 - ✓ Arbiters
 - ✓ Bus

Bit-Sliced Design

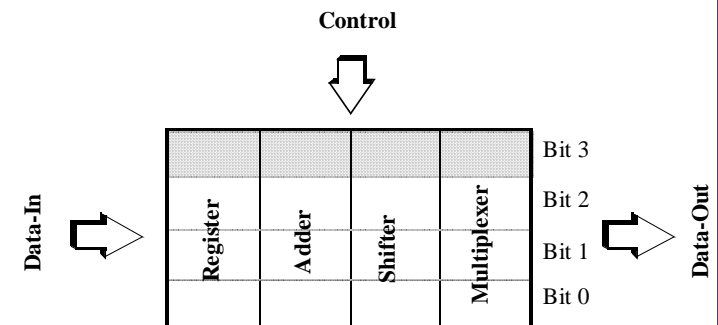


Full-Adder

 - Addition: most commonly used arithmetic operation, also speed-limiting element.



A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 

$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

Express Sum and Carry as a function of P, G, D

- Define 3 new variable which only depend on A, B:
- ✓ $G=1$ ($D=1$) ensures that a carry bit will be generated (deleted) at C_o independent of C_i .
- ✓ $P=1$ ensures that an incoming carry will propagate to C_o .

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$

$$\text{Delete} = \bar{A} \bar{B}$$


- ✓ Sometimes P is also taken as $P=A+B$
- S and C_o can be rewritten as functions of P and G (or D):

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

The Ripple-Carry Adder

- N-bit ripple-carry adder: cascading N full-adder circuits in series, connecting $C_{o,k-1}$ to $C_{i,k}$ ($k=1 \sim N-1$), and set $C_{i,0}=0$.
- Carry-bit “ripples” from one stage to the other
- Delay depends on input patterns: some input patterns has no rippling effect at all, while for others the carry has to ripple all the way from LSB to MSB (worst-case delay).
- Worst-case delay: $t_{\text{adder}} \approx (N-1)t_{\text{carry}} + t_{\text{sum}}$ where t_{carry} and t_{sum} : propagation delays from C_i to C_o and S.
- Goal: make the fastest possible carry path circuit

 


N-bit Ripple Carry Adder

Worst case delay linear with the number of bits: $t_d = O(N)$

The Ripple-Carry Adder

 - Propagation delay of ripple-carry adder is linearly proportional to N.
- For a fast ripple-carry adder, it's far more important to optimize t_{carry} than t_{sum} , since the latter has only a minor influence on the total value of t_{adder} .




Inversion Property

- Inversion property of full adder: inverting all inputs to a full adder results in inverted values for all outputs.

$$\overline{S}(A, B, C_i) = S(\overline{A}, \overline{B}, \overline{C_i})$$


$$\overline{C_o}(A, B, C_i) = C_o(\overline{A}, \overline{B}, \overline{C_i})$$

 - Inversion property is useful for optimizing speed of ripple-carry adder
- The following two circuits are identical



Complimentary Static CMOS Full Adder

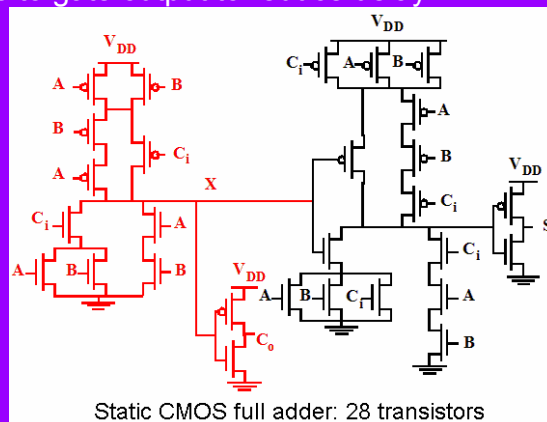- Static CMOS full adder is implemented as below :
 $C_o = AB + BC_i + AC_i$ $S = ABC_i + \overline{C_o}(A + B + C_i)$
- Design tricks: C_i are placed as close as possible to output → transistors on critical path should be placed as close as possible to gate output to reduce delay.




Complimentary Static CMOS Full Adder

- Static CMOS full adder has large area with slow speed
- ✓ Long chains of series PMOS in carry and sum circuits
- ✓ load capacitance of C_o is large (consists of 2 diffusion and 6 gate capacitances plus wiring capacitance) (C_o connects to C_i of next stage which takes 6 C_i inputs)
- ✓ carry circuit requires 2 inverting stages per bit (! C_o plus inverter to get C_o)


Minimize Critical Path by Reducing Inverting Stages

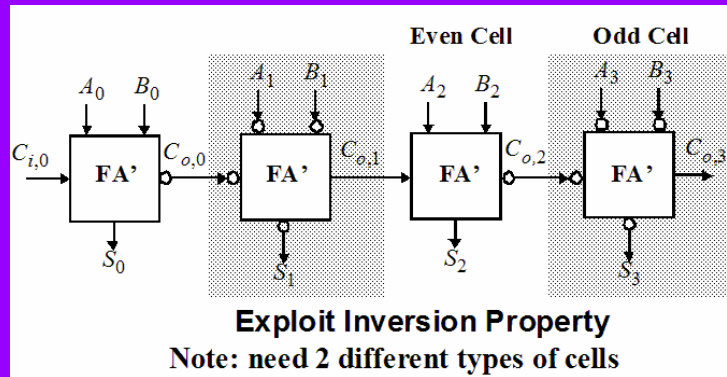- By cascading CMOS full adder and its inversion equivalent alternately, the extra inverters in carry path to get C_o from $\overline{!}C_o$ can be eliminated \rightarrow worst case delay of adder is reduced.



The Better Structure: Mirror Adder

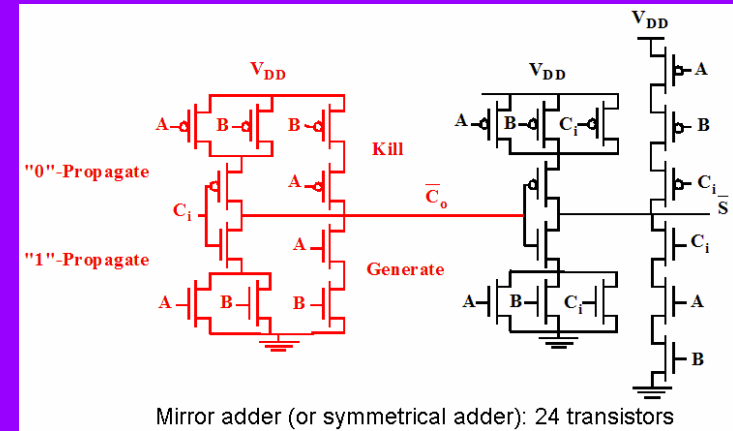- Mirror adder: utilize propagate/generate/delete functions
- $G=AB$, $D=\overline{A} \overline{B}$, $P=A+B$
- When $D=1$ or $G=1$, $\overline{C}_o=1$ or 0.
- When $P=1$, C_i is propagated (in inverted format) to \overline{C}_o .




The Mirror Adder


- The NMOS and PMOS chains are completely symmetrical. This guarantees identical rising and falling transitions if the NMOS and PMOS devices are properly sized. A maximum of two series transistors can be observed in the carry-generation circuitry.
- When laying out the cell, the most critical issue is the minimization of the capacitance at node C_o . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node C_o is composed of four diffusion capacitances, two internal gate capacitances, and six gate capacitances in the connecting adder cell.
- Transistors connected to C_i are placed closest to output.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be minimal size.

Quasi-Clocked Adder

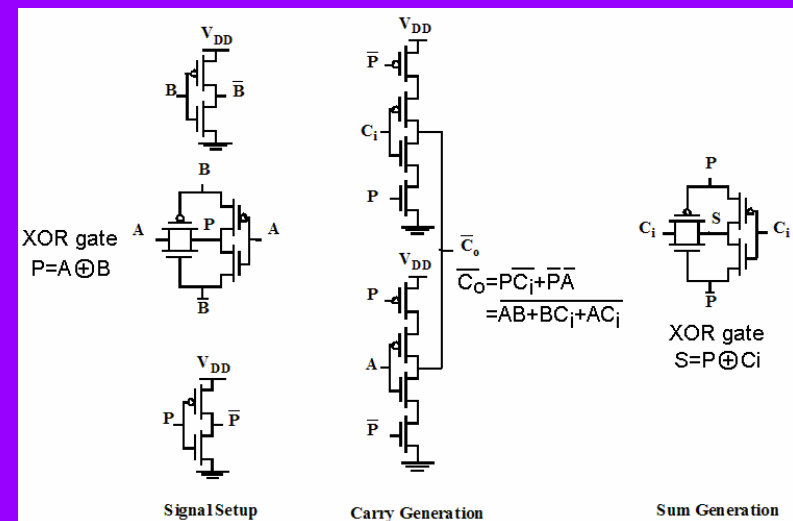- Transmission-gate (TG) based quasi-clocked adder circuit




NMOS-Only Pass Transistor Logic

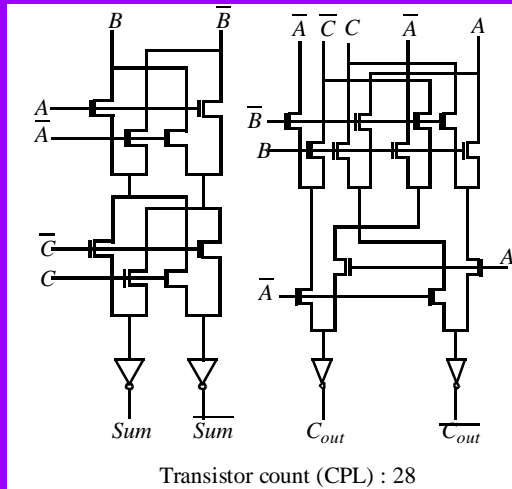


CPL Full Adder

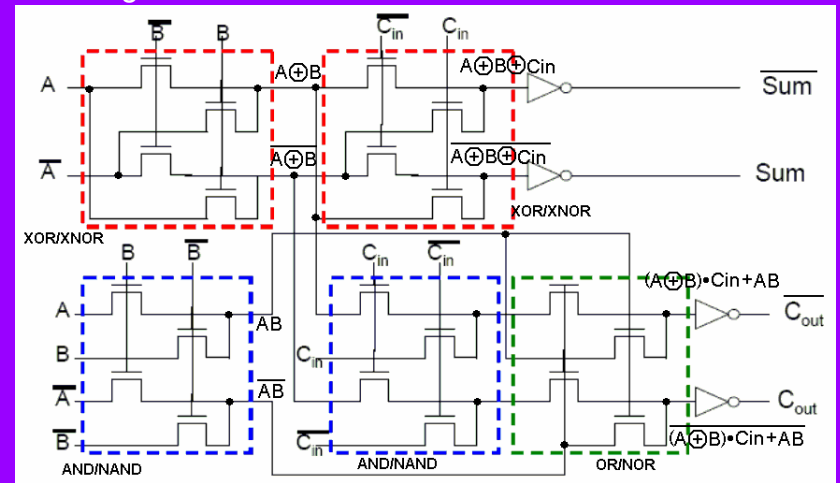- 20+4×2=28 transistors
- Problems with (more than one) threshold drops due to chaining CPL blocks




NP-CMOS Adder

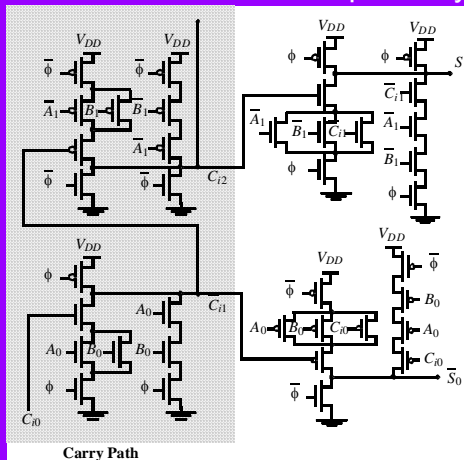- Dynamic np-CMOS adder: only 17 transistors ignoring extra inverters required for input/output signals
- The alternating even and odd carry stages are realized using NMOS and PMOS networks respectively



NP-CMOS Adder

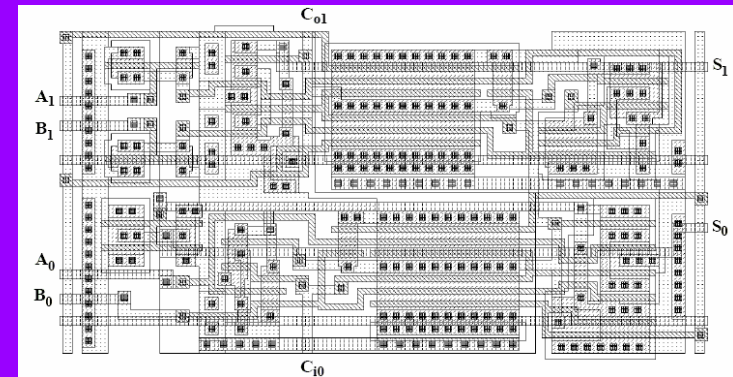
- Reduced capacitance of dynamic circuits results in substantial speed-up over static implementation
- Load capacitance on carry bit includes 3 diffusion and 4 gate capacitances.



Layout of np-CMOS full adder


Manchester Carry Chain

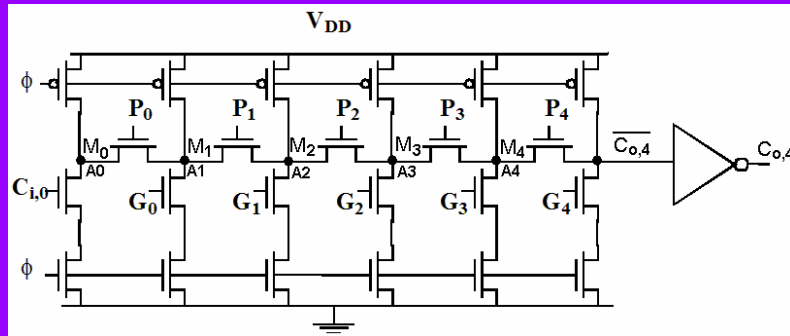- Manchester carry-chain adder: uses a cascade of pass-transistors to implement carry chain.
- In precharge phase ($\Phi=0$), all intermediate nodes $A_0 \sim A_4$ of pass-transistor chain are precharged to "1".
- In evaluation phase ($\Phi=1$), M_k node is discharged to 0 when incoming carry=1 and propagate signal $P_k=1$, or when generate signal for stage k (G_k) is 1.




Sizing Manchester Carry Chain

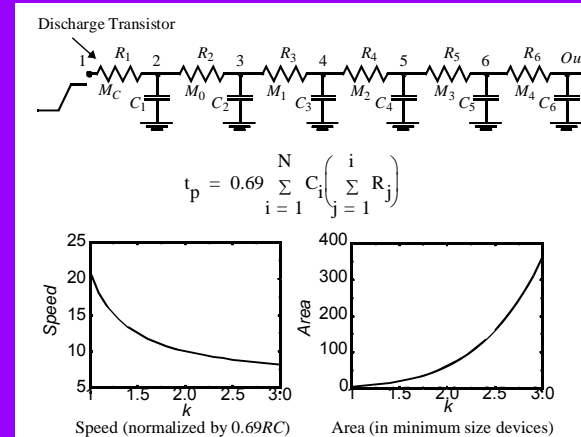- Carry-chain is a distributed RC-network $\rightarrow t_d = O(N^2)$
- Reducing delay of carry-chain:
 - insert signal-buffering inverters with optimum stages/sizing
 - Sizing transistors progressively ($I_{M_0} > I_{M_1} > \dots > I_{M_4}$, thus size of M_4 to M_0 should be increased progressively.)



Carry-Bypass Adder

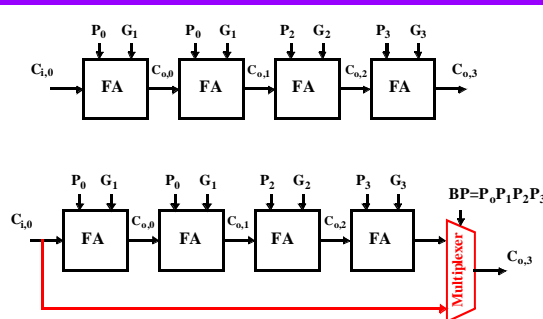
- For ripple-carry adder, if ($P_0 P_1 P_2 P_3 = 1$) then $C_{0,3} = C_{i,0}$ else either DELETE or GENERATE occurred.
- Thus if ($P_0 P_1 P_2 P_3 = 1$), we can directly bypass carry-in $C_{i,0}$ to $C_{0,3}$ to reduce the delay caused by carry propagation. \rightarrow carry-bypass adder.



Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$) then $C_{0,3} = C_0$, else "kill" or "generate".

Manchester-Carry Implementation

 - Manchester-carry implementation: either carry propagates through bypass path, or carry is generated somewhere in the chain
- In both cases, delay is smaller than normal ripple configuration.
- Area overhead due to adding bypass path: 10~20%.




Delay of Carry-Bypass Adder

- Assume total adder is divided in (N/M) equal by-pass stages, each contains M bits. Total propagation time

$$t_p \approx t_{\text{setup}} + Mt_{\text{carry}} + (N/M-1)t_{\text{bypass}} + Mt_{\text{carry}} + t_{\text{sum}}$$


- where: t_{setup} : fixed overhead time to create G and P signals,
- t_{carry} : propagation delay through a single bit. The worst-case carry-propagation delay through a single stage is Mt_{carry}
- t_{bypass} : propagation delay through bypass MUX of a single stage
- t_{sum} : time to generate sum of final stage.

- Carry-bypass adder delay $t_p = O(N)$

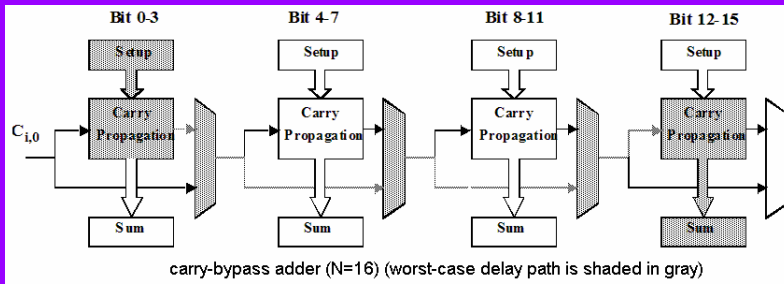


Carry Ripple versus Carry Bypass

 - Propagation delay of carry ripple adder vs carry-bypass adder
- ✓ Difference is substantial for larger adders (large N)
- ✓ Ripple carry adder is actually faster for smaller N
- ✓ Overhead of extra bypass MUX makes bypass structure not interesting for small N
- ✓ Crossover point depends on technology considerations and is normally situated between 4 and 8 bits



Linear Carry-Select Adder

- Ripple carry adder: every full adder cell waits for incoming carry before outgoing carry can be generated
- To avoid the waiting, anticipate both possible values (0 and 1) of carry input and evaluate result for both cases in advance
- Once the real value of incoming carry is known, the correct output is selected with a simple MUX \rightarrow carry-select adder
- Hardware overhead: 30% (due to additional carry path and a MUX)

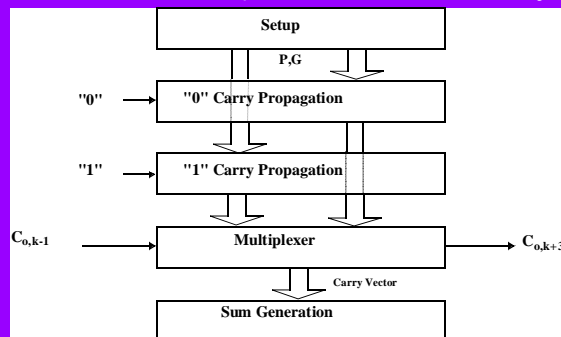


Carry Select Adder: Critical Path

- Assume total adder is divided in (N/M) equal by-pass stages, each contains M bits. Total propagation time


$$t_{\text{add}} = t_{\text{setup}} + Mt_{\text{carry}} + (N/M)t_{\text{mux}} + t_{\text{sum}}$$

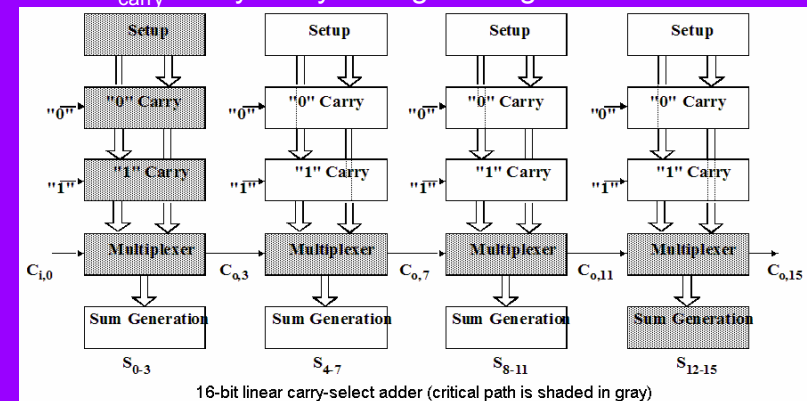- where t_{carry} : carry delay through a single bit,
- Mt_{carry} : carry delay through a single block




Linear Carry Select

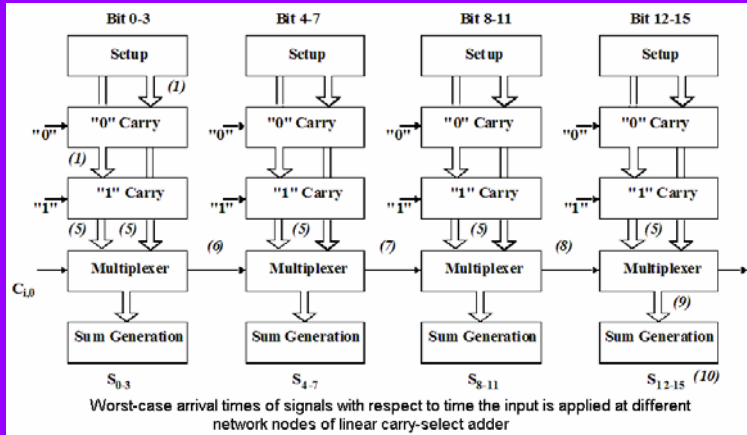- Assume full-adder and MUX cells have 1 unit delay each
- A major mismatch between the signal arrival times is observed in the MUX gate of last adder stage
- Total delay can be reduced if we equalize the delay through both inputs of the MUX gate → square-root carry select adder




Square Root Carry Select

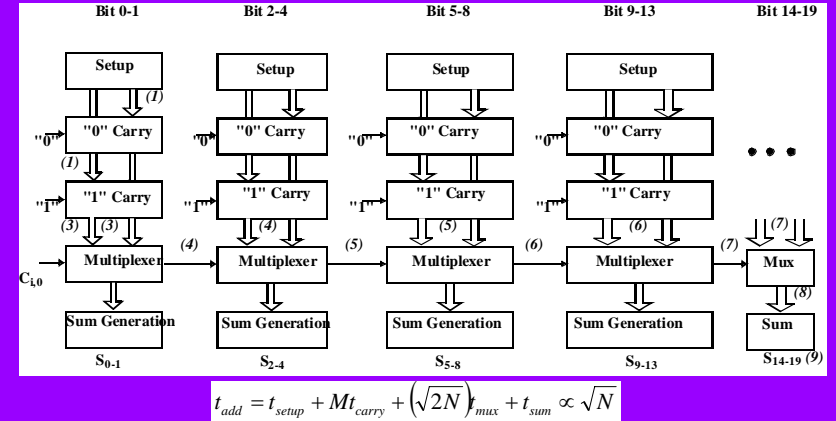- To equalize the inputs to MUX gates of all stages: progressively adding more bits to subsequent stages in the adder, requiring more time for the generation of carry signals
- E.g. 1st stage add 2 bits, 2nd stage add 3 bits, 3rd stage add 4 bits, etc.




Adder Delays - Comparison

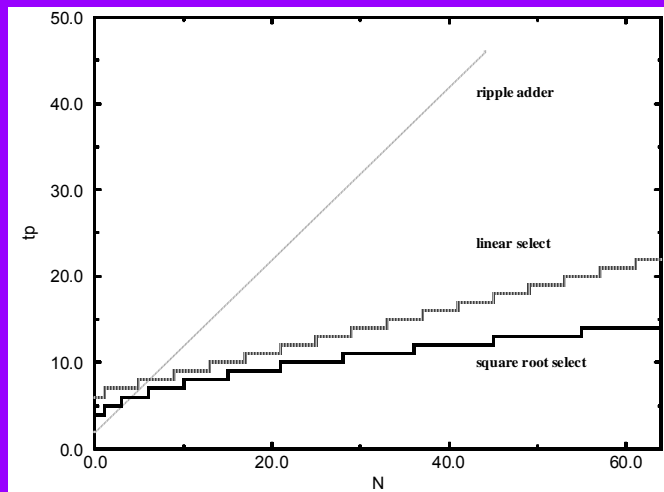


Carry-Lookahead Adder - Basic Idea

- Carry-lookahead adder: avoid rippling effect of carry in both carry-bypass and carry-select adders
- For each bit position in an N-bit adder:
 - $C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$
 - Dependency between $C_{o,k}$, $C_{o,k-1}$ can be avoided by expanding $C_{o,k-1}$: $C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$
 - Finally: $C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_0 + P_0C_{i,0})))$ ($C_{i,0} = 0$)
- For every bit, carry and sum outputs are independent of previous bit. The ripple effect has been eliminated. → addition time should be independent of N.

 


Carry Lookahead Adder: Topology

 - ❑ Example carry lookahead adder for N=4
- ✓ It contains some hidden dependencies
- ✓ Large fan-in makes it prohibitively slow for large N




Logarithmic Look-Ahead Adder

- ❑ Consider a generic associative operator – dot operation (\bullet)
- ✓ associativity property: $(a \bullet b) \bullet c = a \bullet (b \bullet c)$
- ✓ Dot operation of N arguments can be executed with critical path of $(\log_2 N)t$. (t : propagation delay of dot operation)
- ❑ Ex: For N=8, both designs have same number of operators.
- ✓ Linear (ripple) topology: critical path delay = $7t$.
- ✓ Logarithmic (tree-like fashion): critical path delay = $3t$.

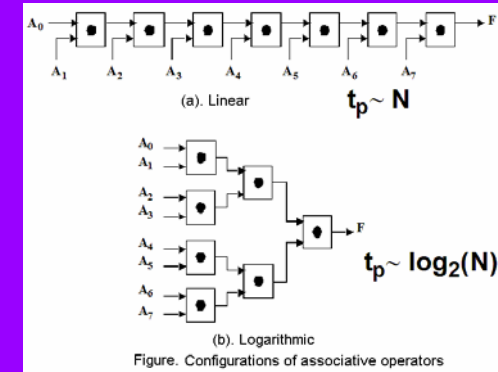

Logarithmic Lookahead Adder: Brent-Kung Adder

- ❑ Addition operation is associative

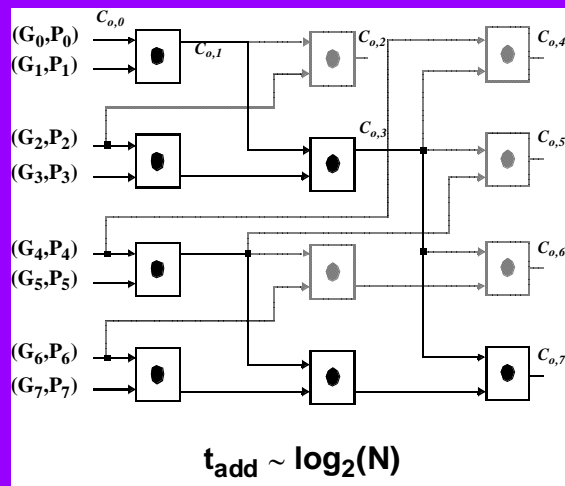


The Binary Multiplication

- ❑ Multiplication: expensive and slow operation
- ❑ Multipliers are in effect complex adder arrays
- ❑ Consider 2 unsigned binary numbers X(M bits) and Y(N bits)

$$\begin{aligned}
 Z = X \times Y &= \sum_{k=0}^{M+N-1} Z_k 2^k \\
 &= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) \quad \text{with} \quad X = \sum_{i=0}^{M-1} X_i 2^i \\
 &= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right) \quad Y = \sum_{j=0}^{N-1} Y_j 2^j
 \end{aligned}$$


The Binary Multiplication

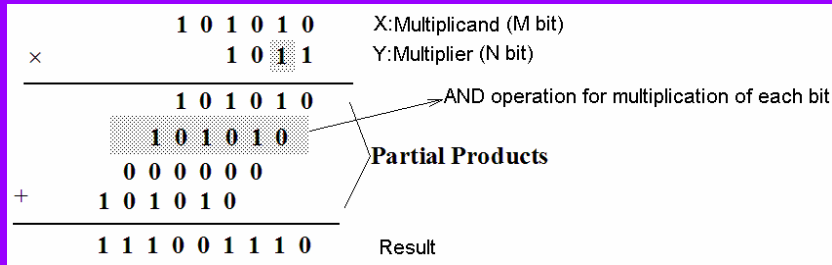- Common implementation of binary multiplier: similar to manually computing a multiplication
- Multiplicand is consecutively multiplied (AND operation) with every bit of multiplier → partial products
- Intermediate results are added after proper shifting



The Array Multiplier

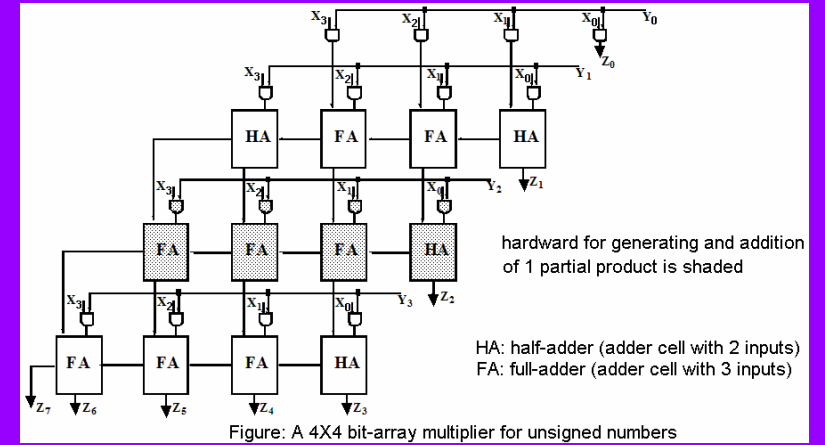- Array multiplier:
 - Generating N partial products needs N M-bit AND gates
 - Requires (N-1) M-bit adders to add N partial results
 - Shifting of partial results: simple routing (not active logic)
 - Can be compacted into a rectangle → efficient layout



The M×N Array Multiplier — Critical Path

- Propagation delay of M×N array multiplier
- Partial sum adders: ripple-carry structures
- There are many almost identical-length paths
- Propagation delay $t_{mult} \approx [(M-1)+(N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$
- t_{carry} : delay between C_{in} and C_{out}
- t_{sum} : delay between C_{in} and Sum of full adder
- t_{and} : delay of AND gate


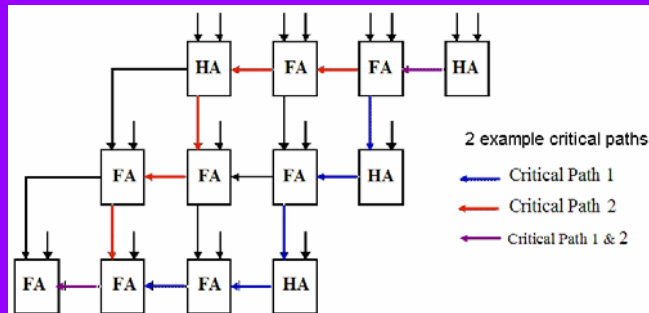


Figure: simplified ripple-carry based 4X4 multiplier

$$t_{mult} \approx [(M-1)+(N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$$

Adder Cells in Array Multiplier

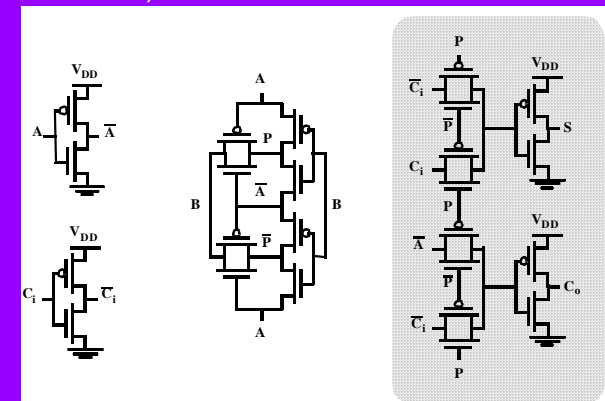
- Minimizing delay of array multiplier requires minimization of both t_{carry} and t_{sum} → It helps if $t_{carry} = t_{sum}$
- A full adder with comparable t_{sum} and t_{carry} delays using TG EXOR (24 transistors)



Identical Delays for Carry and Sum


Carry-Save Multiplier

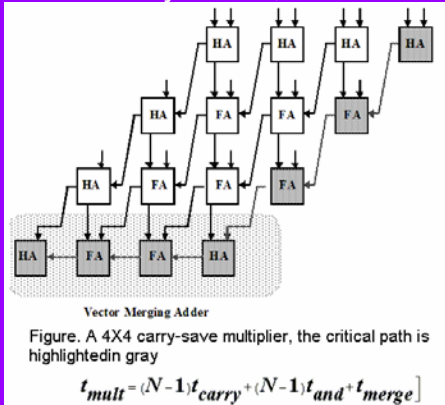- ❑ Carry-save multiplier: more efficient
- ✓ Fact: multiplication result does not change when output carry bits are passed diagonally downwards instead of to the right
- ✓ An extra M-bit full-adder is added (vector-merging adder) to generate final result
- ✓ carry bits are not immediately added, but are rather “saved” for next adder stage




Multiplier Floorplan

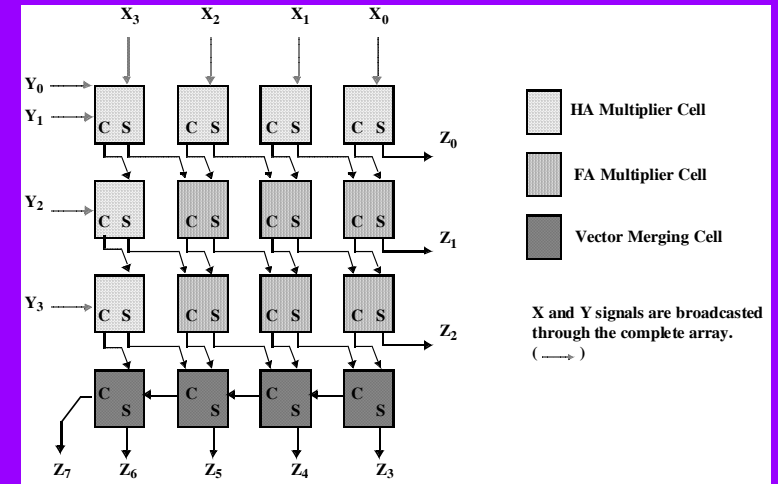- ❑ Rectangle floorplan of carry-save multiplier



Wallace-Tree Multiplier

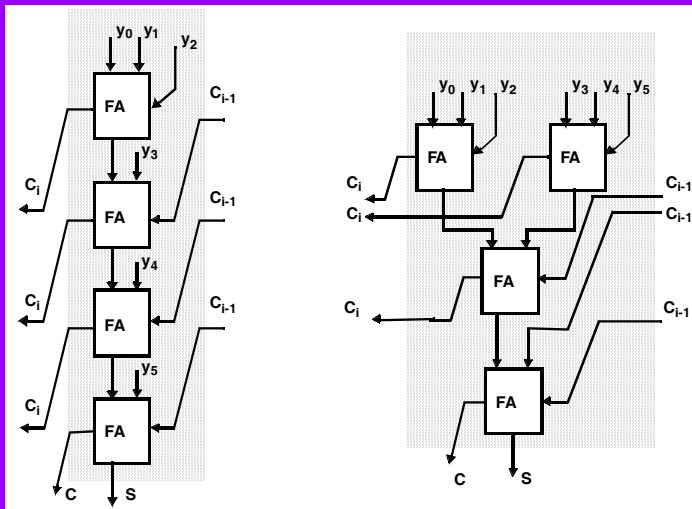


Multipliers —Summary


- ❑ Optimization goals different from binary adder
- ❑ Once again: identify critical path
- ❑ Other possible techniques
- ✓ Logarithmic versus linear (Wallace tree multiplier)
- ✓ Data encoding (Booth)
- ✓ Pipelining
- ❑ First Glimpse at System Level Optimization

The Binary Shifter

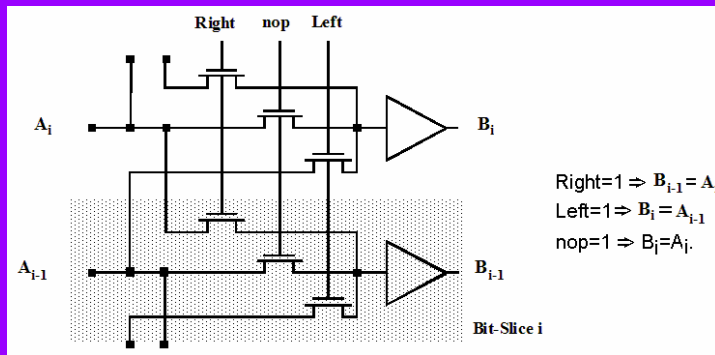- ❑ Shifter: used in floating-point units, scalars, multiplications by constant numbers.
- ❑ It can be implemented by appropriate signal wiring
- ❑ A 1-bit left-right shifter: depending on control signals, input word is either shifted left or right or remain unchanged.
- ❑ N-bit shifters can be built by cascading 1-bit shifters, but very slow for large N




The Barrel Shifter

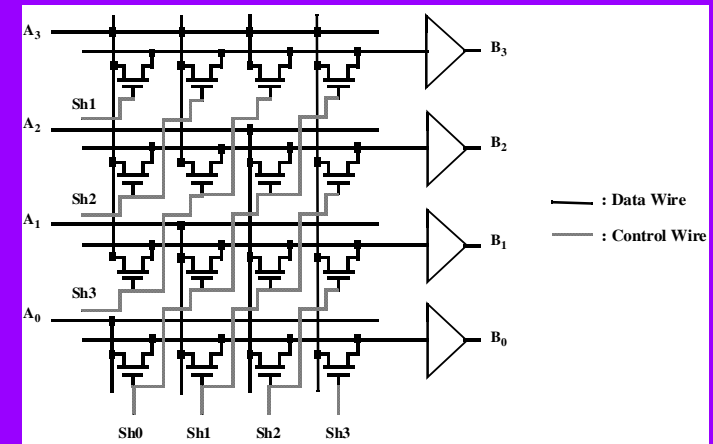


Area Dominated by Wiring

4x4 barrel shifter

 


$Width_{\text{barrel}} \sim 2 p_m M$

Logarithmic Shifter

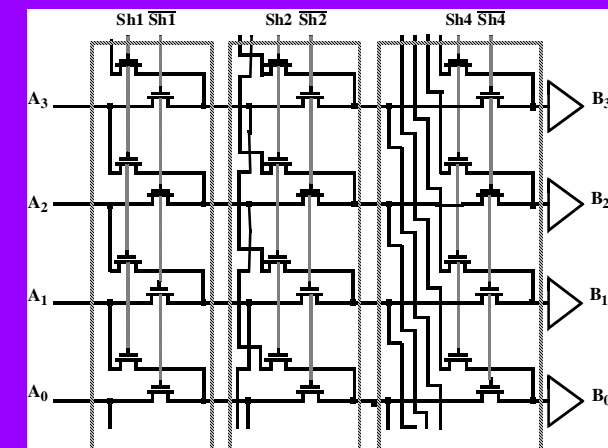


0-7 bit Logarithmic Shifter

 


$$width_{log} \approx p_m(2K + (1 + 2 + \dots + 2^{K-1})) = p_m(2^K + 2K - 1)$$


Design as a Trade-Off

 

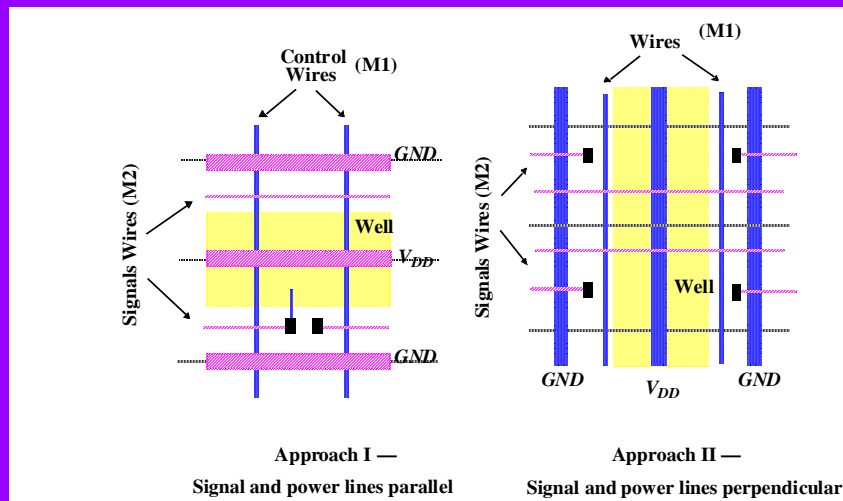Layout Strategies for Bit-Sliced Datapaths



Layout of Bit-sliced Datapaths

 

Layout of Bit-sliced Datapaths

(a) Datapath without feedthroughs and without pitch matching (area = 4.2 mm²).
(b) Adding feedthroughs (area = 3.2 mm²).
(c) Equalizing the cell height reduces the area to 2.2 mm².

