



DECIBEL

❖ *Power Levels*

The term *decibel* has its origin in the fact that power or voltage levels are related on a logarithmic basis. Amplifier gains are often not expressed as simple ratios. rather they are mapped into a logarithmic scale. For standardization, the bel (B) is defined by the following equation relating two power levels, P_1 and P_2 .

$$G = \log_{10} \frac{P_2}{P_1} \quad \text{bel}$$

It was found, however, that the bel was too large a unit of measurement for practical purposes, so the decibel (dB) is defined such that 10 decibels = 1 bel. Therefore,

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} \quad \text{dB}$$

and

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1} \quad \text{dB}$$

❖ *Cascaded Stages*

One of the advantages of the logarithmic relationship is the manner in which it can be applied to cascaded stages. For example, the magnitude of the overall voltage gain of a cascaded system is given by:

$$|A_{v_T}| = |A_{v_1}| \cdot |A_{v_2}| \cdot |A_{v_3}| \cdots |A_{v_n}|$$



Applying the proper logarithmic relationship results in

$$G_v = 20 \log_{10} |A_{v_T}| = 20 \log_{10} |A_{v_1}| + 20 \log_{10} |A_{v_2}| + 20 \log_{10} |A_{v_3}| + \cdots + 20 \log_{10} |A_{v_n}| \quad (\text{db})$$

In words, the equation states that the decibel gain of a cascaded system is simply the sum of the decibel gains of each stage, that is,

$$G_{\text{dB}_T} = G_{\text{dB}_1} + G_{\text{dB}_2} + G_{\text{dB}_3} + \cdots + G_{\text{dB}_n} \quad \text{dB}$$

EXAMPLE : Find the magnitude gain corresponding to a voltage gain of 100 dB.

Solution:

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1} = 100 \text{ dB} \Rightarrow \log_{10} \frac{V_2}{V_1} = 5$$

So that

$$\frac{V_2}{V_1} = 10^5 = 100,000$$

H.W The input power to a device is 10,000 W at a voltage of 1000 V. The output power is 500 W and the output impedance is 20 Ω .

- Find the power gain in decibels.
- Find the voltage gain in decibels.



GENERAL FREQUENCY CONSIDERATIONS

❖ *Typical Frequency Response*

The magnitudes of the gain response curves of an RC-coupled and direct-coupled, amplifier system are provided in Fig. 1. Note that the horizontal scale is a logarithmic scale to permit a plot extending from the low to the high frequency regions. For each plot, a low, a high, and a mid-frequency region have been defined. For the RC-coupled amplifier, the drop at low frequencies is due to the increasing reactance of C_C , C_S , or C_E , whereas its upper frequency limit is determined by either the parasitic capacitive elements of the network or the frequency dependence of the gain of the active device. For the direct-coupled amplifier, there are no coupling or bypass capacitors to cause a drop in gain at low frequencies. As the figure indicates, it is a flat response to the upper cutoff frequency.

❖ *Frequency Response of Amplifiers:*

➤ Terms and Definitions

In real amplifiers, gain changes with frequency. "Frequency response" is changing the Voltage gain (*amplitude & phase*) with the frequency:

$$\mathbf{A_v} = \frac{\mathbf{V_o}}{\mathbf{V_i}} = \frac{|\mathbf{V_o}| \angle \mathbf{V_o}}{|\mathbf{V_i}| \angle \mathbf{V_i}} = |\mathbf{A_v}| \angle \mathbf{A_v}$$

Both $|\mathbf{A_v}|$ and $\angle \mathbf{A_v}$ are functions of frequency and can be plotted.



➤ *Magnitude Response:*

A plot of $|A_v|$ is called the magnitude response of the amplifier.

➤ *Phase Response:*

A plot of $\angle A_v$ is called the phase response of the amplifier.

➤ *Frequency Response:*

Taken together the two responses are called the frequency response.

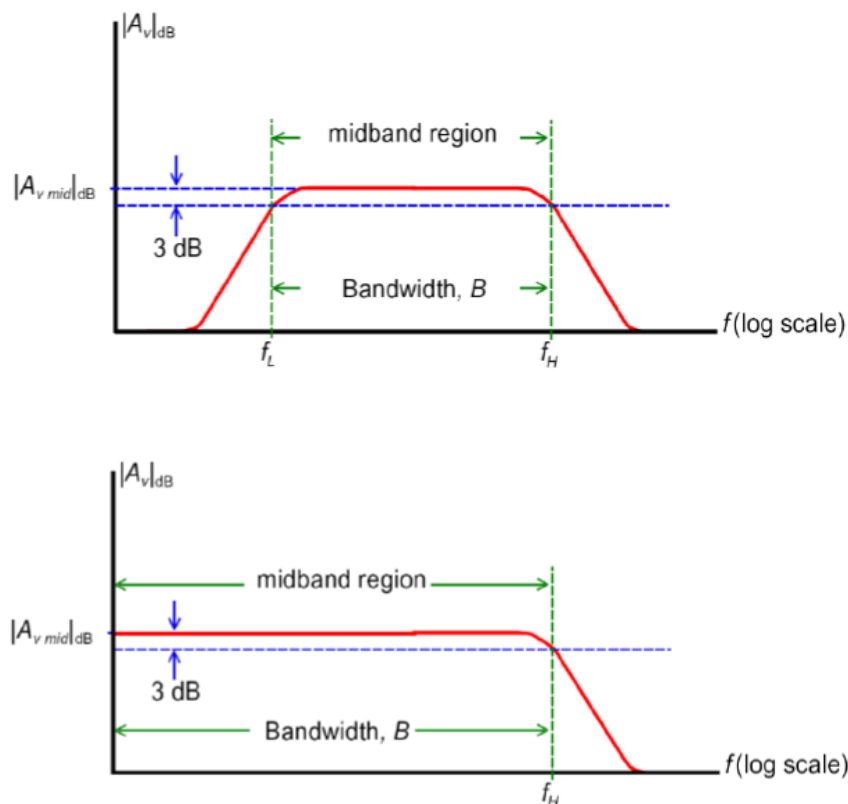


Fig.1

Gain versus frequency: (a) RC-coupled amplifiers; (b) direct-coupled amplifiers



For each system of Fig.1, there is a band of frequencies in which the magnitude of the gain is either equal or relatively close to the midband value. To fix the frequency boundaries of relatively high gain, $0.707A_{v\ mid}$ was chosen to be the gain at the cutoff levels. The corresponding frequencies f_1 and f_2 are generally called the *corner, cutoff, band, break, or half-power frequencies*. The multiplier 0.707 was chosen because at this level the output power is half the midband power output, that is, at midfrequencies,

$$P_{o\ mid} = \frac{|V_o^2|}{R_o} = \frac{|A_{v\ mid} V_i|^2}{R_o}$$

And at the half-power frequencies,

$$P_{o\ HPF} = \frac{|0.707 A_{v\ mid} V_i|^2}{R_o} = 0.5 \frac{|A_{v\ mid} V_i|^2}{R_o}$$

And

$$P_{o\ HPF} = 0.5 P_{o\ mid}$$

The bandwidth (or passband) of each system is determined by f_H and f_L , that is,

$$\text{bandwidth (BW)} = f_H - f_L$$

With f_H and f_L defined in each curve of Fig. 1.