

**Department of Communications
Engineering**

Communication Systems

Third Year Class

Dr. Montadar Abas Taher


montadar@ieee.org

Lecture 10

Phase Locked Loop


Phase-Locked Loop ∴ PLL

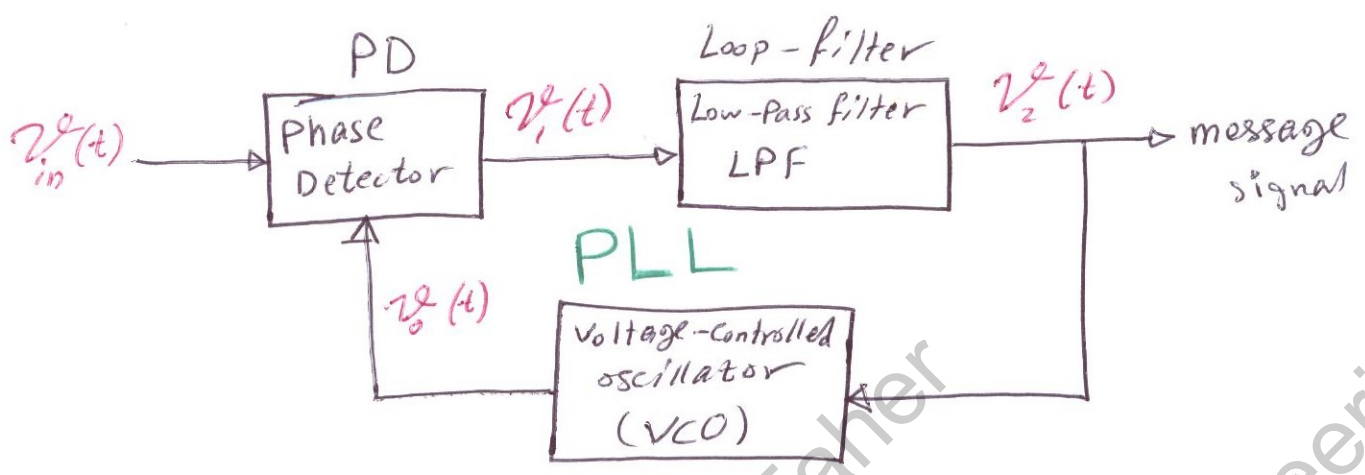- * All the previous methods are non-coherent Demodulation method for FM signals.
- * PLL is a coherent method indirect FM Demodulation.
- * PLL consists of ∴
 - ① Phase Detector (PD).
 - ② Loop Filter (Low pass filter).
 - ③ Voltage Controlled oscillator (VCO).
- * There are two types of PLL
 - ① Analog
 - ② Digital




The PLL has three states:

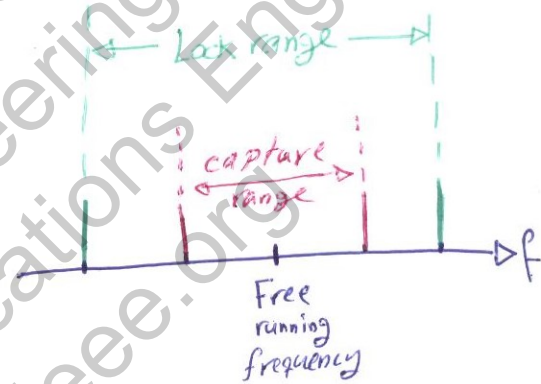- ① Free running state,
 - ② Capture state,
 - ③ Lock range (Hold-in range) state
- will be defined soon



* Free running ω is the frequency when there is no input to the VCO.
 or $v_2^{\phi}(t) = 0$.

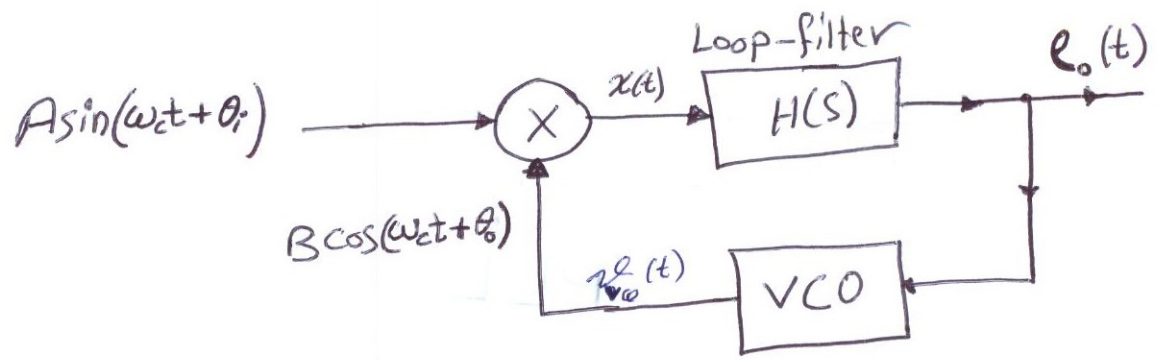Dr. Montadar Abbas Taher
 University of Diyala,
 College of Engineering
 Department of Communications Engineering
 montadar@iee.org



* Suppose the VCO frequency oscillation is:

$$\omega(t) = \omega_c + c e_o(t) \quad \text{--- (1)}$$

c is the VCO constant
 ω_c is the free running VCO frequency.

* Let the VCO output be

$$z_{VCO}(t) = B \cos(\omega_c t + \theta_0) \quad \text{--- (2)}$$

* Let the input to the PLL be

$$z_{in}(t) = A \cos(\omega_c t + \theta_i) \quad \text{--- (3)}$$

$$x(t) = AB \sin(\omega_c t + \theta_i) \cos(\omega_c t + \theta_0)$$

$$x(t) = \frac{AB}{2} \left[\sin(\theta_i - \theta_0) + \sin(2\omega_c t + \theta_i + \theta_0) \right] \quad \text{--- (4)}$$

suppressed by the narrow band LPF Loop filter

$$e_o(t) = \frac{AB}{2} \sin(\theta_i - \theta_0) \quad \text{--- (5)}$$

$\underbrace{\hspace{10em}}_{\theta_e}$

* Suppose that the Loop is Locked ∴

∴ input frequency to the PD & output frequency from the PLL are identical.

∴ θ_i , θ_o , & θ_e are constants

* Suppose the input frequency increased suddenly ∴

$$v_{in}^e(t) = A \cos[(\omega_c + k)t + \theta_i] \quad (6)$$

or
$$v_{in}^e(t) = A \cos(\omega_c t + \hat{\theta}_i) \quad (7)$$

where
$$\hat{\theta}_i = kt + \theta_i \quad (8)$$

Thus, the increase in the incoming frequency causes θ_i to increase

$$\theta_i \longrightarrow \theta_i + kt \longrightarrow \theta_e \text{ increased}$$

Hence $\theta_o(t)$ increases, leading to increase in the output of the VCO frequency

* Suppose the incoming frequency decreases suddenly :-

$\therefore \theta_i \longrightarrow \theta_i - kt \longrightarrow \theta_e$ decreases

\therefore the output frequency of the VCO decreases

Thus, the PLL tracks the input sinusoid. The two signals are said to be mutually Phase Coherent or in phase Lock.

* A PLL can track the incoming frequency over a finite range :-

* the PLL tracks the frequency change over a range of frequencies,

* the tracking range is called Hold-in or Lock range.

* If input/output frequencies are not close enough the loop may not lock.

The range of frequencies over which the input will cause the Loop to Lock is called pull-in or capture range.