
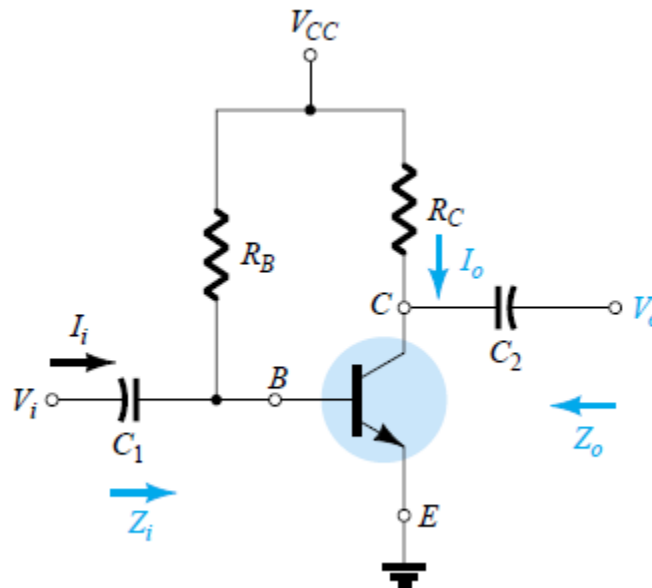



**BJT Small-Signal Analysis**  
**Common –Emitter Fixed-Bias Configuration**

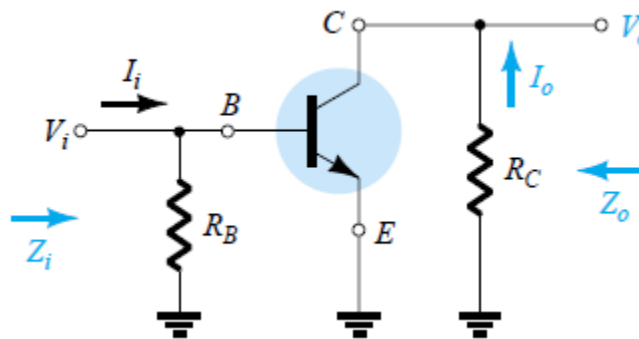

**Fig.1:** Common-emitter fixed-bias configuration.



**Fig.2:** Network of Fig.1 following the removal of the effects of VCC, C1, and C2.

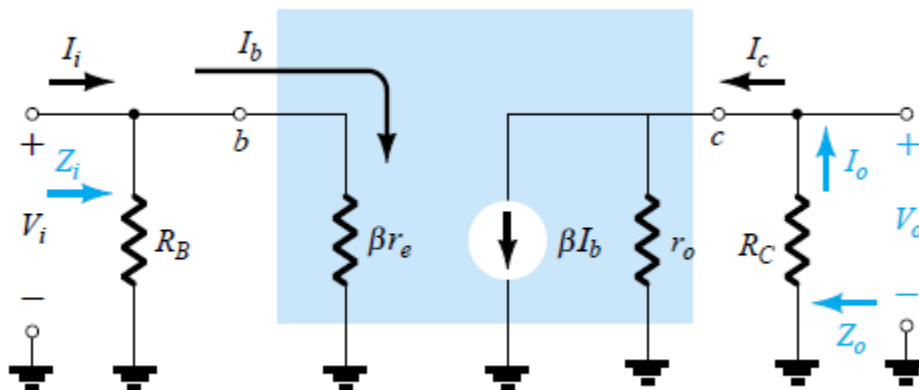

**Fig.3:** Substituting the  $r_e$  model into the network of Fig.2


$$Z_i = R_B \parallel \beta r_e \quad \text{ohms}$$

$$\boxed{Z_i \cong \beta r_e} \quad \text{ohms} \quad R_B \geq 10\beta r_e$$

**Zo:** Recall that the output impedance of any system is defined as the impedance  $Z_o$  determined when  $V_i = 0$ . For Fig.3, when  $V_i = 0$ ,  $I_i = I_b = 0$ , resulting in an open-circuit equivalence for the current source. The result is the configuration of Fig.4.

$$\boxed{Z_o = R_C \parallel r_o} \quad \text{ohms}$$

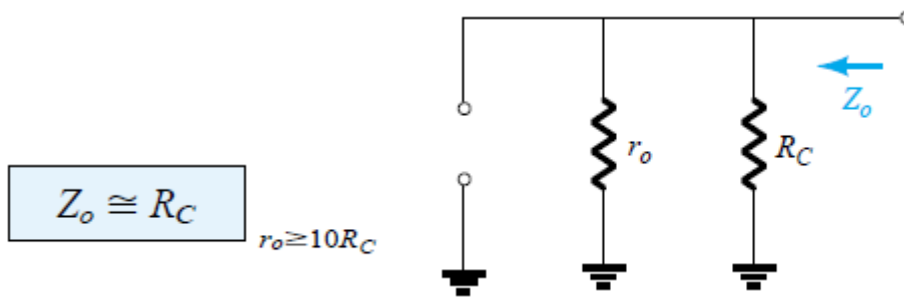If  $r_o \geq 10 R_C$ , the approximation  $R_C \parallel r_o = R_C$  is frequently applied and



$$\boxed{Z_o \cong R_C} \quad r_o \geq 10R_C$$

Fig.4 Determining  $Z_o$

**$A_v$ :** The resistors  $r_o$  and  $R_C$  are in parallel,

and

$$V_o = -\beta I_b (R_C \parallel r_o)$$

but

$$I_b = \frac{V_i}{\beta r_e}$$

so that

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

and

$$\boxed{A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}}$$

If  $r_o \geq 10R_C$ ,

$$\boxed{A_v = -\frac{R_C}{r_e}} \quad r_o \geq 10R_C$$

**$A_i$ :** The current gain is determined in the following manner: Applying the current-divider rule to the input and output circuits,

$$I_o = \frac{(r_o)(\beta I_b)}{r_o + R_C} \quad \text{and} \quad \frac{I_o}{I_b} = \frac{r_o \beta}{r_o + R_C}$$

with

$$I_b = \frac{(R_B)(I_i)}{R_B + \beta r_e} \quad \text{or} \quad \frac{I_b}{I_i} = \frac{R_B}{R_B + \beta r_e}$$

The result is

$$A_i = \frac{I_o}{I_i} = \left(\frac{I_o}{I_b}\right)\left(\frac{I_b}{I_i}\right) = \left(\frac{r_o\beta}{r_o + R_C}\right)\left(\frac{R_B}{R_B + \beta r_e}\right)$$

and

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$$

which is certainly an unwieldy, complex expression.

However, if  $r_o \geq 10R_C$  and  $R_B \geq 10\beta r_e$ , which is often the case,

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R_B r_o}{(r_o)(R_B)}$$

and

$$A_i \cong \beta$$

$r_o \geq 10R_C, R_B \geq 10\beta r_e$

Recall from chapter 7 we can use equation below to avoid complexity

$$A_i = -A_v \frac{Z_i}{R_C}$$

**Phase Relationship:** The negative sign in the resulting equation for  $A_v$  reveals that a  $180^\circ$  phase shift occurs between the input and output signals

For the network of Fig. 5 :

- Determine  $r_e$ .
- Find  $Z_i$  (with  $r_o = \infty \Omega$ ).
- Calculate  $Z_o$  (with  $r_o = \infty \Omega$ ).
- Determine  $A_v$  (with  $r_o = \infty \Omega$ ).
- Find  $A_i$  (with  $r_o = \infty \Omega$ ).
- Repeat parts (c) through (e) including  $r_o = 50 \text{ k}\Omega$  in all calculations and compare results.

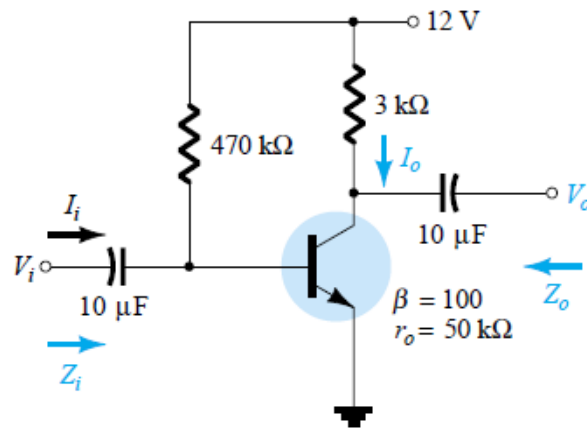


Figure 5 Example 8.1.

### Solution

(a) DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = \mathbf{10.71 \Omega}$$

(b)  $\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = \mathbf{1.069 \text{ k}\Omega}$$

(c)  $Z_o = R_C = \mathbf{3 \text{ k}\Omega}$

(d)  $A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-280.11}$

(e) Since  $R_B \geq 10\beta r_e (470 \text{ k}\Omega > 10.71 \text{ k}\Omega)$

$$A_i \cong \beta = \mathbf{100}$$

$$(f) Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 2.83 \text{ k}\Omega \text{ vs. } 3 \text{ k}\Omega$$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = -264.24 \text{ vs. } -280.11$$


$$A_i = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)} = \frac{(100)(470 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 3 \text{ k}\Omega)(470 \text{ k}\Omega + 1.071 \text{ k}\Omega)} = 94.13 \text{ vs. } 100$$

As a check:

$$A_i = -A_v \frac{Z_i}{R_C} = \frac{-(-264.24)(1.069 \text{ k}\Omega)}{3 \text{ k}\Omega} = 94.16$$

which differs slightly only due to the accuracy carried through the calculations.

### VOLTAGE-DIVIDER BIAS

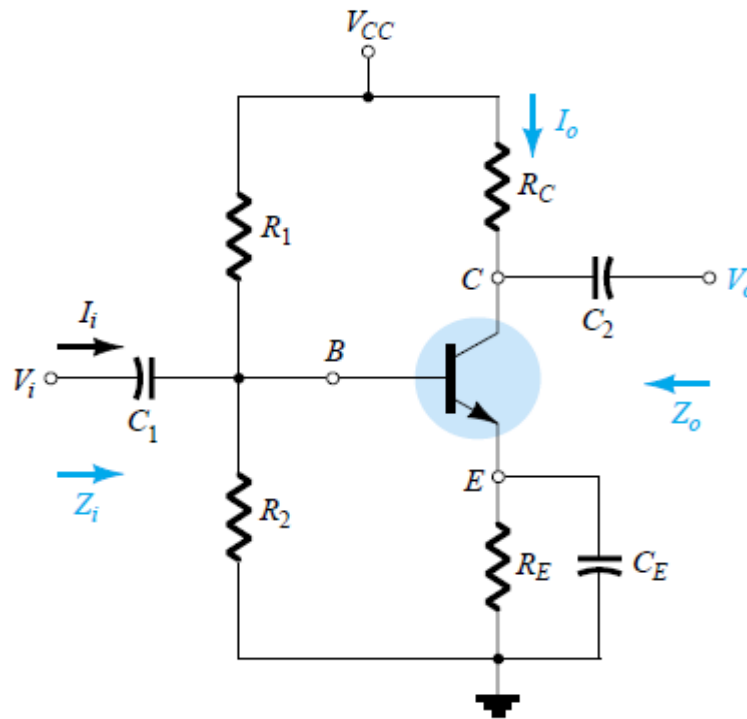

**Fig.6:** Voltage-divider bias configuration.

Substituting the  $r_e$  equivalent circuit will result in the network of Fig.7. Note the absence of  $R_E$  due to the low-impedance shorting effect of the bypass capacitor,  $C_E$ . That is, at the frequency (or frequencies) of operation, the reactance of the capacitor is so small compared to  $R_E$  that it is treated as a short circuit across  $R_E$ .

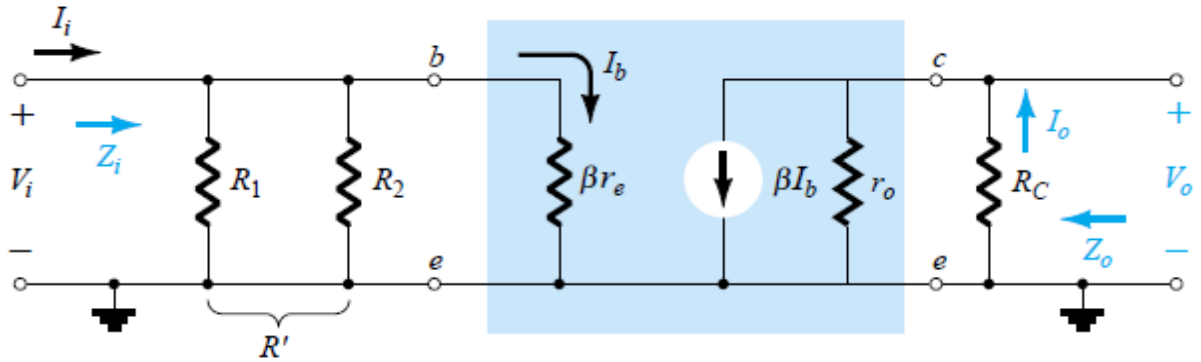


Fig.7: Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig.6

When  $V_{CC}$  is set to zero, it places one end of  $R_1$  and  $R_C$  at ground potential as shown in Fig.7. In addition, note that  $R_1$  and  $R_2$  remain part of the input circuit while  $R_C$  is part of the output circuit. The parallel combination of  $R_1$  and  $R_2$  is defined by:

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

From Fig.7  $Z_i$  is

$$Z_i = R' \parallel \beta r_e$$

**Zo:** From Fig.7 with  $V_i$  set to 0 V resulting in  $I_b = 0 \mu\text{A}$  and  $\beta I_b = 0 \text{ mA}$ ,

$$Z_o = R_C \parallel r_o$$

If  $r_o \geq 10R_C$ ,

$$Z_o \cong R_C \quad r_o \geq 10R_C$$

**$A_v$ :** Since  $R_C$  and  $r_o$  are in parallel,

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

and

$$I_b = \frac{V_i}{\beta r_e}$$

so that

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

and

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

$A_i$ : Since the network of Fig.7 is so similar to that of Fig.3 except for the fact that  $R' = R1 \parallel R2 = RB$ . That is,

$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)}$$

For  $r_o \geq 10R_C$ ,

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R' r_o}{r_o(R' + \beta r_e)}$$

and

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e} \quad r_o \geq 10R_C$$

And if  $R' \geq 10\beta r_e$ ,

$$A_i = \frac{I_o}{I_i} = \frac{\beta R'}{R'}$$

and

$$A_i = \frac{I_o}{I_i} \cong \beta \quad r_o \geq 10R_C, R' \geq 10\beta r_e$$

As an option,

$$A_i = -A_v \frac{Z_i}{R_C}$$

**EXAMPLE 8.2**

For the network of Fig. 8 , determine:

- $r_e$ .
- $Z_i$ .
- $Z_o$  ( $r_o = \infty \Omega$ ).
- $A_v$  ( $r_o = \infty \Omega$ ).
- $A_i$  ( $r_o = \infty \Omega$ ).
- The parameters of parts (b) through (e) if  $r_o = 1/h_{oe} = 50 \text{ k}\Omega$  and compare results.

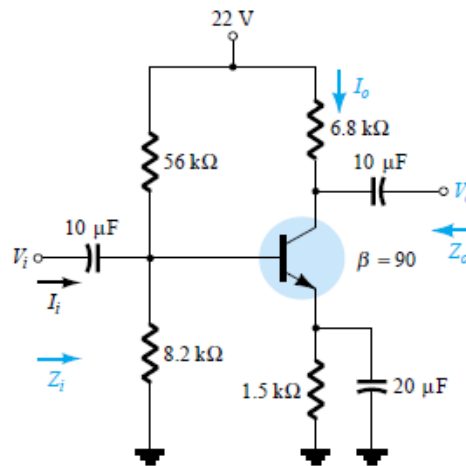


Figure 8. Example 8.2.

**Solution**

- (a) DC: Testing  $\beta R_E > 10R_2$

$$(90)(1.5 \text{ k}\Omega) > 10(8.2 \text{ k}\Omega)$$

$$135 \text{ k}\Omega > 82 \text{ k}\Omega \text{ (satisfied)}$$

Using the approximate approach,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{(8.2 \text{ k}\Omega)(22 \text{ V})}{56 \text{ k}\Omega + 8.2 \text{ k}\Omega} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 \text{ V} - 0.7 \text{ V} = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}\Omega} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = \mathbf{18.44 \Omega}$$

- (b)  $R' = R_1 || R_2 = (56 \text{ k}\Omega) || (8.2 \text{ k}\Omega) = 7.15 \text{ k}\Omega$

$$Z_i = R' || \beta r_e = 7.15 \text{ k}\Omega || (90)(18.44 \Omega) = 7.15 \text{ k}\Omega || 1.66 \text{ k}\Omega$$

$$= \mathbf{1.35 \text{ k}\Omega}$$

- (c)  $Z_o = RC = \mathbf{6.8 \text{ k}\Omega}$



$$(d) A_v = -\frac{R_C}{r_e} = -\frac{6.8 \text{ k}\Omega}{18.44 \text{ }\Omega} = -368.76$$

(e) The condition  $R' \geq 10\beta r_e$  ( $7.15 \text{ k}\Omega \geq 10(1.66 \text{ k}\Omega) = 16.6 \text{ k}\Omega$ ) is *not* satisfied. Therefore,

$$A_i \cong \frac{\beta R'}{R' + \beta r_e} = \frac{(90)(7.15 \text{ k}\Omega)}{7.15 \text{ k}\Omega + 1.66 \text{ k}\Omega} = 73.04$$

(f)  $Z_i = 1.35 \text{ k}\Omega$

$$Z_o = R_C \parallel r_o = 6.8 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 5.98 \text{ k}\Omega \text{ vs. } 6.8 \text{ k}\Omega$$

$$A_v = -\frac{R_C \parallel r_o}{r_e} = -\frac{5.98 \text{ k}\Omega}{18.44 \text{ }\Omega} = -324.3 \text{ vs. } -368.76$$

The condition

$$r_o \geq 10R_C \text{ (} 50 \text{ k}\Omega \geq 10(6.8 \text{ k}\Omega) = 68 \text{ k}\Omega \text{)}$$

is *not* satisfied. Therefore,

$$A_i = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)} = \frac{(90)(7.15 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 6.8 \text{ k}\Omega)(7.15 \text{ k}\Omega + 1.66 \text{ k}\Omega)} = 64.3 \text{ vs. } 73.04$$

There was a measurable difference in the results for  $Z_o$ ,  $A_v$ , and  $A_i$  because the condition  $r_o \geq 10R_C$  was *not* satisfied.

## CE EMITTER-BIAS CONFIGURATION

### Unbypassed

The  $r_e$  equivalent model is substituted in Fig. 10, but note the absence of the resistance  $r_o$ . The effect of  $r_o$  is to make the analysis a great deal more complicated.

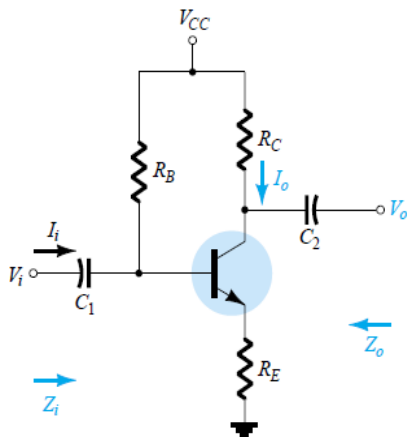


Fig.9: CE emitter-bias configuration.

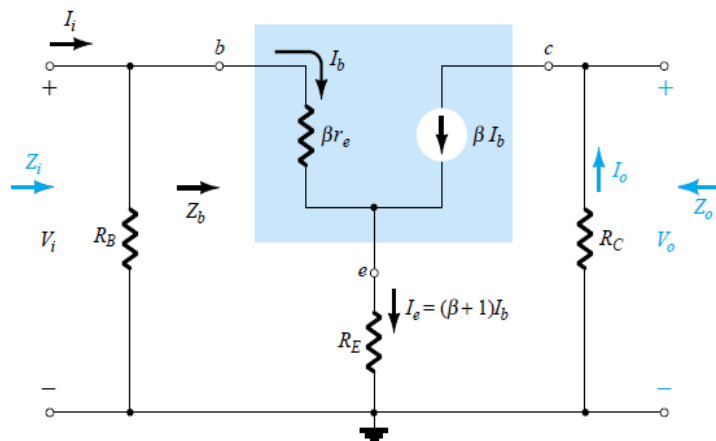


Fig.10: Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig.9.

Applying Kirchhoff's voltage law to the input side of Fig.9 will result in:

$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

And the input impedance looking into the network to the right of  $R_B$  is

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

The result as displayed in Fig.11 reveals that the input impedance of a transistor with an unbypassed resistor  $R_E$  is determined by

$$Z_b = \beta r_e + (\beta + 1) R_E$$

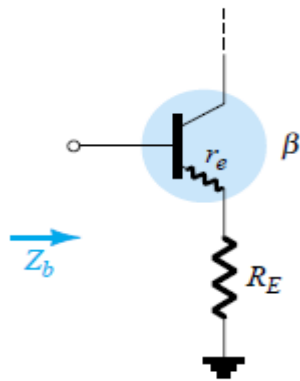


Fig.11: Defining the input impedance of a transistor with an unbypassed emitter resistor.

Since  $\beta$  is normally much greater than 1, the approximate equation is the following:

$$Z_b \cong \beta r_e + \beta R_E$$

and

$$Z_b \cong \beta(r_e + R_E)$$

Since  $R_E$  is often much greater than  $r_e$ , can be further reduced to

$$Z_b \cong \beta R_E$$

**Zi:** Returning to Fig.10, we have

$$Z_i = R_B \parallel Z_b$$

**Zo:** With  $V_i$  set to zero,  $I_b = 0$  and  $\beta I_b$  can be replaced by an open-circuit equivalent. The result is:

$$Z_o = R_C$$

$A_v$ :

$$I_b = \frac{V_i}{Z_b}$$

and

$$\begin{aligned} V_o &= -I_o R_C = -\beta I_b R_C \\ &= -\beta \left( \frac{V_i}{Z_b} \right) R_C \end{aligned}$$

with

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

Substituting  $Z_b = \beta(r_e + R_E)$  gives

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E}$$

and for the approximation  $Z_b \cong \beta R_E$ ,

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

Note again the absence of  $\beta$  from the equation for  $A_v$ .

**$A_i$ :** The magnitude of  $R_B$  is often too close to  $Z_b$  to permit the approximation  $I_b = I_i$ . Applying the current-divider rule to the input circuit will result in

$$I_b = \frac{R_B I_i}{R_B + Z_b}$$

and

$$\frac{I_b}{I_i} = \frac{R_B}{R_B + Z_b}$$

In addition,

$$I_o = \beta I_b$$

and

$$\frac{I_o}{I_b} = \beta$$

so that

$$\begin{aligned} A_i &= \frac{I_o}{I_i} = \frac{I_o}{I_b} \frac{I_b}{I_i} \\ &= \beta \frac{R_B}{R_B + Z_b} \end{aligned}$$

and

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B}{R_B + Z_b}$$

or

$$A_i = -A_v \frac{Z_i}{R_C}$$

**Phase relationship:** The negative sign in Eq. again reveals a 180° phase shift between  $V_o$  and  $V_i$ .

**Bypassed**

If  $R_E$  of Fig.9 is bypassed by an emitter capacitor  $C_E$ , the complete  $r_e$  equivalent model can be substituted resulting in the same equivalent network as Fig.3 so all Equations are therefore applicable.

EXAMPLE 8.3: For the network of Fig.12, without  $C_E$  (unbypassed), determine:

- (a)  $r_e$ .
- (b)  $Z_i$ .
- (c)  $Z_o$ .
- (d)  $A_v$ .
- (e)  $A_i$ .

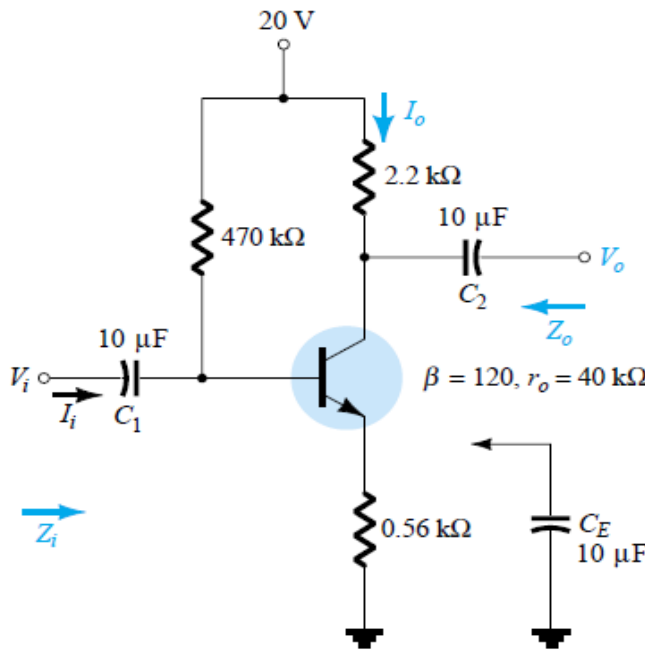


Fig.12: for EXAMPLE 8.3

**Solution**

(a) DC: 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega + (121)0.56 \text{ k}\Omega} = 35.89 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (121)(35.89 \mu\text{A}) = 4.34 \text{ mA}$$

and 
$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{4.34 \text{ mA}} = 5.99 \Omega$$

(b) Testing the condition  $r_o \geq 10(R_C + R_E)$ ,

$$40 \text{ k}\Omega \geq 10(2.2 \text{ k}\Omega + 0.56 \text{ k}\Omega)$$

$$40 \text{ k}\Omega \geq 10(2.76 \text{ k}\Omega) = 27.6 \text{ k}\Omega \text{ (satisfied)}$$

Therefore,

$$Z_b \cong \beta(r_e + R_E) = 120(5.99 \Omega + 560 \Omega) \\ = 67.92 \text{ k}\Omega$$

and

$$Z_i = R_B \parallel Z_b = 470 \text{ k}\Omega \parallel 67.92 \text{ k}\Omega \\ = 59.34 \text{ k}\Omega$$

(c)  $Z_o = R_C = 2.2 \text{ k}\Omega$

(d)  $r_o \geq 10R_C$  is satisfied. Therefore,

$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b} = -\frac{(120)(2.2 \text{ k}\Omega)}{67.92 \text{ k}\Omega} \\ = -3.89$$

compared to  $-3.93$  using Eq.  $A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$ .

(e)  $A_i = -A_v \frac{Z_i}{R_C} = -(-3.89) \left( \frac{59.34 \text{ k}\Omega}{2.2 \text{ k}\Omega} \right) \\ = 104.92$

compared to  $104.85$  using Eq.  $A_i = \frac{I_o}{I_i} = \frac{\beta R_B}{R_B + Z_b}$

#### EXAMPLE 8.4

Repeat the analysis of Example 8.3 with  $C_E$  in place.

#### Solution

(a) The dc analysis is the same, and  $r_e = 5.99 \Omega$ .

(b)  $R_E$  is “shorted out” by  $C_E$  for the ac analysis. Therefore,

$$Z_i = R_B \parallel Z_b = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel (120)(5.99 \Omega) \\ = 470 \text{ k}\Omega \parallel 718.8 \Omega \cong 717.70 \Omega$$

(c)  $Z_o = R_C = 2.2 \text{ k}\Omega$


(d)  $A_v = -\frac{R_C}{r_e} \\ = -\frac{2.2 \text{ k}\Omega}{5.99 \Omega} = -367.28 \text{ (a significant increase)}$

(e)  $A_i = \frac{\beta R_B}{R_B + Z_b} = \frac{(120)(470 \text{ k}\Omega)}{470 \text{ k}\Omega + 718.8 \Omega} \\ = 119.82$

**EXAMPLE 8.5**

For the network of Fig. 13, determine (using appropriate approximations):

- (a)  $r_e$ .
- (b)  $Z_i$ .
- (c)  $Z_o$ .
- (d)  $A_v$ .
- (e)  $A_i$ .

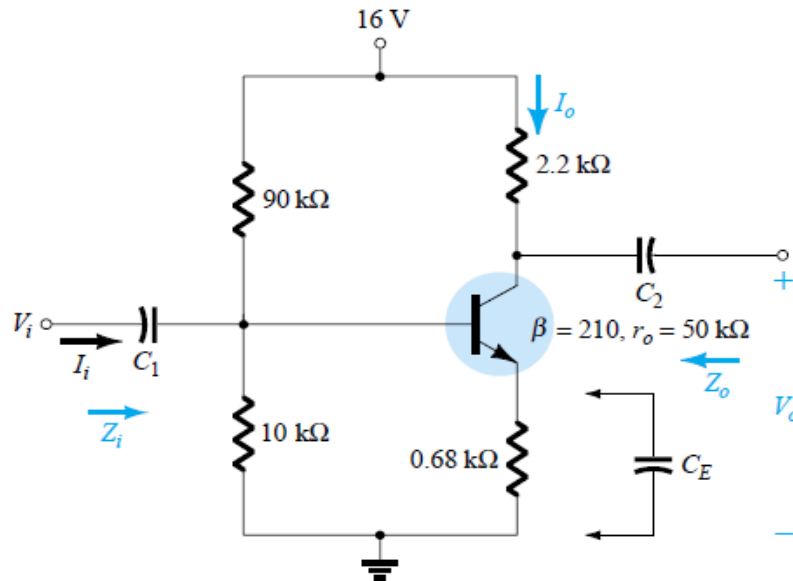

**Fig.13**

**Solution**

(a) Testing  $\beta R_E > 10R_2$

$$(210)(0.68 \text{ k}\Omega) > 10(10 \text{ k}\Omega)$$

$$142.8 \text{ k}\Omega > 100 \text{ k}\Omega \text{ (satisfied)}$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{10 \text{ k}\Omega}{90 \text{ k}\Omega + 10 \text{ k}\Omega} (16 \text{ V}) = 1.6 \text{ V}$$

$$V_E = V_B - V_{BE} = 1.6 \text{ V} - 0.7 \text{ V} = 0.9 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{0.9 \text{ V}}{0.68 \text{ k}\Omega} = 1.324 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.324 \text{ mA}} = \mathbf{19.64 \Omega}$$

(b) The ac equivalent circuit is provided in Fig.14. The resulting configuration is now different from Fig.10 only by the fact that now

$$R_B = R' = R_1 || R_2 = 9 \text{ k}\Omega$$

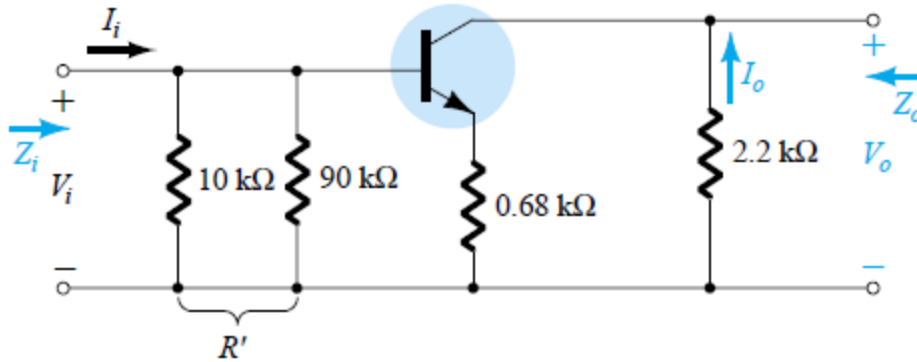


Fig.14: The ac equivalent circuit of Fig.13.

The testing conditions of  $r_o \geq 10(R_C + R_E)$  and  $r_o \geq 10R_C$  are both satisfied. Using the appropriate approximations yields

$$Z_b \cong \beta R_E = 142.8 \text{ k}\Omega$$

$$Z_i = R_B \parallel Z_b = 9 \text{ k}\Omega \parallel 142.8 \text{ k}\Omega \\ = 8.47 \text{ k}\Omega$$

(c)  $Z_o = R_C = 2.2 \text{ k}\Omega$

(d)  $A_v = -\frac{R_C}{R_E} = -\frac{2.2 \text{ k}\Omega}{0.68 \text{ k}\Omega} = -3.24$

(e)  $A_i = -A_v \frac{Z_i}{R_C} = -(-3.24) \left( \frac{8.47 \text{ k}\Omega}{2.2 \text{ k}\Omega} \right) \\ = 12.47$