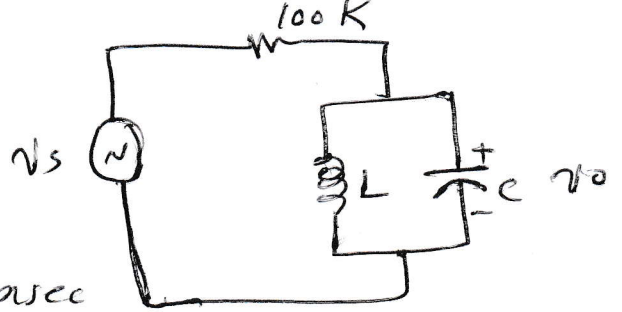


EX for figure below.

$$v_s(t) = \begin{cases} 10 & 0 < t < \pi \text{ msec} \\ 0 & \pi \text{ msec} < t < 2\pi \text{ msec} \end{cases}$$



$$L = 1 \text{ H}, \quad C = 1 \mu\text{F}$$

Determine the value of  $v_o(t)$ .

The first step is to find the Fourier series for  $v_s(t)$ .

$$f(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t + b_n \sin n\omega_0 t$$

$$T = 2\pi \times 10^{-3} \text{ and } \omega_0 = 1000$$

$$a_0 = \frac{1}{2\pi \times 10^{-3}} \left[ \int_0^{\pi \times 10^{-3}} 10 dt + \int_{\pi \times 10^{-3}}^{2\pi \times 10^{-3}} 0 dt \right] = \frac{1}{2\pi \times 10^{-3}} (10t - 0) \Big|_0^{\pi \times 10^{-3}}$$

$$a_0 = 5 \text{ volt}$$

$$a_n = \frac{1}{T} \int_0^T f(t) \cdot \cos n\omega_0 t dt$$

$$a_n = \frac{1}{2\pi \times 10^{-3}} \int_0^{\pi \times 10^{-3}} 10 \cdot \cos(n \times 1000) t dt$$

$$= \frac{10}{2\pi \times 10^{-3}} \times \frac{\sin(1000n)t}{1000n} \Big|_0^{\pi \times 10^{-3}}$$

$$= \frac{5}{2\pi n} [\sin(1000 \times n \times \pi \times 10^{-3}) - \sin 0]$$

$$= 0$$

(78)

$$b_n = \frac{2}{2\pi \times 10^3} \int_0^T f(t) \sin(1000\pi t) dt$$

$$= \frac{1}{\pi \times 10^3} \left[ \int_0^{\pi \times 10^{-3}} 10 \sin(1000\pi t) dt + 0 \right]$$

$$= - \frac{1}{\pi \times 10^3 \times 10^3 \pi} \times 10 \cos(1000\pi t) \Big|_0^{10^{-3}}$$

$$= \frac{-10}{n\pi} (\cos(n\pi) - 1)$$

Thus,  $b_n = \begin{cases} \frac{20}{n\pi} & \text{for } n = \text{odd} \\ 0 & \text{for } n = \text{even} \end{cases}$

therefore,  $v_s(t) = \left[ 5 + \sum_{k=1}^{\infty} \frac{20}{(1+2k)\pi} \sin(1000(1+2k)t) \right]$  Volt

for d.c term,  $v_0 = 0$  since the inductor looks like a short for d.c.

For all the other values of  $n$ ,  $v_0 = \frac{V \times Z}{Z + R}$

$$v_0 = \frac{\frac{20}{n\pi}}{10^5 + \frac{L/C}{j(\omega L - \frac{1}{\omega C})}}, \omega = 1000n \text{ for odd}$$

$$= \frac{\frac{20L}{n\pi C}}{j10^5(\omega L - \frac{1}{\omega C}) + \frac{L}{C}} = \frac{\frac{20 \times 10^6}{n\pi}}{j10^5(1000n - \frac{1000}{n}) + 10^6}$$

For  $n=1$ ,  $\omega=1000$ , therefore  $V_0 = \frac{20}{\pi}$

For  $n=3$ ,  $\omega=3000$ , therefore,

$$\text{the value of } L/C = \frac{L/C}{j(\omega L - \frac{1}{\omega C})} = \frac{1000}{j2667}$$

$$= -j0.375 \Omega$$

The value of impedance is so much smaller than the value of the resistor that can neglect this term and all of the others.

thus,

$$V_0 = \frac{20}{\pi} \sin(1000t) \text{ volts.}$$