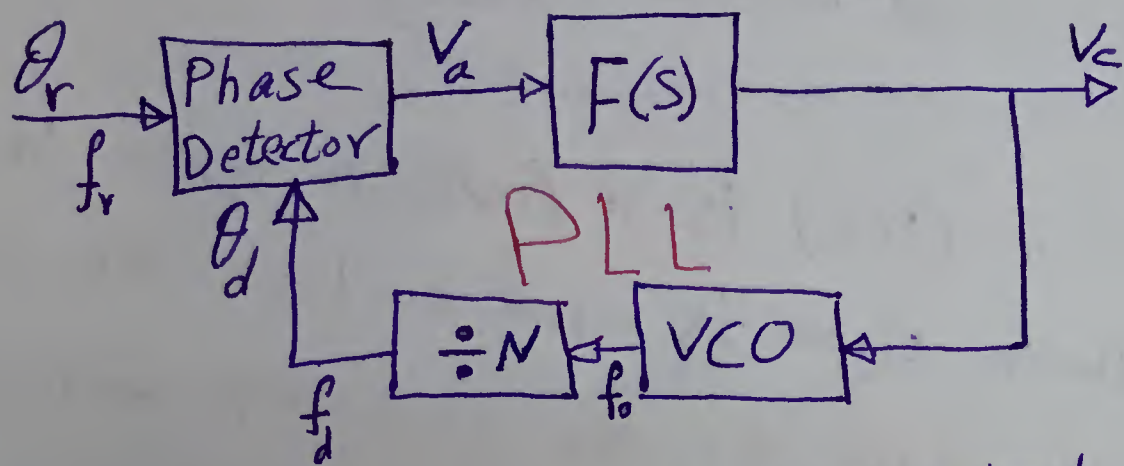


Phase-Locked Loop (PLL)

- * A phase-locked loop (PLL) is a feedback system in which the feedback signal is used to lock the output frequency and phase to the frequency and phase of an input signal.
- * The input waveform can be of many different types, including sinusoidal or digital.
- * PLL used for the first time in 1932 for the synchronous detection of radio signals.
- * Next PLL used by NASA in 1960s in its satellite programs.
- * PLL can be analogue or digital.



- * The Phase detector generates an output signal that is a function of the difference between the two signals.
- * The detector output is filtered and the dc component of the error signal is applied to the voltage-controlled oscillator (VCO).
- * The signal fed back to the PD is the VCO output frequency divided by N .
- * The VCO control voltage $V_c(t)$ forces the VCO to change frequency in the direction that reduces the difference between the input frequency and the divider output frequency.
- * If the two frequencies are sufficiently close, the PLL feedback mechanism forces the two-PD input frequencies to be equal, and the VCO is 'Locked' with the incoming frequency.

$$f_r = f_d$$

where f_r is the reference signal
 f_d is the second i/p to PD
 or, divider output frequency.

$$f_d = \frac{f_0}{N}$$

OR

$$f_0 = N f_d$$

* If a divider is not used, $N = 1$.

$$V_a = K_d (\theta_r - \theta_d) \quad \text{————— (1)}$$

K_d is the phase detector gain factor. (V/rad)

* The VCO output frequency deviates from its free-running frequency by an increment of frequency

$$\Delta\omega = K_o V_c \quad \text{————— (2)}$$

where: V_c is the input voltage to VCO,

K_o is the VCO gain factor rad/sec/Vol.
 or the conversion factor



∴ The output frequency is ∴

$$\omega_o = \omega_c + \Delta\omega = \omega_c + k_o V_c$$

where: ω_c is the free running frequency of the VCO.

Ex. 1 The output frequency of a VCO changes from 100 kHz when a change of 0.5 V occurs at the VCO input. Calculate the conversion gain factor k_o .

Solution

$$k_o = \frac{\Delta\omega}{\Delta V} = \frac{(150 \text{ kHz} - 100 \text{ kHz}) 2\pi}{0.5 \text{ V}} = \left(\frac{50 \text{ kHz}}{0.5 \text{ V}} \right) 2\pi$$

$$k_o = 2\pi(100 \text{ kHz}) / \text{Volt}$$

OR

$$[\omega_o = \omega_c + k_o V_c] \div 2\pi$$

$$f_o = f_c + \frac{k_o V_c}{2\pi}$$


$$k_o = \frac{150 - 100}{0.5} \text{ kHz/V} = 100 \text{ kHz/V}$$

NOTE ∴

* Increasing V_c , decreases f_o ,

* Decreasing V_c , increases f_o .

$$\therefore f_o = f_c \pm \Delta f$$

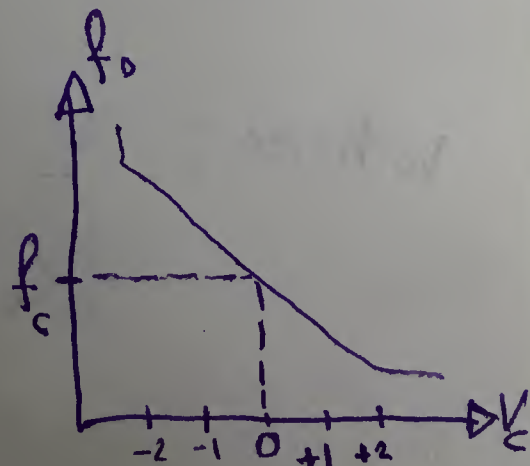

* The VCO operation can be described as:-


$$\Delta\omega = \frac{d\theta_o}{dt} = K_o V_c \quad \text{--- (3)}$$

$$\rightarrow f_d = \frac{f_o}{N}$$

Since phase is the time integral of frequency,

$$\theta_d = \frac{\theta_o}{N}$$

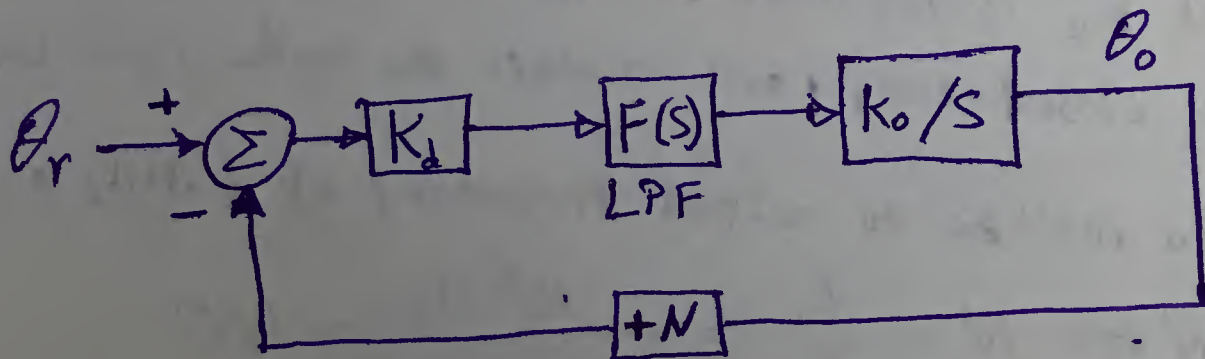∴ The PLL can be represented by the linear model shown below.



$$\frac{\theta_o(s)}{\theta_r(s)} = \frac{K_o K_d F(s)/s}{1 + K_d K_o F(s)/(Ns)} = \frac{G(s)}{1 + G(s)/N} \quad \text{--- (4)}$$

* If NO LPF, then

$$\frac{\theta_o}{\theta_r} = \frac{K_d K_o}{s + K_d K_o/N} = \frac{N K_{2e}}{s + K_{2e}}$$

which is equivalent to the transfer function of a simple LPF with a dc gain of N and a bandwidth equal to K_{2e} .

where: $K_{ze} = \frac{K_d K_o}{N}$

* This type of PLL is referred to as **first-order Loop** since it can be described by a first order differential equation and is also of **type I**.

EX. 2 A frequency synthesizer uses PLL to synthesize a 1 MHz signal from a 25 kHz reference frequency. Assume there is no filtering included, and $K_d = 2 \text{ V/rad}$ and K_o is 100 Hz/V. Find the transfer function of the closed-loop, and calculate the synthesizer bandwidth.

Solution : To realize an output frequency of 1 MHz,

$$f_o = f_d N \Rightarrow N = \frac{f_o}{f_d} = \frac{10^6 \text{ Hz}}{25 \times 10^3 \text{ Hz}} = 40$$

$$\frac{\theta_o}{\theta_r} = \frac{K_d K_o / s}{1 + K_d K_o / (sN)} = \frac{K_d K_o}{s + K_d K_o / N}$$

$$\frac{\theta_o}{\theta_r} = \frac{(2 \times 100) 2\pi}{s + (2 \times 100 \times 2\pi) / 40} = \frac{16000\pi}{40s + 16000\pi}$$

* The synthesizer bandwidth $K_{ze} = \frac{K_d K_o}{N}$

$$K_{ze} = \frac{2 \times 100}{40} = 5 \text{ Hz} \\ = 10 \text{ rad/s}$$

End of
solution

* Normally, the loop will also contain a filter to filter out undesirable components from the phase detector, and to provide further control over the Loop's frequency response.

* Let the filter is a simple LPF,

$$F(s) = \left(\frac{s}{\omega_L} + 1 \right)^{-1}$$

then,

$$\frac{\theta_o(s)}{\theta_r(s)} = \frac{NK_2}{s(s/\omega_L + 1) + K_2} = \frac{N}{s^2/\omega_n^2 + (2\zeta/\omega_n)s + 1} \quad \text{---(5)}$$

where ω_n $K_2 = \frac{K_d K_o}{N}$ ---(6)

$$\omega_n^2 = K_2 \omega_L \quad \text{---(7)}$$

$$2\zeta = \frac{\omega_n}{K_2} = \left(\frac{\omega_L}{K_2} \right)^{1/2} \quad \text{---(8)}$$

Equation(5) is the general form of the second-order Low-Pass transfer function.

The magnitude of the steady-state frequency response is

$$\left| \frac{\theta_o}{\theta_r}(j\omega) \right| = \frac{N}{\left[\left(1 - \frac{\omega^2}{\omega_n^2}\right)^2 + \left(2\zeta \frac{\omega}{\omega_n}\right)^2 \right]^{1/2}} \quad (9)$$


and the phase shift is

$$\arg \frac{\theta_o}{\theta_r}(j\omega) = \left| \frac{\theta_o}{\theta_r}(j\omega) \right| = -\tan^{-1} \left[\frac{2\zeta\omega}{\omega_n \left(1 - \frac{\omega^2}{\omega_n^2}\right)} \right] \quad (10)$$

* The function of Eq. (9) is plotted in the next page, for selected values of ζ .

* For $\zeta = 0.707$, the transfer function becomes the second-order "maximally flat" Butterworth response.

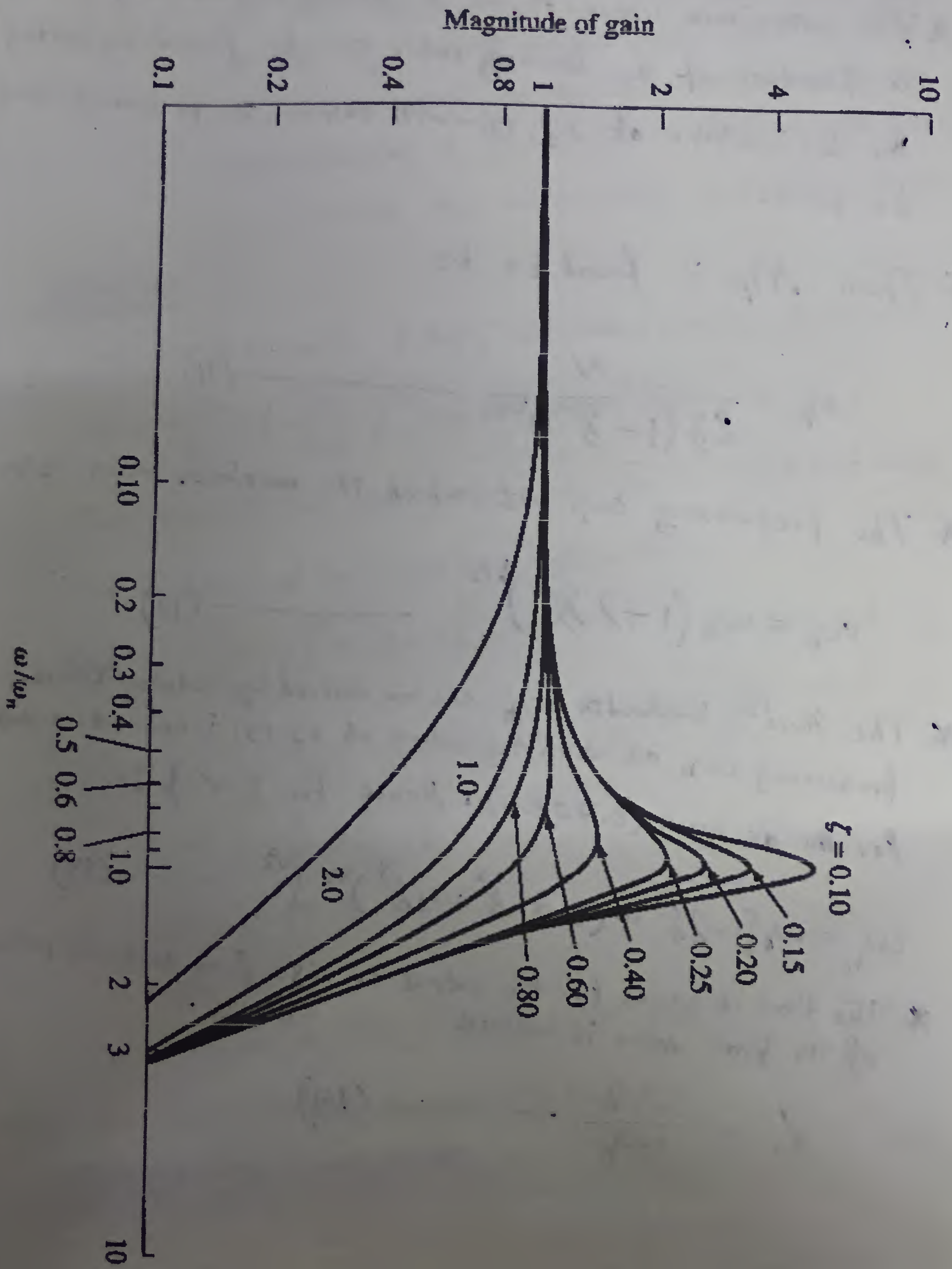* For values of $\zeta < 0.707$, the gain exhibits peaking in the frequency domain.



* The maximum value of the frequency response M_p as a function of the damping ratio can be found by setting the derivative of Eq. (9) - with respect to frequency - equal to zero.

* Then M_p is found to be

$$M_p = \frac{N}{2\zeta(1-\zeta^2)^{1/2}} \quad \text{--- (11)}$$

* The frequency ω_p at which the maximum occurs is

$$\omega_p = \omega_n(1-2\zeta^2)^{1/2} \quad \text{--- (12)}$$

* The 3-dB bandwidth ω_h can be derived by solving for the frequency ω_n at which the value of Eq. (9) is equal to 0.707 for the dc gain (0.707N). Hence for $\zeta < 1$

$$\omega_h = \omega_n \left[1 - 2\zeta^2 + (2 - 4\zeta^2 + 4\zeta^4)^{1/2} \right]^{1/2} \quad \text{--- (13)}$$

* The time it takes for the output to rise from 10 to 90 percent of its final value is called the rise time t_r .

$$t_r = \frac{2.2}{\omega_h} \quad \text{--- (14)}$$

Ex. 3 A phase-locked loop with closed loop bandwidth $K_{v2} = 10\pi$ rad/s. What value of LPF should be used so that the closed-loop system approximates a second-order Butterworth filter? Determine the corresponding system rise time.

solution

For Butterworth filter, the damping ratio $\zeta = 0.707$

$$2\zeta = \frac{\omega_n}{K_{v2}} = \left(\frac{\omega_L}{K_{v2}}\right)^{1/2} \Rightarrow 2(0.707) = \left(\frac{\omega_L}{10\pi}\right)^{1/2}$$

The required low-pass filter bandwidth is $\omega_L = 20\pi$ rad/s

the bandwidth of the closed-loop system is

$$\omega_h = \omega_n \left[1 - 2\zeta^2 + (2 - 4\zeta^2 + 4\zeta^4)^{1/2} \right]^{1/2} \Leftarrow \zeta = 0.707 = \frac{1}{\sqrt{2}}$$

$$\omega_h = \omega_n \left[1 - 2\left(\frac{1}{\sqrt{2}}\right)^2 + \left(2 - 4\left(\frac{1}{\sqrt{2}}\right)^2 + 4\left(\frac{1}{\sqrt{2}}\right)^4\right)^{1/2} \right]^{1/2}$$

$$= \omega_n \left[1 - \frac{2}{2} + \left(2 - \frac{4}{2} + \frac{4}{4}\right)^{1/2} \right]^{1/2}$$

$$= \omega_n \left[1 - 1 + (2 - 2 + 1)^{1/2} \right]^{1/2}$$

$$= \omega_n [1]$$

$$\omega_h = \omega_n = (K_{v2} \omega_L)^{1/2} = 14.14\pi \text{ rad/s}$$

then the corresponding system rise time is

$$t_r = \frac{2.2}{\omega_h} = 49.4 \text{ ms}$$


Phase Detectors (PD)

- * PD is also called Phase comparator (PC).
- * PLLs performance vary depending on the PD type.
- * In PLL, different types of PDs can be used, such as
 - ① Digital PD,
 - ② Analog mixer, or multiplier,
 - ③ Sampling phase Detector.

* We shall focus on Digital PD only.

⇒ The output of a logic circuit PD is a constant-amplitude pulse whose width is proportional to the phase difference between the two input signals (which can be either analog or digital).

* The X-OR gate serves as a PD.

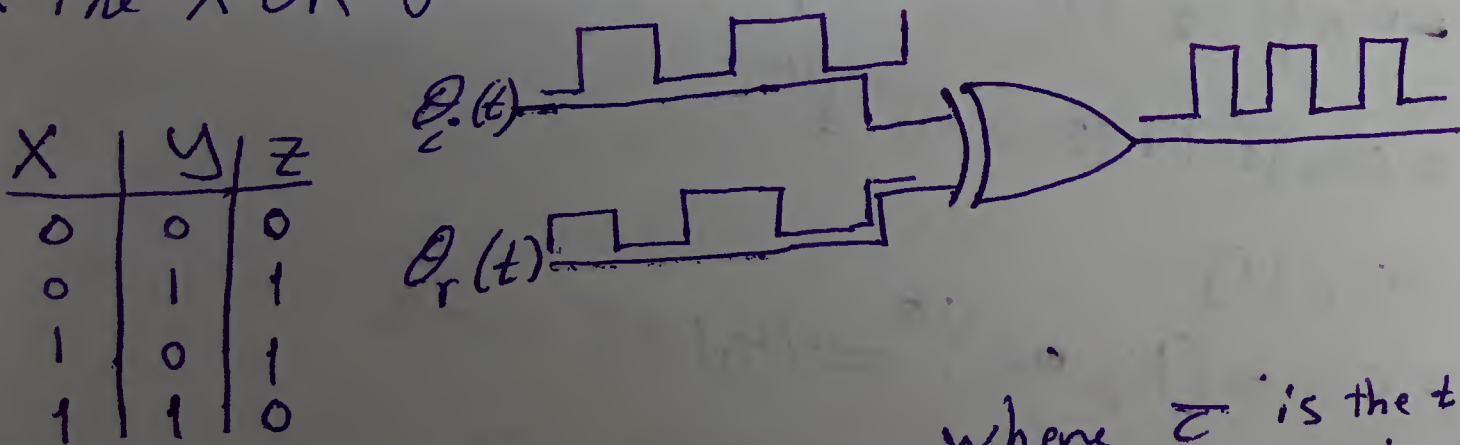


where τ is the time difference between the two signals.
 T is the period of the input signals.

* The phase error is

$$\phi_e = \frac{\tau}{T} 2\pi \quad (15)$$

* The average error is shown here

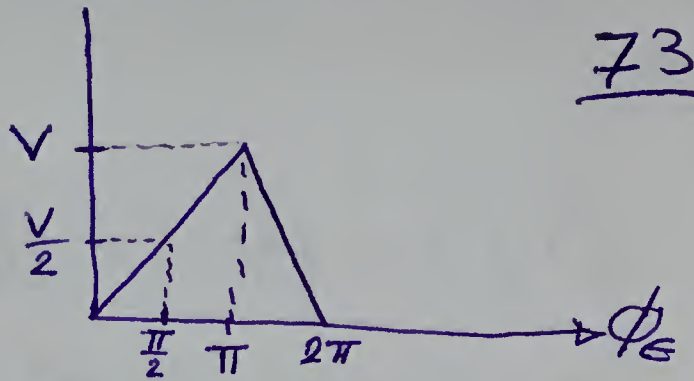

* The output is a maximum $\%0$

⇒ the gate output is high at all times, when the two signals are 180° out of phase.

* There are two values of phase error Φ_E $^\circ$

- 1) One value corresponds to negative Loop gain,
- 2) Second value corresponds to positive Loop gain

For the positive value of Loop gain, the closed-loop system is unstable, and the error will adjust itself to the phase error corresponding to a negative-feedback Loop.

Voltage Controlled Oscillator (VCO)

A voltage controlled oscillator VCO is a free-running oscillator whose frequency of operation is controlled by an external dc bias voltage.

PLL Applications

Many applications for the PLL such as:-

- i) Frequency Modulation,
- ii) Frequency demodulation, detection,
- iii) Tracking,
- iv) Synthesis applications.

PLL Operation

* Important parameters of PLL must be defined to understand its operation,


Lock Range \therefore The range of frequencies over which a PLL can maintain phase lock is called its **Lock range**. The Lock-range width, designated B_L , can be specified as \therefore

$$B_L = f_{\max} - f_{\min} \quad \text{--- (16)}$$

* f_{\max} and f_{\min} \therefore maximum & minimum frequencies over which phase lock can be maintained.

* The factors limiting the Lock-range include the maximum frequency deviation of the VCO and the dc voltage range of the phase detector output.

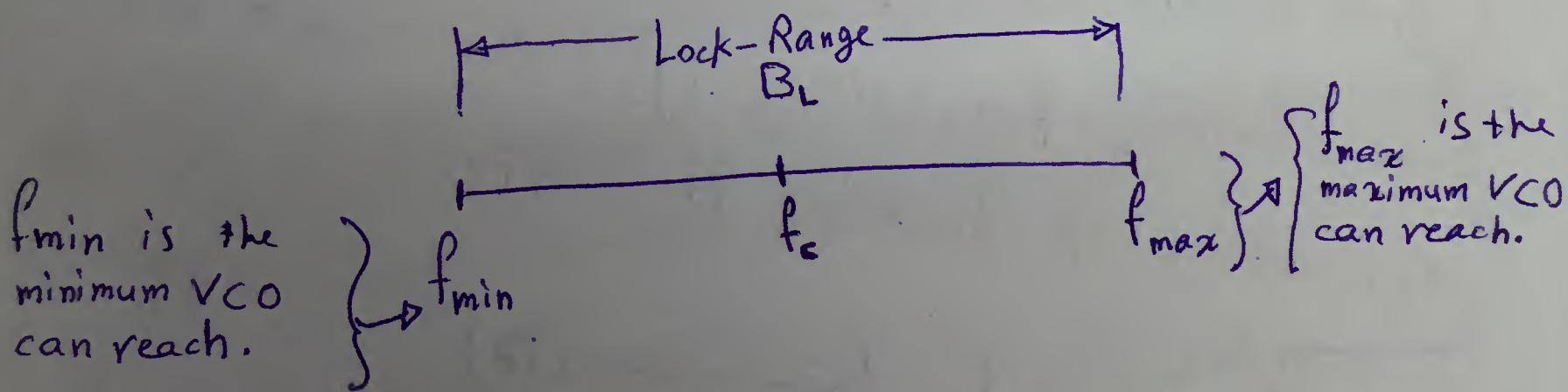* The Lock-range is independent of the LPF frequency response, because when the PLL is in phase lock, the difference frequency $f_r - f_o = 0$.



* Lock-range is also called tracking-range.

* If the frequency deviation of the VCO ~~is~~ which is $|\Delta\omega|$ or $|\Delta f|$ not equal to f_{max} or f_{min} , then the PLL can not track the input frequency.

Capture Range :-

* The capture range width B_{cap} , is the range of frequencies over which a PLL can acquire Phase Lock when phase lock does not yet exist.


⇒ In other words :-

If PLL is not in locked condition, the input signal to the PLL (f_r) must be close to the free running frequency (f_c) to start the operation of locking the loop.

$$B_{cap} = f_2 - f_1 \quad (17)$$

Where :-

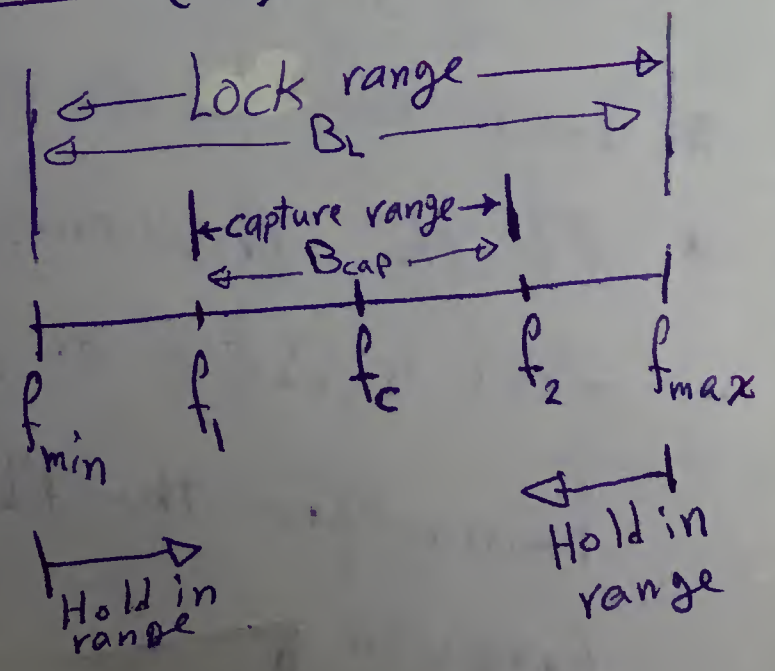- f_1 :- Lowest frequency the PLL can lock onto.
- f_2 :- Highest frequency the PLL can lock onto.



* Another words for the capture range:

Capture Range: Range of input frequencies around the VCO center frequency f_c onto which the loop will lock when starting from unlocked condition.


* In order for a PLL to acquire phase lock, the difference frequency $f_r - f_c$ must not exceed the bandwidth of the LPF.

* If $f_r - f_c$ exceeds the bandwidth of the LPF, Phase Lock cannot be acquired.

* If the bandwidth of the LPF $> f_r - f_c$, then Phase Lock can be achieved.

* If the bandwidth of the LPF $< f_r - f_c$, then Phase Lock cannot be achieved.

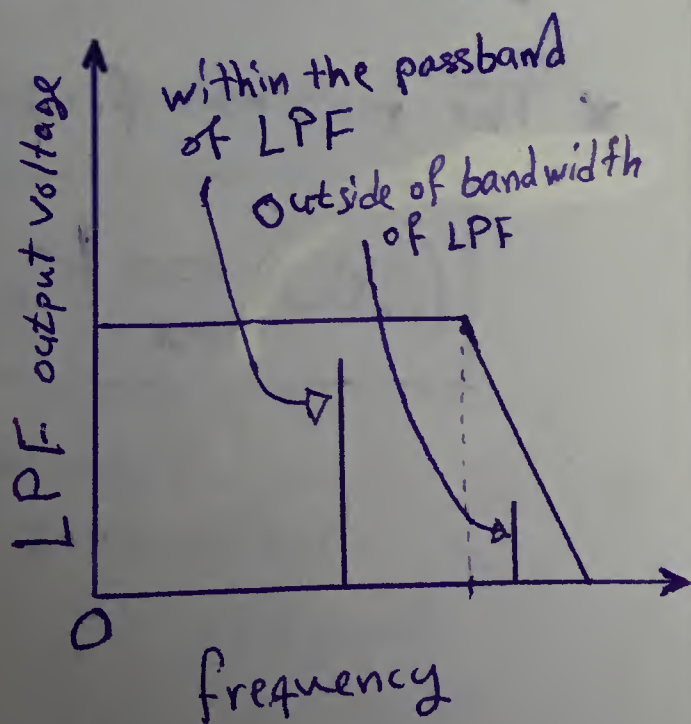this is because the amplitude of the filter output voltage falls off sharply outside the bandwidth of the LPF.



Frequency Demodulation

*

* If the PLL is locked on an input frequency, the VCO control voltage is proportional to the VCO's frequency shift from its free-running frequency.

* If the input frequency f_r shifts, the control voltage shifts accordingly (provided the frequency shift is within the loop's tracking range).

* If the input signal is frequency-modulated, then the VCO control voltage will be the demodulated output.

* If the maximum phase detector output voltage is V volts, then the maximum control voltage applied to the VCO is KV volts, where K is the dc gain of the LPF.

* The maximum frequency deviation of the VCO is then

$$(\Delta\omega)_{\max} = K_o KV \text{ rad/s}$$

* This of course, assumes that the VCO is designed to be linear over this frequency range.

* If the phase detector output can deviate between $\pm V$ volts, the tracking range (TR) will be:

$$TR = 2(\Delta\omega)_{\max} = 2K_o KV$$

* This tracking range must be greater than the frequency deviation of the input signal.

* FM demodulation can then be obtained by setting the free-running frequency of the VCO equal to the center frequency of the input signal.

* This detection method assumes that the envelope of the input waveform has a constant amplitude.

* In many applications, an amplifier and amplitude limiter are added before the PLL to ensure that this is the case.

Assignment $\circ \circ$ To the student, How to Demodulate the AM signal $V(t) = A_c [1 + m_a m(t)] \cos(\omega_c t)$ using PLL? Do all the mathematical analysis. You can use any reference.

EX. 4 The output frequency of a VCO changes from 50 to 75 kHz when the dc input voltage changes by 0.5 V. Calculate the conversion gain.

Solution
$$K_o = \frac{\Delta f}{\Delta V} = \frac{75 \text{ kHz} - 50 \text{ kHz}}{0.5 \text{ V}} = 50 \text{ kHz/V}$$

EX. 5 A certain VCO has a natural frequency of 1 MHz with a dc input of 0 V. If the VCO has a conversion gain of 50 kHz/V, calculate the VCO output frequency for a voltage change of 1 V.

Solution
$$K_o = \frac{\Delta f}{\Delta V} \Rightarrow \Delta f = K_o \Delta V = 50,000 \text{ Hz/V} \times 1 \text{ V} = 50 \text{ kHz}$$

The VCO frequency equals:


$$f_o = f_c \pm \Delta f = 1 \text{ MHz} \pm 50 \text{ kHz}$$

$\therefore f_o = 950 \text{ kHz}$ or $f_o = 1.05 \text{ MHz}$ depending on the transfer-function slope.

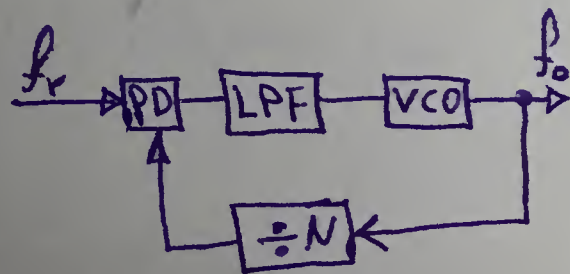Problem 1 For the figure shown aside:

① what is f_o if $f_r = 25 \text{ kHz}$ and $N = 100$?
Ans. $f_o = 2.5 \text{ MHz}$.

② what is f_o if $f_r = 100 \text{ kHz}$ and $N = 35$?
Ans. $f_o = 3.5 \text{ MHz}$.



Problem 2 Use the datasheet of the Motorola CMOS IC MC14046B to design FM modulation and demodulation.