

"1st order cct"

"First order circuits"

1 - The Source-free RC circuit

Consider a series combination of a resistor and an initially charged capacitor, as shown in figure. (1)

assume that at $t=0$

$$V(0) = V_0$$

the energy stored in the capacitor

$$W(0) = \frac{1}{2} C V_0^2$$

Apply KCL

$$i_c + i_R = 0$$

by definition $i_c = C \frac{dv}{dt}$ * $i_R = \frac{V}{R}$

$$C \frac{dv}{dt} + \frac{V}{R} = 0$$

$$\frac{dv}{dt} + \frac{V}{RC} = 0$$

this is a first-order differential equation, we rearrange the item as


$$\frac{dv}{v} = -\frac{1}{RC} dt$$

$$\int \frac{dv}{v} = \int -\frac{1}{RC} dt$$

$$\ln v = -\frac{t}{RC} + \ln A$$

where $\ln A$ is the integration constant, thus
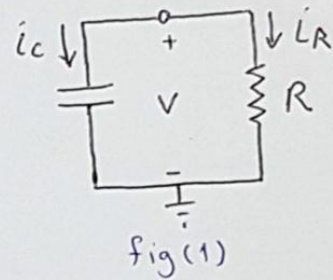
$$\ln v - \ln A = \ln \frac{v}{A} = -\frac{t}{RC}$$



taking powers of e produces

$$v(t) = A e^{-\frac{t}{RC}}$$

but the initial condition $v(0) = A = V_0$, hence $v(t)$


$$v(t) = V_0 e^{-\frac{t}{RC}}$$

$$v(t) = V_0 e^{-\frac{t}{\tau}}$$

where $RC = \tau$

and


$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-\frac{t}{\tau}}$$

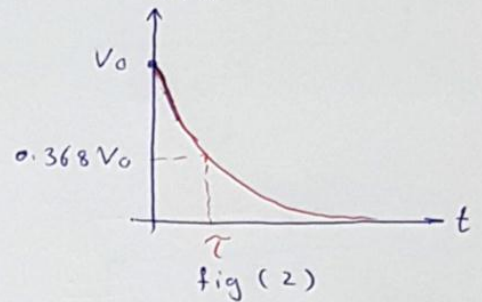


Ex 1: - in fig(3) let $v(0) = 15V$; find v_c , v_x and i_x for $t > 0$

solution:-

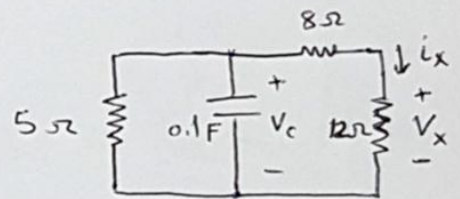① we need to make the circuit shown in fig(3) conform with the standard RC circuit in fig(1)



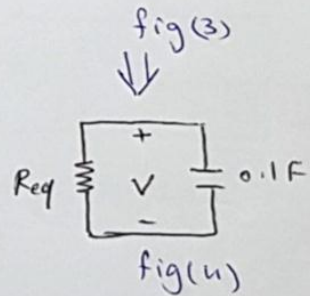fig(4) represent the equivalent ckt. in fig(3)



$$\Rightarrow R_{eq} = (8 + 12) // 5$$

$$= \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\tau = R_{eq} \cdot C = 4 \times 0.1 = 0.4 \text{ s}$$

thus

$$v(t) = v_0 e^{-\frac{t}{\tau}} = 15 e^{-\frac{t}{0.4}} \Rightarrow v = v_c = 15 e^{-2.5t} \text{ V}$$

by voltage division

$$v_x(t) = \frac{12}{12 + 8} v = 0.6 (15 e^{-2.5t}) = 9 e^{-2.5t} \text{ V}$$

$$i_x = \frac{v_x}{12} = \frac{9}{12} e^{-2.5t} \text{ A} = 0.75 e^{-2.5t} \text{ A}$$

Ex 2:- for the fig. (5), the switch has been closed for a long time, and open at $t=0$. Find $v(t)$ for $t \geq 0$, calculate stored energy in the capacitor.

Solution:-

Now, there are two kind of solution.

① for $t < 0$, the switch is closed

\Rightarrow the capacitor is open ct. to dc, fig (6) is illustrate this principle by voltage division the voltage across $R = 9\Omega$ represent $V_C(0)$

$$V_C(0) = \frac{9}{9+3} (20) = 15 \text{ V}$$

$$V_C(0) = V_0 = 15 \text{ V}$$

② for $t > 0$ the switch is open, and the circuit in fig (6) becomes as shown in fig (7)

\Rightarrow Now, the voltage across capacitor will become the source to the ct.

$$R_{eq} = 1 + 9 = 10\Omega$$

$$\tau = R_{eq} \cdot C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

$$\Rightarrow v(t) = V_C(0) e^{-\frac{t}{\tau}} = 15 e^{-\frac{t}{0.2}} \text{ V} = 15 e^{-5t}$$

$$W_C(0) = \frac{1}{2} C V_C^2 = \frac{1}{2} 20 \times 10^{-3} \times 15^2 = 2.25 \text{ J}$$

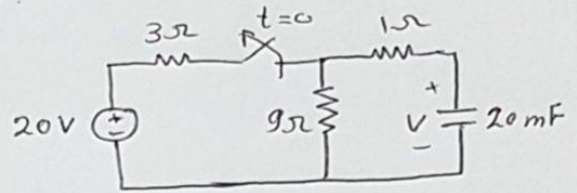


fig (5)

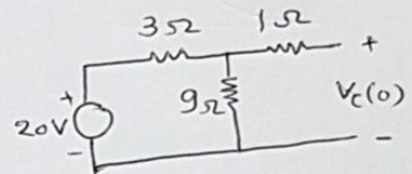


fig (6)

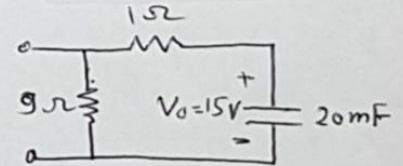


fig (7)

2. The source-free RL circuit.

At $t=0$ we assume that the inductor has an initial current I_0 , or

$$i(0) = I_0$$

energy stored in the inductor as

$$w(t) = \frac{1}{2} L I_0^2$$

Apply KVL

$$V_L + VR = 0$$

$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

Rearranging terms and integrating gives

$$\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

$$\ln i \Big|_{I_0}^{i(t)} = - \frac{Rt}{L} \Big|_0^t \Rightarrow \ln i(t) - \ln I_0 = - \frac{Rt}{L} + 0$$

$$\ln \frac{i(t)}{I_0} = - \frac{R}{L} t$$

$$\Rightarrow i(t) = I_0 e^{-\frac{Rt}{L}}$$

$$\Rightarrow i(t) = I_0 e^{-\frac{t}{\tau}} \quad \text{where } \tau = \frac{L}{R}$$

$$v(t) = i(t) \cdot R = I_0 R e^{-\frac{t}{\tau}}$$

$$P = v_R i = I_0^2 R e^{-\frac{2t}{\tau}}$$

$$w_R(t) = \int_0^t P dt = \int_0^t I_0^2 R e^{-\frac{2t}{\tau}} dt = -\frac{1}{2} \tau I_0^2 R e^{-\frac{2t}{\tau}} \Big|_0^t$$

$$= \frac{1}{2} L I_0^2 (1 - e^{-\frac{2t}{\tau}})$$

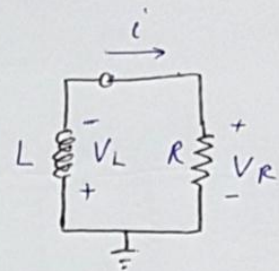


fig (8)

Ex 1: - The switch in the circuit shown in fig (10) has been closed for a long time. At $t=0$ the switch is open. Calculate $i(t)$ for $t > 0$.

Solution

for $t < 0$

the circuit as shown in fig (11)

the inductor became short and from this, you can calculate initial current I_0

$$R_{eq} = 2 + 4 // 12$$

$$= 2 + \frac{4 \times 12}{4 + 12} = 5 \Omega$$

$$i_1 = \frac{40}{5} = 8 \text{ A}$$

and the current $i(t)$ by using current division.

$$i(t) = \frac{12}{12+4} i_1 = 6 \text{ A } t < 0$$

$$i(0) = 6 \text{ A}$$

for $t > 0$ (switch open)

the circuit as shown in fig (12)

$$R_{eq} = (12+4) // 16 = 8 \Omega$$

$$\Rightarrow \tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4} = 0.25 \text{ s}$$

$$i(t) = i(0) e^{-\frac{t}{\tau}} = 6 e^{-4t}$$

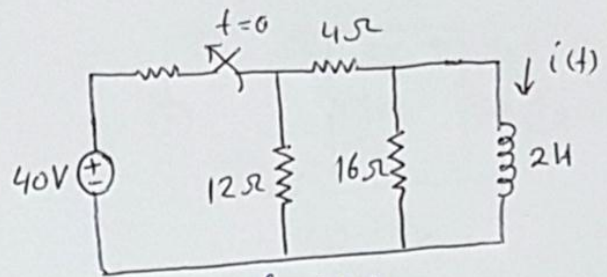


fig (10)

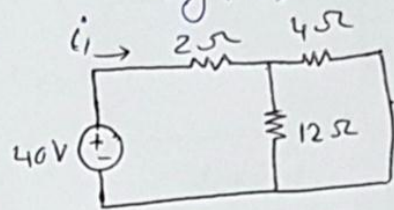


fig (11)

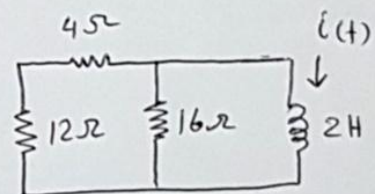


fig (12)

EX 21 - In the circuit shown in fig. (13) find i_0 , V_0 and i for all time. Assuming that the switching was open for a long time

Solution:-

for $t < 0$ (switch is open)

fig (14) illustrate for $t < 0$

from this circuit we find I_0 and V_0
resistor (6) became short and

$$i(t) = \frac{10}{2+3} = 2 \text{ A} = I_0$$

$$V_0(t) = 3i(t) = 6 \text{ V}$$

for $t > 0$ (switch is closed)

fig (15) illustrate for $t > 0$

$$R_{th} = 3 // 6 = \frac{3 \times 6}{3+6} = 2 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{2}{2} = 1$$

$$i(t) = i(0) e^{-\frac{t}{\tau}} = 2 e^{-t} \text{ A}$$

$$V_0 = -V_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}$$

$$i_0(t) = \frac{V}{L} = -\frac{2}{3} e^{-t} \text{ A}$$

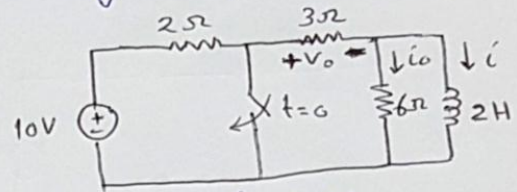


fig. (13)

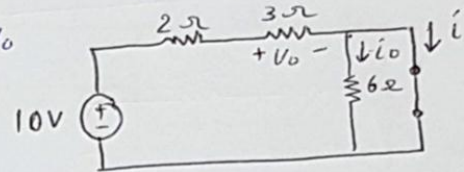


fig (14)

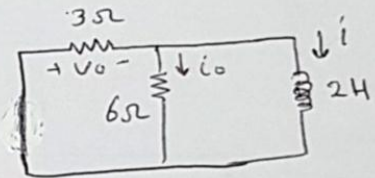



fig (15)

3. Singularity functions

The Three most widely used singularity functions in circuit analysis are *unit step*; *unit impulse* and *unit ramp* functions.

① unit step function

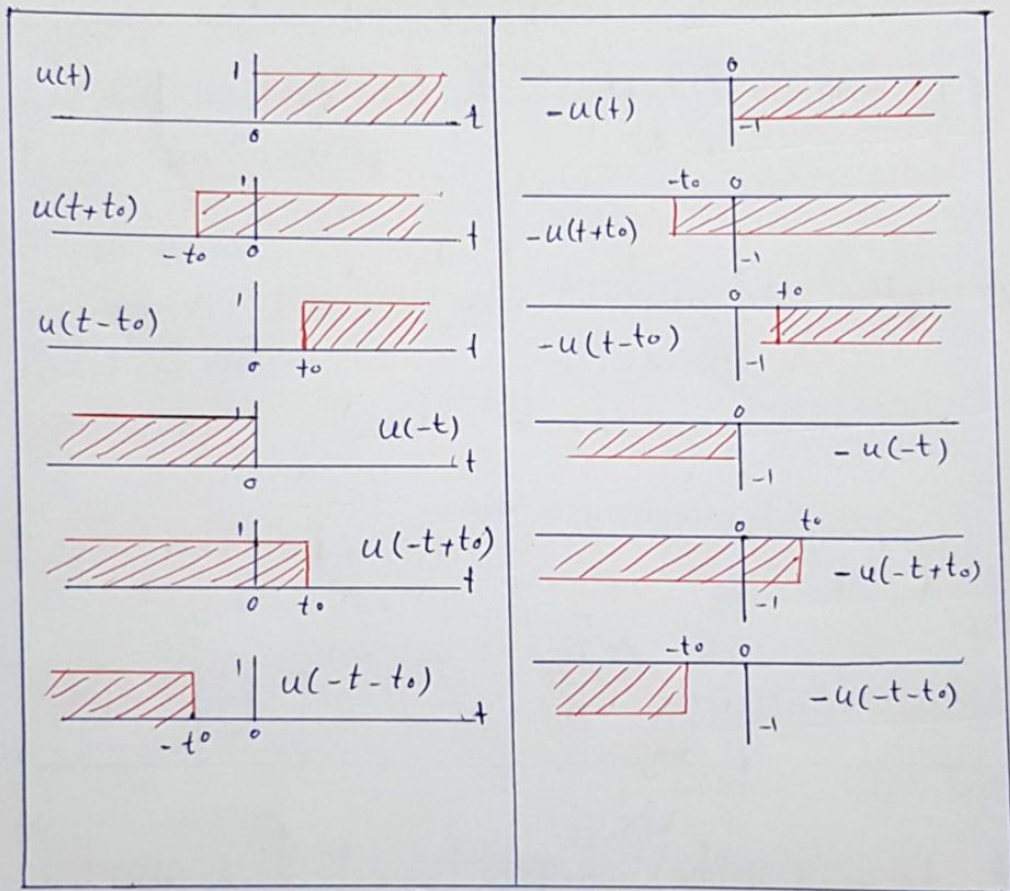in mathematical terms
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$




this table represent all type of unit step.
table (1)

② unit impulse

The derivative of a unit step function $u(t)$ is the unit impulse function $\delta(t)$ which we write as:
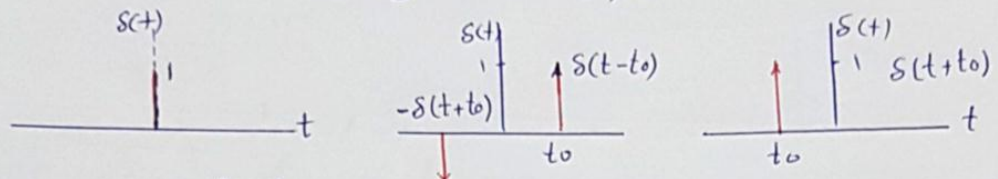
$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0 & t < 0 \\ \text{undefined} & t = 0 \\ 0 & t > 0 \end{cases}$$




and all kind of unit step in table (1) can be derivative to get unit impulse.

③ unit ramp

The integrate of a unit step function $u(t)$ is the unit ramp function $r(t)$

$$r(t) = \int_{-\infty}^t u(t) dt = t u(t)$$
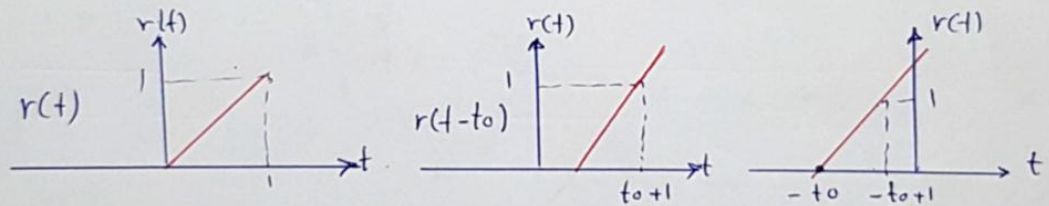
$$r(t) = \begin{cases} 0 & t \leq 0 \\ t & t \geq 0 \end{cases}$$



and all kind of unit step in table (1) can be integrate to get unit ramp.