

Sheet No. 2

Problems

1-.For the network in Fig. 1:

a. Determine currents I_4 and I_s and voltage V_2 .

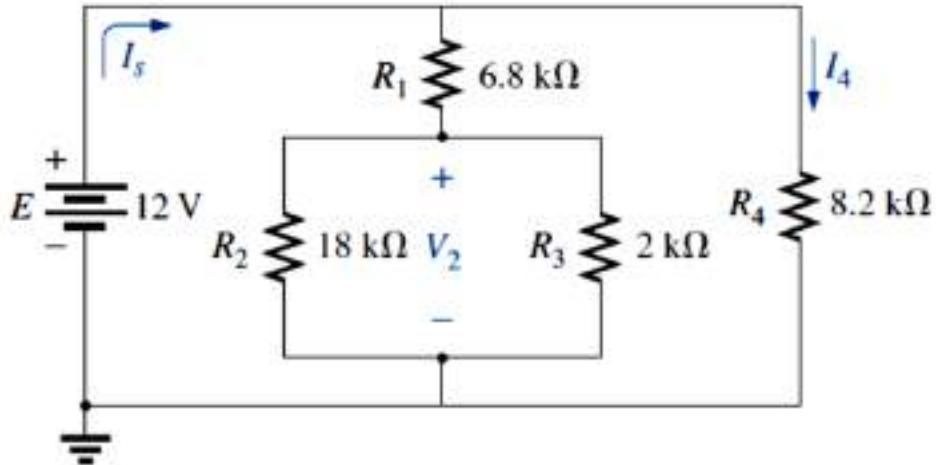


Fig. 1

Answer: $I_4 = 1.64 \text{ mA}$, $I_s = 2.86 \text{ mA}$, $V_2 = 2.51 \text{ V}$

2- Find the indicated currents and voltages for the network in Fig. 2.

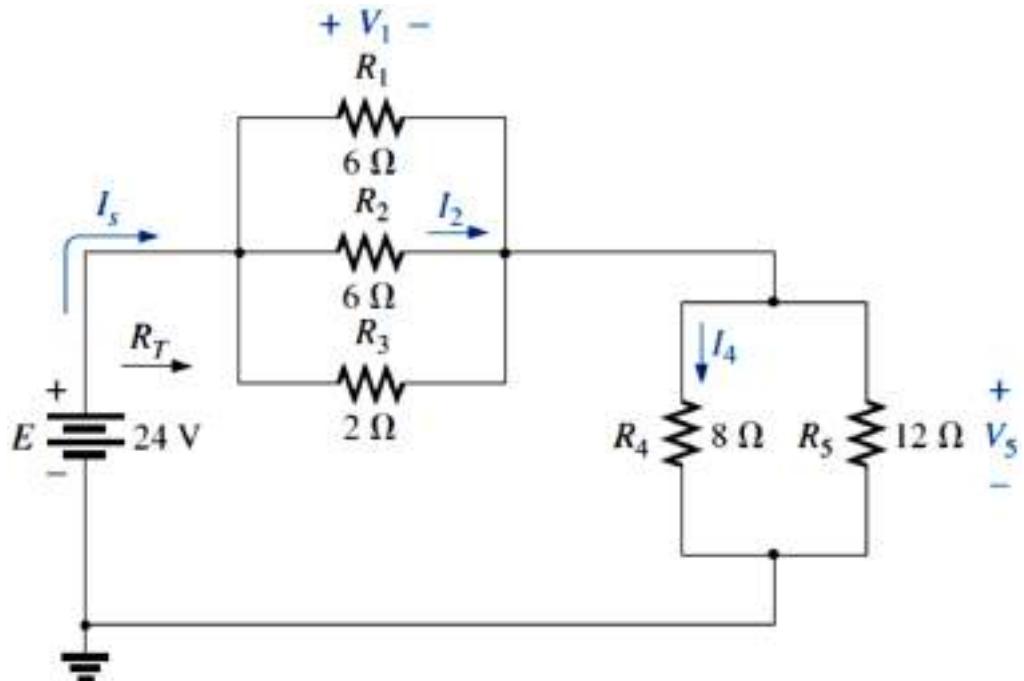


Fig. 2

Answer: $I_s = 4 \text{ A}$, $V_1 = 4.8 \text{ V}$, $V_5 = 19.2 \text{ V}$, $I_2 = 0.8 \text{ A}$, $I_4 = 2.4 \text{ A}$

3- Find the indicated currents and voltages for the network in Fig. 3.


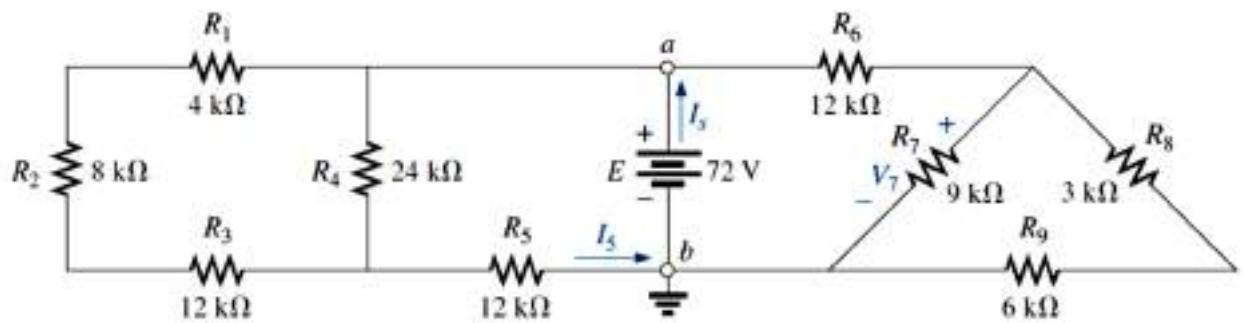



Fig. 3

Answer: $I_s = 7.35\text{ mA}$, $V_7 = 19.6\text{ V}$, $I_2 = 3\text{ mA}$

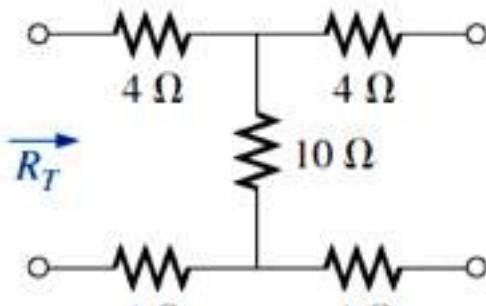
4- Determine R_{eq} for the networks in Fig. 4




(a)

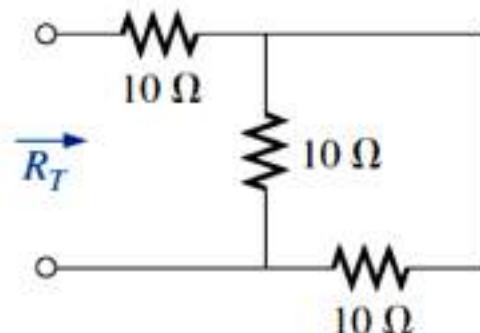

(b)

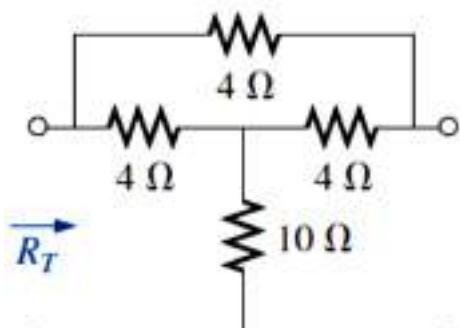

(c)

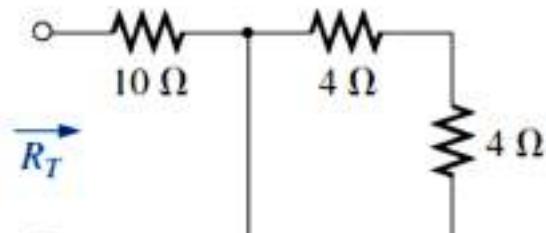

(d)

Fig. 4

Answer: (a) 18Ω , (b) 15Ω , (c) 12.67Ω , (d) 10Ω ,

5- For the network in Fig. 5:

a. Determine the currents I_s , I_1 , I_3 , and I_4 .

b. Calculate V_{bc} .

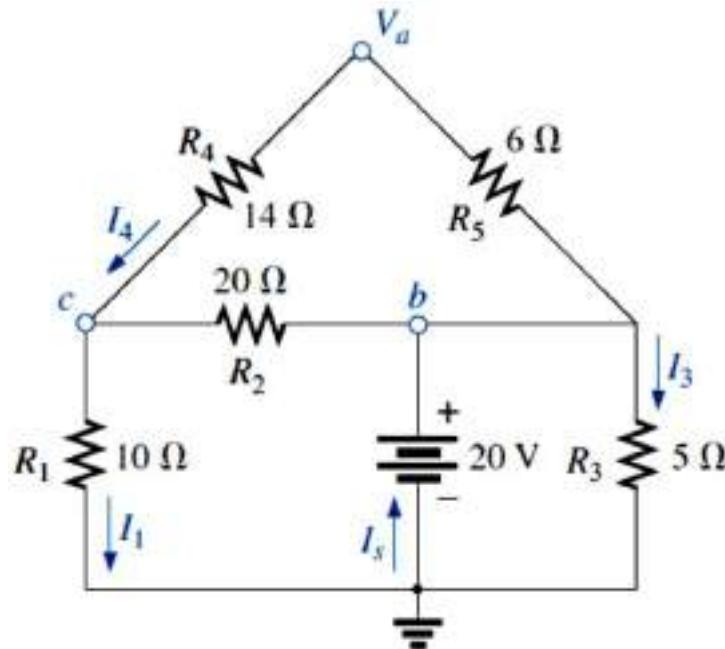


Fig. 5

Answer: $I_s = 5 \text{ A}$, $I_1 = 1 \text{ A}$, $I_3 = 4 \text{ A}$, $I_4 = 0.5 \text{ A}$, $V_{bc} = 10 \text{ A}$,

6- For the network in Fig. 6. Find R_{eq} , V_1 and V_2

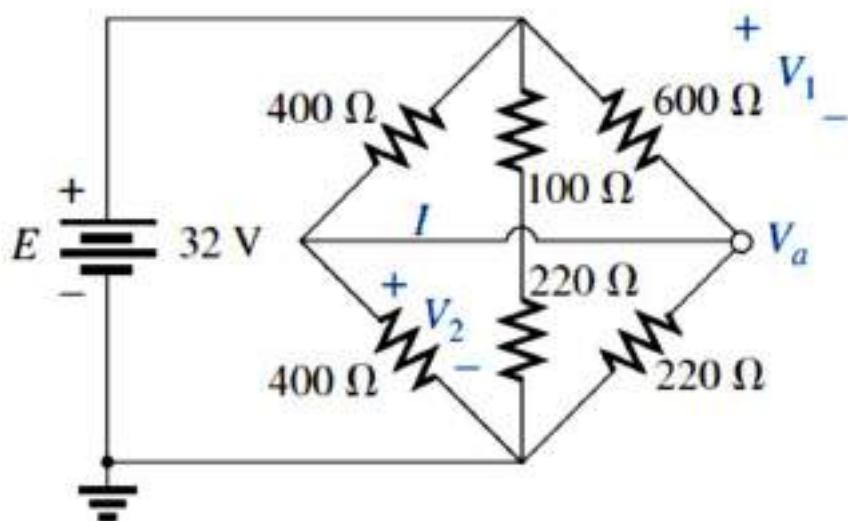


Fig. 6

Answer: $R_{eq} = 174.12 \Omega$, $V_1 = 20.11 \text{ V}$, $V_2 = 11.89 \text{ V}$

7- For the network in Fig. 7. Find I , I_4 , I_6 and I_{10}

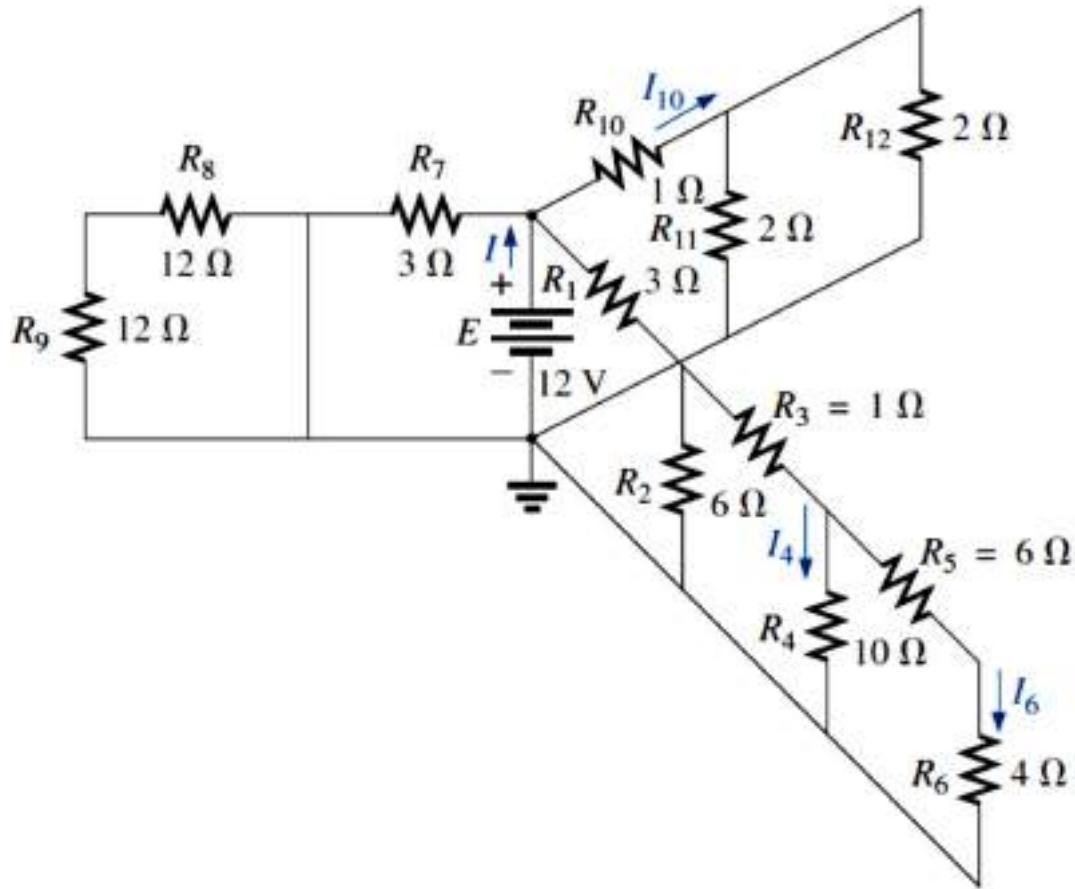


Fig. 7

Answer: $I = 12 \text{ A}$, $I_4 = 0.5 \text{ A}$, $I_6 = 0.5 \text{ A}$, $I_{10} = 6 \text{ A}$

8- For the network in Fig. 8, determine v_x and the power absorbed by the 12Ω resistor.

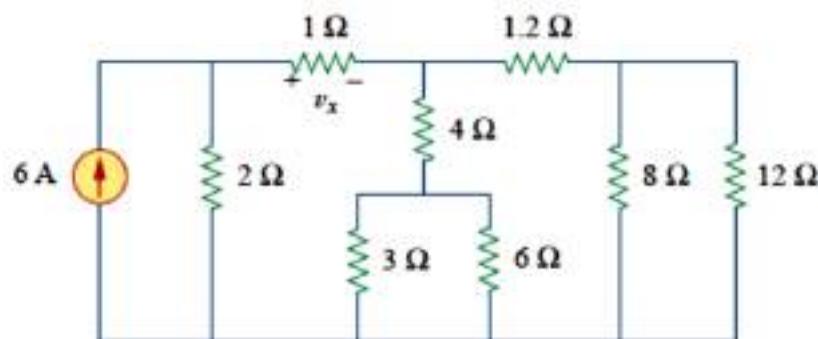


Fig. 8

Answer: $v_x = 2 \text{ V}$, $P = 1.92 \text{ W}$

9- For the network in Fig.9 Find the current, voltage and power associated with the $20\text{ k}\Omega$ resistor.

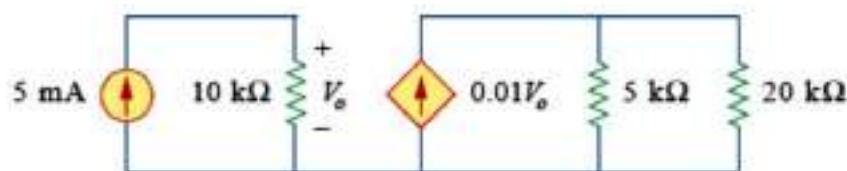


Fig. 9

Answer: $I_{20} = 0.1\text{ A}$, $V_{20} = 2\text{ kV}$, $P_{20} = 0.2\text{ kW}$

10- For the network in Fig.10, Find i_1 through i_4

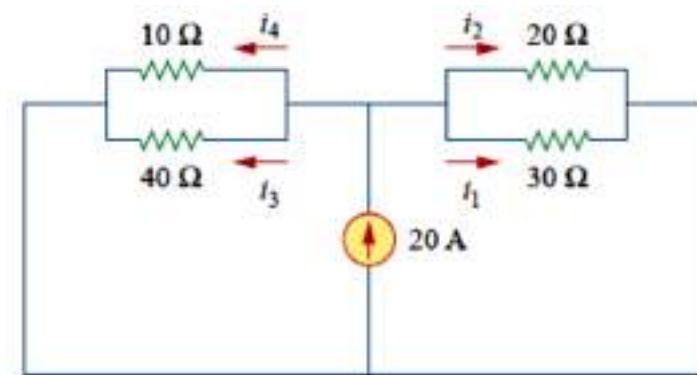


Fig. 10

Answer: $i_1 = 3.2\text{ A}$, $i_2 = 4.8\text{ A}$, $i_3 = 2.4\text{ A}$, $i_4 = 9.6\text{ A}$