

- 2.3** A bar of silicon is 4 cm long with a circular cross section. If the resistance of the bar is 240Ω at room temperature, what is the cross-sectional radius of the bar?

$$Ans: r = 0.1843m$$

- 2.12** In the circuit of Fig. 2.76, obtain v_1 , v_2 , and v_3 .


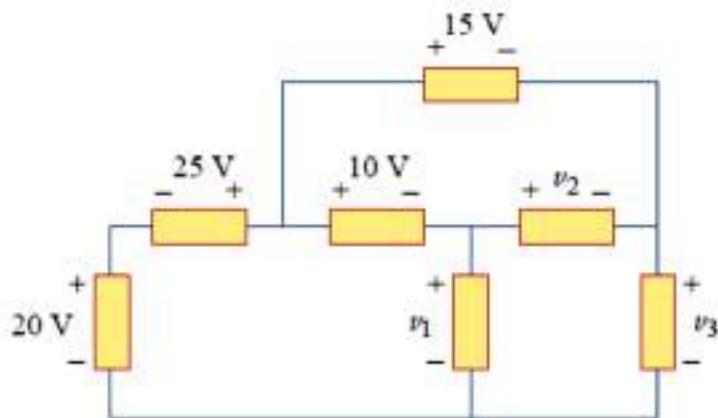


Figure 2.76

For Prob. 2.12.

$$Ans: v_1 = 35V, v_2 = 5V, v_3 = 30V$$

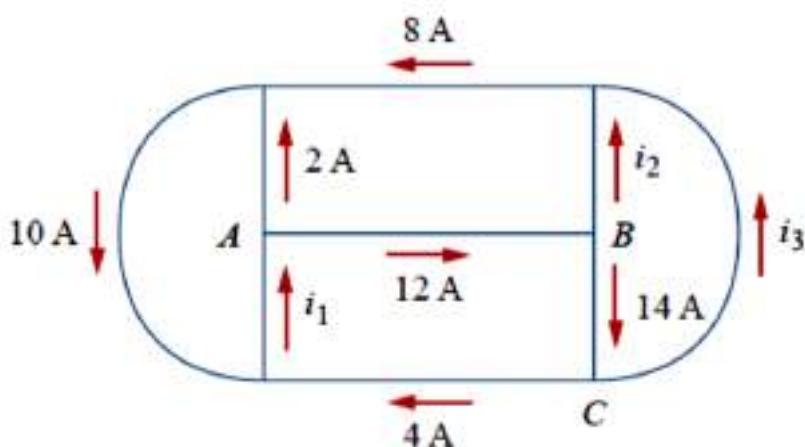- 2.9** Find i_1 , i_2 , and i_3 in Fig. 2.73.



$$Ans: i_1 = 14A, i_2 = -2A, i_3 = 10A$$

2.10 Determine i_1 and i_2 in the circuit of Fig. 2.74.

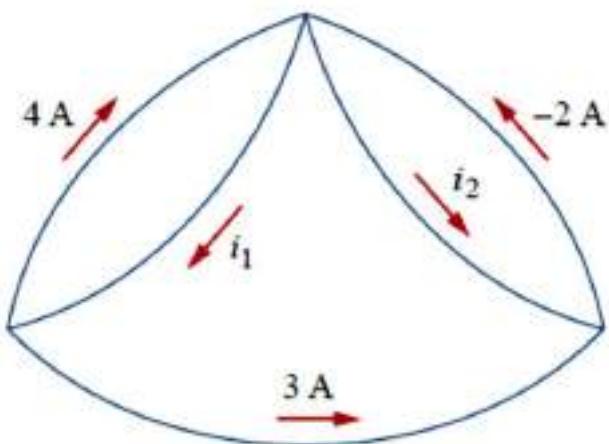


Figure 2.74

For Prob. 2.10.

$$Ans: i_1 = 7A, i_2 = -5A$$

2.14 Given the circuit in Fig. 2.78, use KVL to find the branch voltages V_1 to V_4 .

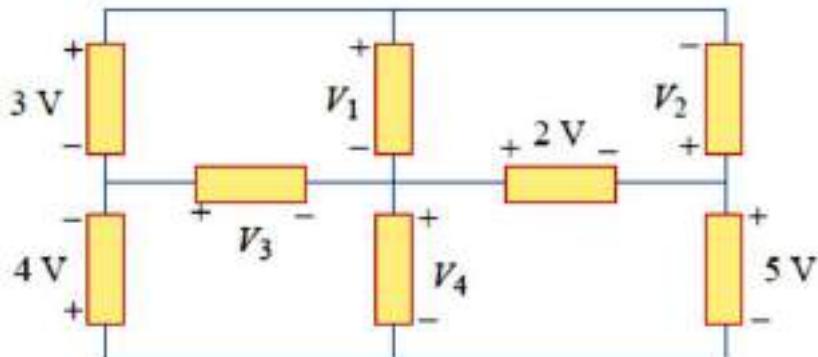


Figure 2.78

For Prob. 2.14.

$$Ans: V_1 = -8V, V_2 = 6V, V_3 = -11V, V_4 = 7V$$

2.15 Calculate v and i_x in the circuit of Fig. 2.79.

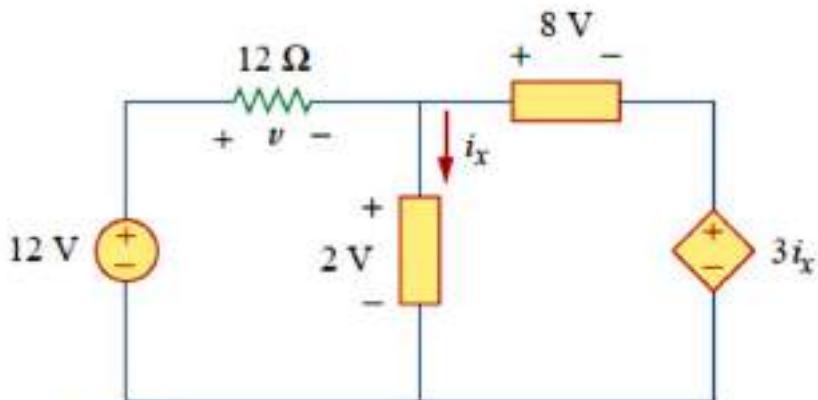


Figure 2.79

For Prob. 2.15.

$$Ans: v = 10V, i_x = -2A$$

2.16 Determine V_o in the circuit of Fig. 2.80.

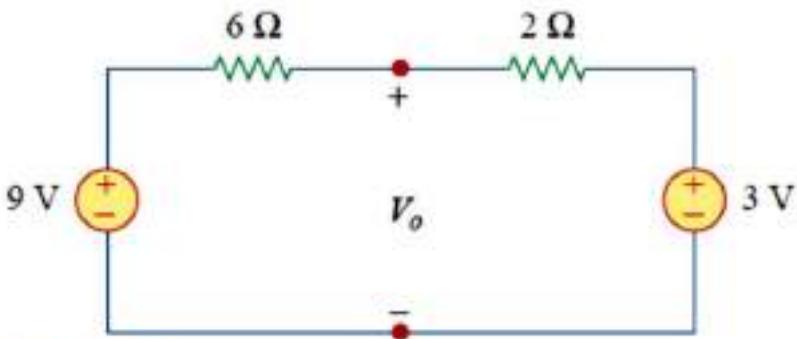


Figure 2.80

For Prob. 2.16.

$$Ans: v_o = 4.5V$$

2.17 Obtain v_1 through v_3 in the circuit of Fig. 2.81.

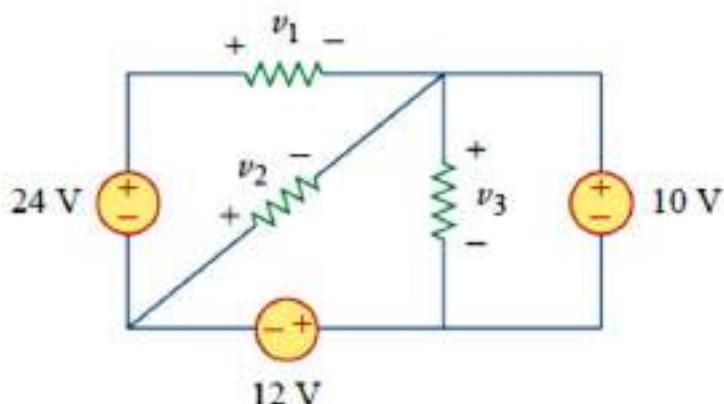


Figure 2.81

For Prob. 2.17.

$$Ans: v_1 = 2V, v_2 = -22V, v_3 = 10V$$

2.18 Find I and V_{ab} in the circuit of Fig. 2.82.

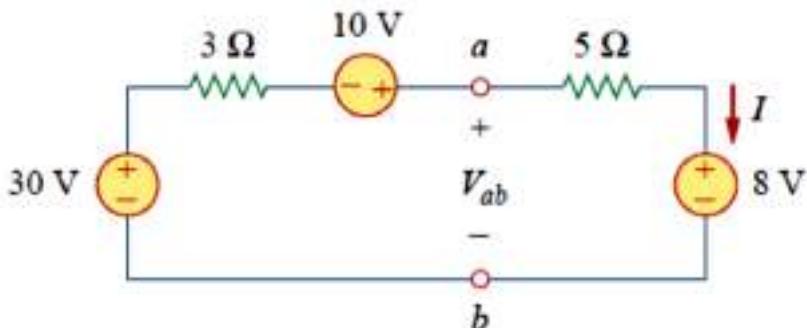


Figure 2.82

For Prob. 2.18.

$$Ans: I = 4A, V_{ab} = 28V$$

- 2.19** From the circuit in Fig. 2.83, find I , the power dissipated by the resistor, and the power absorbed by each source.

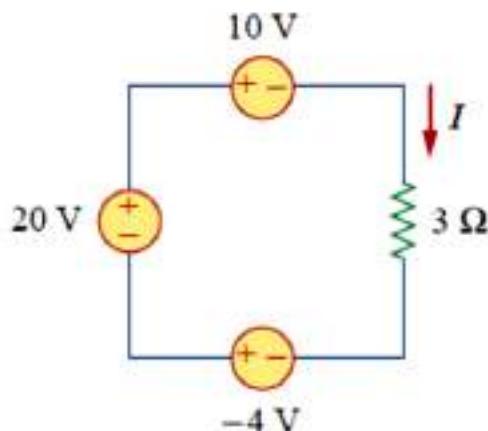


Figure 2.83
For Prob. 2.19.

Ans: $I = -2A$, $P_{3\Omega} = 12W$, $P_{12V} = -24W$, $P_{10V} = 20W$, $P_{8V} = 16W$

- 2.20** Determine i_o in the circuit of Fig. 2.84.

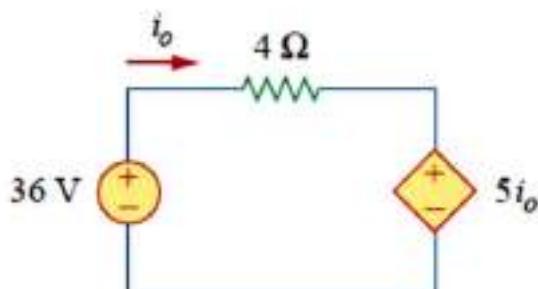


Figure 2.84
For Prob. 2.20.

Ans: $i_o = 4A$

2.21 Find V_x in the circuit of Fig. 2.85.

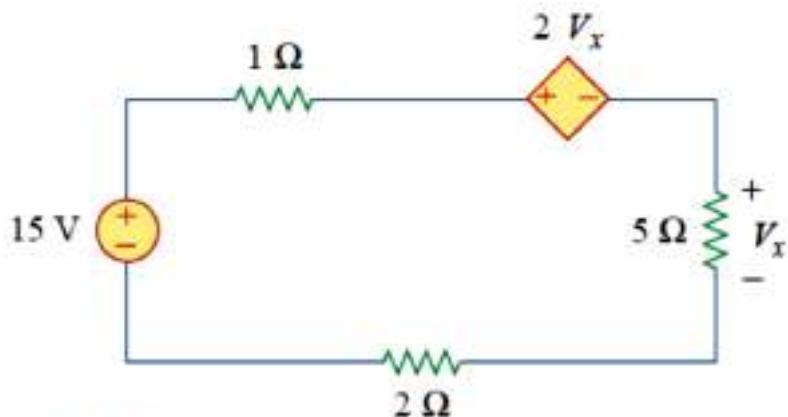


Figure 2.85

For Prob. 2.21.

$$Ans: V_x = 4.167V$$

2.22 Find V_o in the circuit of Fig. 2.86 and the power dissipated by the controlled source.

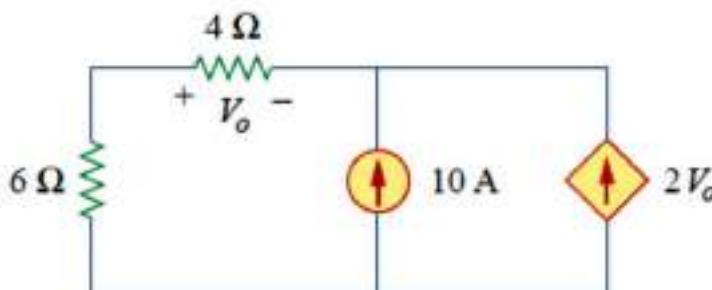


Figure 2.86

For Prob. 2.22.

$$Ans: V_o = -4.444V, P = 98.75$$

- 2.23** In the circuit shown in Fig. 2.87, determine v_x and the power absorbed by the $12\text{-}\Omega$ resistor.

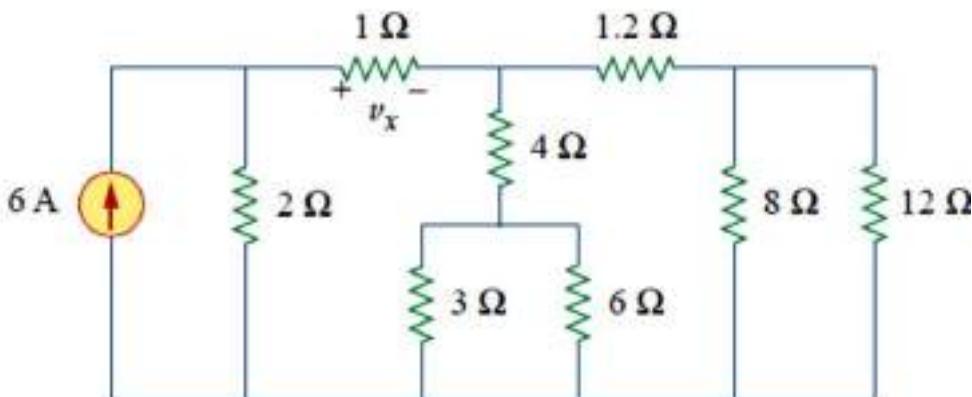


Figure 2.87

For Prob. 2.23.

$$Ans: V_x = 2V, P = 1.92W$$

- 2.25** For the network in Fig. 2.89, find the current, voltage, and power associated with the $20\text{-k}\Omega$ resistor.

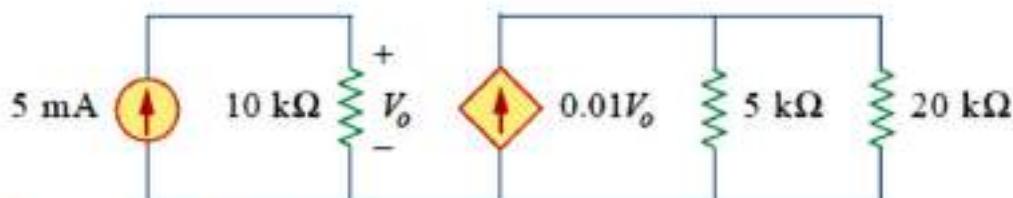


Figure 2.89

For Prob. 2.25.

$$Ans: I_{20} = 0.1A, V_{20} = 2kV, P_{20} = 0.2kW$$

- 2.26** For the circuit in Fig. 2.90, $i_o = 2 \text{ A}$. Calculate i_x and the total power dissipated by the circuit.

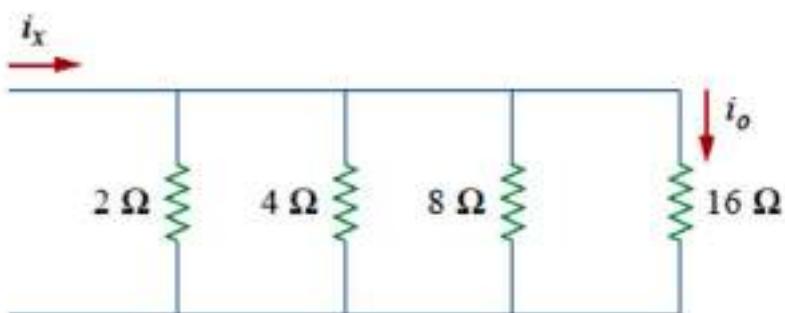


Figure 2.90
For Prob. 2.26.

$$\text{Ans: } i_x = 30V, P = 960W$$

- 2.31** For the circuit in Fig. 2.95, determine i_1 to i_5 .

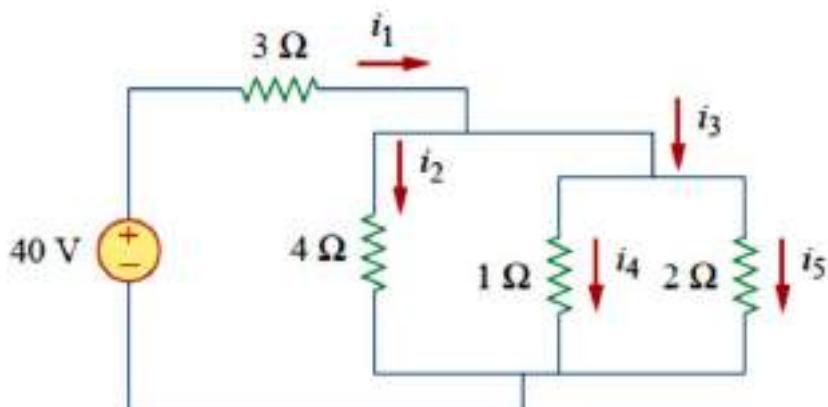


Figure 2.95
For Prob. 2.31.

$$\text{Ans: } i_1 = 11.2A, i_2 = 1.6A, i_3 = 9.6A, i_4 = 6.4A, i_5 = 3.2A$$

2.32 Find i_1 through i_4 in the circuit of Fig. 2.96.

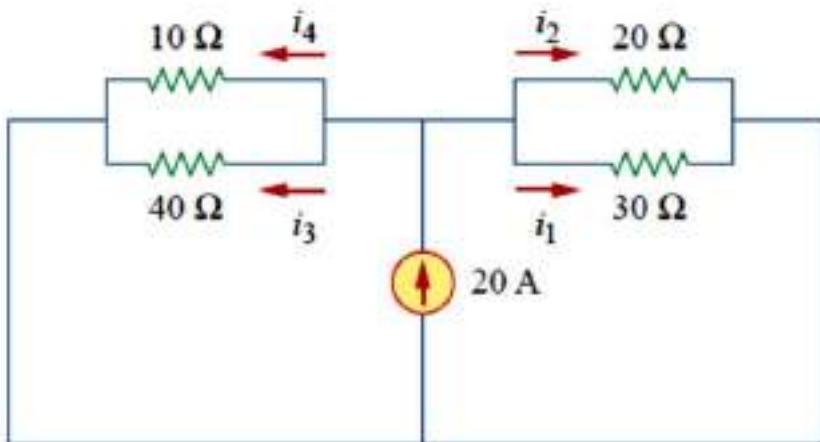


Figure 2.96

For Prob. 2.32.

Ans: $i_1 = 3.2A, i_2 = 4.8A, i_3 = 2.4A, i_4 = 9.6A$

2.35 Calculate V_o and I_o in the circuit of Fig. 2.99.

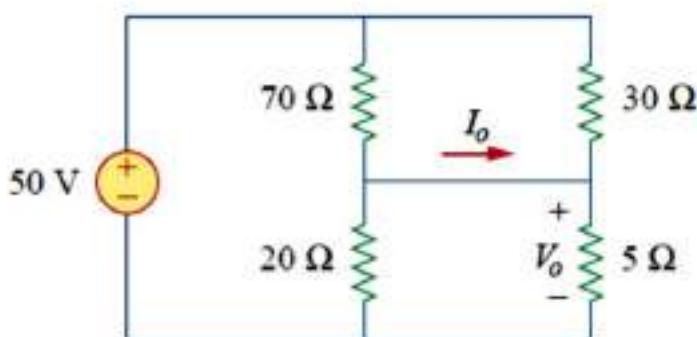


Figure 2.99

For Prob. 2.35.

Ans: $V_o = 8V, i_o = 0.2A$

2.36 Find i and V_o in the circuit of Fig. 2.100.

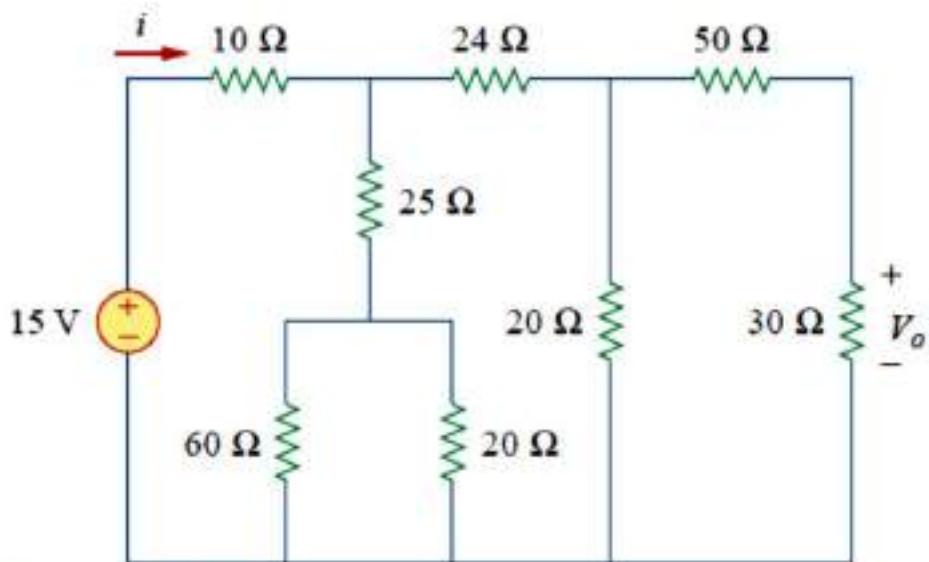


Figure 2.100

For Prob. 2.36.

$$Ans: i = 0.5A, V_o = 1.5A$$

2.37 Find R for the circuit in Fig. 2.101.

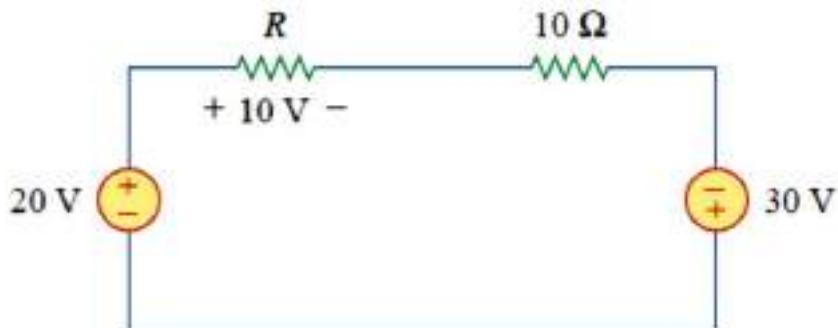


Figure 2.101

For Prob. 2.37.

$$Ans: R = 2.5\Omega$$

2.38 Find R_{eq} and i_o in the circuit of Fig. 2.102.

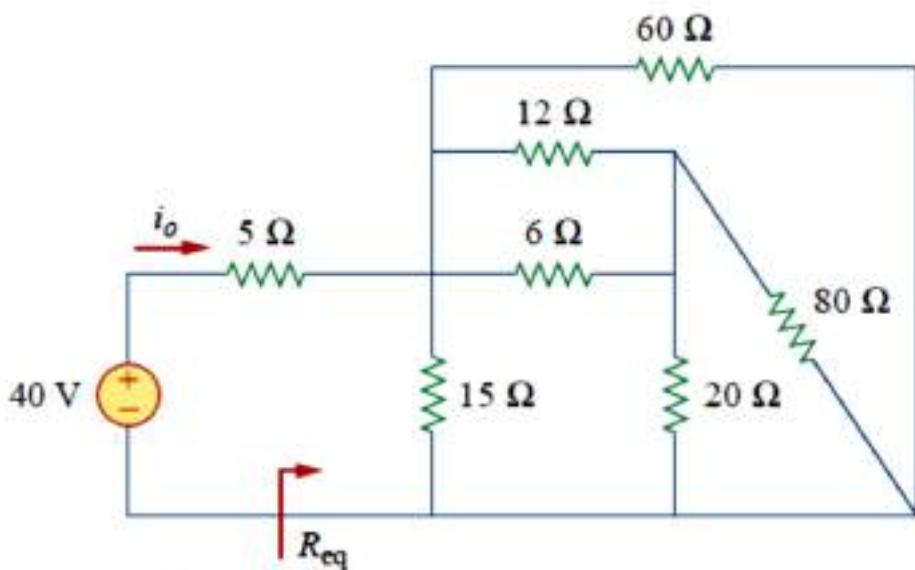


Figure 2.102
For Prob. 2.38.

$$Ans: R_{eq} = 12.5\Omega, i_o = 3.2A$$

2.41 If $R_{eq} = 50 \Omega$ in the circuit of Fig. 2.105, find R .


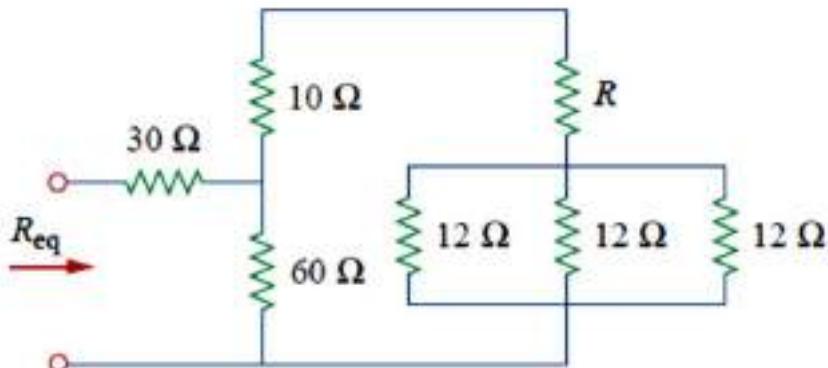



Figure 2.105
For Prob. 2.41.

$$Ans: R = 16\Omega$$

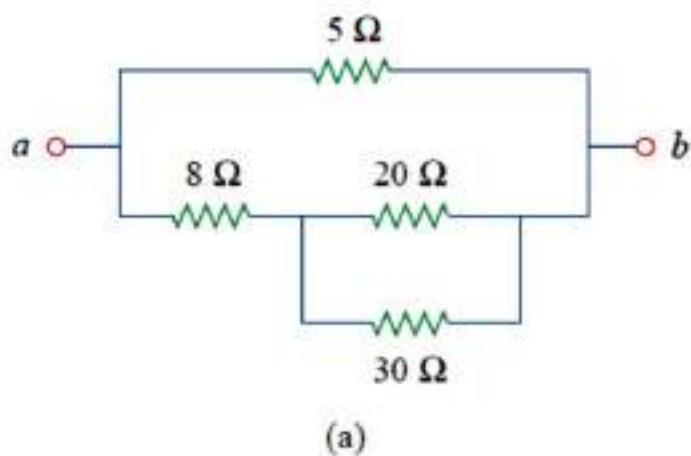- 2.42** Reduce each of the circuits in Fig. 2.106 to a single resistor at terminals $a-b$.



(a)

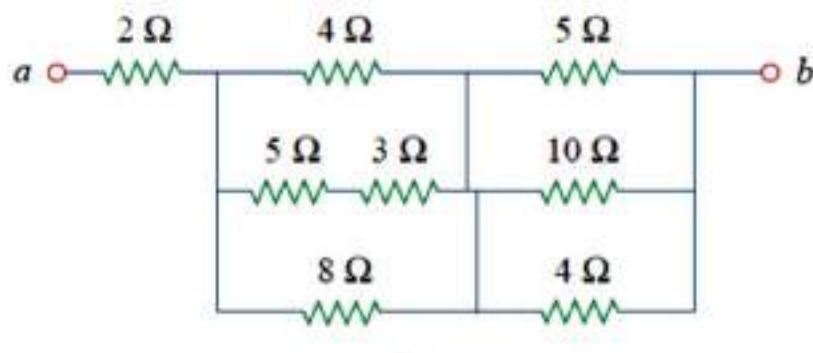


(b)

Figure 2.106


For Prob. 2.42.

Ans: (a) $R_{ab} = 4\ \Omega$, (b) $R_{ab} = 5.818\ \Omega$

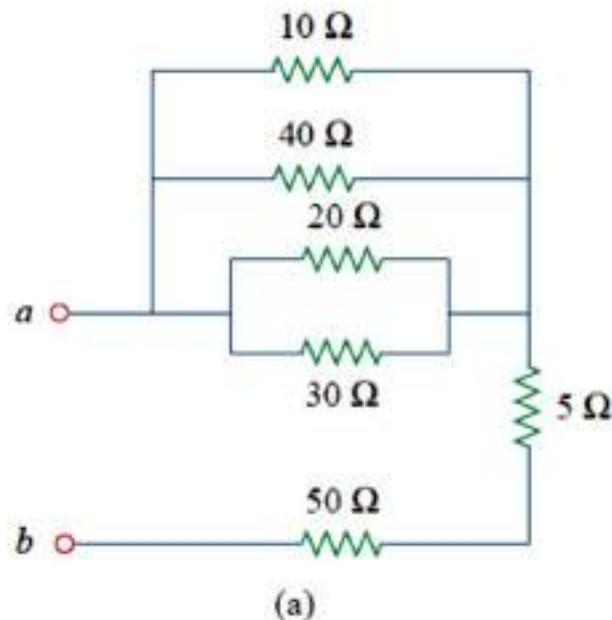- 2.45** Find the equivalent resistance at terminals *a-b* of each circuit in Fig. 2.109.



(a)

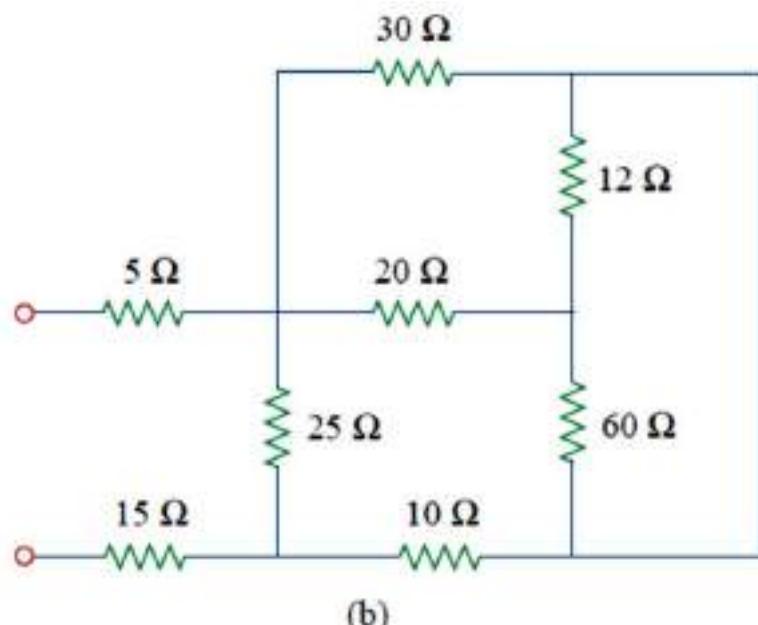

(b)

Figure 2.109
For Prob. 2.45.

Ans: (a) $R_{ab} = 59.8\ \Omega$, (b) $R_{ab} = 32.5\ \Omega$

