

**Department of Communications
Engineering**

Communication Systems

Third Year Class

Dr. Montadar Abas Taher

montadar@ieee.org

Lecture 14

**Super heterodyne Receivers III,
Image Problem**


Image Problem

The main disadvantage of superheterodyne receiver is the image problem.

* The heterodyne selects two frequencies not only one.
 * These two frequencies mirrored about the LO, hence they are image to each other.


* Hence the main purpose of the RF BPF is to reject the image signal.

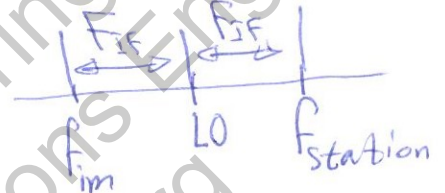* The IF-filter will also attenuate the image frequency.



There are two cases for the image frequency (F_{Im}):

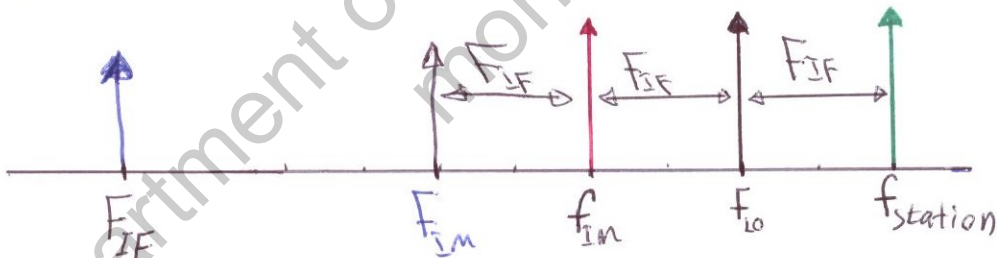
① Low side injection ($F_{LO} < F_{station}$)



$$F_{LO} = F_{station} - F_{IF}$$

$$F_{image} = F_{Im} = F_{station} - 2F_{IF} \iff F_{LO} - F_{IF} = F_{Im}$$

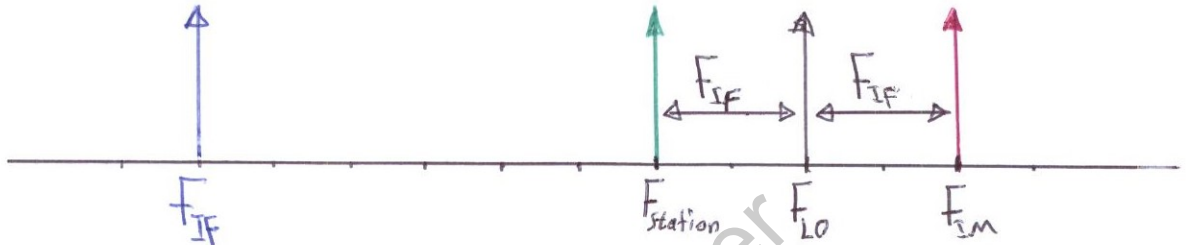② High side injection ($F_{LO} > F_{station}$)



$$F_{LO} = F_{station} + F_{IF}$$

$$F_{IM} = F_{station} + 2F_{IF}$$

$$F_{IM} = F_{LO} + F_{IF} = F_{station} + 2F_{IF}$$

Summary

Down-side injection $L O < F_c$

UP-side injection $L O > F_c$

$$F_{LO} = F_c - F_{IF}$$

$$F_{LO} = F_c + F_{IF}$$

$$F_{IM} = F_{LO} - F_{IF}$$

$$F_{IM} = F_{LO} + F_{IF}$$


$$F_{IM} = F_c - 2F_{IF}$$

$$F_{IM} = F_c + 2F_{IF}$$


Always IMAGE frequency $\pm 2F_{IF}$

AM Broadcast Stations

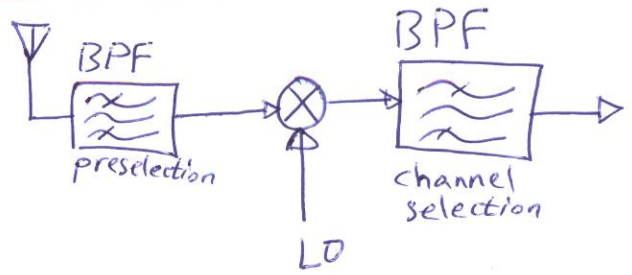AM Band: [530 - to - 1700] kHz
 standard $F_{IF} = 455$ kHz



Often Image is inside

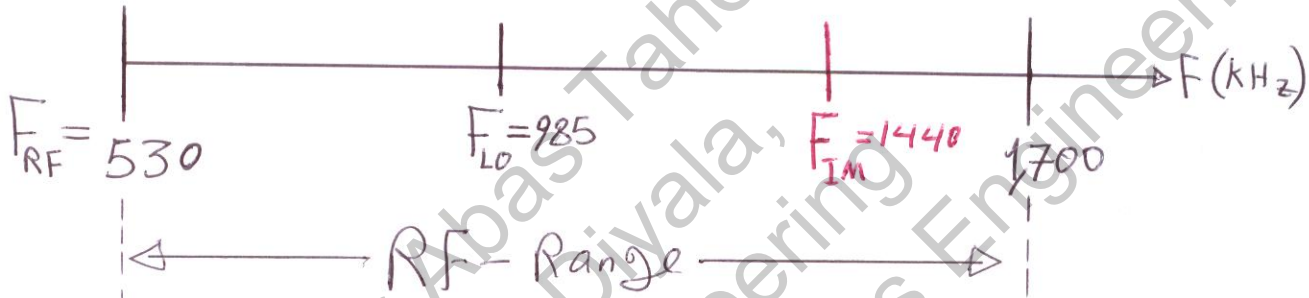

* High Q preselector filter is needed.

EX. For example, $F_{RF} = 530$ kHz, $F_{IM} = 1440$ kHz with high LO. Always we have two solutions;

$$\textcircled{1} \left. \begin{aligned} F_{LO} = F_{RF} - F_{IF} &= 530 - 455 = 75 \text{ kHz} \\ F_{LO} = 1700 - 455 &= 1245 \text{ kHz} \end{aligned} \right\} F_{LO} \text{ ratio} = \frac{1245}{75} \approx 16$$

$$\textcircled{2} \left. \begin{aligned} F_{LO} = F_{RF} + F_{IF} &= 530 + 455 = 985 \text{ kHz} \\ F_{LO} = 1700 + 455 &= 2155 \text{ kHz} \end{aligned} \right\} F_{LO} \text{ ratio} = \frac{2155}{985} \approx 2$$


Thus, the second case is easier to implement.

Department of Communications Engineering
 University of Diyala, Iraq
 Dr. Montazar Abbas Taher

FM-Broadcast Stations

RF Band : [88 - to - 108] MHz


Standard $F_{IF} = 10.7$ MHz

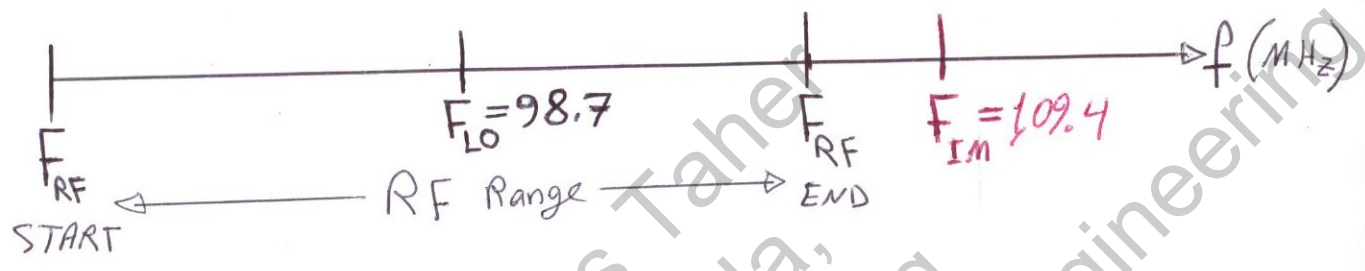

* F_{IM} is always out of band

$$F_{IM} = F_{RF} + 2 F_{IF}$$

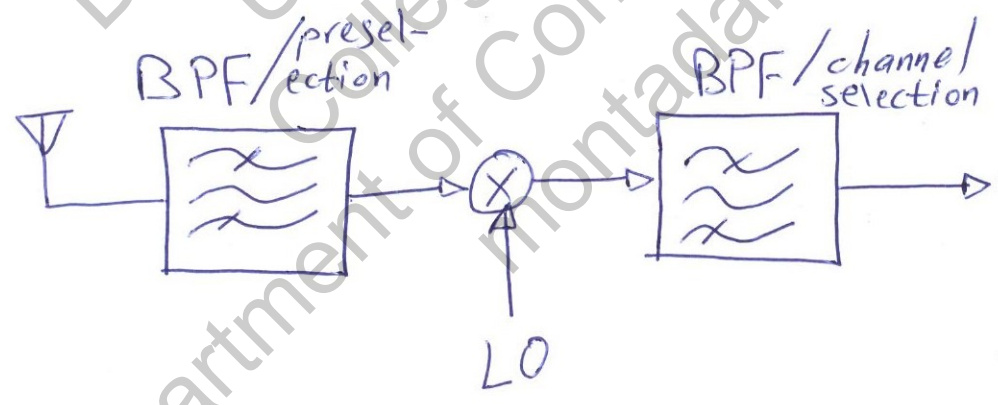even with very low F_{LO} , F_{IM} is out of band.



EX. consider $F_{IF} = 10.7 \text{ MHz}$

There are two cases

① $F_{LO} < F_{IF}$

$$\left. \begin{aligned} F_{RF} + F_{LO} &= F_{IF} \quad \text{--- (1)} \\ F_{IM} - F_{LO} &= F_{IF} \quad \text{--- (2)} \end{aligned} \right\}$$

Lower end RF-frequency = 0.53 MHz
 Higher end RF-frequency = 1.7 MHz

$F_{LO} = 10.17 \text{ MHz}$ (Eq. (1))
 Lower


$F_{LO} = 9 \text{ MHz}$ (Eq. (2))
 Higher

$F_{IM} - F_{LO} = F_{IF} \Rightarrow F_{IM} = F_{IF} + F_{LO} = 10.7 + 10.17 = 20.87 \text{ MHz}$
 Lower

$F_{IM} = F_{IF} + F_{LO} = 10.7 + 9 = 19.7 \text{ MHz}$
 Higher

② $F_{LO} > F_{IF}$ $F_{LO} - F_{RF} = F_{IF}$ --- (1) & $F_{IM} - F_{LO} = F_{IF}$ --- (2)

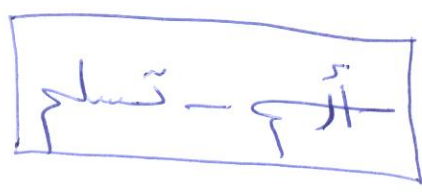$F_{RF_{lower}} = 0.53 \text{ MHz}$ & $F_{RF_{higher}} = 1.7 \text{ MHz}$




$F_{LO_{lower}} = F_{IF} + F_{RF_{lower}} = 10.7 + 0.53 = 11.23 \text{ MHz}$

$F_{LO_{higher}} = F_{IF} + F_{RF_{higher}} = 10.7 + 1.7 = 12.4 \text{ MHz}$

$F_{IM_{lower}} = F_{IF} + F_{LO_{lower}} = 10.7 + 11.23 = 21.93 \text{ MHz}$

$F_{IM_{higher}} = F_{IF} + F_{LO_{higher}} = 10.7 + 12.4 = 23.1 \text{ MHz}$

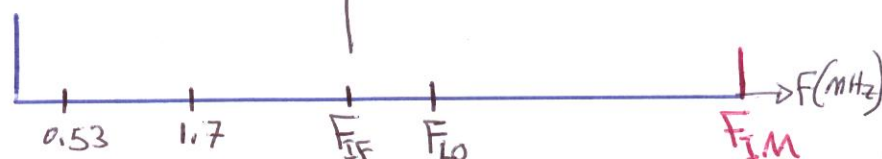NOTE: Higher LO frequency \rightarrow better image rejection.




Dual Conversion Receiver ∞

82


Dr. Montadar Abbas Taher
University of Diyala,
College of Engineering
Department of Communications Engineering
montadar@ieee.org

Dual Conversion Receiver

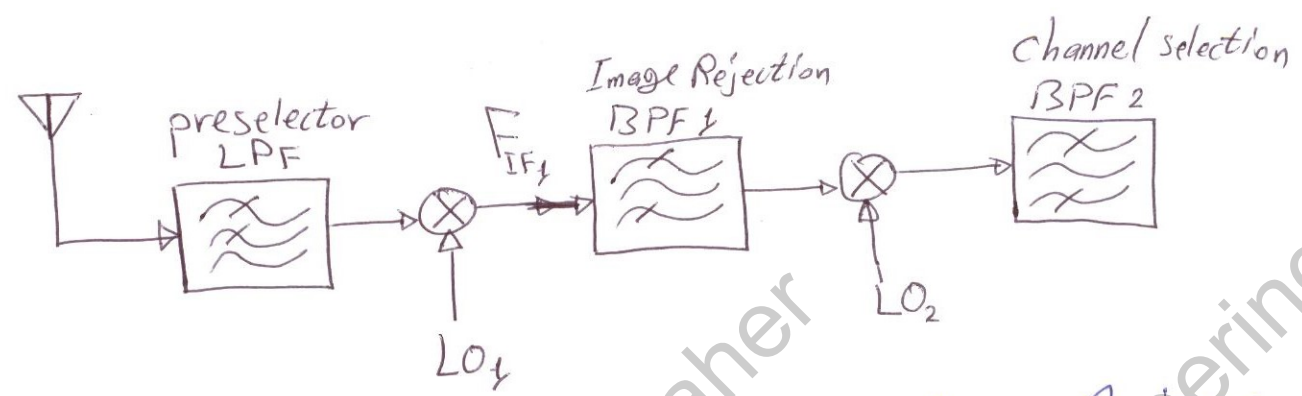

The dual conversion receiver can be used for good image frequency rejection.

The Cellphone Receiver

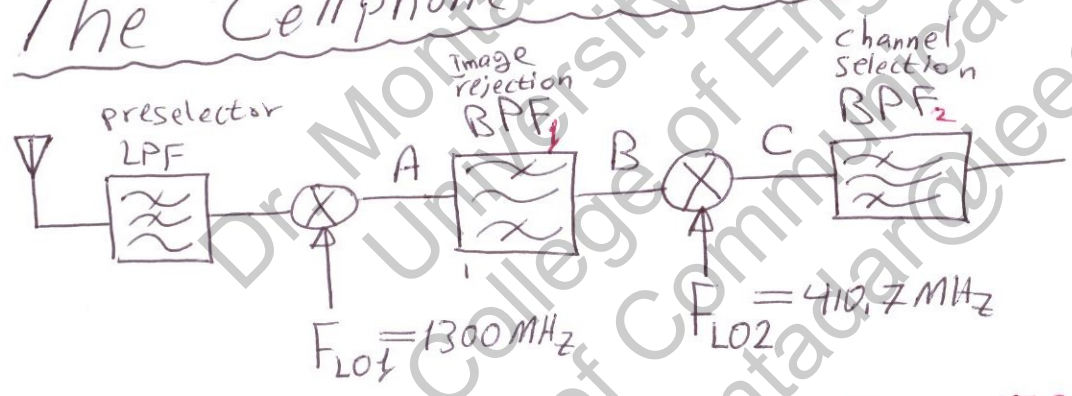

* At the antenna: $F_{RF} = 900 \text{ MHz}$, $F_{IM} = 1700 \text{ MHz}$
 * At point (A) 400 MHz & 2100 MHz , the 2100 MHz filter-out by BPF_1

$$F_{IF} = 400 \text{ MHz} \quad \& \quad F_{IM} = 410.7 \text{ MHz}$$

* At point (B) $F_{IF} = 400 \text{ MHz}$, $F_{IM} = 421.4 \text{ MHz}$

* At point (C) 10.7 MHz & 810.7 MHz .

$$F_{IF2} = F_{LO2} - F_{IF1}, \text{ the sum term will be removed by } BPF_2$$