

Transistor

Example (1)

Transistor 2N3055 has the following parameters: maximum power dissipation at $25^{\circ}\text{C} = 115\text{ mW}$, and derating factor = $0.66\text{ 281 mW}/^{\circ}\text{C}$. This transistor is used at 78°C . Draw its new maximum power dissipation curve.

Solution:-

Temperature increment = $78^{\circ}\text{C} - 25^{\circ}\text{C} = 53^{\circ}\text{C}$

Power dissipation of transistor = $0.66\text{ 281 mW}/^{\circ}\text{C} \times 53^{\circ}\text{C} = 35\text{ mW}$

New maximum power dissipation = $115\text{ mW} - 35\text{ mW} = 80\text{ mW}$

$$P = 80 \text{ mW} = V_{CE} \times I_C \text{ or } I_C = \frac{P_{Cmax}}{V_{CE}}$$

$$\text{When } V_{CE} = 60 \text{ V, then } I_C = \frac{80 \text{ mW}}{60} = 1.3 \text{ mA (point 1 in figure (1))}$$

To get some other points with different V_{CE} values:

$$V_{CE} = 20 \text{ V, then } I_C = \frac{80 \text{ mW}}{60} = 4 \text{ mA (point 2 in figure (1))}$$

$$V_{CE} = 10 \text{ V, then } I_C = \frac{80 \text{ mW}}{10} = 8 \text{ mA (point 3 in figure (1))}$$


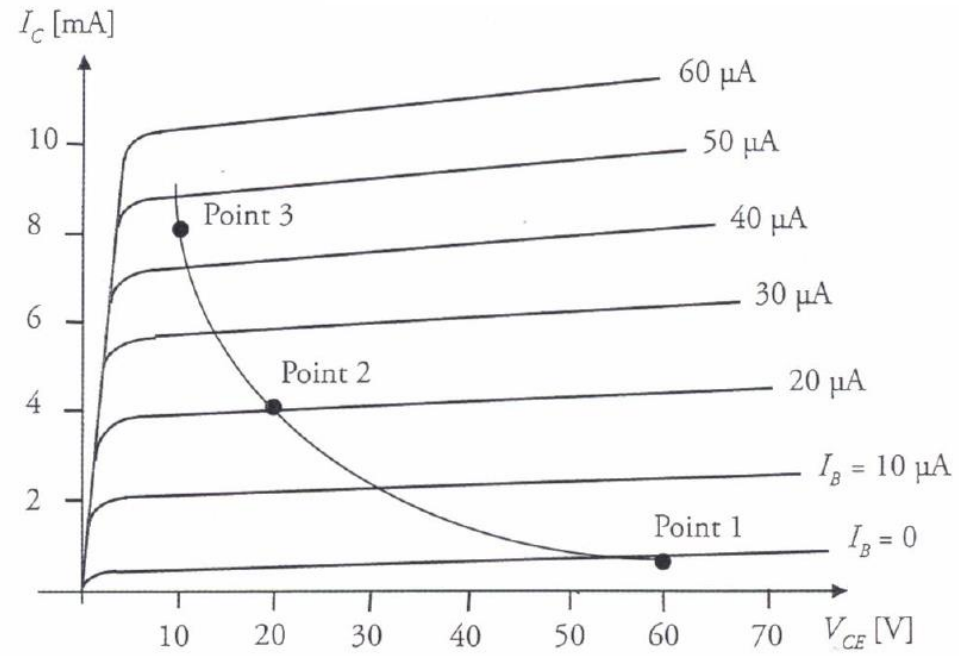


Figure (1)
Maximum power dissipation

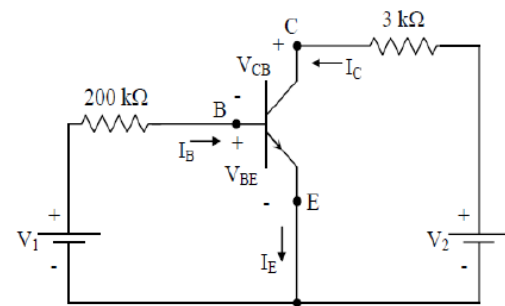Example (2)

For circuit shown in figure (1). Determine I_C , V_{CB} , $V_1 = 5V$, $V_2 = 10V$, $\beta = 100$, $R_B = 200 K\Omega$, $R_C = 3 K\Omega$



npn-type BJT in
Common-emitter Configuration

Figure (2)

Solution:-

$$I_B = \frac{V_1 - V_{BE}}{R_B}$$

$$I_B = \frac{5 - 0.7}{200 \times 10^3} = 0.0215 \text{ mA}$$

$$I_C = \beta \times I_B$$

$$I_C = 100 \times 0.0215 = 2.15 \text{ mA}$$

$$V_{CB} = V_{CE} - V_{BE}$$

$$V_{CE} = V_2 - I_C \times R_C$$

$$V_{CE} = 10 - 2.15 \times 3 = 3.55 \text{ V}$$

$$V_{CB} = 3.55 - 0.7 = 2.85 \text{ V}$$

Example (3)

An NPN Transistor has a DC base bias voltage, V_B of 10 V and an input base resistor, R_B of 100 k Ω . What will be the value of the base current into the transistor?

Solution:-

$$I_B = \frac{V_B - V_{BE}}{R_B} = \frac{10 - 0.7}{100 \times 10^3} = 93 \mu A$$

Example (4)

An NPN Transistor has a DC current gain, β value of 200. Calculate the base current I_B required to switch a resistive load of 4 mA ?

Solution:-

$$I_B = \frac{I_C}{\beta} = \frac{4 \times 10^{-3}}{200} = 20 \mu A$$

Example (5)

Find for the given npn BJT circuit shown in figure (3). Determine I_B , I_C , I_E , V_{CB} , β , α ?

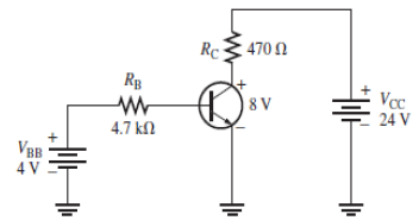


Figure (3)

Solution:-

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4 - 0.7}{4.7 \times 10^3} = 0.7 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{24 - 8}{470} = 34 \text{ mA}$$

$$I_E = I_C + I_B = 0.7 \text{ mA} + 34 \text{ mA} = 34.7 \text{ mA}$$

$$V_{CB} = V_{CE} - V_{BE} = 8 - 0.7 = 7.3 \text{ V}$$

$$\beta = \frac{I_C}{I_B} = \frac{34 \text{ mA}}{0.7 \text{ mA}} = 48.57$$

$$\alpha = \frac{I_C}{I_E} = \frac{34 \text{ mA}}{34.7 \text{ mA}} = 0.9798$$

Example (6)

A fixed bias circuit shown in figure (4) has $V_{CC} = 24 \text{ V}$; $R_B = 390 \text{ k}\Omega$; $R_C = 3.3 \text{ k}\Omega$ and $V_{CE} = 10 \text{ V}$. Calculate β and determine new value of V_{CE} if $\beta = 100$?

Solution:-

$$V_{CE} = V_{CC} - I_C \times R_C$$

$$10 = 24 - I_C \times 3.3 \times 10^3$$

$$I_C = \frac{24 - 10}{3.3 \times 10^3} = 4.24 \text{ mA}$$

$$I_B = \frac{V_B - V_{BE}}{R_B} = \frac{24 - 0.7}{390 \times 10^3} = 59.74 \text{ }\mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = \frac{4.24 \times 10^{-3}}{59.74 \times 10^{-6}} = 71$$

If $\beta = 100$

$$I_C = \beta \times I_B$$

$$I_C = 100 \times 59.74 \text{ }\mu\text{A} = 5.974 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C \times R_C$$

$$V_{CE} = 24 - 5.974 \times 3.3 = 4.2858 \text{ mA}$$

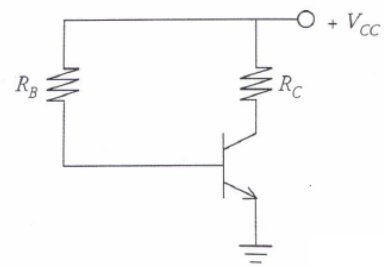


Figure (4)

Q7) Determine the operating point for the transistor shown in figure(5), which has $\beta = 100$, $R_B = 500 \text{ k}\Omega$, $R_C = 2.5 \text{ k}\Omega$, $V_{CC} = 20 \text{ V}$. Show the load line and the operating point on the load line?

Solution:-

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.7}{500 \times 10^3} = 38.6 \text{ } \mu\text{A}$$

$$I_C = \beta \times I_B = 100 \times 36.8 = 3.68 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C \times R_C$$

$$V_{CE} = 20 - 3.68 \times 2.5 = 10.35 \text{ V}$$

The coordinates of load line are $\left(0, \frac{V_{CC}}{R_C}\right)$ and $(V_{CC}, 0)$ which are $(0, 8 \text{ mA})$ and $(20 \text{ V}, 0)$. The load-line and operating points are shown in figure (6).

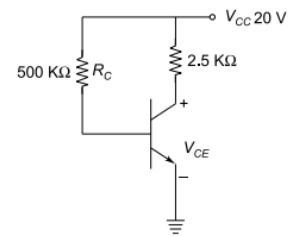


Figure (5)

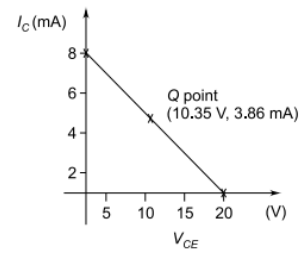


Figure (6)

Q8) For the circuit shown in figure (7). Determine I_E , I_B , I_C and V_{CE} if $\beta=75$ and $R_C=2.5 \text{ k}\Omega$, $R_B=10 \text{ k}\Omega$, $R_E=1 \text{ k}\Omega$, $V_{CC} = 8 \text{ V}$, $V_E = 2 \text{ V}$, $V_{BE} = 0.7 \text{ V}$?

Solution:-

For input loop:-

$$V_E - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_E - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_E - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$I_B = \frac{2 - 0.7}{10 \times 10^3 + (75 + 1) \times 1 \times 10^3} = 15.1 \mu\text{A}$$

$$I_C = \beta \times I_B = 75 \times 15.1 = 1.13 \text{ mA}$$

$$I_E = I_C + I_B = 15.1 \times 10^{-3} \text{ mA} + 1.13 \text{ mA} = 1.15 \text{ mA}$$

$$V_{CC} - I_C \times R_C - V_{CE} - I_E \times R_E + V_E = 0$$

$$8 - 1.13 \times 2.5 - V_{CE} - 1.15 \times 1 + 2 = 0$$

$$V_{CE} = 7.01 \text{ V}$$

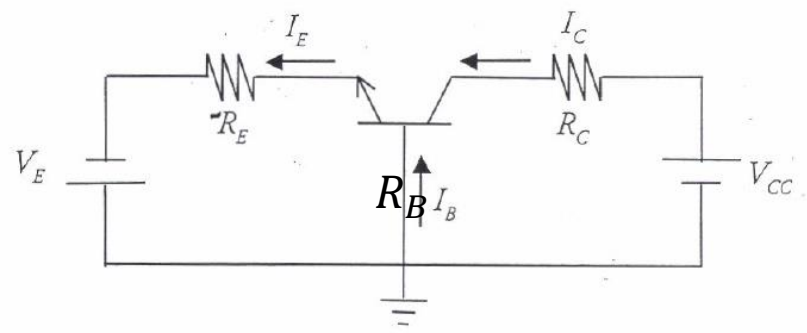


Figure (7)

Q9) For figure (8). Determine Q-point and DC load-line.

Solution:-

$$I_B = \frac{V_{CC} - V_{BE}}{R_1 + (\beta + 1) R_E}$$

$$I_B = \frac{20 - 0.7}{2.7 \times 10^6 + (100 + 1) \times 3.3 \times 10^3} = 6.363 \mu A$$

$$I_C = \beta \times I_B = 100 \times 6.363 = 0.636 \text{ mA}$$

$$I_E = I_C + I_B = 0.643 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C \times R_C - I_E \times R_E$$

$$V_{CE} = 20 - 0.636 \times 10 - 0.643 \times 3 = 11.52 \text{ V}$$

Q point at $I_C = 0.636 \text{ mA}$ and $V_{CE} = 11.52 \text{ V}$.

$$V_{CE} = V_C - V_E = V_{CC} - I_C \times R_C - I_E \times R_E$$

$$I_C \cong I_E$$

$$V_{CE} = V_{CC} - I_C \times (R_C + R_E)$$

When $V_{CE} = 0$

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

$$I_C = \frac{20\text{V}}{(10 + 3.3)\text{k}\Omega} = 1.504 \text{ mA}$$

When $I_C = 0$

$$V_{CE} = V_{CC}$$

$$V_{CE} = 20 \text{ V}$$

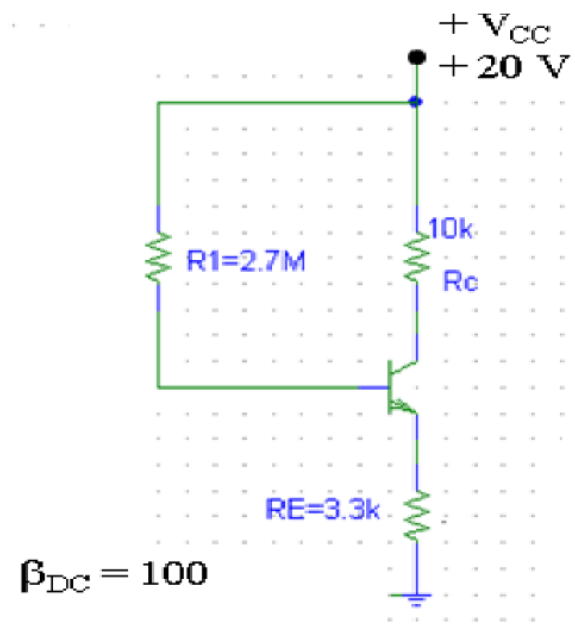


Figure (8)

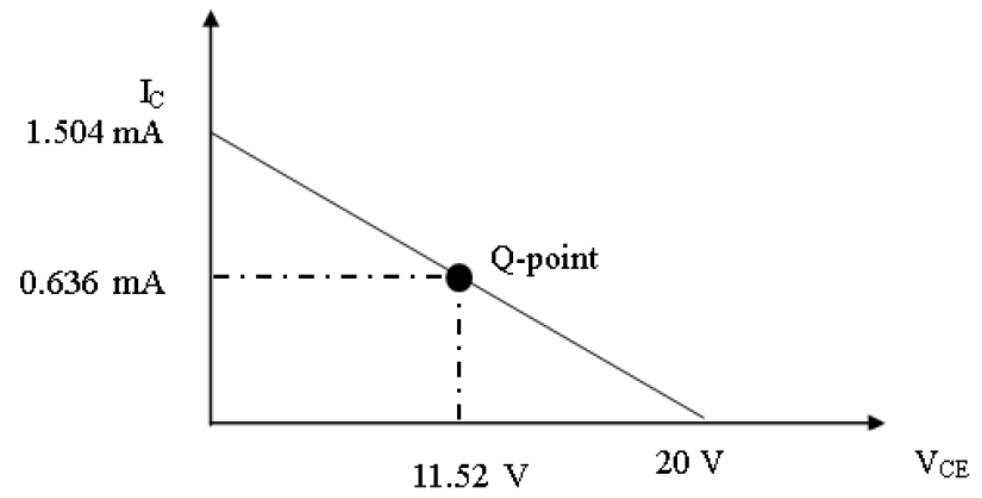


Figure (9)

Q10) Calculate Q point values for circuit shown in figure (10), $V_{CC}=10V$,
 $R_B=100\text{ k}\Omega$, $R_C=10\text{ k}\Omega$, $\beta=100$?

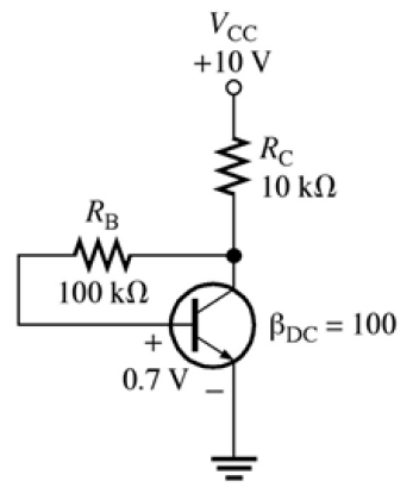


Figure (10)

Solution:-

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_C} = \frac{(10 - 0.7)}{100 + (100 + 1) \times 10} = 8.38 \mu A$$

$$I_C = \beta \times I_B = 100 \times 8.38 = 0.838 \text{ mA}$$

$$V_{CE} = V_{CC} - R_C \times (I_C + I_B) = 10 - 10 \times (0.838 + 0.00838) = 1.536 \text{ V}$$

Q point at V_{CE} 1.536 V and $I_C = 0.838 \text{ mA}$

At cut-off and saturation mode

$$V_{CE} = V_{CC} - R_C \times (I_C + I_B)$$

$$I_C \gg I_B$$

$$V_{CE} = V_{CC} - R_C \times I_C$$

When $V_{CE} = 0$

$$I_C = \frac{V_{CC}}{R_C} = \frac{10}{10\text{k}\Omega} = 1 \text{ mA}$$

When $I_C = 0$

$$V_{CE} = V_{CC}$$

$$V_{CE} = 10$$