

Transistor

1-Emitter-stabilized circuit

This circuit is also known as fixed bias circuit with an emitter resistance . Figure (1) shows the location of resistor, R_E . This circuit is more stable because I_B is not fixed as shown in previous example (fixed biased circuit). I_B will change if β change, which causes operating point to experience changes but not a much as fixed bias circuit.

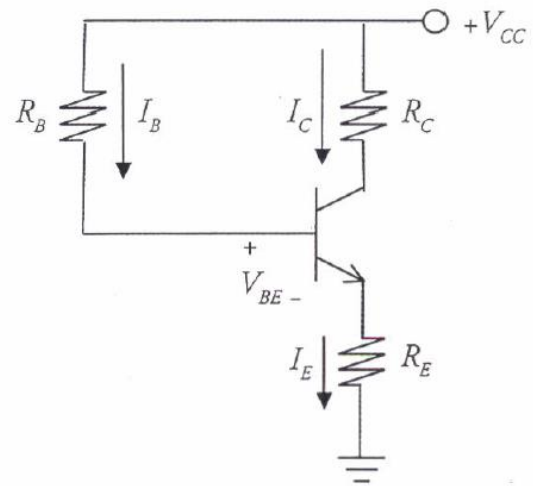


Figure (1)
An emitter-stabilized bias circuit

The DC analysis to determine the operating point of a circuit shown in figure (1) is as follows:-

Using KVL for the input loop (figure (1))

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Substitute $I_E = (\beta + 1) I_B$ into above equation, it becomes

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0 \quad \text{and} \quad I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Therefore $I_C = \beta I_B$ and $I_E = I_C + I_B = (\beta + 1) I_B$

Equation for the output loop in figure (1):-

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\text{Therefore } V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Or $V_{CE} = V_{CC} - I_C (R_C + R_E)$ if an assumption $I_C \approx I_E$ is made.

The DC load-line of this circuit is shown in figure (2). Its difference as compared to a fixed bias circuit load-line is the $I_{C(sat)}$ value, where

$I_{C(sat)} = \frac{V_{CC}}{R_C + R_E}$. The same effect as revealed as shown in previous lectures will happen if R_C and V_{CC} experience change.

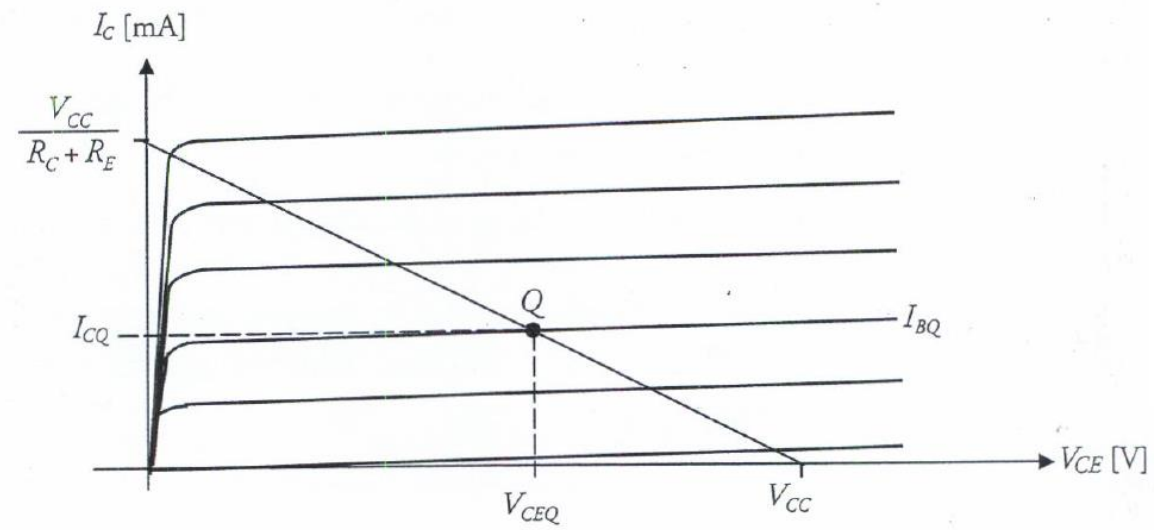


Figure (2)
DC load-line for an emitter stabilized bias circuit

2- Voltage-divider Bias

Another bias circuit is voltage divider circuit (figure (3-a)). This circuit can be simplified further as shown in (figure (3-b)) using Thevenin's theorem for the DC analysis to determine the transistor operating point. For this, an equivalent of R_{TH} or R_{BB} and V_{TH} or V_{BB} that can be seen at the base terminal should be found.

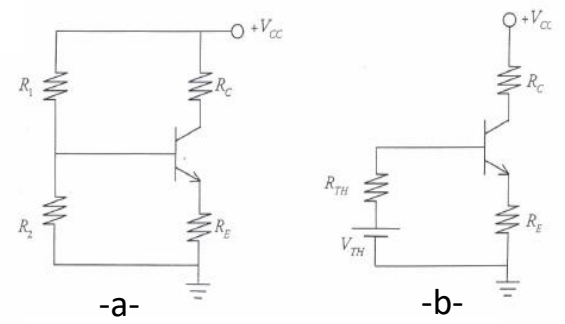


Figure (3)
a- Voltage divider circuit b- simplified circuit

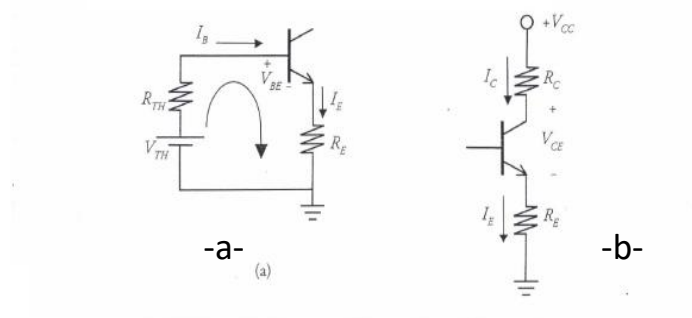


Figure (4) Voltage divider circuit
(a) Input loop (b) output loop

Using Thevenin's theorem, the following obtained:

$$R_{th} = R_1 \parallel R_2 \text{ and } V_{th} = V_{cc} \frac{R_2}{R_1 + R_2}$$

Using KVL for the input loop (figure(4-a)):-

$$V_{TH} - I_B R_{th} - V_{BE} - I_E R_E = 0 \text{ but } I_E = (\beta + 1) I_B$$

Hence:-

$$V_{TH} - I_B R_{th} - V_{BE} - (\beta + 1) I_E R_E = 0$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

So that

$$I_C = \beta I_B \text{ and } I_E = I_C + I_B = (\beta + 1) I_B$$

Equation for the output loop figure (figure (4-b)):-

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Or $V_{CE} = V_{CC} - I_C (R_C + R_E)$ with an assumption $I_C \approx I_E$.

The DC load line for this circuit is same as figure (2).

The voltage divider bias circuit is very stable circuit. It does not depend on the value β if circuit parameters, i.e., resistance values are chosen correctly. This is shown as follows:

For voltage divider circuit, it is known that:
$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

Normally $\beta \gg 1$, an assumption of $(\beta + 1) = \beta$ can be made.

For a good amplifier, $(\beta + 1) R_E \gg R_{th}$, therefore R_{th} value can be ignored.

Then

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + \beta R_E} = \frac{V_{TH} - V_{BE}}{\beta R_E}$$

$$I_C = \beta I_B = \beta \left(\frac{V_{TH} - V_{BE}}{\beta R_E} \right) \rightarrow I_C = \frac{V_{TH} - V_{BE}}{R_E}$$

The equation of I_C clearly shows that it does not depend on β . But condition $(\beta + 1) R_E \gg R_{th}$ must be complied. Since I_C does not depend on β value, therefore V_{CE} is also not depended on β .

3- DC Bias with Voltage feedback

This circuit is also known as collector feedback bias circuit. A bias circuit is shown in figure (5).

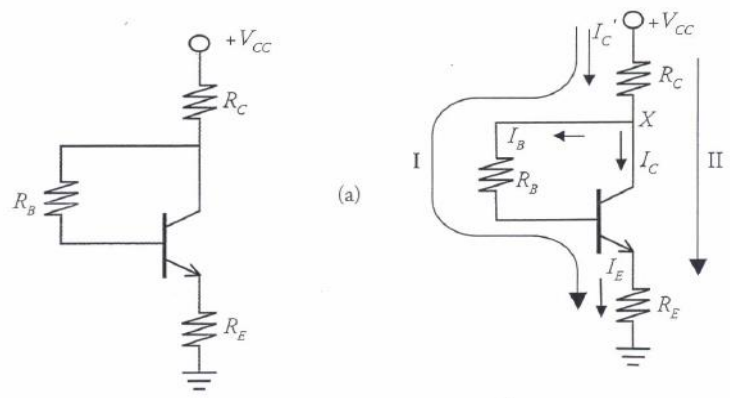


Figure (5)
Bias circuit with a voltage feedback

At node X, using KCL : $I'_C = I_B + I_{C'}$

$$I_E = I_B + I_{C'}$$

Then current that flows through R_C is emitter current, I_E , so $I'_C = I_E$

Using Loop I:

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Known that $I_E = (\beta + 1) I_B$

$$\text{Then, } V_{CC} - (\beta + 1) I_B R_C - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_E + R_C)}$$

Hence, $I_C = \beta I_B$ and $I_E = I_C + I_B = (\beta + 1) I_B$

Equation for loop II:

$$V_{CC} - I_E R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_E (R_E + R_C)$$

$$\text{Or } V_{CE} = V_{CC} - I_C (R_E + R_C)$$

With as assumption $I_C \approx I_E$

Q1- For a given BJT: $I_B = 50 \mu A$ and $I_C = 3.65 mA$. Find the dc current gain β_{dc} , I_E , α_{dc} ?

Solution:-

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{3.65 mA}{50 \mu A} = \frac{3.65 \times 10^{-3}}{50 \times 10^{-6}} = 73$$

$$I_E = I_C + I_B = 50 \times 10^{-6} + 3.65 \times 10^{-3} = 3.7 \times 10^{-3} mA$$

$$\alpha_{dc} = \frac{I_C}{I_E} = \frac{3.65 mA}{3.7 mA} = \frac{3.65 \times 10^{-3}}{3.7 \times 10^{-3}} = 0.986$$

Q2- For given NPN BJT circuit shown in figure(6) ,if $\beta_{dc}=150$. Find I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} ?

Solution:-

$$V_{BE} \cong 0.7 \text{ Volt}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{5V - 0.7V}{10 \text{ K}\Omega} = 430 \mu A$$

$$I_C = \beta_{dc} I_B = (150)(430 \mu A) = 64.5 \text{ mA}$$

$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu A = 64.9 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 10V - (64.5 \text{ mA})(100\Omega) = 3.55 \text{ V}$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$

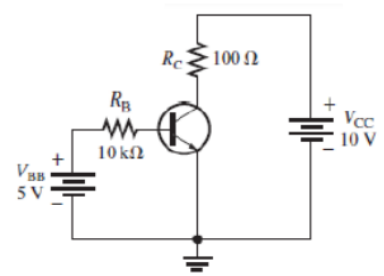


Figure (6)

Q3- Using ideal BJT switch of $\beta_{dc}=200$, $V_{CC}=10V$ and $I_B=20 \mu A$.

- 1) Find the value of base resistor R_B required to switch the load "ON" when the input terminal voltage exceeds 2.5 V and $V_{BE}= 0.7V$.
- 2) Calculate the R_C of point (1).
- 3) Find the minimum base current I_B required to turn the transistor "Fully -ON " (saturated) for a load that requires 200 mA when the input voltage increased to 5.0 V. Also calculate the new value of R_B .

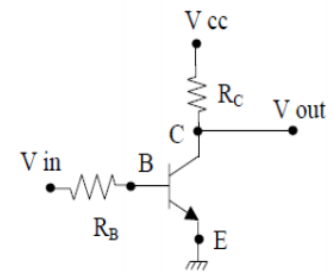


Figure (7)

Solution:-

$$1- R_B = \frac{V_{in} - V_{BE}}{I_B} = \frac{2.5V - 0.7V}{20 \times 10^{-6}} = 90 \text{ K}\Omega.$$

2- For ideal BJT at saturation $V_{CE} = 0$ Volt

$$I_C = \beta_{dc} I_B = 200 \times 20 \times 10^{-6} = 4 \text{ mA}$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{10 - 0}{4 \times 10^{-3}} = 2.5 \text{ K}\Omega.$$

3- At ON state, the load current is equal to I_C

$$I_B = \frac{I_C}{\beta_{dc}} = \frac{200 \text{ mA}}{200} = 1 \text{ mA}$$

$$R_B = \frac{V_{in} - V_{BE}}{I_B} = \frac{5V - 0.7V}{1 \times 10^{-3}} = 4.3 \text{ K}\Omega.$$

Q4- For fixed bias circuit shown in figure (8), if $R_B = 240 \text{ K}\Omega$, $R_C = 2.2 \text{ K}\Omega$, $\beta_{dc} = 50$. $V_{CC} = 12 \text{ V}$. Determine

1- I_B, I_C

2- V_{CE}

3- V_B, V_C

4- V_{BC}

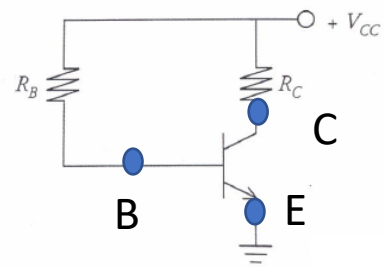


Figure (8)

Solution:-

$$1 - I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12V - 0.7V}{240 K\Omega} = 47.08 \mu A$$

$$I_C = \beta_{dc} I_B = 50 \times 47.08 \times 10^{-6} = 2.35 mA$$

$$2 - V_{CE} = V_{CC} - I_C R_C = 12V - (2.35 mA)(2.2 K\Omega) = 6.83 V$$

$$3 - V_B = V_{BE} = 0.7 V$$

$$4 - V_C = V_{CE} = 6.83 V$$

$$5 - V_{BC} = V_B - V_C = 0.7 V - 6.83V = -6.13 V$$

Q5- For figure (10) Determine:-

1- V_{CC}

2- R_C

3- R_B

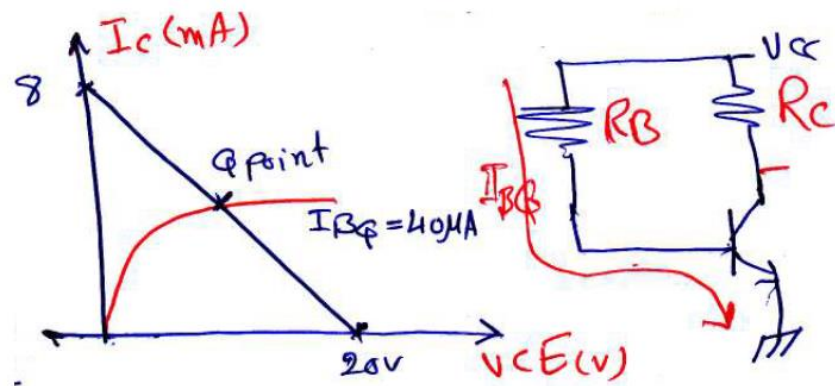


Figure (10)

Solution:-

1- $V_{CC} = 20 \text{ V}$

2- $I_C = 8 \text{ mA} \rightarrow R_C = \frac{V_{CC}}{I_C} = \frac{20 \text{ V}}{8 \text{ mA}} = 2.5 \text{ K}\Omega$

3- $R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20 - 0.7}{40 \times 10^{-6}}$

$= 482.5 \text{ K}\Omega$

Q6- For emitter-bias circuit shown in figure (11). Determine:-

$I_B, I_C, V_{CE}, V_C, V_E, V_B$ and V_{BC}

Where:-

$V_{CC}=20\text{ V}, R_B=430\text{ K}\Omega, R_E=1\text{ K}\Omega, R_C=2\text{ K}\Omega, \beta_{dc}=50$

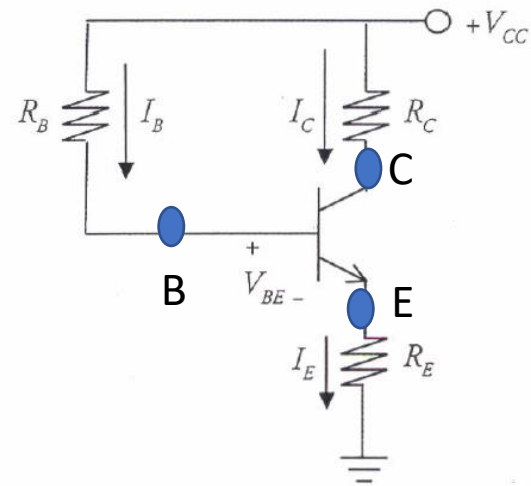


Figure (11)

Solution:-

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{20 - 0.7}{430 \text{K}\Omega + (50 + 1)(1 \text{K}\Omega)} = 40.1 \mu\text{A}$$

$$I_C = \beta_{dc} I_B = 50 \times 40.1 \times 10^{-6} = 2.01 \text{mA}$$

$$I_E = I_C + I_B = 2.01 \text{mA} + 40.1 \mu\text{A} = 2.05 \text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 20\text{V} - (2.01 \text{mA})(2. \text{K}\Omega) - (2.05 \text{mA})(1. \text{K}\Omega) \\ = 13.93 \text{V}$$

$$V_C = V_{CE} + I_E R_E = 13.93 + (2.05 \text{mA})(1. \text{K}\Omega) = 15.98 \text{V}$$

$$V_E = I_E R_E = (2.05 \text{mA})(1. \text{K}\Omega) = 2.05 \text{V}$$

$$\text{Or } V_E = V_C - V_{CE}$$

$$V_E = 15.98 - 13.93 = 2.05 \text{ V}$$

$$V_B = V_E + V_{BE}$$

$$V_B = 0.7 + 2.05 = 2.75 \text{ V}$$

$$V_{BC} = V_B - V_C$$

$$V_{BC} = 2.75 - 15.98 = -13.89$$

Q7- For circuit shown in figure (12), $R_1 = 39 \text{ K}\Omega$, $R_2 = 3.9 \text{ K}\Omega$, $R_c = 10 \text{ K}\Omega$,
 $R_E = 1.5 \text{ K}\Omega$, $\beta_{dc} = 100$, $V_{CC} = 22 \text{ V}$

determine:- V_{CE} , I_c

Solution:-

$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = \frac{(39)(3.9)}{(39+3.9)} = 3.55 \text{ K}\Omega$$

$$V_{th} = \frac{V_{CC}R_2}{R_1+R_2} = \frac{(22)(3.9)}{(39+3.9)} = 2 \text{ V}$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$


$$I_B = \frac{2-0.7}{3.5K+(101)(1.5K)} = 8.38 \mu A$$

$$I_C = \beta_{dc} I_B = 100 \times 8.38 \times 10^{-6} = 0.84 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 22 - 0.84 \text{ mA}(10K\Omega + 1.5K\Omega) = 12.34 \text{ V}$$

Figure (12)

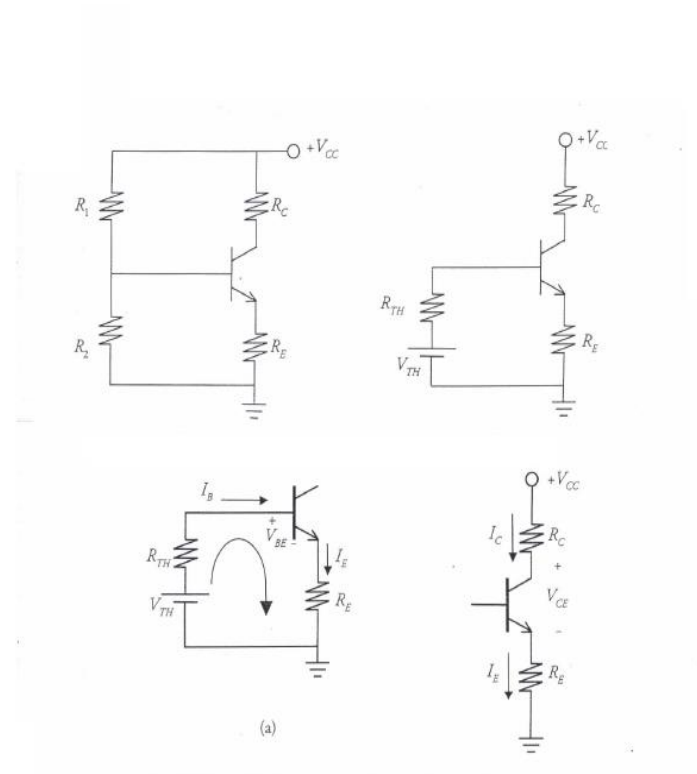

Q7- For circuit shown in figure (13), $R_C = 4.7 \text{ K}\Omega$, $R_B = 250 \text{ K}\Omega$, $R_E = 1.2 \text{ K}\Omega$, $\beta_{dc} = 90$, $V_{CC} = 10 \text{ V}$. Find I_C , V_{CE} . Repeat previous example if $\beta_{dc} = 150$

Solution:-

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_E + R_C)}$$

$$I_B = \frac{10 - 0.7}{250 + (90 + 1)(1.2 + 4.7)} = 11.91 \mu\text{A}$$

$$I_C = \beta_{dc} I_B = 90 \times 11.91 \times 10^{-6} = 1.07 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 10 - 1.07 \text{ mA}(4.7\text{K} + 1.2\text{K}) = 3.69 \text{ V}$$

If $\beta_{dc} = 150$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_E + R_C)}$$

$$I_B = \frac{10 - 0.7}{250 + (150 + 1)(1.2 + 4.7)} = 8.89 \mu A$$

$$I_C = \beta_{dc} I_B = 150 \times 8.89 \times 10^{-6} = 1.2 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 10 - 1.2 \text{ mA}(4.7\text{K} + 1.2\text{K}) = 2.92 \text{ V}$$

Level β_{dc} increase 50%

Level of I_C increased by 12%

Level of V_{CE} decreased by 20.9%

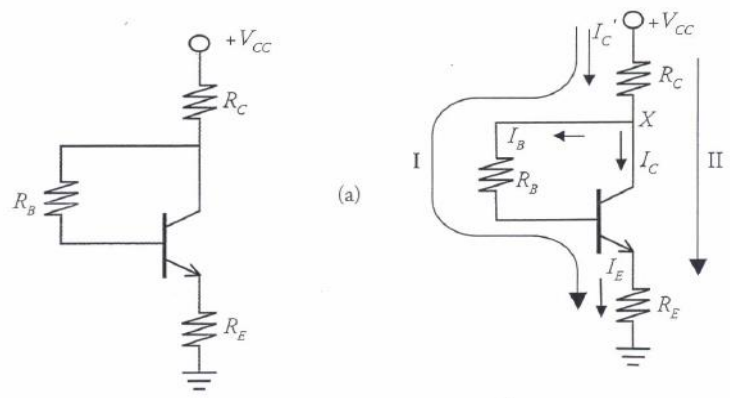


Figure (13)