

FET Small Signal Analysis


Mathematical Definition of gm


$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{\partial I_D}{\partial V_{GS}} \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$g_m = \frac{2I_{DSS}}{|V_p|} \left[1 - \frac{V_{GS}}{V_p}\right]$$


$$g_m \text{ for } V_{GS} = 0V: \quad g_{m0} = \frac{2I_{DSS}}{|V_p|}$$
 
$$\text{for } 1 - \frac{V_{GS}}{V_p} = \sqrt{\frac{I_D}{I_{DSS}}} \quad g_m = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$




 

FET AC Equivalent Circuit


 


 JFET Common-Source (CS) Fixed-Bias Configuration



- The input is on the gate and the output is on the drain.
- Fixed bias configuration includes the coupling capacitors c_1 and c_2 that isolate the dc biasing arrangements from the applied signal and load.
- They act as short circuit equivalents for the ac analysis.

AC Equivalent Circuit

  


Input impedance $Z_i = R_G$

Output Impedance: $Z_o = r_d \parallel R_D$

$$Z_o \cong R_D \quad | \quad I_d \geq 10R_D$$

Voltage gain

 


$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad | \quad r_d \geq 10R_D$$

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

JFET Self bias configuration


- Main disadvantage of fixed bias configuration requires two dc voltage sources.
- Self bias circuit requires only one DC supply to establish the desired operating point.

Self bias configuration

 


If C_S is removed, it affects the gain of the circuit

AC Equivalent Circuit

 

- The capacitor across the source resistance assumes its short circuit equivalent for dc allowing R_S to define the operating point.
- Under ac conditions the capacitor assumes short circuit state and short circuits the R_S .
- If R_S is left un-shortened, then ac gain will be reduced.

Redrawn equivalent circuit:

 

Here R_s is bypassed by X_{C_s}


Circuit parameters:

- Since the resulting circuit is same as that of fixed bias configuration, all the parameter expression remains same as evaluated for fixed bias configuration.
- Input impedance $Z_i = R_G$
- Output Impedance : $Z_o = r_d \parallel R_D$
- Leaving R_s un-bypassed helps to reduce gain variations from device to device by providing degenerative current feedback. However, this method for minimizing gain variations is only effective when a substantial amount of gain is sacrificed.

$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = -g_m R_D \quad | \quad r_d \geq 10R_D$$

 Self bias configuration with un bypassed R_s




- Here R_s is part of the equivalent circuit .

- Here R_s is part of the equivalent circuit .
- There is no way to reduce the network with lowest complexity.
- Carefully all the parameters have to be calculated by considering all polarities properly.

Output impedance is defined by

- $Z_O = V_o / I_o$ at $v_i = 0$
- Setting $V_i = 0$ results in following circuit

 Setting $V_i=0$ results in following circuit.



$$Z_o = \frac{RD}{1 + gmR_s + \frac{RD + R_s}{r_d}}$$

$$r_d > 10(RD + |R_s|)$$


$$Z_o = \frac{RD}{1 + gmR_s}$$

Voltage gain:


$$A_v = \frac{V_o}{V_i} = \frac{gmRD}{1 + gmR_s + \frac{RD + R_s}{rd}}$$

$$rd \geq 10(RD + R_s), A_v = -\frac{gmRD}{1 + gmR_s}$$

JFET voltage divider configuration

 


AC equivalent circuit

 


Input Impedance: $Z_i = R_1 \parallel R_2$

Output Impedance: $Z_o = r_d \parallel R_D$

$$Z_o \cong R_D \Big|_{I_d \geq 10I_{DQ}}$$

 

Voltage gain:

 


$$A_v = -g_m(r_d \parallel R_D)$$



$$A_v = -g_m R_D \Big|_{r_d \geq 10R_D}$$

Note


- Equations for Z_O and A_v are same as in fixed bias.
- Only Z_i is now dependent on parallel combination of R_1 and R_2 .

JFET source follower

 

  

 - Input and output impedance:
- **Input impedance** : $Z_i = R_G$
- **Output impedance** :
- setting $V_i = 0V$ will result in the gate terminal being connected directly to ground as shown in figure below.



- Applying KCL at output node

$$\begin{aligned}
 I_o + g_m V_{gs} &= I_{rd} + I_{Rs} \\
 &= \frac{V_o}{r_d} + \frac{V_o}{R_s} \\
 \text{result : } I_o &= V_o \left[\frac{1}{r_d} + \frac{1}{R_s} \right] - g_m V_{gs}
 \end{aligned}$$

$$= V_o \left[\frac{1}{r_d} + \frac{1}{R_s} \right] - g_m V_{gs}$$

$$Z_o = \frac{V_o}{I_o} = \frac{V_o}{\left[\frac{1}{r_d} + \frac{1}{R_s} + g_m \right] V_o} \frac{1}{V_o}$$

$$= \frac{1}{\left[\frac{1}{r_d} + \frac{1}{R_s} + g_m \right]}$$

$$Z_o \cong R_s \parallel \frac{1}{g_m} \quad \left| \quad r_d \geq 10R_s \right.$$

r_d , R_s and g_m are all in parallel.


Voltage gain

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_s)}{1 + g_m (r_d \parallel R_s)}$$



$$A_v = \frac{g_m R_s}{1 + g_m R_s} \quad \left| \quad r_d \geq 10R_s \right.$$

- Since denominator is larger by a factor of one, the gain can never be equal to or greater than one. (as in the case of emitter follower of BJT)

JFET common gate configuration

 

  - The input is on source and the output is on the drain. Same as the common base in BJT




Input Impedance: $Z_i = R_s \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$

$$Z_i \cong R_s \parallel \frac{1}{g_m} \Big|_{r_d \geq 10R_D}$$

Output Impedance: $Z_o = R_D \parallel r_d$

$$Z_o \cong R_D \Big|_{r_d \geq 10R_D}$$

 


$$A_v = \frac{V_o}{V_i} = \frac{\left[g_m R_D + \frac{R_D}{r_d} \right]}{\left[1 + \frac{R_D}{r_d} \right]}$$


$$A_v = g_m R_D \quad |_{r_d \geq 10 R_D}$$

D-MOSFET ac equivalent model



EMOSFET drain feedback configuration

 

 


Input Impedance: $Z_i = \frac{R_F + r_d \parallel R_D}{1 + g_m (r_d \parallel R_D)}$

$$Z_i \cong \frac{R_F}{1 + g_m R_D} \quad \left| \begin{array}{l} R_F \gg r_d \parallel R_D, \\ r_d \geq 10R_D \end{array} \right.$$

Output Impedance: $Z_o = R_F \parallel r_d \parallel R_D$

$$Z_o \cong R_D \quad \left| \begin{array}{l} R_F \gg r_d \parallel R_D, \\ r_d \geq 10R_D \end{array} \right.$$

 


$$A_v = -g_m (R_F \parallel r_d \parallel R_D)$$

$$A_v \cong -g_m R_D \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10R_D}$$

JFET small signal Model
 
$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$



$$g_m = \frac{2I_{DSS}}{|V_p|} \left[1 - \frac{V_{GS}}{V_p} \right]$$

 





FIG. 8.8
JFET ac equivalent circuit.

$$Z_i(\text{JFET}) = \infty \Omega$$

$$Z_o(\text{JFET}) = r_d = \frac{1}{g_{os}} = \frac{1}{y_{os}}$$

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS}=\text{constant}}$$

Fixed-Bias Configuration

   

$$Z_i = R_G$$

$$Z_o = R_D \parallel r_d$$



$$Z_o \cong R_D \quad r_d \approx 10R_D$$

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad r_d \approx 10R_D$$

phase shift of 180° between input and output voltages.

VOLTAGE-DIVIDER CONFIGURATION

  

$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad r_d \geq 10R_D$$

$$V_{gs} = V_i$$

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (r_d \parallel R_D)}{V_{gs}}$$

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} \cong -g_m R_D \quad r_d \geq 10R_D$$

Design FET Amplifier Network

EXAMPLE 8.14 Choose the values of R_D and R_S for the network of Fig. 8.44 that will result in a gain of 8 using a relatively high level of g_m for this device defined at $V_{GS_Q} = \frac{1}{4}V_P$.

 


FIG. 8.44

Network for desired voltage gain in Example 8.14.

Solution: The operating point is defined by

$$V_{GS_Q} = \frac{1}{4}V_P = \frac{1}{4}(-4\text{ V}) = -1\text{ V}$$

and
$$I_D = I_{DSS} \left(1 - \frac{V_{GS_Q}}{V_P}\right)^2 = 10\text{ mA} \left(1 - \frac{(-1\text{ V})}{(-4\text{ V})}\right)^2 = 5.625\text{ mA}$$

Determining g_m , we obtain

$$\begin{aligned} g_m &= g_{m0} \left(1 - \frac{V_{GS_Q}}{V_P}\right) \\ &= 5\text{ mS} \left(1 - \frac{(-1\text{ V})}{(-4\text{ V})}\right) = 3.75\text{ mS} \end{aligned}$$

The magnitude of the ac voltage gain is determined by

$$|A_v| = g_m(R_D \parallel r_d)$$

Substituting known values results in

$$8 = (3.75\text{ mS})(R_D \parallel r_d)$$

so that

$$R_D \parallel r_d = \frac{8}{3.75\text{ mS}} = 2.13\text{ k}\Omega$$

The level of r_d is defined by

$$r_d = \frac{1}{g_{os}} = \frac{1}{20\text{ }\mu\text{S}} = 50\text{ k}\Omega$$

and

$$R_D \parallel 50\text{ k}\Omega = 2.13\text{ k}\Omega$$

with the result that

$$R_D = 2.2\text{ k}\Omega$$

which is a standard value.

The level of R_S is determined by the dc operating conditions as follows:





$$\begin{aligned} V_{GS_Q} &= -I_D R_S \\ -1\text{ V} &= -(5.625\text{ mA})R_S \end{aligned}$$





and

$$R_S = \frac{1\text{ V}}{5.625\text{ mA}} = 177.8\text{ }\Omega$$

The closest standard value is **180 Ω** . In this example, R_S does not appear in the ac design because of the shorting effect of C_S .

Summary Table

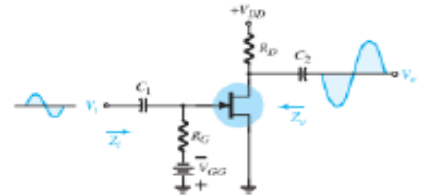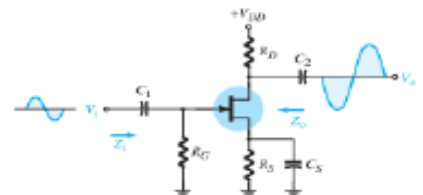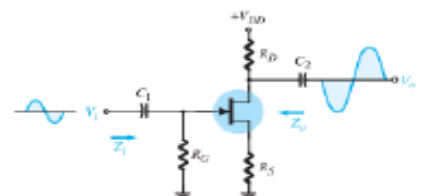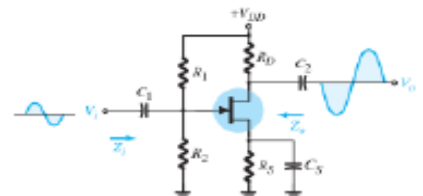Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Fixed-bias (JFET or D-MOSFET) 	High (10 M Ω) $= R_G$	Medium (2 k Ω) $= R_D \parallel r_d$ $\approx R_D$ ($r_d \gg 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\approx -g_m R_D$ ($r_d \gg 10 R_D$)
Self-bias bypassed R_S (JFET or D-MOSFET) 	High (10 M Ω) $= R_G$	Medium (2 k Ω) $= R_D \parallel r_d$ $\approx R_D$ ($r_d \gg 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\approx -g_m R_D$ ($r_d \gg 10 R_D$)
Self-bias unbypassed R_S (JFET or D-MOSFET) 	High (10 M Ω) $= R_G$	$= \frac{\left[1 + g_m R_S + \frac{R_S}{r_d}\right] R_D}{\left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d}\right]}$ $\approx R_D$ ($r_d \gg 10 R_D$ or $r_d \gg 10 R_S$)	Low (-2) $= \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$ $\approx \frac{g_m R_D}{1 + g_m R_S}$ ($r_d \gg 10 R_D$ or $r_d \gg 10 R_S$)
Voltage-divider bias (JFET or D-MOSFET) 	High (10 M Ω) $= R_1 \parallel R_2$	Medium (2 k Ω) $= R_D \parallel r_d$ $\approx R_D$ ($r_d \gg 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\approx -g_m R_D$ ($r_d \gg 10 R_D$)

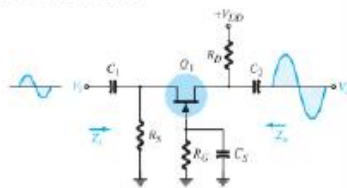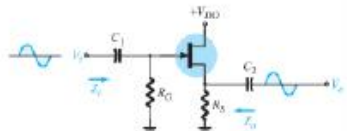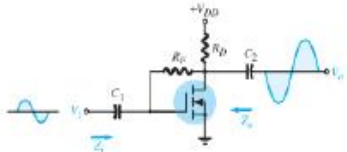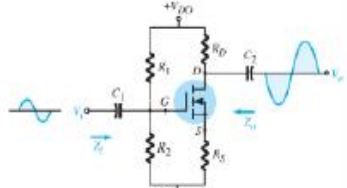Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Common-gate [JFET or D-MOSFET] 	Low (1 k Ω) $= R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$ $= R_S \parallel \frac{1}{g_m} \quad (r_d \gg 1/g_m)$	Medium (2 k Ω) $= R_D \parallel r_d$ $= R_D \quad (r_d \gg R_D)$	Medium (+10) $= \frac{g_m R_D + \frac{R_D}{r_d}}{1 + \frac{R_D}{r_d}}$ $\approx g_m R_D \quad (r_d \gg 10R_D)$
Source-follower [JFET or D-MOSFET] 	High (10 M Ω) $= R_G$	Low (100 k Ω) $= r_d \parallel R_S \parallel 1/g_m$ $= R_S \parallel 1/g_m \quad (r_d \gg 1/g_m)$	Low (<1) $= \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$ $\approx \frac{g_m R_S}{1 + g_m R_S} \quad (r_d \gg 10R_S)$
Drain-feedback bias E-MOSFET 	Medium (1 M Ω) $= \frac{R_F + r_d \parallel R_D}{1 + g_m (r_d \parallel R_D)}$ $= \frac{R_F}{1 + g_m R_D} \quad (r_d \gg 10R_D)$	Medium (2 k Ω) $= R_F \parallel r_d \parallel R_D$ $= R_D \quad (r_d, r_f \gg 10R_D)$	Medium (-10) $= \frac{-g_m (R_F \parallel r_d \parallel R_D)}{1 + g_m R_D}$ $\approx -g_m R_D \quad (r_d, r_f \gg 10R_D)$
Voltage-divider bias E-MOSFET 	Medium (1 M Ω) $= R_1 \parallel R_2$	Medium (2 k Ω) $= R_D \parallel r_d$ $= R_D \quad (r_d \gg 10R_D)$	Medium (-10) $= \frac{-g_m (r_d \parallel R_D)}{1 + g_m R_D}$ $\approx -g_m R_D \quad (r_d \gg 10R_D)$

Cascaded Configuration

$$A_v = A_{v1}A_{v2} = (-g_{m1}R_{D1})(-g_{m2}R_{D2}) = g_{m1}g_{m2}R_{D1}R_{D2}$$

