

**University Of Diyala**  
**College Of Engineering**  
**Computer Engineering Department**



# **COMPUTER ARCHITECTURE I**

## **PART 3: LOGIC MICRO- OPERATIONS**

**Asst. Prof. Ahmed Salah Hameed**

**Second stage**

**2022-2023**

# CONTENTS

- **Logic Micro-operations**
- **Shift Micro-operations**
- **Arithmetic Logic Shift Unit**


# 4-5 LOGIC MICRO-OPERATIONS

## THE FOUR BASIC MICRO-OPERATIONS

### OR Microoperation

Symbol:  $\vee$ , +

Gate:

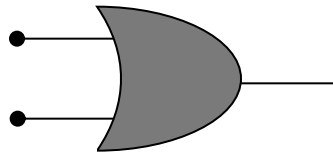

Example:  $100110_2 \vee 1010110_2 = 1110110_2$


# 4-5 LOGIC MICRO-OPERATIONS

## THE FOUR BASIC MICRO-OPERATIONS

### AND Microoperation

Symbol:  $\wedge$

Gate:

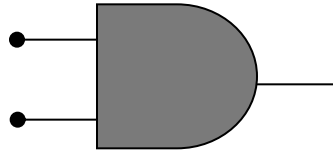

Example:  $100110_2 \wedge 1010110_2 = 0000110_2$


# 4-5 LOGIC MICRO-OPERATIONS

## THE FOUR BASIC MICRO-OPERATIONS

### Complement (NOT) Microoperation

Symbol:  $\overline{\quad}$

Gate:

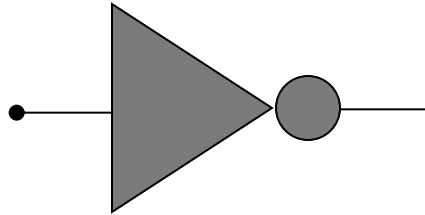

Example:  $\overline{1010110_2} = 0101001_2$


# 4-5 LOGIC MICRO-OPERATIONS

## THE FOUR BASIC MICRO-OPERATIONS

### XOR (Exclusive-OR) Micro-operation

Symbol:  $\oplus$

Gate:

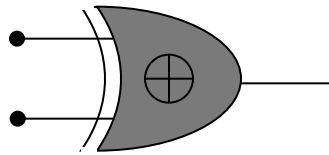

Example:  $100110_2 \oplus 1010110_2 = 1110000_2$


# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### NAND Micro-operation

Symbols:  $\wedge$  and  $\overline{\quad}$

Gate:

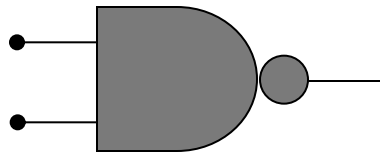

Example:  $\overline{100110_2 \wedge 1010110_2} = 1111001_2$


# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### NOR Micro-operation

Symbols:  $\vee$  and  $\overline{\quad}$

Gate:

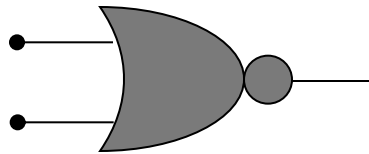

---

Example:  $100110_2 \vee 1010110_2 = 0001001_2$



# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### Selective-set Operation


Used to force selected bits of a register into logic-1 by using the OR operation

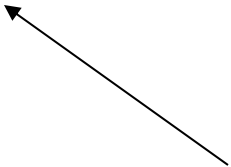Example:  $0100_2 \vee 1000_2 = 1100_2$

In a processor register



Loaded into a register from memory to perform the selective-set operation



# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### Selective-complement (toggling) Operation

Used to force selected bits of a register to be complemented by using the XOR operation

Example:  $0001_2 \oplus 1000_2 = 1001_2$

In a processor register

Loaded into a register from memory to perform the selective-complement operation

# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### Insert Operation

**Step1:** mask the desired bits

**Step2:** OR them with the desired value

**Example:** suppose  $R1 = 0110\ 1010$ , and we desire to replace the leftmost 4 bits (0110) with 1001 then:

- Step1:  $0110\ 1010 \wedge 0000\ 1111$
- Step2:  $0000\ 1010 \vee 1001\ 0000$

**→  $R1 = 1001\ 1010$**

# 4-5 LOGIC MICRO-OPERATIONS

## OTHER LOGIC MICRO-OPERATIONS

### Set (Preset) Micro-operation

Force all bits into 1's by ORing them with a value in which all its bits are being assigned to logic-1

**Example:**  $100110_2 \vee 111111_2 = 111111_2$

### Clear (Reset) Micro-operation

Force all bits into 0's by ANDing them with a value in which all its bits are being assigned to logic-0


**Example:**  $100110_2 \wedge 000000_2 = 000000_2$

# **4-5 LOGIC MICRO-OPERATIONS HARDWARE IMPLEMENTATION**

- ❑ The hardware implementation of logic micro-operations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function**
- ❑ Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.**

# 4-5 LOGIC MICRO-OPERATIONS

## HARDWARE IMPLEMENTATION CONT.

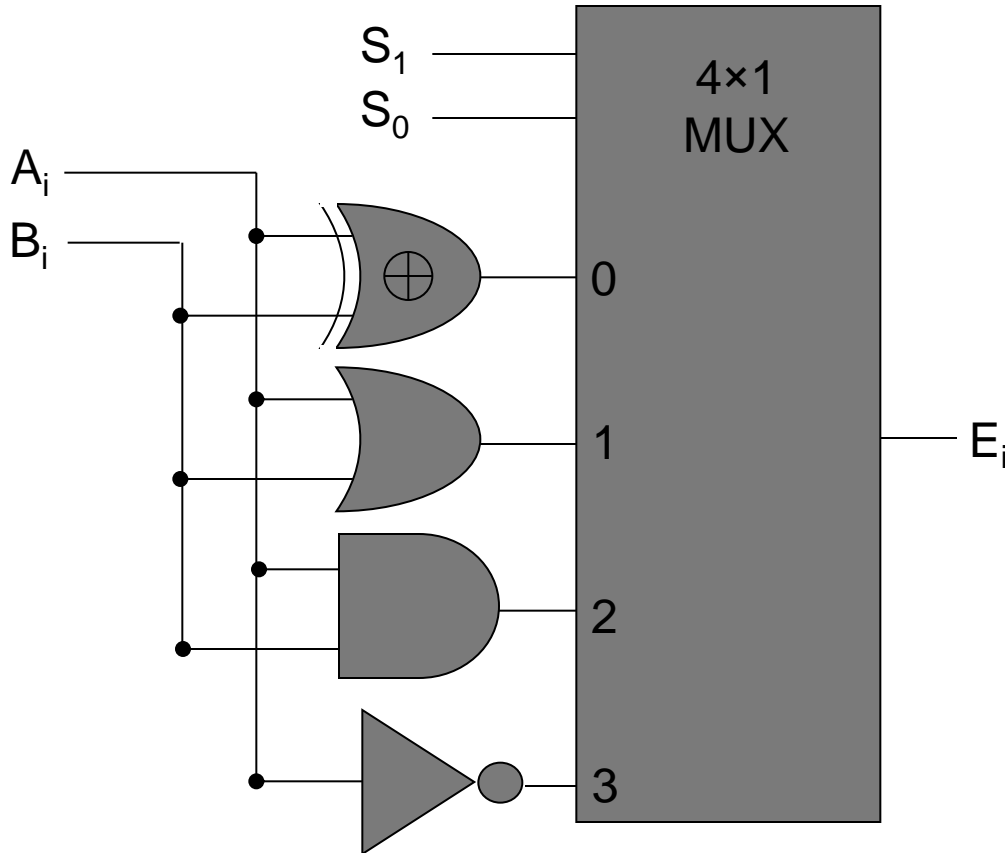

$S_1$	$S_0$	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \vee B$	OR
1	0	$E = A \wedge B$	AND
1	1	$E = A$	Complement

This is for one bit  $i$

Figure B

## **4-6 SHIFT MICROOPERATIONS**


- ❑ Used for serial transfer of data**
- ❑ Also used in conjunction with arithmetic, logic, and other data-processing operations**
- ❑ The contents of the register can be shifted to the left or to the right**
- ❑ As being shifted, the first flip-flop receives its binary information from the serial input**
- ❑ Three types of shift: Logical, Circular, and Arithmetic**

# 4-6 SHIFT MICROOPERATIONS CONT.



**Shift Right**

Determines  
the "shift"  
type

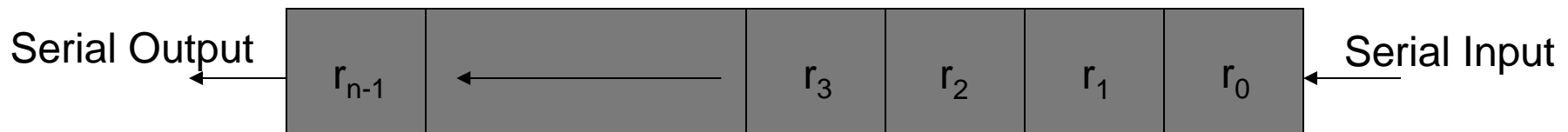

**Shift Left**


\*\*Note that the bit  $r_i$  is the bit at position (i) of the register




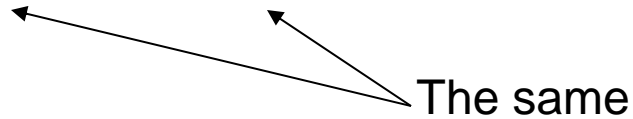
# 4-6 SHIFT MICRO-OPERATIONS: LOGICAL SHIFTS

Transfers 0 through the serial input

Logical Shift Right:  $R1 \leftarrow shr R1$



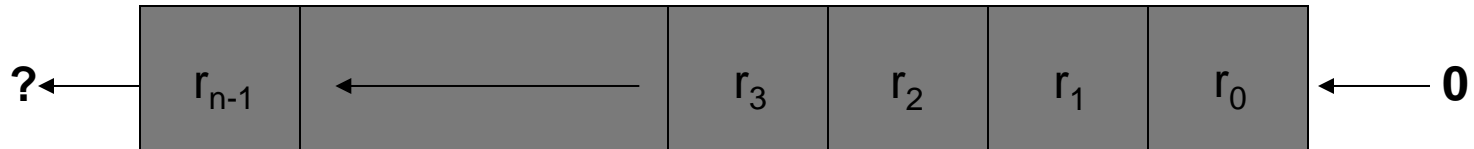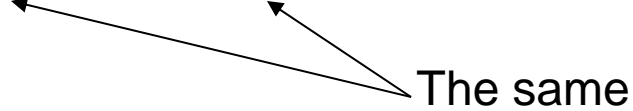Logical Shift Left:  $R2 \leftarrow shl R2$



Logical Shift Left

# 4-6 SHIFT MICRO-OPERATIONS: CIRCULAR SHIFTS (ROTATE OPERATION)


Circulates the bits of the register around the two ends without loss of information

Circular Shift Right:  $R1 \leftarrow \text{cir } R1$

The same

Circular Shift Left:  $R2 \leftarrow \text{cil } R2$

The same

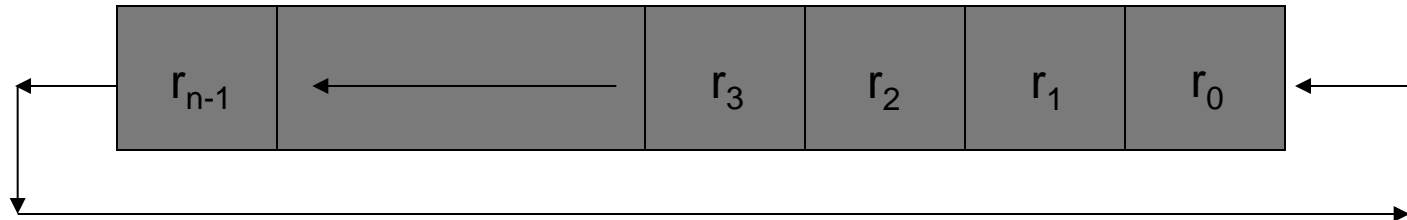

Circular Shift Left

# **4-6 SHIFT MICRO-OPERATIONS**

## **ARITHMETIC SHIFTS**

**Shifts a signed binary number to the left or right**

**An arithmetic shift-left multiplies a signed binary number by 2:**

**ashl (00100): 01000**


**An arithmetic shift-right divides the number by 2**

**ashr (00100) : 00010**

**An overflow may occur in arithmetic shift-left, and occurs when the sign bit is changed (sign reversal)**


# 4-6 SHIFT MICRO-OPERATIONS

## ARITHMETIC SHIFTS CONT.

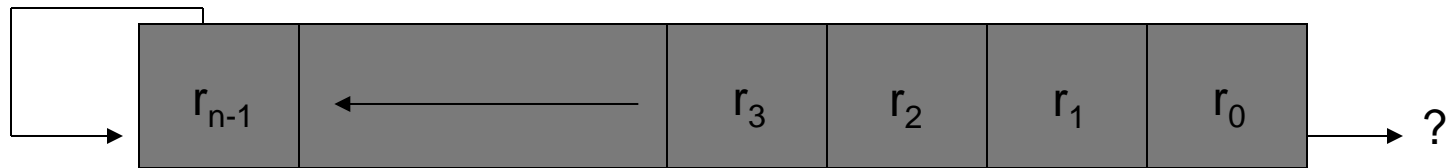

Sign  
Bit

**Arithmetic Shift Right**

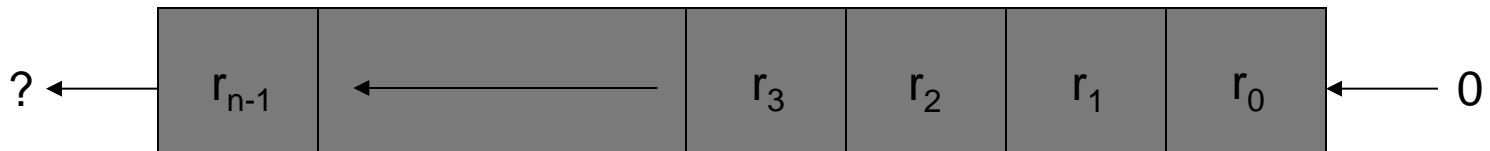

Sign  
Bit

**Arithmetic Shift Left**

## 4-6 SHIFT MICROOPERATIONS CONT.

**Example: Assume  $R1=11001110$ , then:**

- Arithmetic shift right once :  $R1 = 11100111$
- Arithmetic shift right twice :  $R1 = 11110011$
- Arithmetic shift left once :  $R1 = 10011100$
- Arithmetic shift left twice :  $R1 = 00111000$
- Logical shift right once :  $R1 = 01100111$
- Logical shift left once :  $R1 = 10011100$
- Circular shift right once :  $R1 = 01100111$
- Circular shift left once :  $R1 = 10011101$

# **4-6 SHIFT MICRO-OPERATIONS HARDWARE IMPLEMENTATION**


**A possible choice for a shift unit would be a bidirectional shift register with parallel load (refer to Fig 2-9). Has drawbacks:**

- Needs two pulses (the clock and the shift signal pulse)
- Not efficient in a processor unit where multiple number of registers share a common bus

**It is more efficient to implement the shift operation with a combinational circuit**

# 4-6 SHIFT MICRO-OPERATIONS

## HARDWARE IMPLEMENTATION CONT.

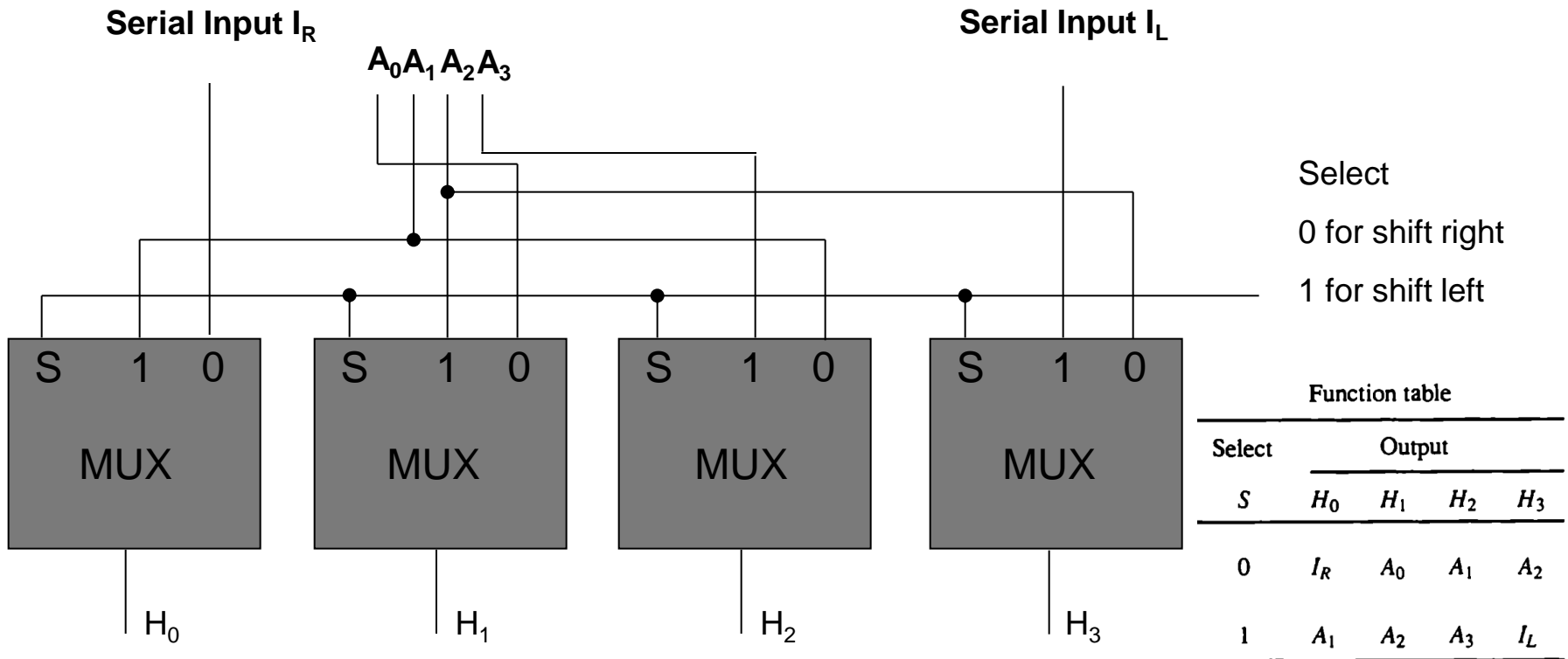


4-bit Combinational Circuit Shifter

# 4-7 ARITHMETIC LOGIC SHIFT UNIT

Instead of having individual registers performing the Microoperations directly, computer systems employ a number of storage registers connected to a common operational unit called an Arithmetic Logic Unit (ALU)



# 4-7 ARITHMETIC LOGIC SHIFT UNIT CONT.

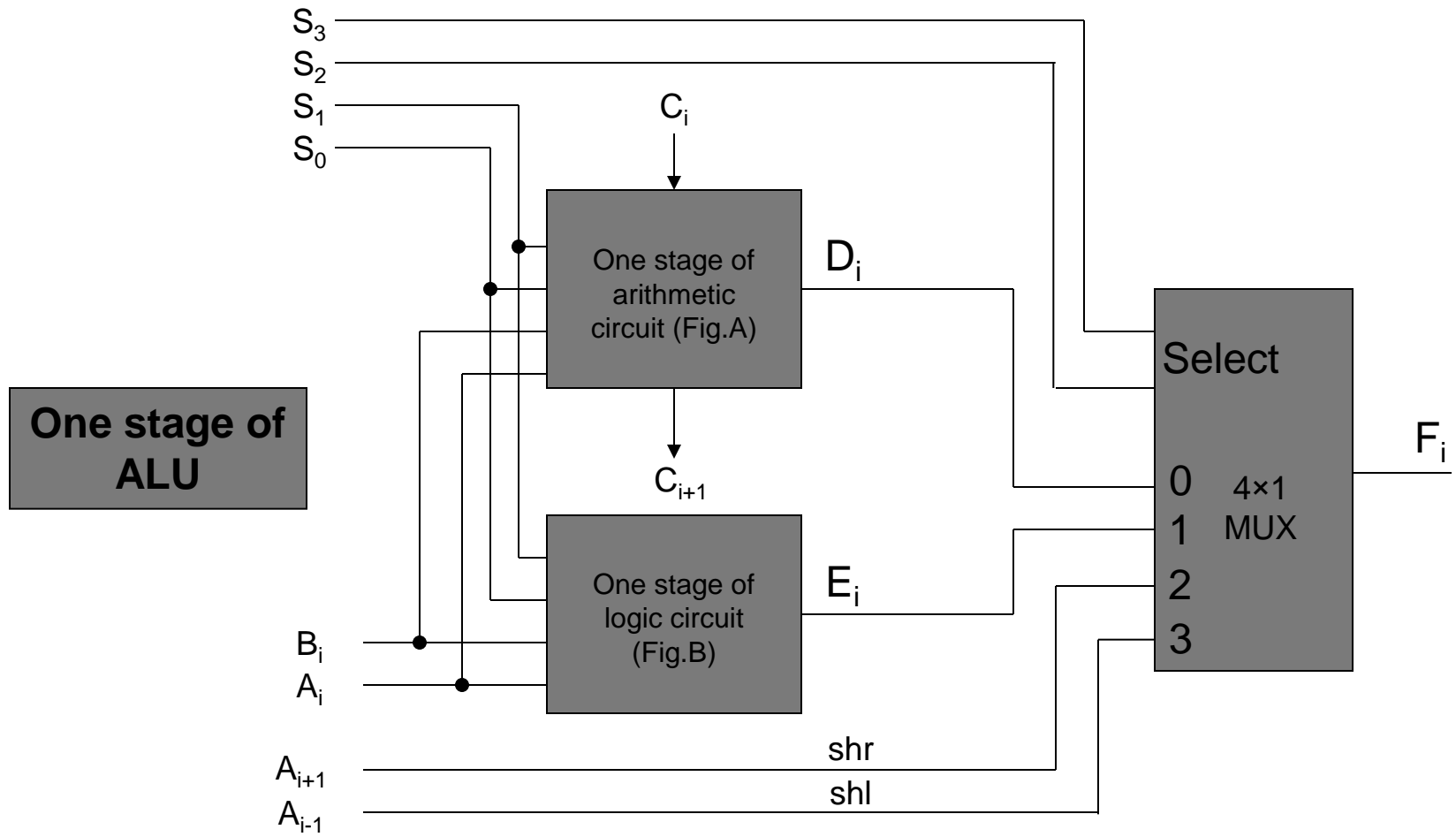

# 4-7 FUNCTION TABLE

## ARITHMETIC LOGIC SHIFT UNIT

Operation select					Operation	Function
$S_3$	$S_2$	$S_1$	$S_0$	$C_{in}$		
0	0	0	0	0	$F = A$	Transfer $A$
0	0	0	0	1	$F = A + 1$	Increment $A$
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + \bar{B}$	Subtract with borrow
0	0	1	0	1	$F = A + \bar{B} + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement $A$
0	0	1	1	1	$F = A$	Transfer $A$
0	1	0	0	x	$F = A \wedge B$	AND
0	1	0	1	x	$F = A \vee B$	OR
0	1	1	0	x	$F = A \oplus B$	XOR
0	1	1	1	x	$F = \bar{A}$	Complement $A$
1	0	x	x	x	$F = \text{shr } A$	Shift right $A$ into $F$
1	1	x	x	x	$F = \text{shl } A$	Shift left $A$ into $F$