 


multiplexers Implementation



5/4/2017

26

X3	X2	X1	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1


1. Put X3 at level 1
2. Put X2 at level 2
3. Put X1 at level 3 o\p

- Example 2 Input LUT

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	1

$f = x_1'x_2' + x_1x_2$, or using Shannon's expansion:
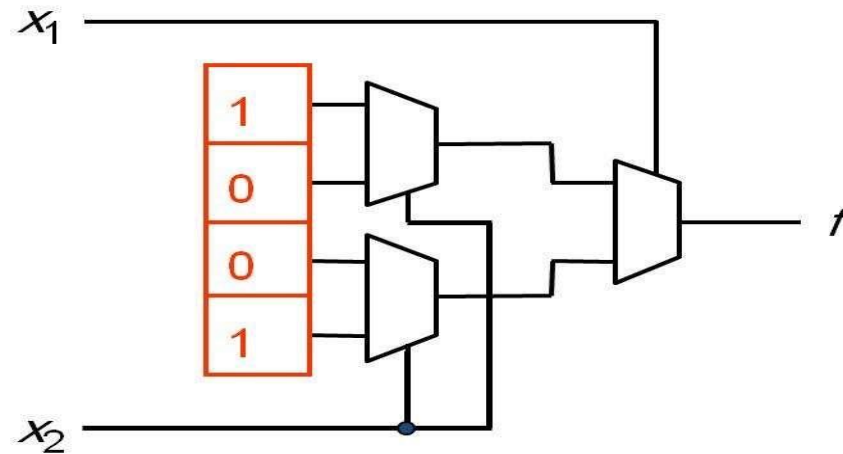
$$\begin{aligned} f &= x_1'(x_2') + x_1(x_2) \\ &= x_1'(x_2'(1) + x_2(0)) + x_1(x_2'(0) + x_2(1)) \end{aligned}$$




Implementation LUT with 3 input

- 3 Input LUT

- 7 2x1 MUXes and 8 storage cells are required

 - Commercial LUTs have 4-5 inputs, and 16-32 storage cells



Q1: you are asked to program an FPGA, whose LUTs and inter-connection wires are shown in **Figure below**. The function to be implemented is $f = f1 _ f2$, where $f1 = a + b$ and $f2 = a + c$. LUT 1 should implement $f1$. LUT 2 should implement $f2$ and LUT 3 should implement $f1-f2$. The horizontally and vertically placed interconnection wires are fabricated in different planes. In order to depict a connection between these wires at a cross-point, place a cross-mark (X). The inputs a ; b ; c and the output f have already been connected to the “input-output pads

