

University Of Diyala
College Of Engineering
Computer Engineering Department



Digital System Design II


Dr. Yasir Al-Zubaidi

Third stage

2019

Multiplexer-Based Single Register Transfers

 - MUX connected to register outputs produce flexible transfer structures
- Transfers: $K1: \underline{R0} \leftarrow R1$
 $K2 \ K1: R0 \leftarrow R2$




Register Design

- Assume: a register consists of identical cells
- Register design can be approached as follows:
 - Design a representative cell for the register
 - Make copies of the cell and connect together to form the register
 - Applying appropriate “boundary conditions” to cells that need to be different and contract if appropriate
- Register cell design is the first step of the above process

Approach I: Multiplexer-based

- An n-input multiplexer with a variety of sources and functions
- Load enable by OR of control signals K_0, K_1, \dots, K_{n-1} (for 00...0, no load)
- Use encoder + multiplexer to select sources and/or transfer functions

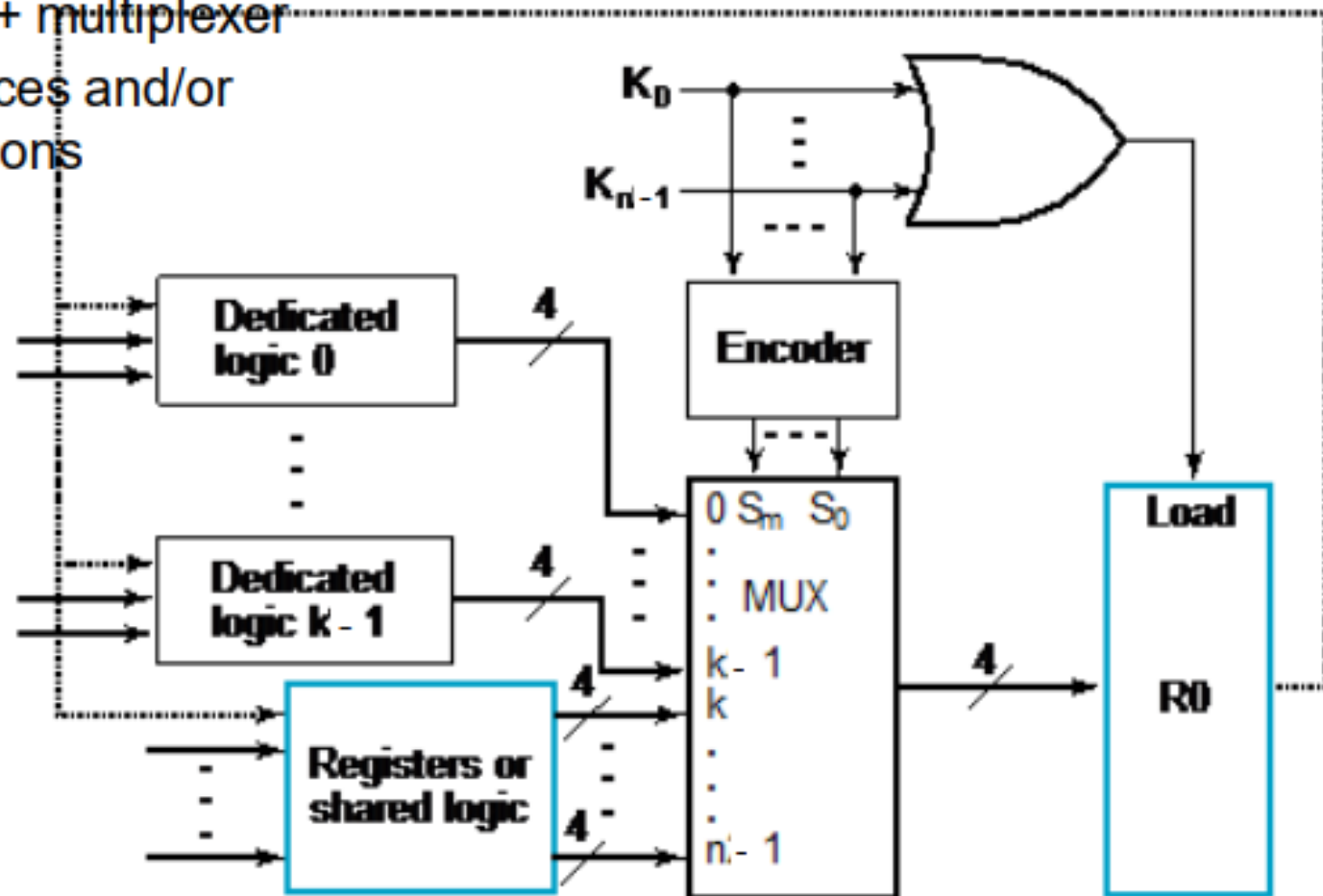

Example 1: Register Cell Design

- Register A (m-bits) Specification:
 - Data input: B; Control inputs (CX, CY): (0,0), (0,1) (1,0)
 - Register transfers:
 - CX: $A \leftarrow B \vee A$; CY : $A \leftarrow B \oplus A$; Hold state: (0,0)
- Load Control: Load = CX + CY
- Since all control combinations appear as if encoded (0,0), (0,1), (1,0), can use multiplexer without encoder:

$$S_1 = CX$$

$$S_0 = CY$$

$$I_0 = A_i$$


$$I_1 = A_i \leftarrow B_i \oplus A_i$$

$$I_2 = A_i \leftarrow B_i \vee A_i$$

Hold A

CY = 1

CX = 1

 

Approach II: Sequential Circuit Design

- Find a state diagram or state table
- For optimization:
 - Use K-maps for up to 4 to 6 variables
 - Otherwise, use computer-aided or manual optimization

Example 1 Again

- State Table for D_i :

	Hold	$A_i \vee B_i$		$A_i \oplus B_i$	
A_i	$CX = 0$ $CY = 0$	$CX = 1$ $CY = 0$ $B_i = 0$	$CX = 1$ $CY = 0$ $B_i = 1$	$CX = 0$ $CY = 1$ $B_i = 0$	$CX = 0$ $CY = 1$ $B_i = 1$
0	0	0	1	0	1
1	1	1	1	1	0

- Four variables (CX, CY, A, B) should give a total of 16 state table entries
- By using:
 - Combinations of variable names and values
 - Don't care conditions (for $CX = CY = 1$)only 12 entries are required to represent the 16 entries

Example 1 Again (Contd.)

- K-map - Use variable ordering CX , CY , A_i , B_i and assume a D flip-flop

				A_i	
D_i	0	0	1	1	
	0	1	0	1	
	X	X	X	X	CY
CX	0	1	1	1	
					B_i

Example 1 Again (Contd.)

- The resulting SOP equation:

$$\begin{aligned}D_i &= CX B_i + CY \bar{A}_i B_i + A_i \bar{B}_i + \bar{C} \bar{Y} A_i \\ &= CX B_i + \bar{A}_i (CY B_i) + A_i (\bar{C} \bar{Y} B_i) \\ &= CX B_i + A_i \oplus (CY B_i)\end{aligned}$$


The gate input cost per cell = 13

- The gate input cost per cell for the previous version is:
 - Per cell: 19
 - Shared decoder logic: 8
- Cost gain by sequential design > 6 per cell
- Also, no Enable on the flip-flop makes it cost less

Serial Transfers and Microoperations

- Serial Transfers
 - Used for “narrow” transfer paths
 - Example 1: Telephone or cable line
 - Parallel-to-Serial conversion at source
 - Serial-to-Parallel conversion at destination

 - Serial microoperations
 - Example 1: Addition
 - A low cost way
 - Loss in performance



Overview

- Datapath and control
- Microoperations
- **Sequencing and control**
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

Control Unit Types

- Two distinct classes:
 - Programmable
 - Non-programmable.
- A programmable control unit:
 - An external memory array for storing instructions and control information
 - A program counter (PC) register points to the next instruction to be executed
 - Decision logic for determining the sequence of operations and logic to interpret the instructions
- A non-programmable control unit: does not fetch instructions from a memory and is not responsible for sequencing instructions

Algorithmic State Machines


- The function of a sequential circuit can be represented by a state table or a state diagram.

- An Algorithmic State Machine (ASM) is a flowchart-like way to specify state diagrams for sequential logic and, optionally, actions performed in a datapath.
 - A flowchart is a way of showing actions and control flow in an algorithm.
 - An ASM explicitly specifies a sequence of actions and their timing relationships
 - An ASM chart directly leads to a hardware realization

- Primitives:
 1. State Box (a rectangle)
 2. Decision Box
 - I. Scalar (a diamond)
 - II. Vector (a hexagon)
 3. Conditional Output Box (an oval)


State Box

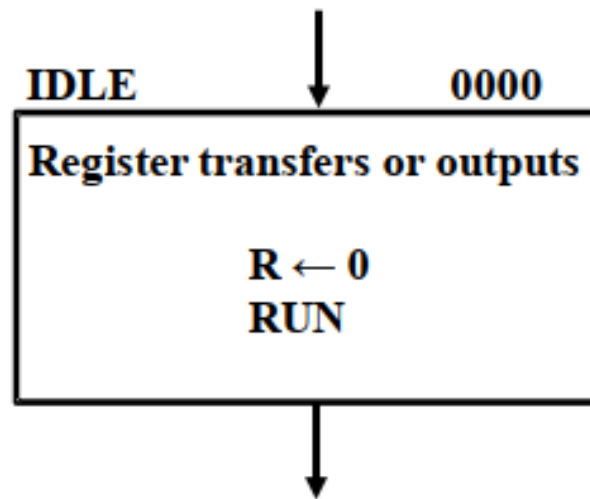- A rectangle with:
 - The symbolic name for the state
 - An optional state code
 - Containing register transfer operations, and outputs activated within or while leaving the state
- The symbolic name for the state marked outside the upper left top
- An optional state code, if assigned, outside the upper right top




Decision Box

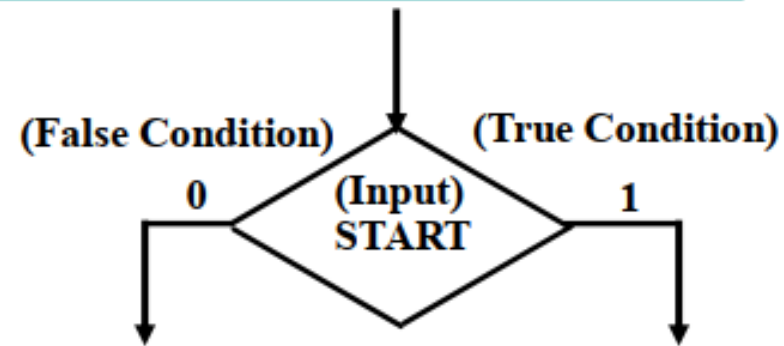- **Scalar** : A diamond with:
 - One input path (entry point).
 - One input condition that is tested.
 - A TRUE/FALSE exit path (logic 1/0).




 - **Vector**: A hexagon with:
 - One input path (entry point).
 - A vector of input conditions tested.
 - Up to 2^n output paths. The path taken has a binary vector value that matches the vector input condition




Conditional Output Box

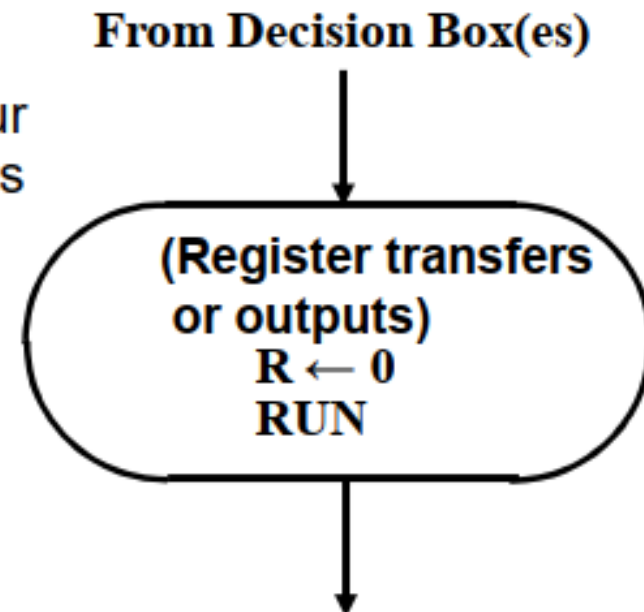- An oval with:
 - One input path from a decision box(es)
 - One output path
 - Register transfers or outputs that occur only if the conditional path to the box is taken.
- Transfers and outputs
 - in a state box are Moore type - dependent only on state
 - in a conditional output box are Mealy type - dependent on both state and inputs



Connecting Boxes Together

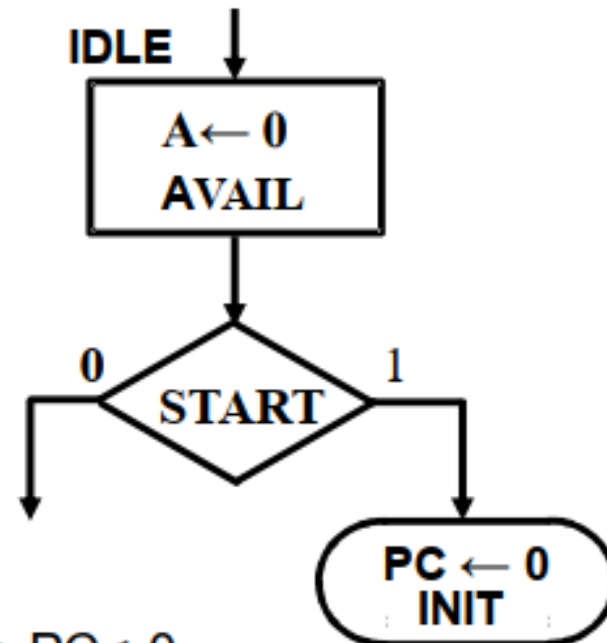
- By connecting boxes together, we see the power of expression.



- What are the:
 - Inputs? start
 - Outputs? Avail, Init
 - Conditional Outputs?
 - Transfers? $A \leftarrow 0$, $PC \leftarrow 0$
 - Conditional Transfers? INIT, transfer: $PC \leftarrow 0$



ASM Blocks

 - One state box along with all decision and conditional output boxes connected to it, called an **ASM Block**. i.e., the ASM Block includes all items on the path from the current state to the same or other states.




ASM Timing

 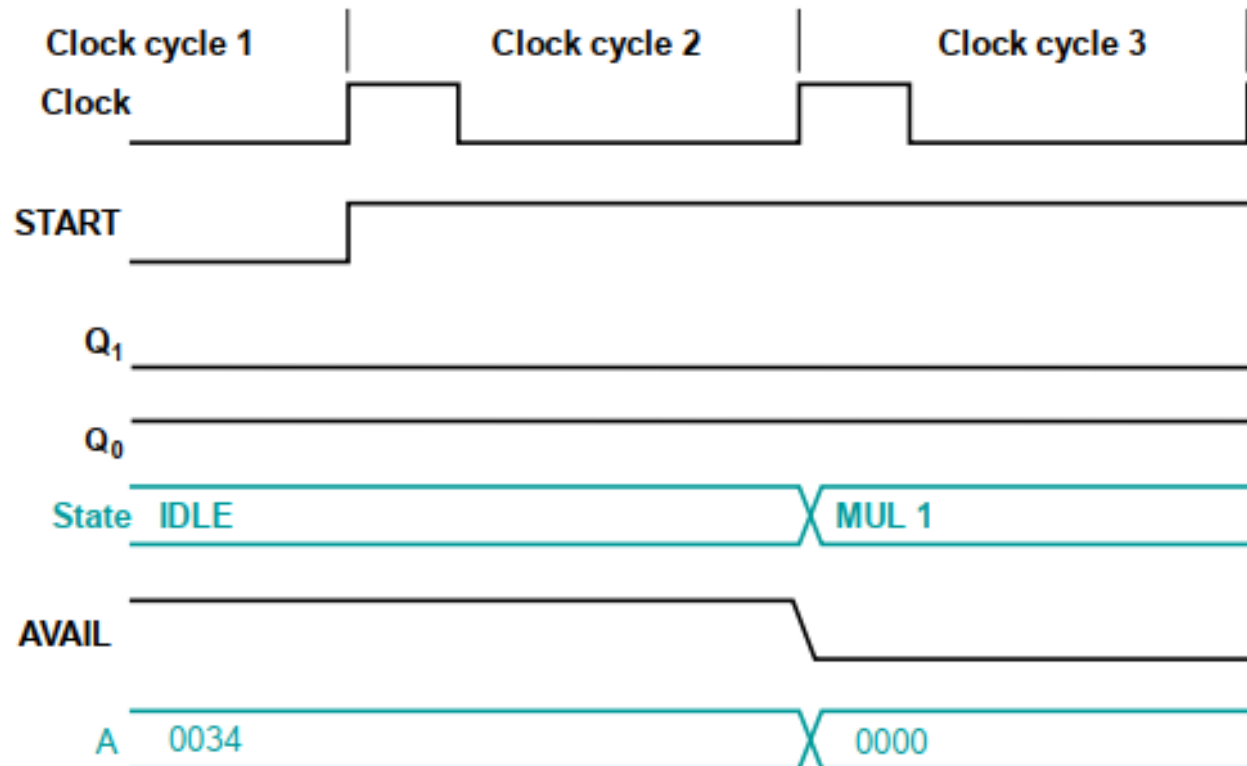- Outputs appear while in the state
- Register transfers and conditional outputs occur at the clock while exiting the state - New value occur in the next state!



Multiply Overview

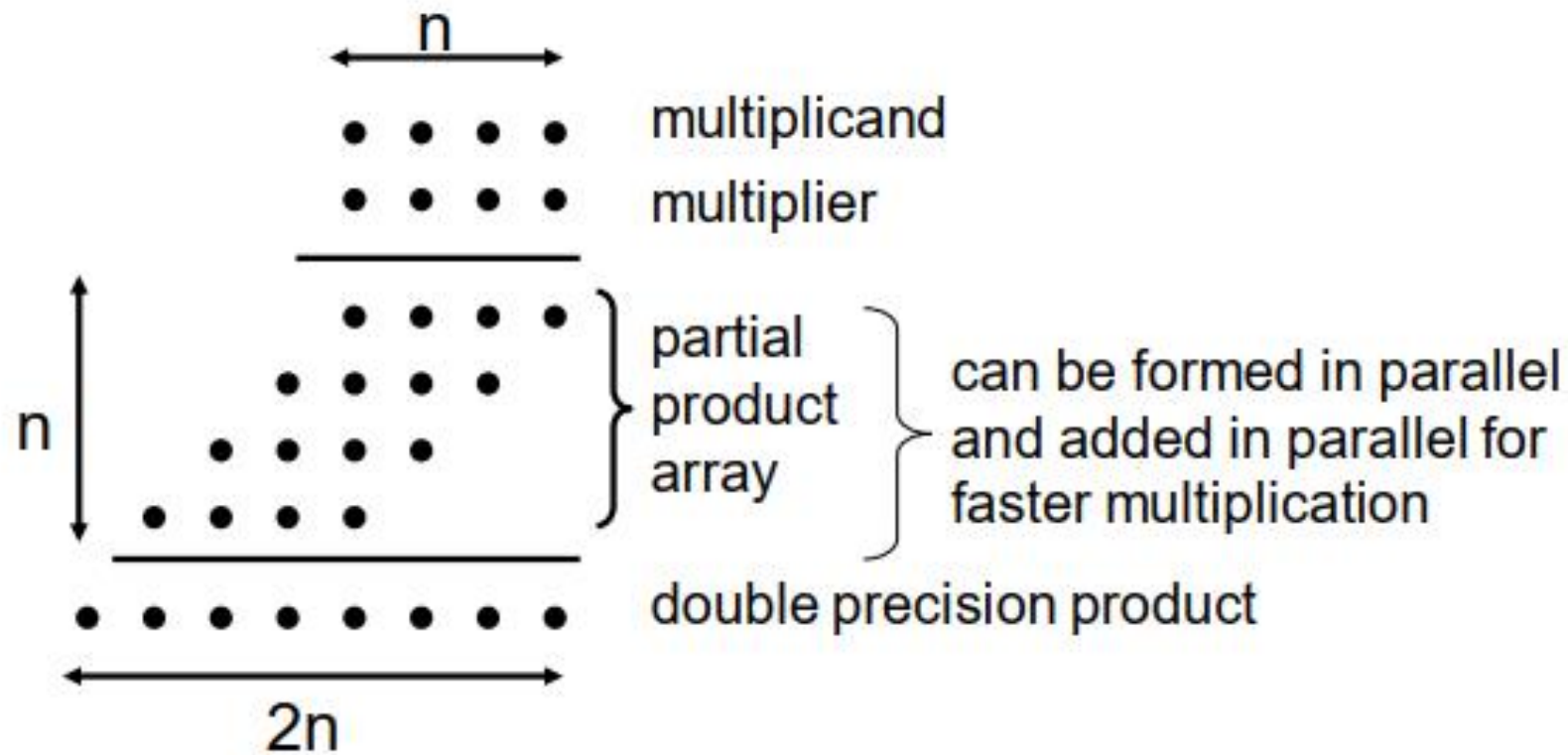- Binary multiplication is just a *bunch* of left shifts and adds




Multiplier Example

- Example: (101 x 011) Base 2
- Partial products are:
101 x 0, 101 x 1, and 101 x 1


				1	0	1	multiplicand	
			x	0	1	1	multiplier	
				<hr/>				
				1	0	1		
				1	0	1		
			0	0	0			
			<hr/>					
0	0	1	1	1	1	1		

 Multiplication: Implementation (version 1)




Unsigned shift-add multiplier (version 1)

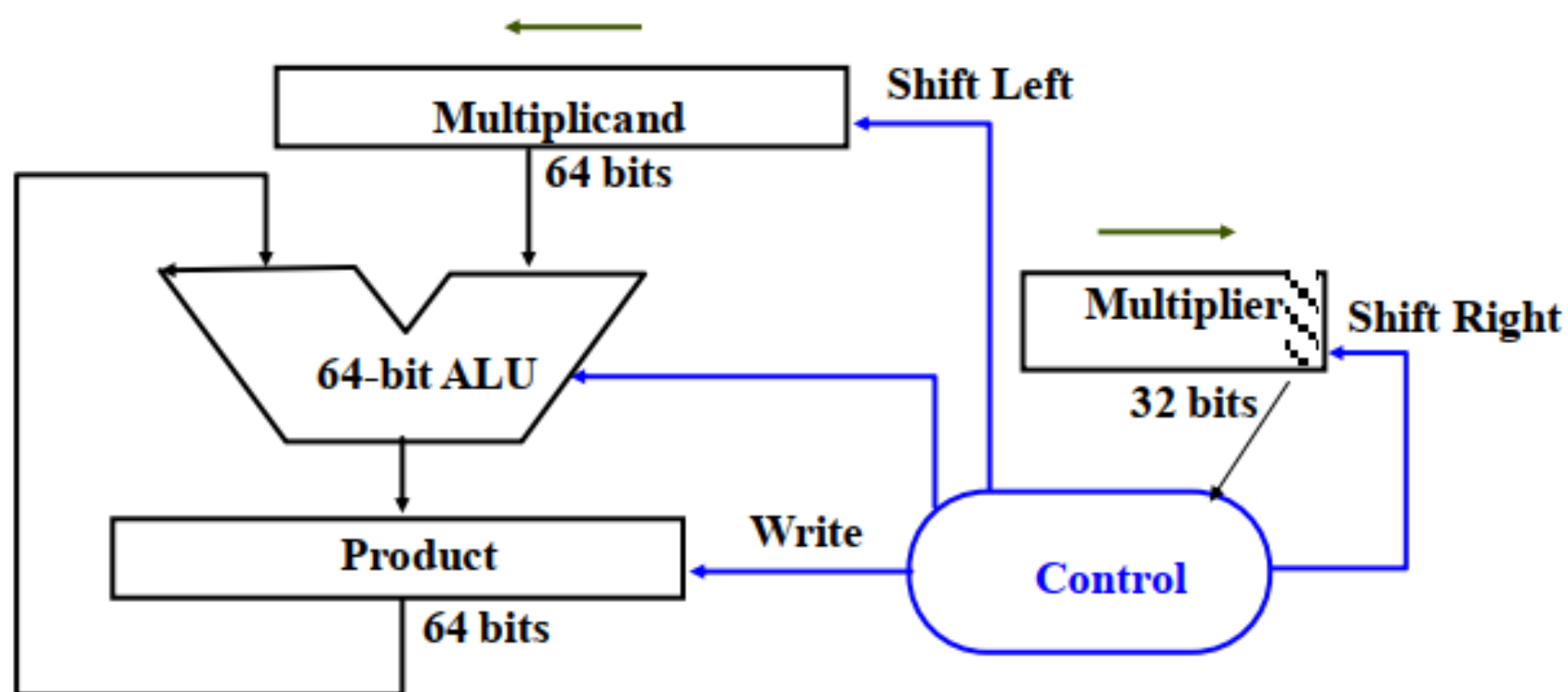- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

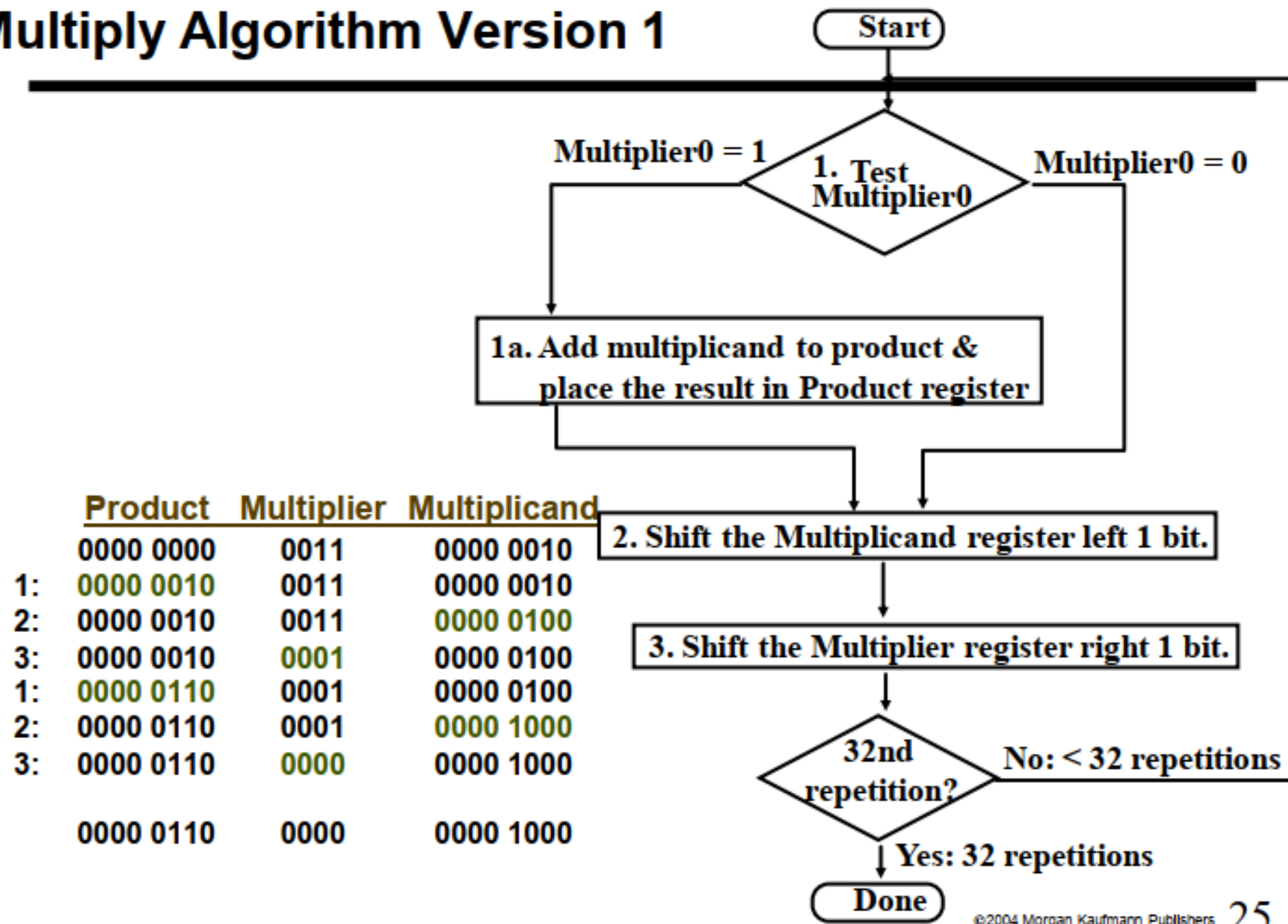


	Product	Multiplier	Multiplicand
	0000 0000	0011	0000 0010
1:	0000 0010	0011	0000 0010
2:	0000 0010	0011	0000 0100
3:	0000 0010	0001	0000 0100
1:	0000 0110	0001	0000 0100
2:	0000 0110	0001	0000 1000
3:	0000 0110	0000	0000 1000
	0000 0110	0000	0000 1000

Observations on Multiply Version 1


- 1 clock per cycle $\Rightarrow \approx 100$ clocks per multiply because of 32 repetitions, 3 steps in one repetition
 - Ratio of add/sub to multiply is from 5:1 to 100:1
 - Slow
- 0's inserted in the rightmost bit of multiplicand as shifting left
 - \Rightarrow least significant bits of product never changed once formed
- 1/2 bits in multiplicand always 0
 - MSB are 0s at the beginning
 - 0 is inserted in LSB as multiplicand shifting left
 - \Rightarrow 64-bit multiplicand register is wasted
 - \Rightarrow 64-bit adder is wasted
- **Instead of shifting multiplicand to left, let's shift product to right**

MULTIPLY HARDWARE Version 2

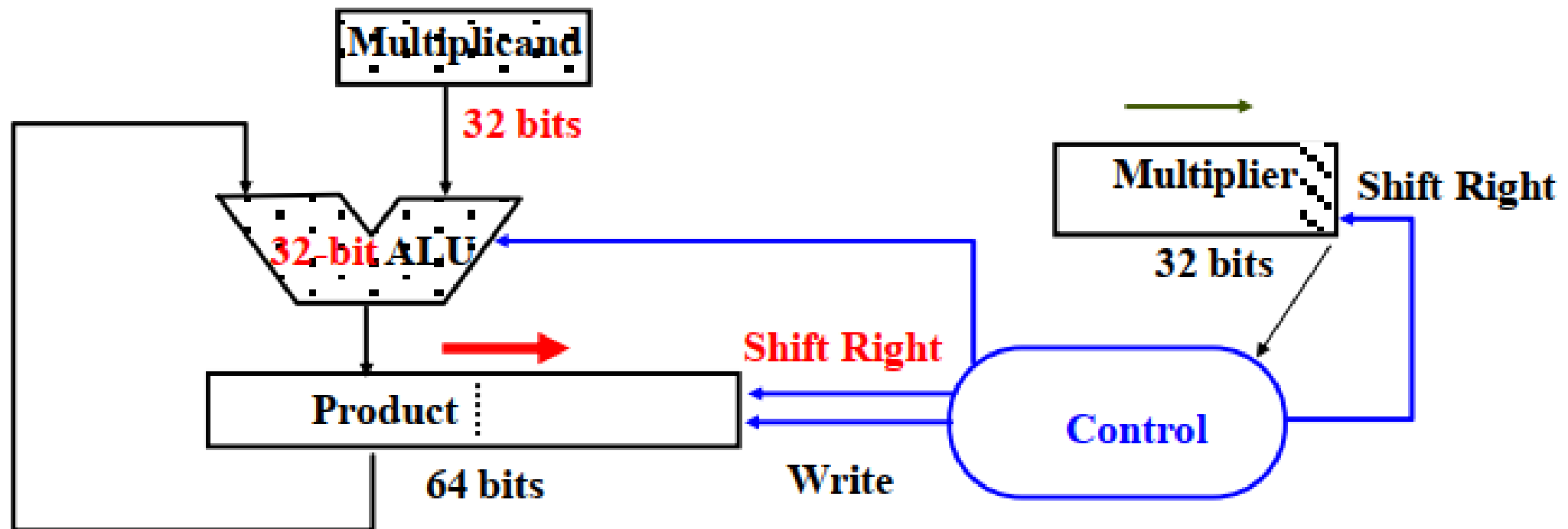- 32-bit Multiplicand reg, 32 -bit ALU, 64-bit Product reg, 32-bit Multiplier reg




Multiply Algorithm Version 2

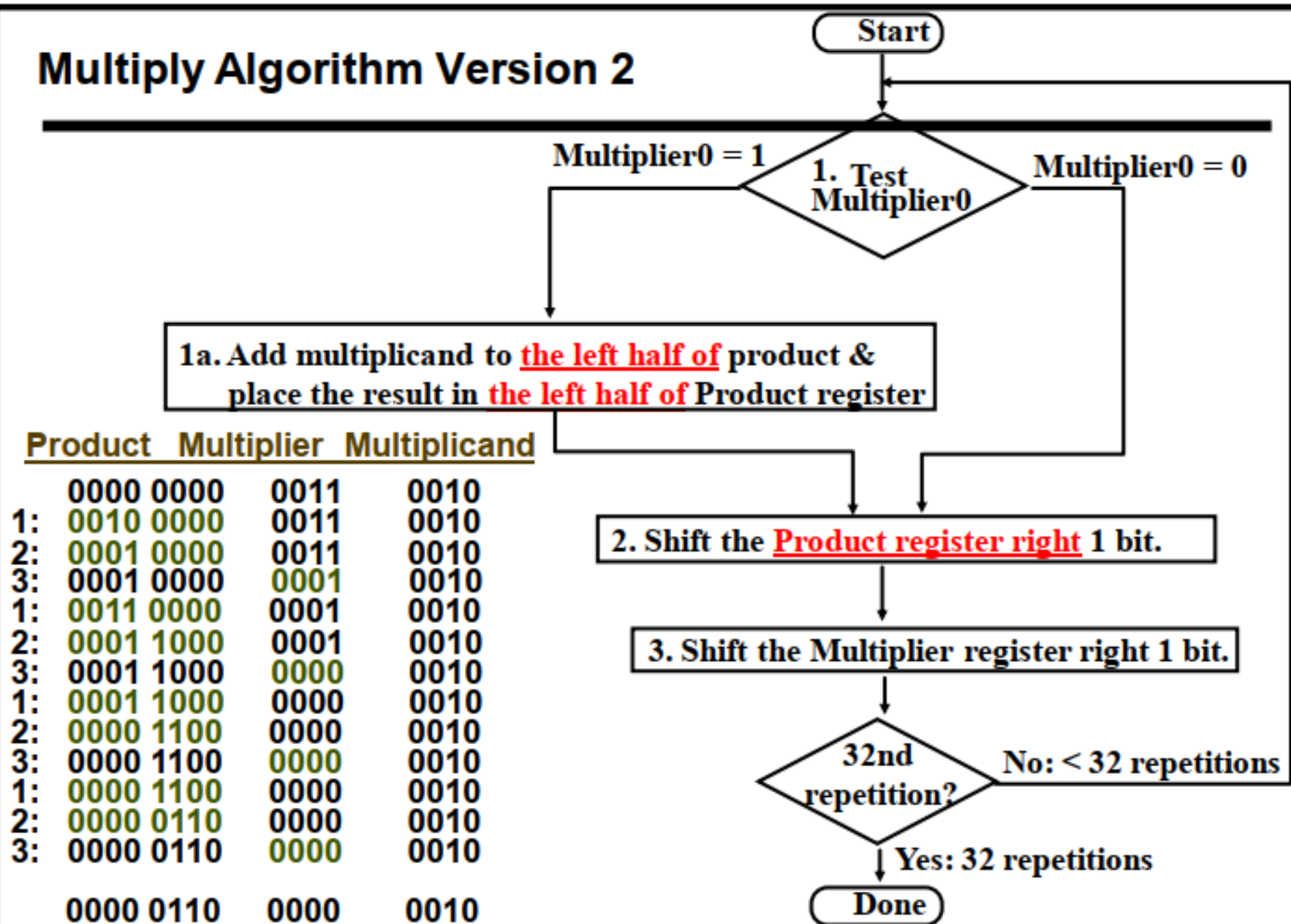

	Product	Multiplier	Multiplicand
	0000 0000	0011	0010
1:	0010 0000	0011	0010
2:	0001 0000	0011	0010
3:	0001 0000	0001	0010
1:	0011 0000	0001	0010
2:	0001 1000	0001	0010
3:	0001 1000	0000	0010
1:	0001 1000	0000	0010
2:	0000 1100	0000	0010
3:	0000 1100	0000	0010
1:	0000 1100	0000	0010
2:	0000 0110	0000	0010
3:	0000 0110	0000	0010
	0000 0110	0000	0010

Still more wasted space in Version2!

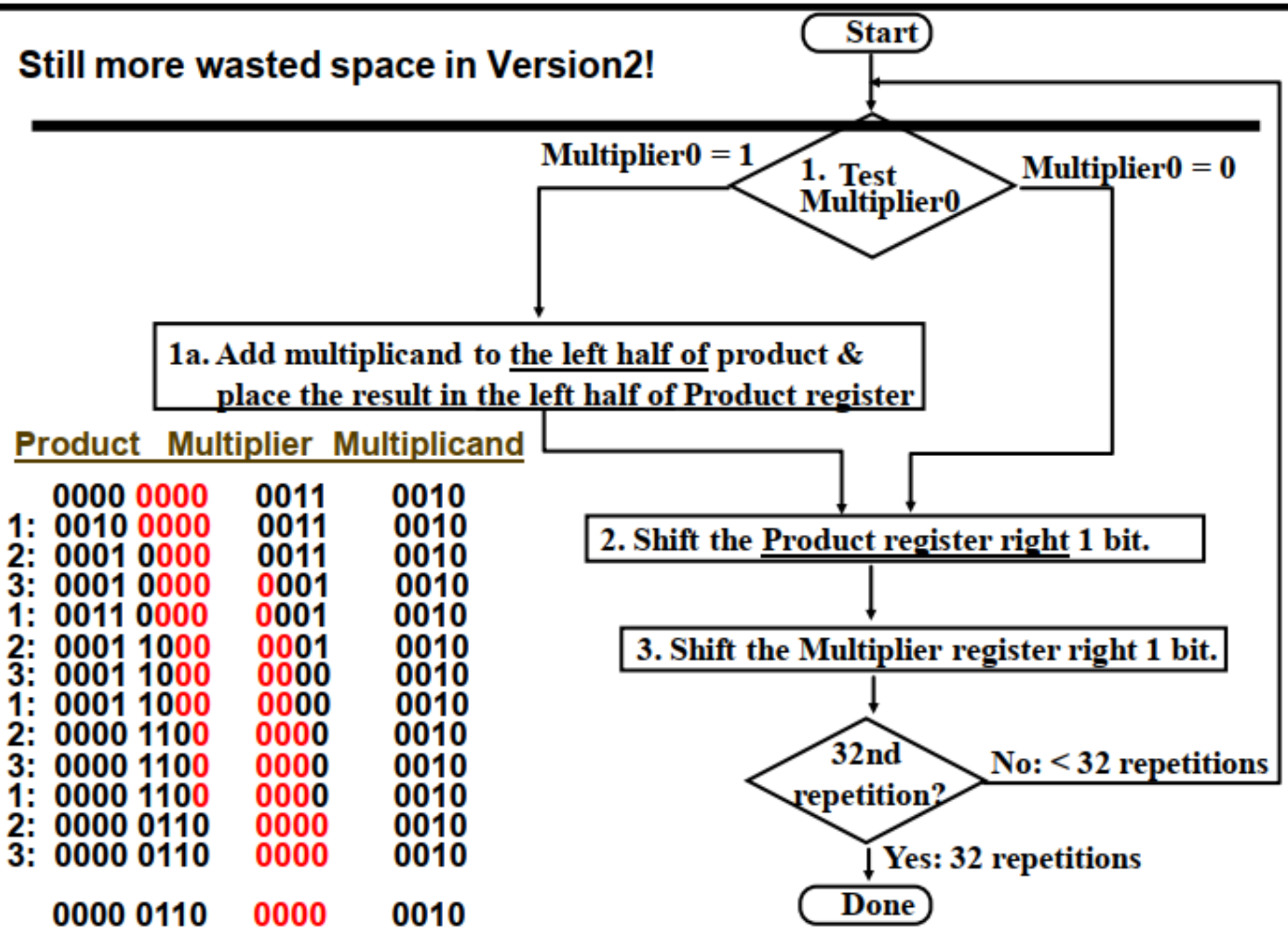

Observations on Multiply Version 2


- Product register **wastes space that exactly matches size of multiplier**
=> **combine Multiplier register and Product register**

Example (1 0 1) x (0 1 1) Again

- Reorganizing example to follow hardware algorithm:

	1	0	1									← Multiplicand (B)
x	0	1	1									← Multiplier (Q)
0	0	0	0									Clear C A (Carry and register A)
+	1	0	1									Multiplier ₀ = 1 => Add B
	<hr/>											Addition
0	1	0	1									Shift Right (Zero-fill C)
0	0	1	0	1								Multiplier ₁ = 1 => Add B
+	1	0	1									Addition
	<hr/>											Addition
0	1	1	1	1								Shift Right
0	0	1	1	1	1							Multiplier ₂ = 0 => No Add, Shift Right
0	0	0	1	1	1	1						Right

Multiplier Example: Block Diagram

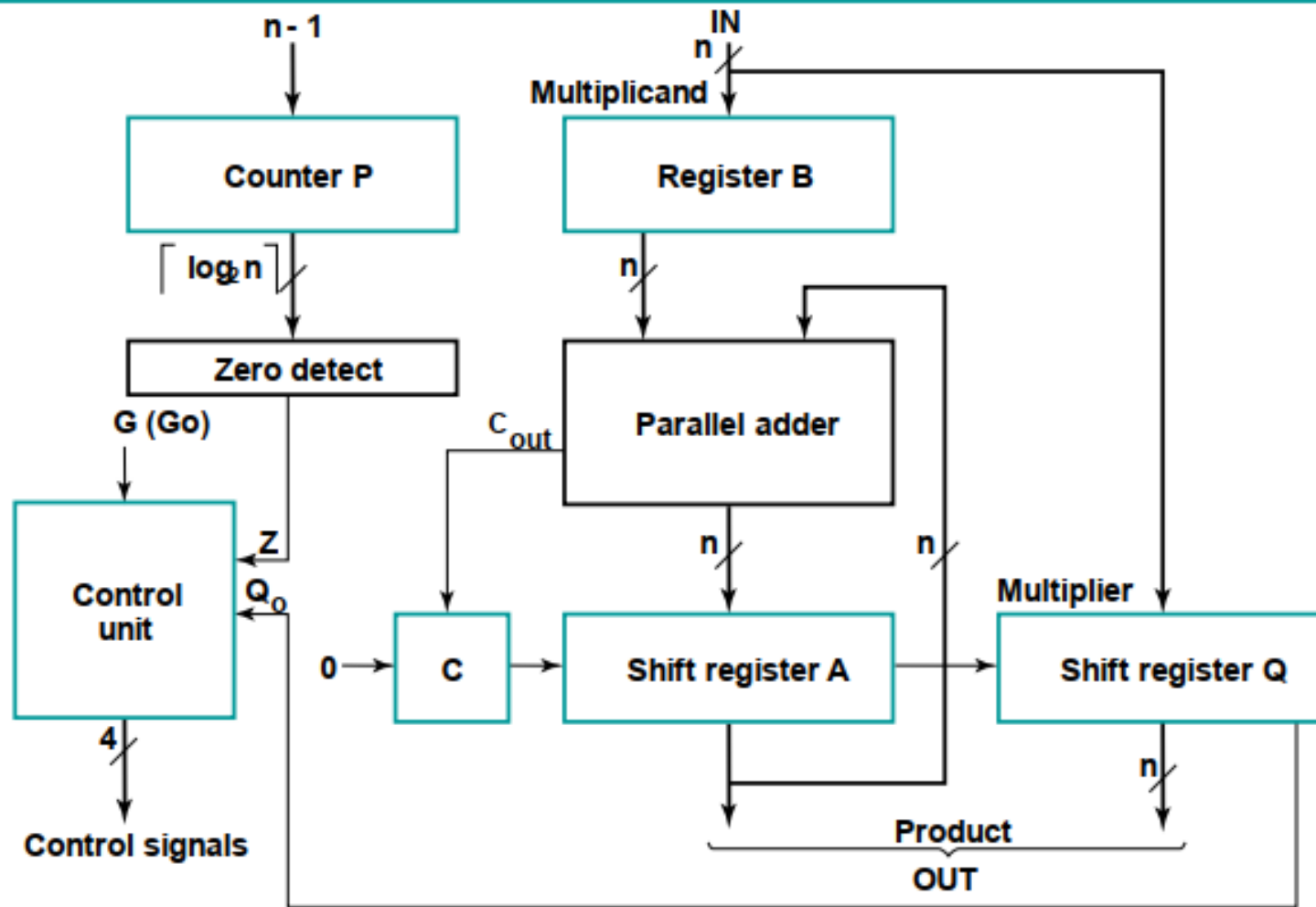

Multiplexer Example: Operation

1. The multiplicand is loaded into register B.
2. The multiplier is loaded into register Q.
3. When G becomes 1, register C|| A is initialized to 0.
4. Down Counter P is initialized to $n - 1$ (n = number of bits in multiplier)
5. The partial products are formed in register C||A||Q.
6. Each multiplier (Q) bit, beginning with the LSB, is processed (if bit is 1, B is added to partial product of A; if bit is 0, do nothing)
7. C||A||Q is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
8. Steps 6 and 7 are repeated until $P = 0$ as detected by Zero detect.