

University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

ASM Based Datapath and Control Design

Dr. Yasir Al-Zubaidi


Third stage

2021

Overview

- Datapath and control
- Microoperations
- **Sequencing and control**
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

Multiplier Example: ASM Chart

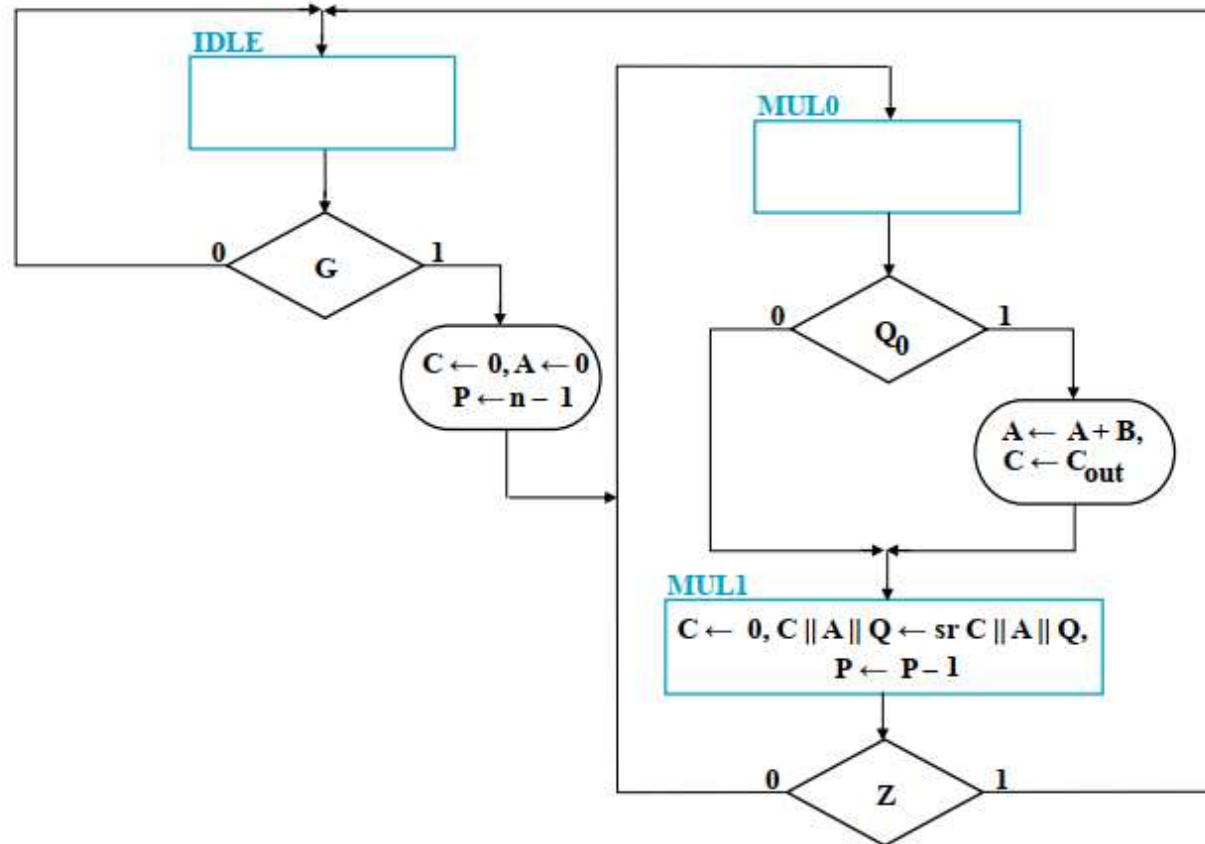

Multiplier Example: ASM Chart (Contd.)

- Three states employed here:
 - IDLE state:
 - input G is used as the condition for starting the multiplication
 - C, A, and P are initialized
 - MUL0 state: conditional addition is performed based on the value of Q_0 .
 - MUL1 state:
 - right shift is performed to capture the partial product and position the next bit of the multiplier in Q_0
 - Down counter $P = P - 1$
 - $P=0$ is used to sense completion or continuation of the multiplication.

Multiplier Example: Control Signal Table

Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register <i>A</i> :	$A \leftarrow 0$ $A \leftarrow A + B$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Initialize Load Shift_dec	IDLE · <i>G</i> MUL0 · Q_0 MUL1
Register <i>B</i> :	$B \leftarrow IN$	<i>Load_B</i>	LOADB
Flip-Flop <i>C</i> :	$C \leftarrow 0$ $C \leftarrow C_{out}$	Clear_C Load	IDLE · <i>G</i> + MUL1 —
Register <i>Q</i> :	$Q \leftarrow IN$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	<i>Load_Q</i> Shift_dec	LOADQ —
Counter <i>P</i> :	$P \leftarrow n - 1$ $P \leftarrow P - 1$	Initialize Shift_dec	— —


Multiplier Example: Control Signal Table (Contd.)

- Signals are defined on a register basis
- LOADQ and LOADB: external signals controlled from the system using the multiplier and will not be considered a part of this design
- Many control signals are “reused” for different registers.
 - These 4 control signals are the “outputs” of the control unit: initialize, load, shift_dec, clear_c

Multiplier Example - Sequencing Part of ASM

- With the outputs represented by the table, they can be removed from the ASM making the ASM to represent only the sequencing (next state) behavior

Similar to FSM 

 

Hardwired Control

- Control Design Methods
 - Procedure specializations that use a single signal to represent each state
 - Sequence Register and Decoder
 - Sequence register with encoded states, e.g., 00, 01, 10, 11.
 - Decoder outputs produce “state” signals, e.g., 0001, 0010, 0100, 1000.
 - One Flip-flop per State
 - Flip-flop outputs as “state” signals, e. g., 0001, 0010, 0100, 1000.

Multiplier Example: Sequencer and Decoder Design - Specification

- Initially, use sequential circuit design techniques
- First, define:
 - States: IDLE, MUL0, MUL1
 - Input Signals: G, Z, Q_0 (Q_0 affects outputs, not next state)
 - Output Signals: Initialize, LOAD, Shift_Dec, Clear_C
 - State Transition Diagram (Use Sequencing ASM)
 - Output Function: Use Control Signal Table
- Second, find
 - State Assignments
 - Use two state bits to encode the three states IDLE, MUL0, and MUL1.



State	M1	M0
IDLE	0	0
MUL0	0	1
MUL1	1	0
Unused	1	1

Multiplier Example: Sequencer and Decoder Design - Formulation

- Assuming that state variables M1 and M0 are decoded into states, the next state part of the state table is:


Current State	Input G Z	Next State M1 M0
IDLE	0 0	0 0
IDLE	0 1	0 0
IDLE	1 0	0 1
IDLE	1 1	0 1
MUL0	0 0	1 0
MUL0	0 1	1 0
MUL0	1 0	1 0
MUL0	1 1	1 0

Current State M1 M0	Input G Z	Next State M1 M0
MUL1	0 0	0 1
MUL1	0 1	0 0
MUL1	1 0	0 1
MUL1	1 1	0 0
Unused	0 0	d d
Unused	0 1	d d
Unused	1 0	d d
Unused	1 1	d d

Multiplier Example: Sequencer and Decoder Design –Equations Derivation/Optimization

- Finding the equations for M1 and M0 using decoded states:
M1 = MUL0
M0 = IDLE · G + MUL1 · \bar{Z}
- The output equations using the decoded states:
Initialize = IDLE · G
Load = MUL0 · Q₀
Clear_C = IDLE · G + MUL1
Shift_dec = MUL1
- Doing multiple level optimization, extract IDLE · G:
START = IDLE · G
M1 = MUL0
M0 = START + MUL1 · \bar{Z}
Initialize = START
Load = MUL0 · Q₀
Clear_C = START + MUL1
Shift_dec = MUL1
- The resulting circuit using flip-flops, a decoder, and the above equations is given on the next slide.

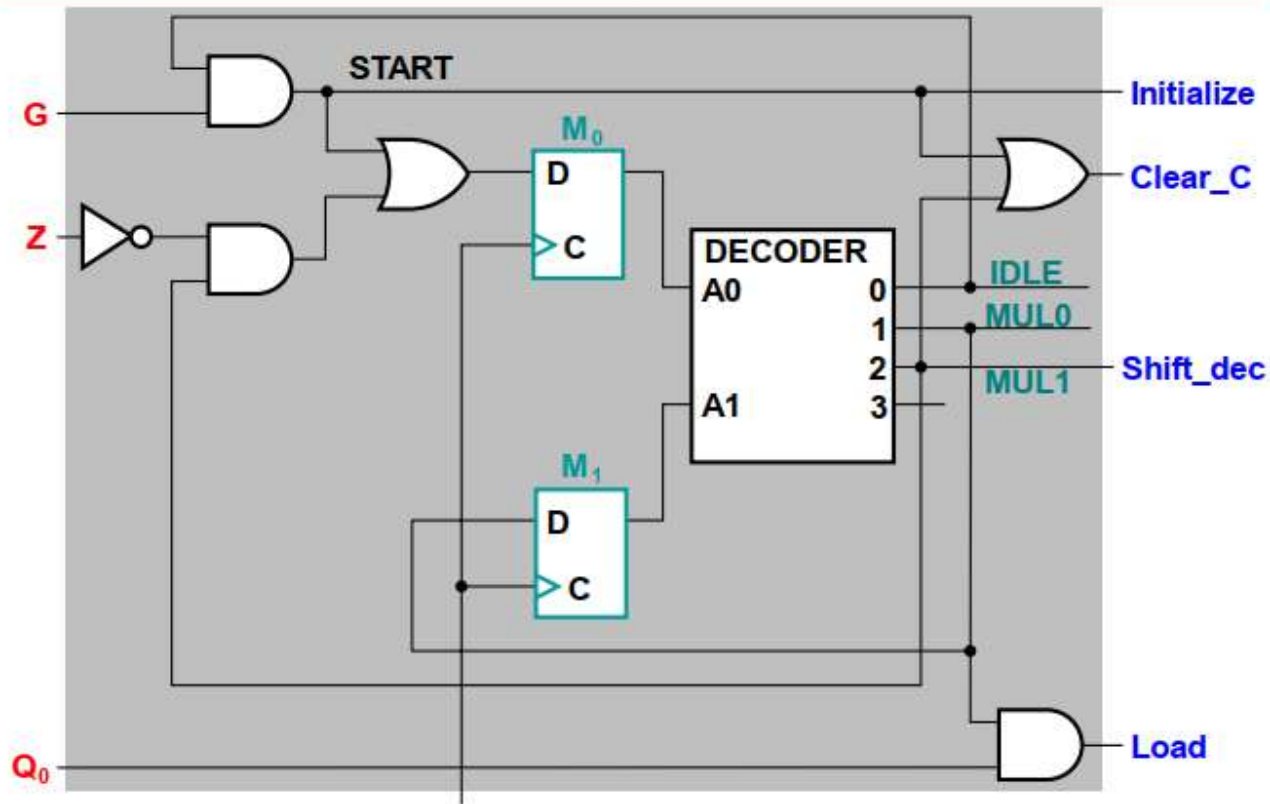Multiplier Example: Sequencer and Decoder Design - Implementation



```

--Binary multiplier with n=4
library ieee;
use ieee.std_logic_unsigned.all;
entity binary_multiplier is
    port(CLK, RESET, G, LOADB, LOADQ: in std_logic;
         MULT_IN : in std_logic_vector (3 downto 0);
         MULT_OUT : out std_logic_vector (7 downto 0));
end binary_multiplier;

```

```

architecture behavior_4 of binary_multiplier is
    type state_type is (IDLE, MUL0, MUL1);
    variable P:=3;
    signal state, next_state : state_type;
    signal A, B, Q:std_logic_vector(3 downto 0);
    signal C, Z:std_logic;

```

```

begin
    Z<= P(1) NOR P(0);
    MULT_OUT <= A & Q;

    state_register : process (CLK, RESET)
    begin
        if (RESET = '1') then
            state <= IDLE;
        elsif (CLK'event and CLK='1') then
            state <= next_state;
        endif;
    end process;

    next_state_func : process (G, Z, state)
    begin
        case state is
            when IDLE =>
                if G='1' then next_state <= MUL0;
                else next_state <= IDLE;
                end if;
            when MUL0 =>
                next_state <= MUL1;
            when MUL1 =>
                if Z='1' then next_state <= IDLE;
                else next_state <= MUL0;
                end if;
        end case;
    end process;

```

```

datapath_func : process (CLK)
variable CA: std_logic_vector (4 downto 0);
begin
    if (CLK'event and CLK='1') then
        if LOADB='1' then
            B <= MULT_IN;
        end if;
        if LOADQ = '1' then
            Q <= MULT_IN;
        end if;
        case state is
            when IDLE =>
                if G = '1' then
                    C <= '0';
                    A <= "0000";
                    P <= "11";
                end if;
            when MUL0 =>
                if Q(0)='1' then
                    CA := ('0' & A) + ('0' & B);
                else
                    CA := C & A;
                end if;
                C <= CA(4);
                A <= CA(3 downto 0);
            when MUL1 =>
                C <= '0';
                A <= C & A(3 downto 1);
                Q <= A(0) & Q(3 downto 1);
                P <= P - "01";
            end case;
        end if;
    end process;

end behavior_4;

```

Speeding Up the Multiplier

- In processing each bit of the multiplier, the circuit visits states MUL0 and MUL1 in sequence.
- By redesigning the multiplier, is it possible to visit only a single state per bit processed?

Speeding Up Multiply (Contd.)


- The operations in MUL0 and MUL1:
 - In MUL0, a conditional add of B
 - In MUL1, a right shift of $C \parallel A \parallel Q$ in a shift register, the decrementing of P, and a test for $P = 0$ (on the old value of P)
- Any solution that uses one state must combine all of the operations listed into one state
 - The operations involving P are already done in a single state, so not a problem.
 - The right shift, however, depends on the result of the conditional addition. So these two operations must be combined!

Speeding Up Multiply (Contd.)

- By replacing the shift register with a combinational shifter and combining the adder and shifter, the states can be merged.

- The C-bit is no longer needed.

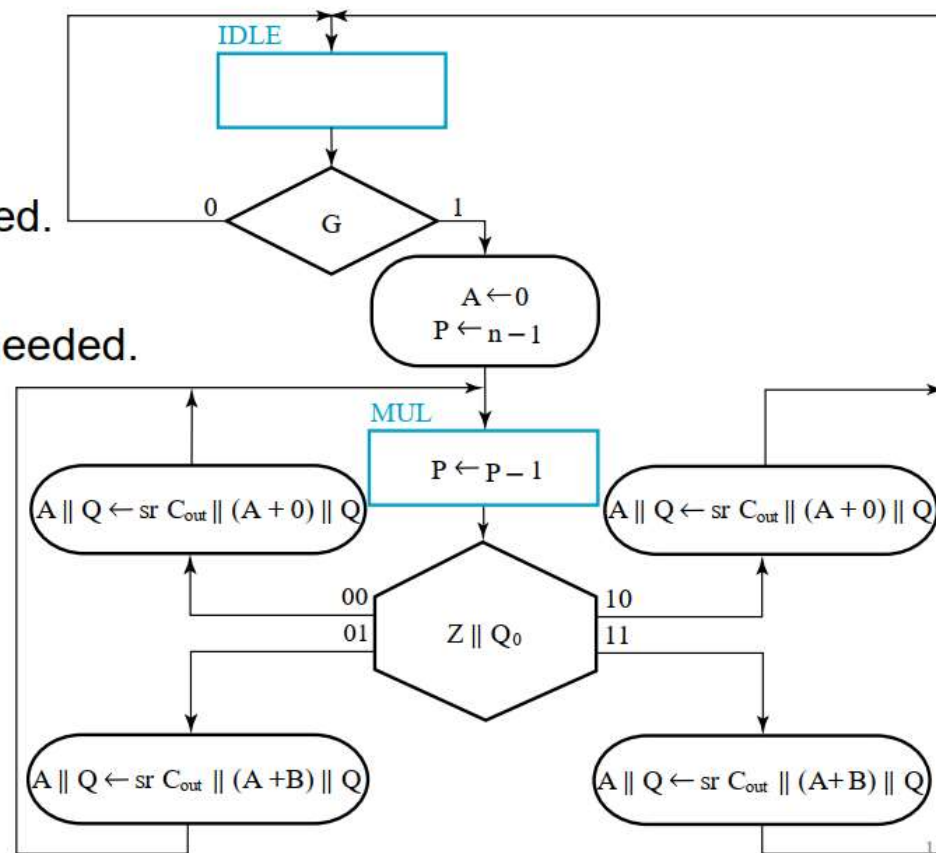- In this case, Z and Q_0 have been made into a vector.



Microprogrammed Control

- *Microprogrammed Control* — a control unit with binary control values stored as words in memory.
- *Microinstructions* — words in the control memory.
- *Microprogram* — a sequence of microinstructions.
- *Control Memory* — RAM or ROM memory holding the microinstructions.
 - *Writeable Control Memory* — RAM Memory into which microinstructions may be written

