

University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

Memories Overview

Dr. Yasir Al-Zubaidi

Third stage

2021

Memories


Read-Write Memory		Read-Only Memory	
Volatile Memory		Non-volatile Memory	Mask-Programmed ROM (PROM) (nonvolatile)
Random Access	Sequential Access	EPROM	
DRAM SRAM	FIFO LIFO Shift Register CAM	EEPROM FLASH	

- **Volatile:** need electrical power
- **Nonvolatile:** magnetic disk, retains its stored information after the removal of power
- **Random access:** memory locations can be read or written in a random order
- **EPROM:** erasable programmable read-only memory
- **EEPROM:** electrically erasable programmable read-only memory
- **FLASH:** memory stick, USB disk
- **Access pattern:** sequential access: (video memory streaming) first-in-first-out (buffer), last-in-first-out (stack), shift register, content-addressable memory

Memories


- k address lines are decoded to address 2^k words of memory.
- Each word is n bits.
- Read and Write are single control lines defining the simplest memory operations.

A basic memory system:

 


Memory Operation Timing - Reading

 - Most basic memories are asynchronous
 - Storage in latches or storage of electrical charge
 - **No clock**
 - Controlled by control inputs and address, which are controlled by CPU and **synchronized** by its own clock
- Timing of signal changes/data observation is critical to the operation



- Read cycle: the access time, the maximum time from the application of the address to the appearance of the data at the Data output.

Memory Operation Timing - Writing

 

- Write cycle: the maximum time from the application of the address to the completion of all internal operations required to store a word
- Critical times measured with respect to edges of write pulse (1-0-1):
 - Address must be established at least a specified time before 1-0 and held for at least a specified time after 0-1 to avoid disturbing stored contents of other addresses
 - Data must be established at least a specified time before 0-1 and held for at least a specified time after 0-1 to write correctly

VHDL code for ROM

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
ENTITY rom8x4 IS  
PORT (  
  addr: in std_logic_vector(2 downto 0);  
  q: out std_logic_vector(3 downto 0));  
END rom8x4;
```

```
ARCHITECTURE behav OF rom8x4 IS  
BEGIN
```


```
PROCESS(addr)  
BEGIN  
  CASE addr IS  
    when "000" => q <= "0001";  
    when "001" => q <= "0000";  
    when "010" => q <= "0111";  
    when "011" => q <= "1101";  
    when "100" => q <= "1000";  
    when "101" => q <= "1100";  
    when "110" => q <= "0110";  
    when "111" => q <= "1011";  
    when others => NULL;  
  END case;  
END process;  
END behav;
```

Random Access Memories (RAMs)


- Read/Write memory
- Types:
 - Static RAM (SRAM):
 - Once a word is written at a location, it remains stored as long as power is applied to the chip, unless the same location is written again.
 - **Fast speed**, but **their cost per bit higher**.
 - Application: Caches memories in Microprocessor
 - Dynamic RAM (DRAM):
 - The data stored at each location must be periodically refreshed by reading it and then writing it back again, otherwise it disappears.
 - **Their density is greater and their cost per bit lower**, but the **speed is slower**.

SRAM Cell

 - Array of storage cells used to implement static RAM




 - Storage Cell
 - SR Latch
 - Input "Select" for control
 - Dual Rail Data
 - Inputs B and \bar{B}
 - Outputs C and \bar{C}




SRAM Bit Slice

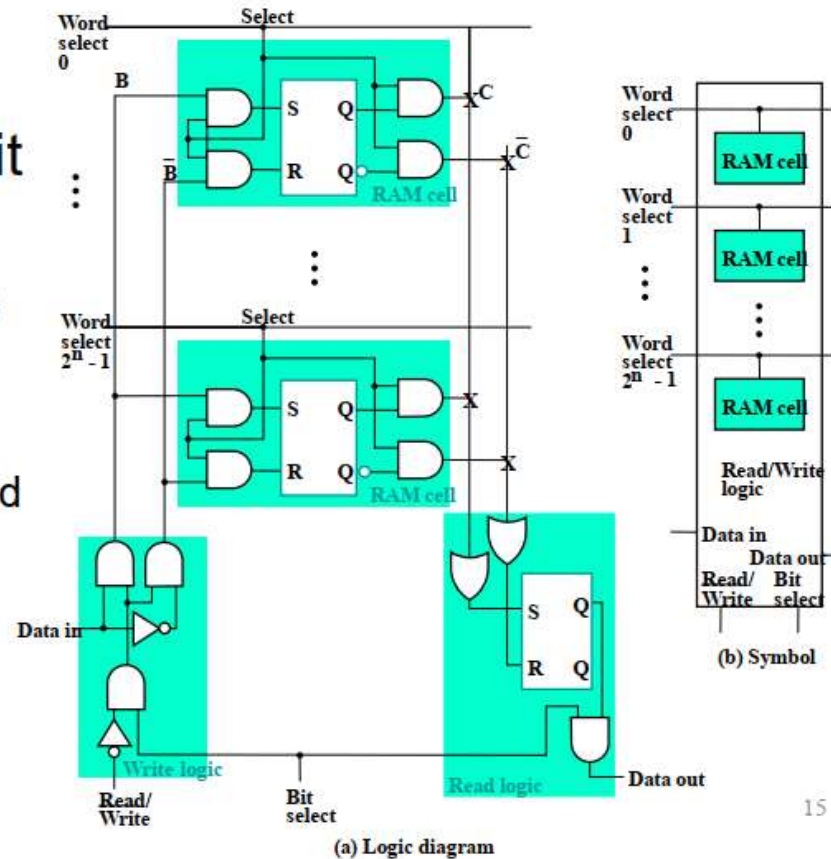- Represents all circuitry that is required for 2^n 1-bit words
 - Multiple RAM cells
 - Control Lines:
 - Word select i
– one for each word
 - $\text{Read}/\overline{\text{Write}}$
 - Bit Select
 - Data Lines:
 - Data in
 - Data out



2ⁿ-Word by 1-Bit RAM IC

 - To build a RAM IC from a RAM slice:
 - Decoder decodes the n address lines to 2^n word select lines
 - A 3-state buffer on the data output permits RAM ICs to be combined into a RAM with $c \times 2^n$ words




Cell Arrays and Coincident Selection

- Memory arrays can be very large =>
 - Large decoders
 - Large fanouts for the input bit lines
 - The decoder size and fanouts can be reduced by approximately \sqrt{n} using a coincident selection in a 2-D array: uses two decoders, one for words and one for bits:
 - Word select becomes Row select
 - Bit select becomes Column select


- See next slide for example

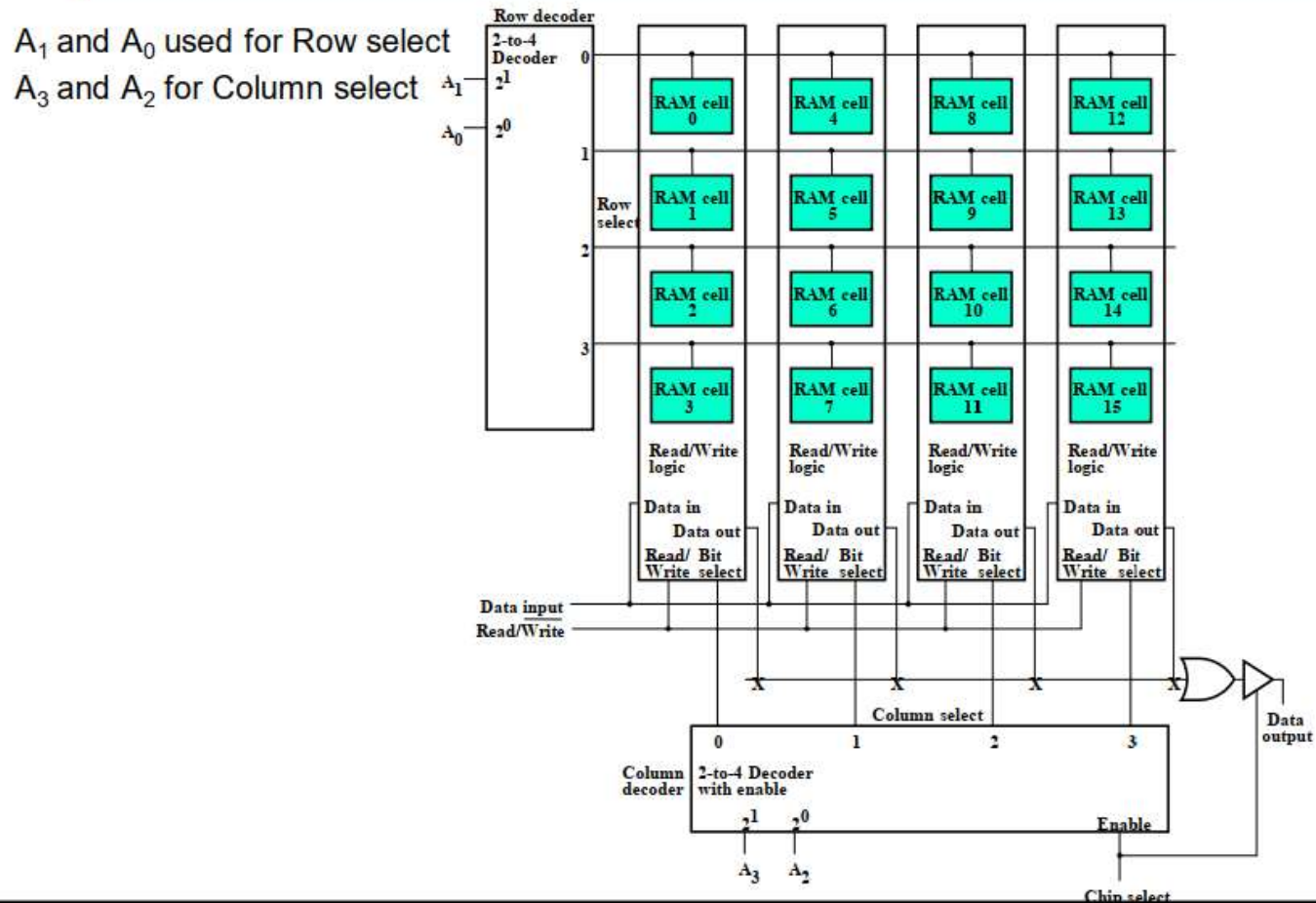Cell Arrays and Coincident Selection (Contd.)




Making Larger Memories

 - We can make larger memories from smaller ones by using the decoded higher order address bits to control CS (chip select) lines, tying all address, data, and R/W lines in parallel.
- A 16-Word by 1-Bit memory constructed using 4-Word by 1-Bit memory.



Making Wider Memories

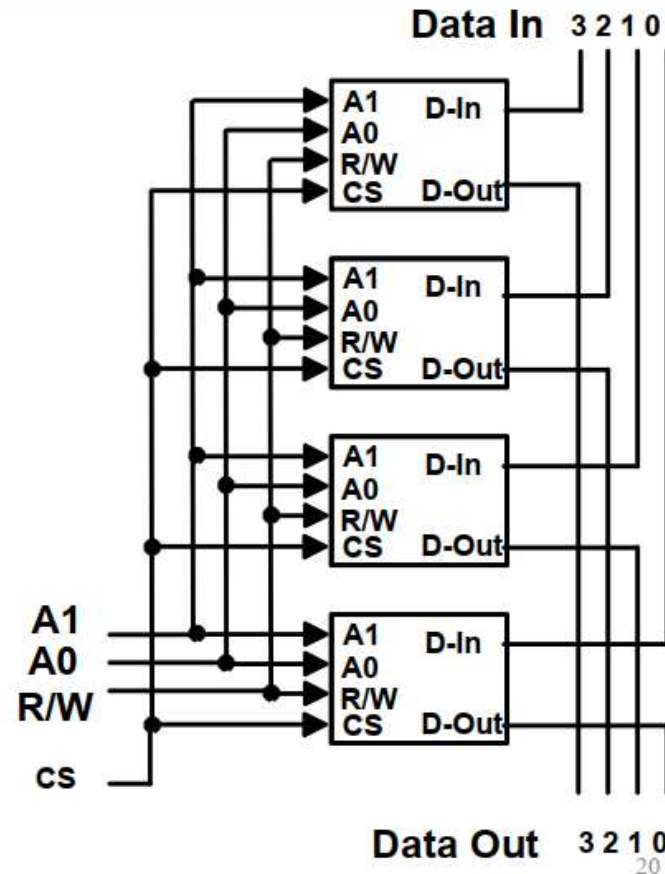- Tie the address and control lines in parallel and keep the data lines separate.
- Example: make a 4-word by 4-bit memory from 4, 4-word by 1-bit memories
- Note: Both 16x1 and 4x4 memories take 4-chips and hold 16 bits of data.



DRAM

- Basic Principle: Storage of information on capacitors.
- Charge and discharge of capacitor to change stored value
- Use of transistor as “switch” to:
 - Store charges
 - Charge or discharge

Dynamic RAM (Contd.)

- Circuit, hydraulic analogy, and logical model.

