

University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

Microprogramming

Dr. Yasir Al-Zubaidi

Third stage

2021

Microprogramming Overview


- **Part 1 – Datapaths**
 - Introduction
 - Datapath Example
 - Arithmetic Logic Unit (ALU)
 - Shifter
 - Datapath Representation and Control Word

- **Part 2 – A Simple Computer**
 - Instruction Set Architecture (ISA)
 - Single-Cycle Hardwired Control

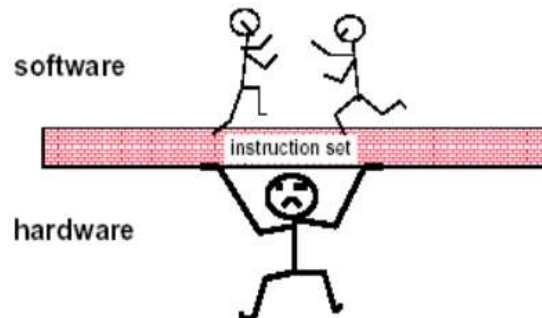- **Part 3 – Multiple Cycle Hardwired Control**
 - Single Cycle Computer Issues
 - Sequential Control Design


Introduction

- Computer Specification
 - *Instruction Set Architecture (ISA)* - the specification of a computer's appearance to a programmer at its lowest level
 - *Computer Architecture* - a high-level description of the hardware implementing the computer derived from the ISA
 - The architecture usually includes additional specifications such as speed, cost, and reliability.




Introduction (Contd.)

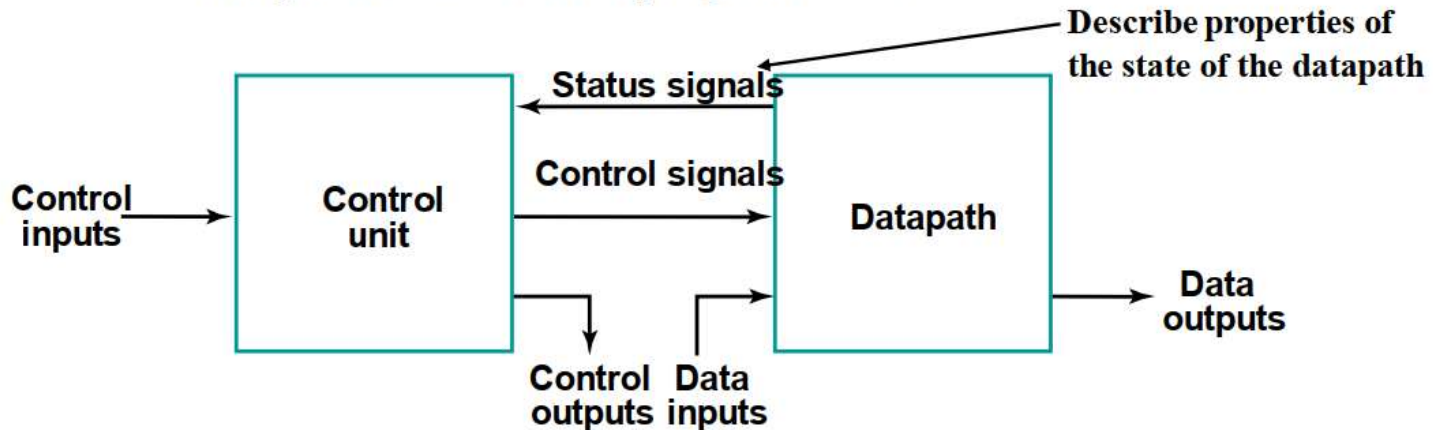- Simple computer architecture decomposed into:
 - Datapath: performing operations
 - A set of registers
 - Microoperations performed on the data stored in the registers
 - A control interface
 - Control unit: controlling datapath operations
 - Programmable & Non-programmable



Datapath Example

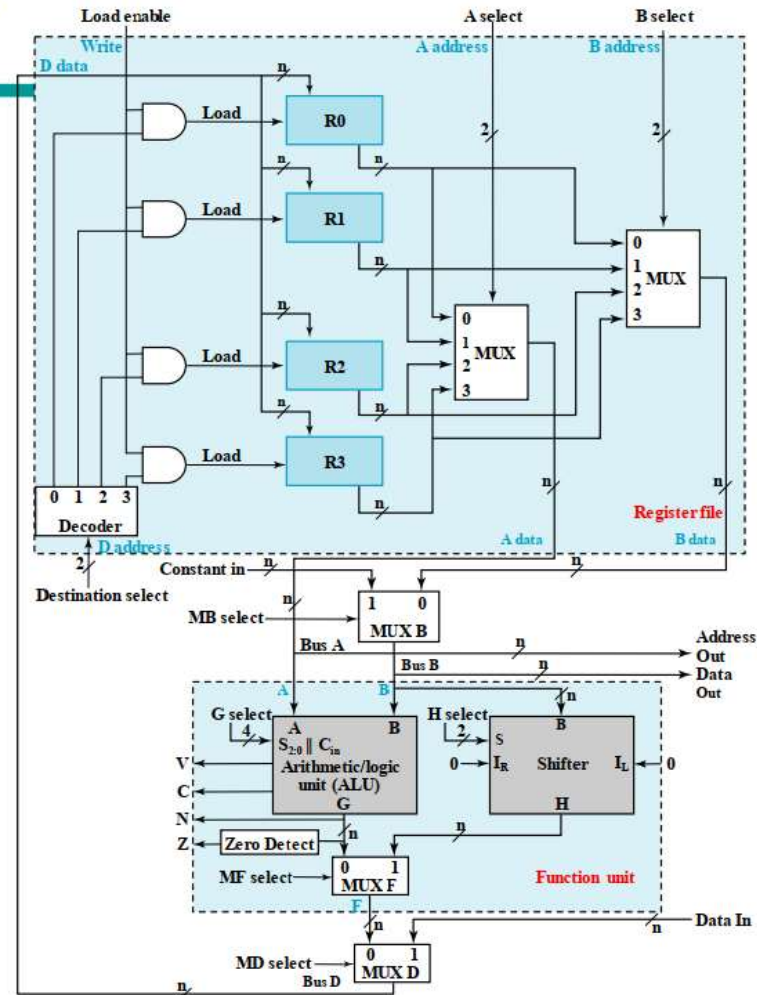
- Register file:
 - Four parallel-load regs
 - Two mux-based register selectors
 - Register destination decoder
- Microoperation Implementation
 - Mux B for external constant input
 - Buses A and B with external address and data outputs
 - Function Unit:
 - ALU and Shifter with Mux F for output select
 - Mux D for external data input
 - Logic for generating status bits V, C, N, Z



Datapath Example: Performing a Microoperation

Microoperation: $R0 \leftarrow R1 + R2$


- Apply 01 to A select to place contents of R1 onto Bus A
- Apply 10 to B select to place contents of R2 onto B data and apply 0 to MB select to place B data on Bus B
- Apply 0010 to G select to perform addition $G = \text{Bus A} + \text{Bus B}$
- Apply 0 to MF select and 0 to MD select to place the value of G onto BUS D
- Apply 00 to Destination select to enable the Load input to R0
- Apply 1 to Load Enable to force the Load input to R0 to 1 so that R0 is loaded on the clock pulse (not shown)
- The overall microoperation requires 1 clock cycle

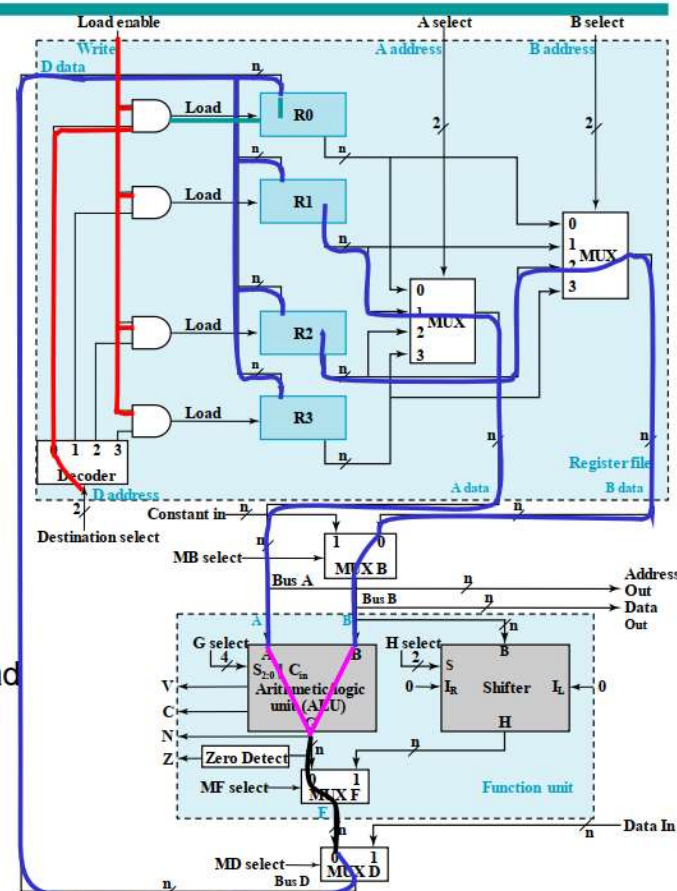

Datapath Example: Key Control Actions for Microoperation Alternatives


Various microoperations:

- Perform a shift microoperation: **apply 1 to MF select**
- Use a constant in a micro-operation using Bus B: apply 1 to MB select
- Provide an address and data for a memory or output write microoperation – apply 0 to Load enable to prevent register loading
- Provide an address and obtain data for a memory or output read microoperation – apply 1 to MD select
- For some of the above, other control signals become don't cares

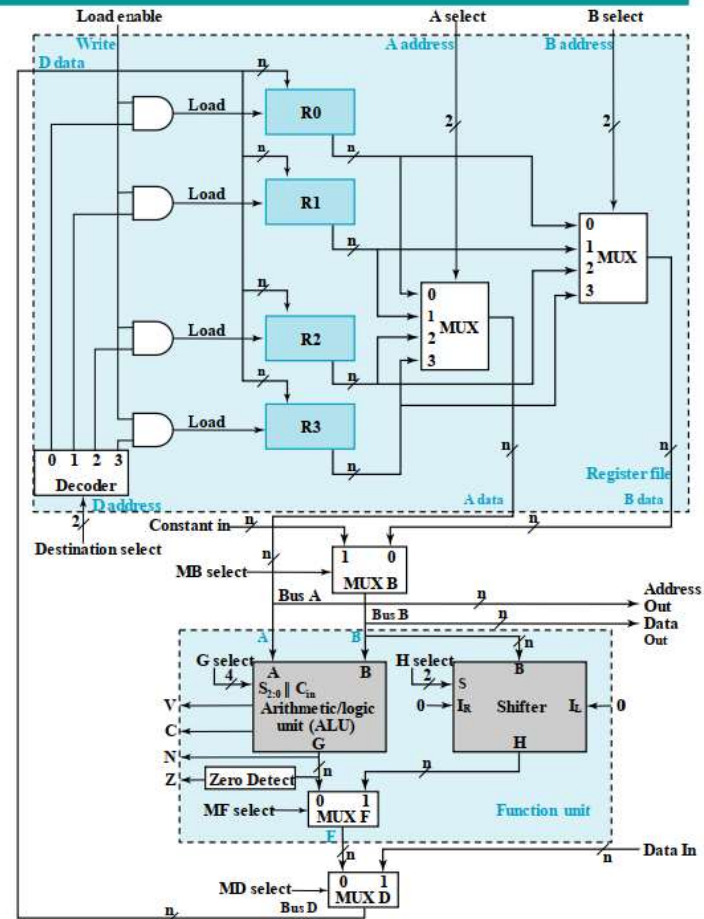

Arithmetic Logic Unit (ALU)

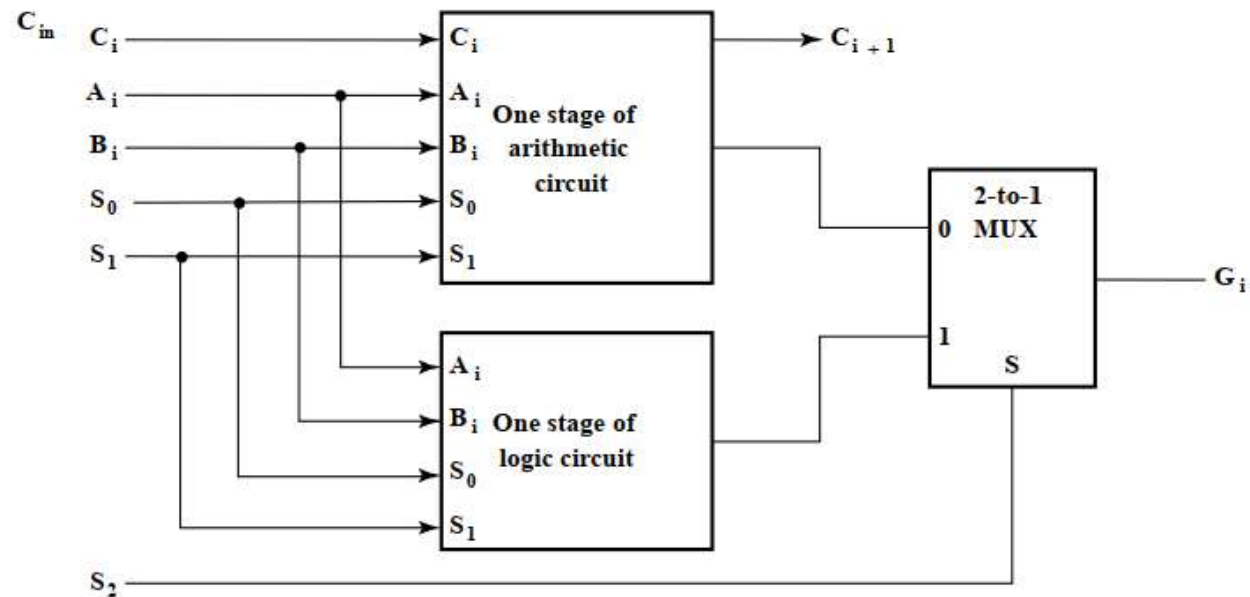- Decompose the ALU into:
 - An arithmetic circuit & A logic circuit
 - A selector to pick between the two circuits




Arithmetic Circuit Design

- Arithmetic circuit design


- Decompose the arithmetic circuit into:
 - An n-bit parallel adder
 - A block of logic that selects four choices for the B input to the adder

- There are only four functions of B to select as Y in $G = A + Y + C_{in}$:

	$C_{in} = 0$	$C_{in} = 1$
• 0	$G = A$	$G = A + 1$
• B	$G = A + B$	$G = A + B + 1$
• \overline{B}	$G = A + \overline{B}$	$G = A + \overline{B} + 1$
• 1	$G = A - 1$	$G = A$

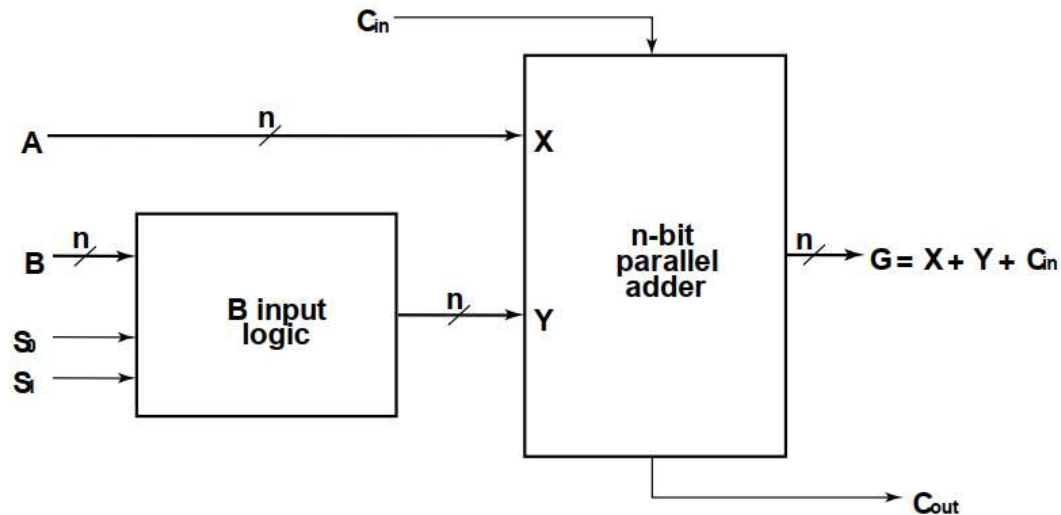


4-Bit Basic Left/Right Shifter

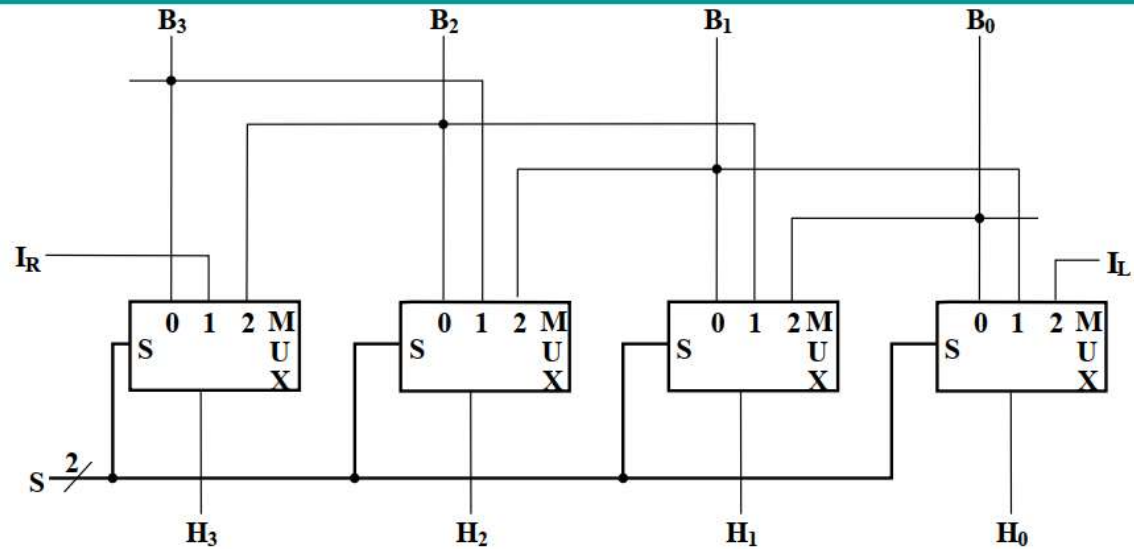

- Serial Inputs:
 - I_R for right shift
 - I_L for left shift
- Shift Functions:
 - $(S_1, S_0) = 00$ Pass B unchanged
 - 01 Right shift
 - 10 Left shift
 - 11 Unused

Barrel Shifter

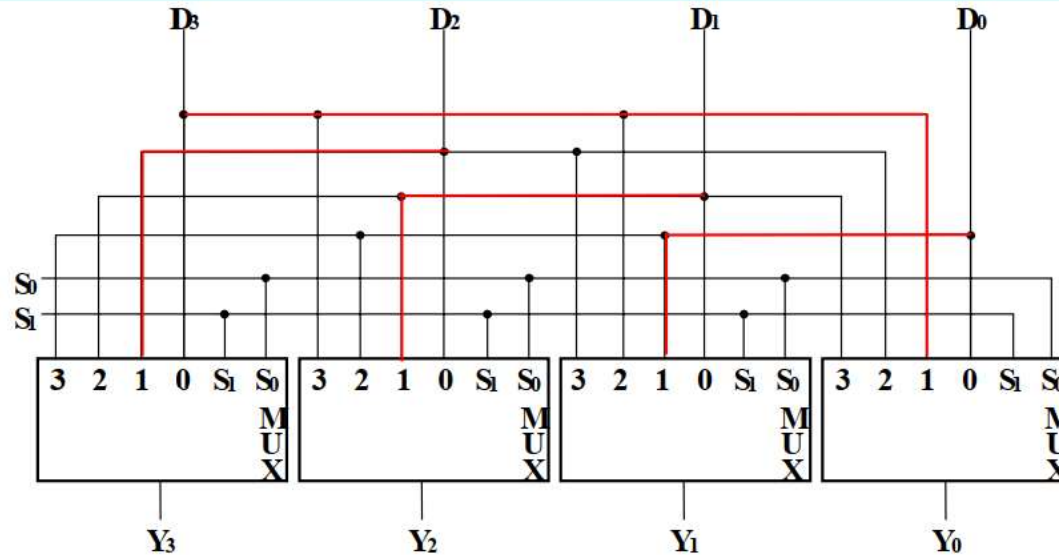


- A rotate is a shift in which the bits shifted out are inserted into the positions vacated
- The circuit rotates its contents left from 0 to 3 positions depending on S :


$S = 00$ position unchanged	$S = 10$ rotate left by 2 positions
$S = 01$ rotate left by 1 positions	$S = 11$ rotate left by 3 positions

Combinational Shifter from MUXes

Basic Building Block

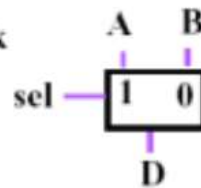

8-bit right shifter

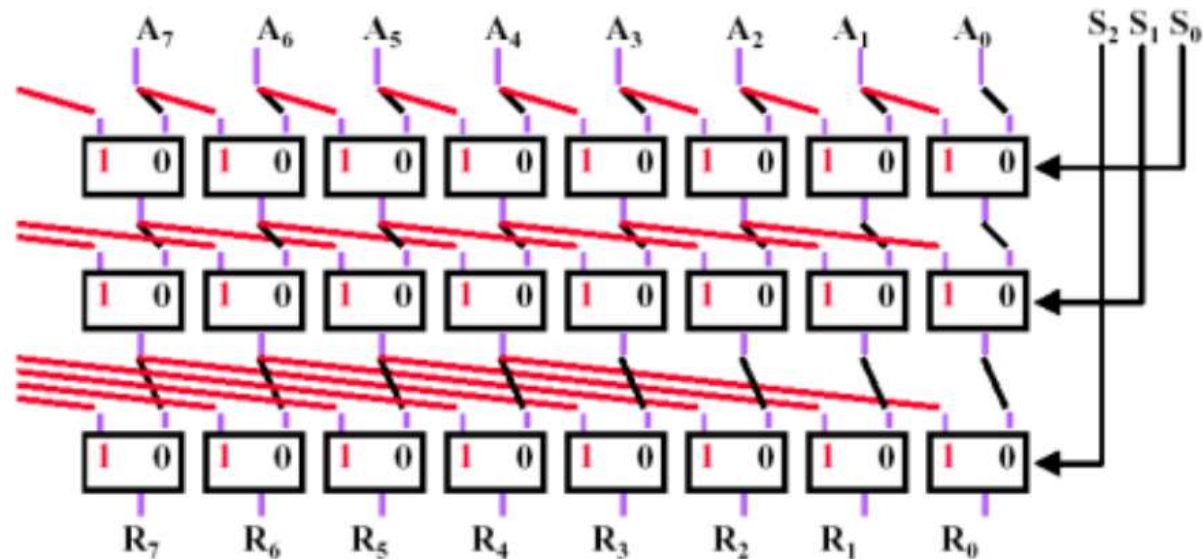

• - Example 8-bit:

- Layer 1 shifts by 0, 4
- Layer 2 shifts by 0, 2
- Layer 3 shifts by 0, 1

▪ Large barrel shifters can be constructed using:

- Layers of multiplexers
- 2 - dimensional array circuits designed at the electronic level