

**University Of Diyala**  
**College Of Engineering**  
**Department of Computer Engineering**



# **Digital System Design II**


## **Microprogramming II-Part2**

**Dr. Yasir Al-Zubaidi**

**Third stage**

**2021**

# Datapath

 

## Instruction Set Architecture (ISA) for Simple Computer (SC)

---

- **Instructions** are stored in RAM or ROM as a *program*, the addresses for instructions are provided by a *program counter (PC)*
  - Count up or load a new address
  - The PC and associated control logic are part of the Control Unit
- A typical instruction specifies:
  - Operands to use
  - Operation to be performed
  - Where to place the result, or which instruction to execute next
- Executing an instruction
  - Activate the necessary sequence of operations specified by the instruction
  - Be controlled by the control unit and performed in:
    - datapath
    - control unit
    - external hardware such as memory or input/output

## Example ISAs


---

- RISC (Reduced Instruction Set Computer)
  - Digital Alpha
  - Sun Sparc
  - MIPS RX000
  - IBM PowerPC
  - HP PA/RISC
- CISC (Complex Instruction Set Computer)
  - Intel x86
  - Motorola 68000
  - DEC VAX
- VLIW (Very Large Instruction Word)
  - Intel Itanium
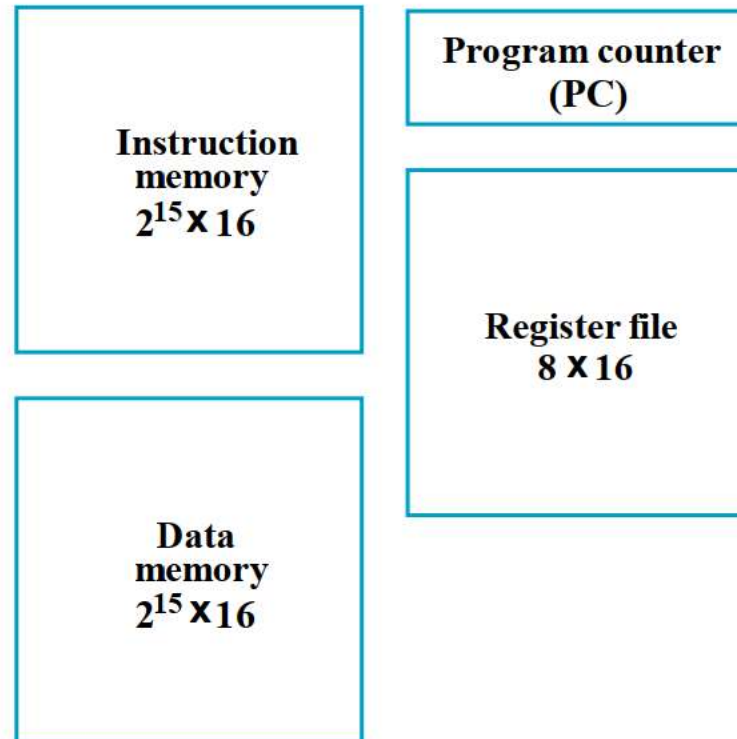
## ISA: Storage Resources

---

- "Harvard architecture":  
Separate instruction and data memories
- Permit use of single clock cycle per instruction implementation
- Due to use of "cache" in modern computer architectures, it is a fairly realistic model



# ISA: Instruction Format


- The three formats are: Register, Immediate, and Jump/Branch



(a) Register



(b) Immediate

 

(c) Jump and Branch

- All formats contain an Opcode field in bits 9 through 15.
  - The Opcode specifies the operation to be performed

# ISA: Instruction Format - Register



(a) Register

- This format supports:
  - $R1 \leftarrow R2 + R3$
  - $R1 \leftarrow sl\ R2$
- Three 3-bit register fields:
  - DR - destination register (R1 in the examples)
  - SA - the A source register (R2 in the first example)
  - SB - the B source register (R3 in the first example and R2 in the second example)
- Why is R2 in the second example SB instead of SA?

## ISA: Instruction Format - Immediate




(b) Immediate

- This format supports:
  - $R1 \leftarrow R2 + 3$
- The B Source Register field is replaced by an Operand field OP specifying a constant. (3-bit constant, values from 0 to 7)
- The constant:
  - Zero-fill (on the left of) the operand to form 16-bit constant
  - 16-bit representation for values 0 through 7


 
## ISA: Instruction Format – Jump & Branch



(c) Jump and Branch

- This instruction supports changes in the sequence of instruction execution by adding an extended, 6-bit, signed 2's-complement *address offset* to the PC value
- The SA field: permits jumps and branches on N or Z based on the contents of *Source register A*
- The Address (AD) field (6-bit) replaces the DR and SB fields
  - Example: Suppose that a jump for the Opcode and the PC contains 45 (0...0101101) and AD contains – 12 (110100). Then the new PC value will be:  
 $0...0101101 + (1...110100) = 0...0100001$  (i.e.,  $45 + (-12) = 33$ )

## ISA: Instruction Specifications


Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move A	0000000	MOVA	RD,RA	$R[DR] \leftarrow R[SA]$	N, Z
Increment	0000001	INC	RD,RA	$R[DR] \leftarrow R[SA] + 1$	N, Z
Add	0000010	ADD	RD,RA,RB	$R[DR] \leftarrow R[SA] + R[SB]$	N, Z
Subtract	0000101	SUB	RD,RA,RB	$R[DR] \leftarrow R[SA] - R[SB]$	N, Z
Decrement	0000110	DEC	RD,RA	$R[DR] \leftarrow R[SA] - 1$	N, Z
AND	0001000	AND	RD,RA,RB	$R[DR] \leftarrow R[SA] \wedge R[SB]$	N, Z
OR	0001001	OR	RD,RA,RB	$R[DR] \leftarrow R[SA] \vee R[SB]$	N, Z
Exclusive OR	0001010	XOR	RD,RA,RB	$R[DR] \leftarrow R[SA] \oplus R[SB]$	N, Z
NOT	0001011	NOT	RD,RA	$R[DR] \leftarrow \overline{R[SA]}$	N, Z
Move B	0001100	MOVB	RD,RB	$R[DR] \leftarrow R[SB]$	
Shift Right	0001101	SHR	RD,RB	$R[DR] \leftarrow sr R[SB]$	
Shift Left	0001110	SHL	RD,RB	$R[DR] \leftarrow sl R[SB]$	
Load Immediate	1001100	LDI	RD, OP	$R[DR] \leftarrow zf OP$	
Add Immediate	1000010	ADI	RD,RA,OP	$R[DR] \leftarrow R[SA] + zf OP$	
Load	0010000	LD	RD,RA	$R[DR] \leftarrow M[R[SA]]$	
Store	0100000	ST	RA,RB	$M[R[SA]] \leftarrow R[SB]$	
Branch on Zero	1100000	BRZ	RA,AD	if ( $R[SA] = 0$ ) $PC \leftarrow PC + se AD$	
Branch on Negative	1100001	BRN	RA,AD	if ( $R[SA] < 0$ ) $PC \leftarrow PC + se AD$	
Jump	1110000	JMP	RA	$PC \leftarrow R[SA]$	

# ISA: Example Instructions and Data in Memory

## Memory Representation of Instruction and Data

Decimal Address	Memory Contents	Decimal Opcode	Other Field	Operation
25	0000101 001 010 011	5 (Subtract)	DR:1, SA:2, SB:3	$R1 \leftarrow R2 - R3$
35	0100000 000 100 101	32 (Store )	SA:4, SB:5	$M[R4] \leftarrow R5$
45	1000010 010 111 011	66 (Add Immediate)	DR: 2, SA :7, OP :3	$R2 \leftarrow R7 + 3$
55	1100000 101 110 100	96 (Branch on Zero)	AD: 44, SA:6	If $R6 = 0$ , $PC \leftarrow PC - 20$
70	0000000 00110 0 000	Data = 192. After execution of instruction in 35, Data = 80.		

# Single-Cycle Hardwired Control:

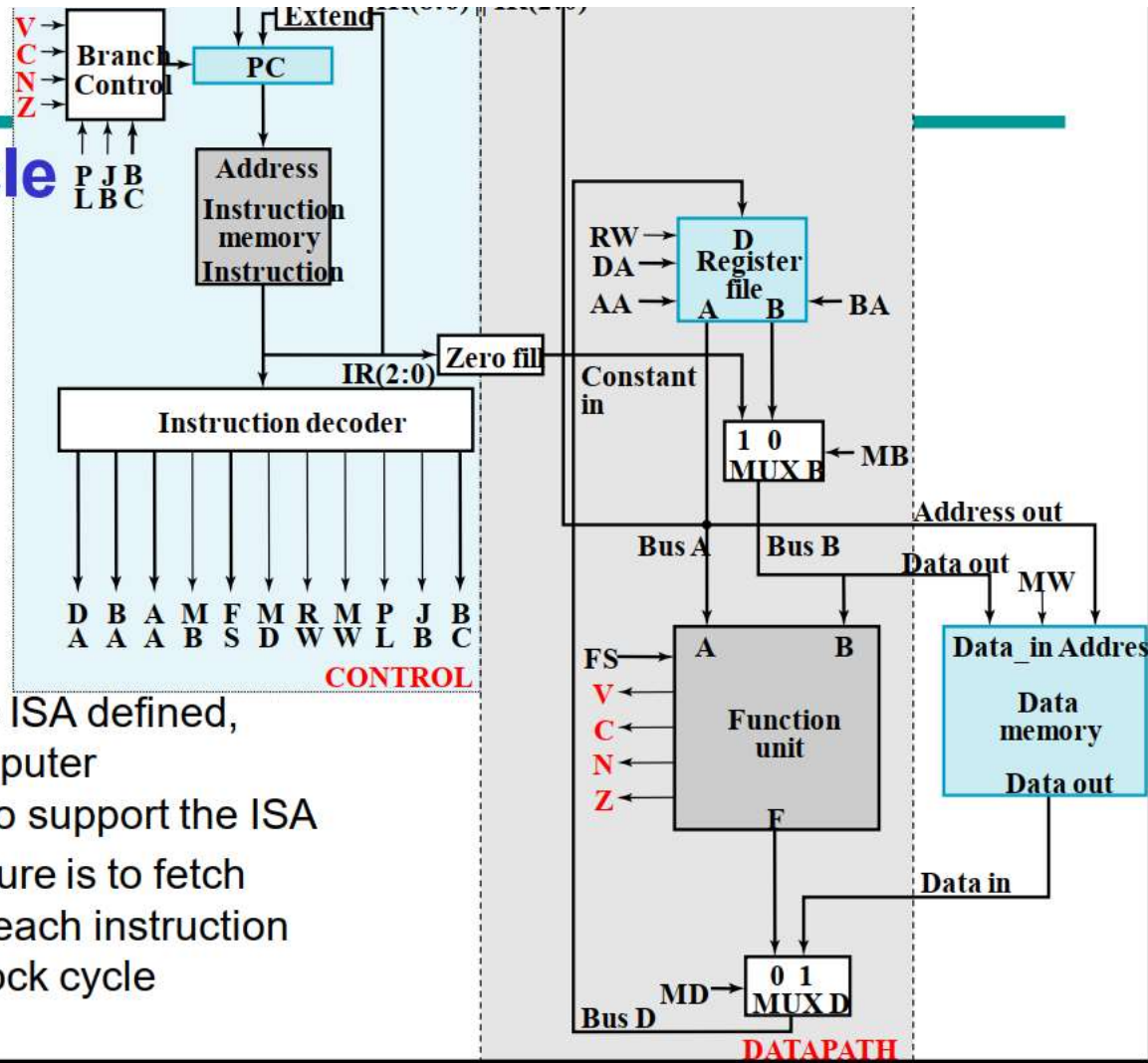

- Based on the ISA defined, design a computer architecture to support the ISA
- The architecture is to fetch and execute each instruction in a single clock cycle

# The Control Unit

---

- Datapath: the Data Memory has been attached to the *Address Out*, *Data Out*, and *Data In* lines of the Datapath.
- Control Unit:
  - The *MW* input to the Data Memory is the Memory Write signal from the Control Unit.
  - The Instruction Memory *address* input is provided by the PC and its *instruction output* feeds the Instruction Decoder.
  - Zero-filled IR(2:0) becomes *Constant In*
  - Extended IR(8:6) || IR(2:0) and Bus A are address inputs to the PC.
  - The PC is controlled by Branch Control logic

# Program Counter (PC) Function

---

- PC function is based on instruction specifications involving jumps and branches:

<b>Branch on Zero</b>	<b>BRZ</b>	<b>if (R[SA] = 0) PC ← PC + seAD</b>
<b>Branch on Negative</b>	<b>BRN</b>	<b>if (R[SA] &lt; 0) PC ← PC + seAD</b>
<b>Jump</b>	<b>JMP</b>	<b>PC ← R[SA]</b>

- The first two transfers require addition to the PC of:
    - Address Offset = Extended IR(8:6) || IR(2:0)
  - The third transfer requires that the PC be loaded with:
    - Jump Address = Bus A = R[SA]
- In addition to the above register transfers, the PC must implement the counting function:
    - PC ← PC + 1

## PC Function (Contd.)

---

- Branch Control determines the PC transfers based on five inputs:
  - N,Z – negative and zero status bits
  - PL – load enable for the PC
  - JB – Jump/Branch select: If JB = 1, Jump, else Branch
  - BC – Branch Condition select: If BC = 1, branch for N = 1, else branch for Z = 1.

PL	JB	BC	PC Operation
0	X	X	Count Up
1	1	X	Jump
1	0	1	Branch on Negative (else Count Up)
1	0	0	Branch on Zero (else Count Up)

# Instruction Decoder

---

- Converts the instruction into the signals necessary to control the computer during the single cycle execution, combinational
  - Inputs: the 16-bit Instruction
  - Outputs: control signals
    - **DA, AA, and BA**: Register file addresses (IR (8:0))
      - simply pass-through signals: DA = DR, AA = SA, and BA = SB
    - **FS**: Function Unit Select
    - **MB** and **MD**: Multiplexer Select Controls
    - **RW** and **MW**: Register file and Data Memory Write Controls
    - **PL, JB, and BC**: PC Controls
- Observe that for other than branches and jumps, FS = IR(12:9)
  - The other control signals should depend as much as possible on IR(15:13)



# Instruction Decoder (Contd.)

Truth Table for Instruction Decoder Logic

Instruction Function Type	Instruction Bits				Control Word Bits						
	15	14	13	9	MB	MD	RW	MW	PL	JB	BC
1. Function unit operations using registers	0	0	0	X	0	0	1	0	0	X	X
2. Memory read	0	0	1	X	0	1	1	0	0	X	X
3. Memory write	0	1	0	X	0	X	0	1	0	X	X
4. Function unit operations using register and constant	1	0	0	X	1	0	1	0	0	X	X
5. Conditional branch on zero (Z)	1	1	0	0	X	X	0	0	1	0	0
6. Conditional branch on negative (N)	1	1	0	1	X	X	0	0	1	0	1
7. Unconditional Jump	1	1	1	X	X	X	0	0	1	1	X


## Instruction Decoder (Contd.)

---

- Instruction types are based on the control blocks and the seven control signals to be generated (MB, MD, RW, MW, PL, JB, BC):
  - Datapath and Memory Control (types 1-4)
    - Mux B
    - Memory and Mux D
  - PC Control (types 5-7)
    - Bit 15 = Bit 14 = 1 => PL
    - Bit 13 => JB.
    - Bit 9 was use as BC which contradicts FS = 0000 needed for branches. To force FS(0) to 0 for branches, Bit 9 into FS(0) is disabled by PL.
 
## Instruction Decoder (Contd.)

- The end result by use of the types, careful assignment of codes, and use of don't cares, yields very simple logic:
- This completes the design of most of the essential parts of the single-cycle simple computer




# Example Instruction Execution

## Six Instructions for the Single-Cycle Computer


Operation code	Symbolic name	Format	Description	Function	MB	MD	RW	MW	PL	JB	BC
1000 010	ADI	Immediate	Add immediate operand	$R[DR] \leftarrow R[SA] + \text{zf} / (2:0)$	1	0	1	0	0	0	0
0010 000	LD	Register	Load memory content in to register	$R[DR] \leftarrow M[R[SA]]$	0	1	1	0	0	1	0
0100 000	ST	Register	Store register content in memory	$M[R[SA]] \leftarrow R[SE]$	0	1	0	1	0	0	0
0001 110	SL	Register	Shift left	$R[DR] \leftarrow s!R[SE]$	0	0	1	0	0	1	0
0001 011	NOT	Register	Complement register	$R[DR] \leftarrow \overline{R[SA]}$	0	0	1	0	0	0	1
1100 000	BRZ	Jump/Branch	If $R[SA] = 0$ , branch to $PC + \text{se AD}$	If $R[SA] = 0$ , $PC \leftarrow PC + \text{se AD}$ , If $R[SA] \neq 0$ , $PC \leftarrow PC + 1$	1	0	0	0	1	0	0

- Decoding, control inputs and paths shown for **ADI**, **LD** and **BRZ** on next 6 slides


# Decoding for ADI

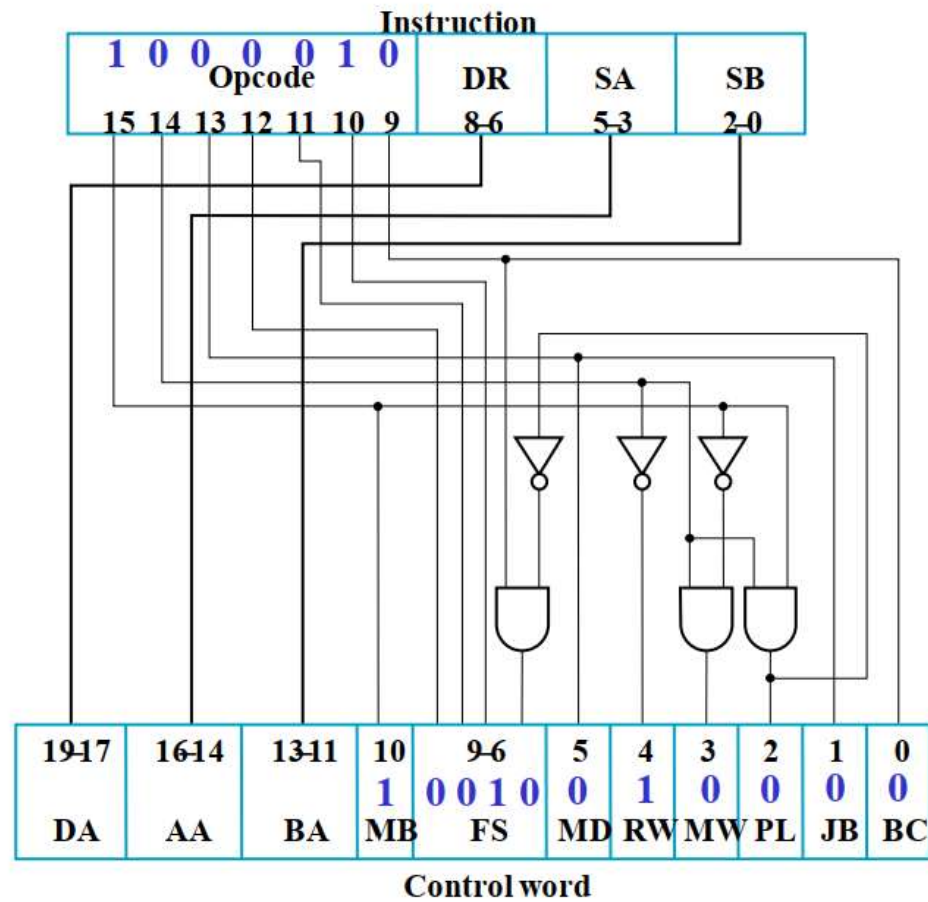


# Control Inputs and Paths for ADI

 

# Decoding for LD

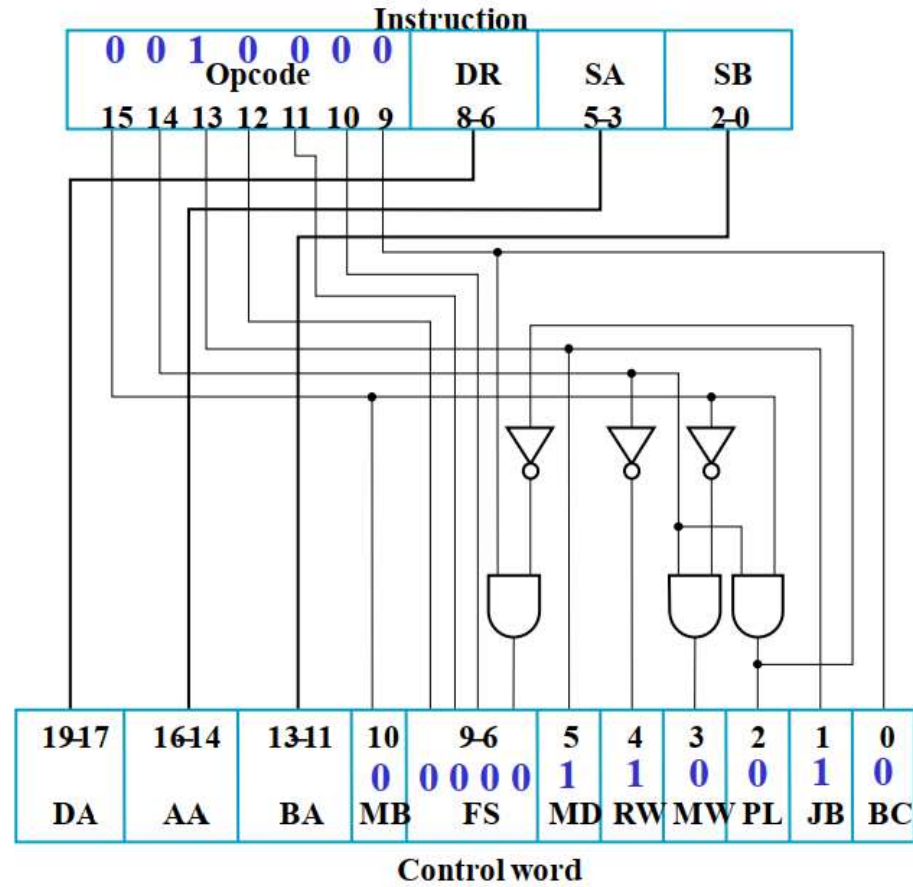


## Control Inputs and Paths for LD

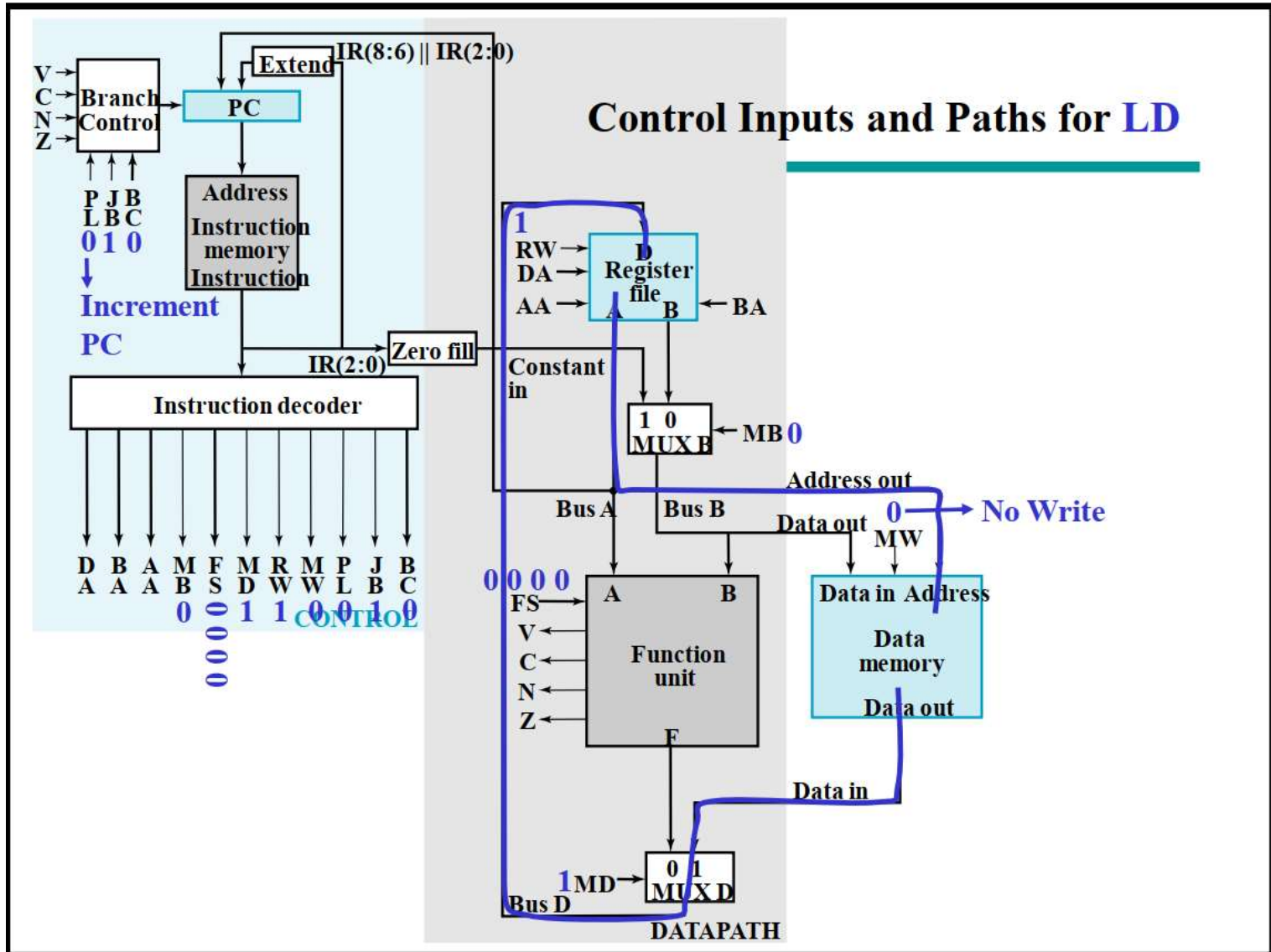




# Decoding for BRZ

 


## Control Inputs and Paths for BRZ

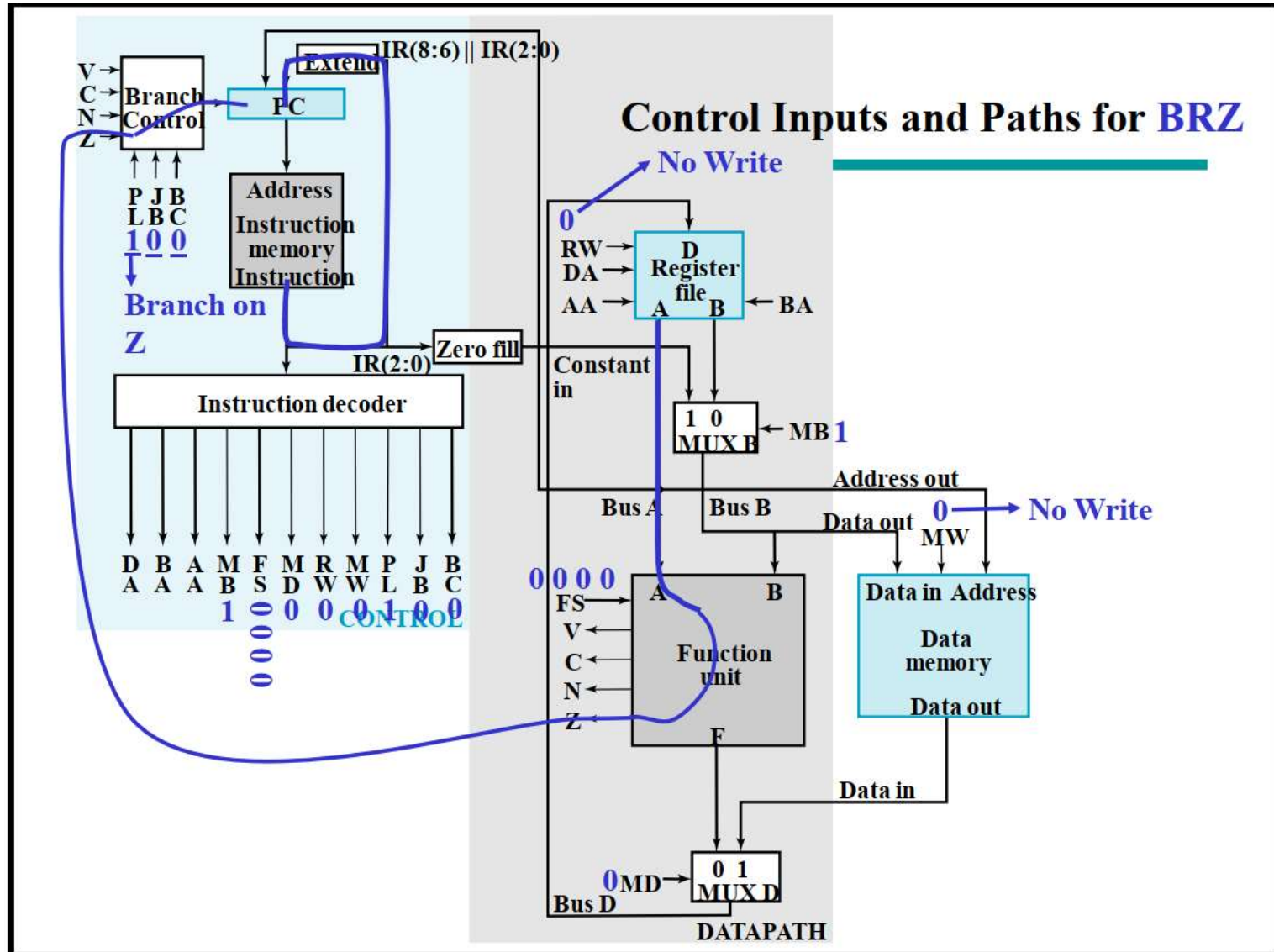
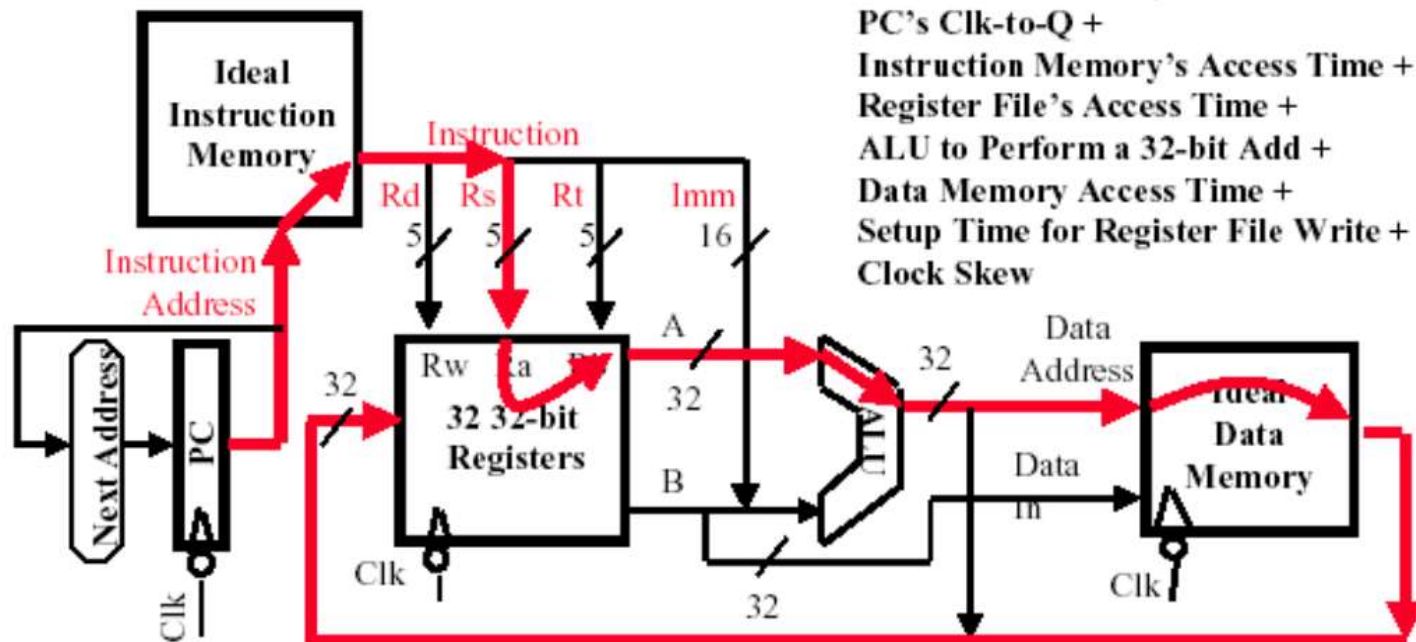
## Abstract View of Critical Path

- Register file and ideal memory:
  - The CLK input is a factor ONLY during write operation
  - During read operation, behave as combinational logic:
    - Address valid => Output valid after “access time.”



Critical Path (Load Operation) =  
PC's Clk-to-Q +  
Instruction Memory's Access Time +  
Register File's Access Time +  
ALU to Perform a 32-bit Add +  
Data Memory Access Time +  
Setup Time for Register File Write +  
Clock Skew