

**University Of Diyala  
College Of Engineering  
Department of Computer Engineering**



# **Digital System Design II**

## **Asynchronous Sequential Logic**

**Dr. Yasir Al-Zubaidi**

**Third stage**

**2021**

# Outline

- **Asynchronous Sequential Circuits**
- Analysis Procedure
- Circuits with Latches
- Design Procedure
- Reduction of State and Flow Tables
- Race-Free State Assignment
- Hazards
- Design Example

# Sequential Circuits

- Consist of a combinational circuit to which storage elements are connected to form a feedback path
- Specified by *a time sequence of inputs, outputs, and internal states*
- Two types of sequential circuits:
  - Synchronous
  - Asynchronous


 



Fig. 5-1 Block Diagram of Sequential Circuit
 
# Synchronous vs. Asynchronous


- **Asynchronous sequential circuits**
  - Internal states can change at *any instant* of time when there is a change in the input variables
  - **No clock signal is required**
  - Have better performance but hard to design due to timing problems



(a) Block diagram

 

(b) Timing diagram of clock pulses

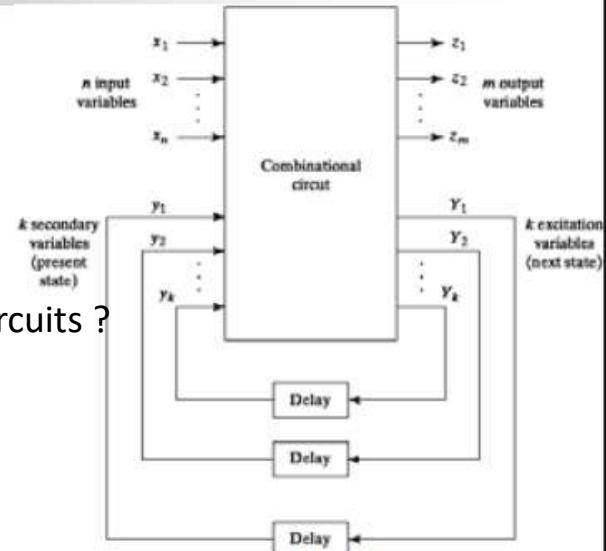

Why Asynchronous Circuits ?


- **Synchronous sequential circuits**
  - Synchronized by a *periodic* train of clock pulses
  - Much easier to design (preferred design style)

# Why Asynchronous Circuits ?

- **Used when speed of operation is important**
  - Response quickly without waiting for a clock pulse
- **Used in small independent systems**
  - Only a few components are required
- **Used when the input signals may change independently of internal clock**
  - Asynchronous in nature
- **Used in the communication between two units that have their own independent clocks**
  - Must be done in an asynchronous fashion
 
# Definitions of Asyn. Circuits

- **Inputs / Outputs**
- **Delay elements:**
  - Only a short term memory
  - May not really exist due to original gate delay
- **Secondary variable:**
  - Current state (small  $y$ )
- **Excitation variable:**
  - Next state (big  $Y$ )
  - Have some delay in response to input changes



# Operational Mode

---

- **Steady-state condition:**
  - Current states and next states are the same
  - Difference between  $Y$  and  $y$  will cause a transition
- **Fundamental mode:**
  - No simultaneous changes of two or more variables
  - The time between two input changes must be longer than the time it takes the circuit to a stable state
  - The input signals change one at a time and only when the circuit is in a stable condition

# Outline


- Asynchronous Sequential Circuits
- **Analysis Procedure**
- Circuits with Latches
- Design Procedure
- Reduction of State and Flow Tables
- Race-Free State Assignment
- Hazards
- Design Example



# Transition Table

- **Transition table is useful to analyze an asynchronous circuit from the circuit diagram**
- **Procedure to obtain transition table:**
  1. **Determine all feedback loops in the circuits**
  2. **Mark the input ( $y_i$ ) and output ( $Y_i$ ) of each feedback loop**
  3. **Derive the Boolean functions of all Y's**
  4. **Plot each Y function in a map and combine all maps into one table**
  5. **Circle those values of Y in each square that are equal to the value of y in the same row**

# An Example of Transition Table

 

$$Y_1 = xy_1 + x'y_2$$

$$Y_2 = xy'_1 + x'y_2$$

inputs

current  
states

	x	
y <sub>1</sub> y <sub>2</sub>	0	1
00	0	0
01	1	0
11	1	1
10	0	1

(a) Map for  
 $Y_1 = xy_1 + x'y_2$

	x	
y <sub>1</sub> y <sub>2</sub>	0	1
00	0	1
01	1	1
11	1	0
10	0	0

(b) Map for  
 $Y_2 = xy'_1 + x'y_2$

	x	
y <sub>1</sub> y <sub>2</sub>	0	1
00	00	01
01	11	01
11	11	10
10	00	10

(c) Transition table

**stable !!**

$$Y = Y_1 Y_2$$

# State Table

- When input  $x$  changes from 0 to 1 while  $y=00$ :
  - $Y$  changes to 01  $\rightarrow$  unstable
  - $y$  becomes 01 after a short delay  $\rightarrow$  stable at the second row
  - The next state is  $Y=01$
- Each row must have *at least one* stable state
- Analyze each state in this way can obtain its state table

		$x$	
		0	1
$y_1y_2$	00	00	01
	01	11	01
	11	11	10
	10	00	10

(c) Transition table

Present State		Next State			
		$X=0$		$X=1$	
0	0	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	1	1	1	1	0

$y_1y_2x$  :  
total state

4 stable  
total states:  
000,011,  
110,101

# Flow Table

- Similar to a transition table except the states are represented by *letter symbols*
- Can also include the output values
- Suitable to obtain the logic diagram from it
- Primitive flow table:  
*only one* stable state in each row (ex: 9-4(a))

	x	
	0	1
a	(a)	b
b	c	(b)
c	(c)	d
d	a	(d)

Equivalent to 9-3(c) if  
a=00, b=01, c=11, d=10

(a) Four states with one input

	x <sub>1</sub> x <sub>2</sub>			
	00	01	11	10
a	(a), 0	(a), 0	(a), 0	b, 0
b	a, 0	a, 0	(b), 1	(b), 0

(b) Two states with two inputs and one output

# Flow Table to Circuits

- Procedure to obtain circuits from flow table:
  - Assign to each state a distinct binary value (convert to a transition table)
  - Obtain circuits from the map
- Two difficulties:
  - The binary state assignment (to avoid race)
  - The output assigned to the unstable states


Ex: from the flow table 9-4(b)

		$x_1 x_2$			
		00	01	11	10
$y$	0	0	0	0	1
	1	0	0	1	1

(a) Transition table  
 $Y = x_1 x_2' + x_1 y$


		$x_1 x_2$			
		00	01	11	10
$y$	0	0	0	0	0
	1	0	0	1	0

(b) Map for output  
 $z = x_1 x_2 y$

 

(c) Logic diagram

# Race Conditions

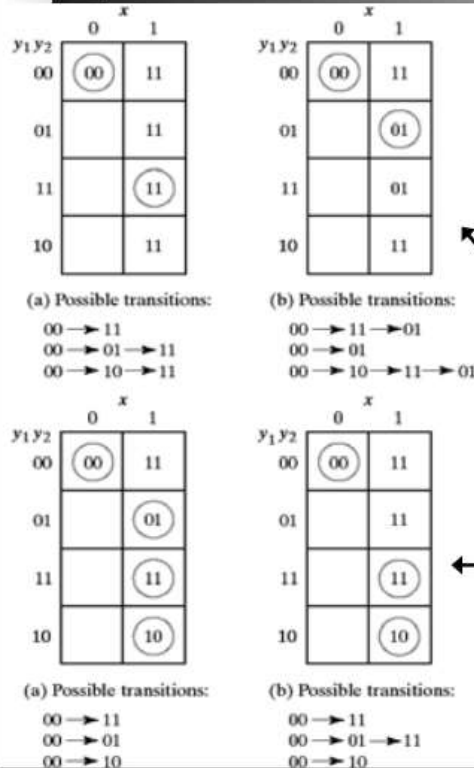

- **Race condition:**
  - *two or more* binary state variables will change value when one input variable changes
  - Cannot predict state sequence if unequal delay is encountered
- **Non-critical race:**
  - The final stable state *does not* depend on the change order of state variables
- **Critical race:**
  - The change order of state variables will result in *different* stable states
  - Should be avoided !!

# Race-Free State Assignment

- Race can be avoided by proper state assignment
  - Direct the circuit through intermediate unstable states with a unique state-variable change
  - It is said to have a *cycle*
- Must ensure that a cycle will terminate with a stable state
  - Otherwise, the circuit will keep going in unstable states
- More details will be discussed in Section 9-6

		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	(00)	01
	01		11
	11		10
	10		(10)


(a) State transition:  
00 → 01 → 11 → 10

		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	(00)	01
	01		11
	11		(11)
	10		(10)

(b) State transition:  
00 → 01 → 11


		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	(00)	01
	01		11
	11		10
	10		01

(c) Unstable

 
 
# Stability Check

- **Asynchronous sequential circuits may oscillate between unstable states due to the feedback**
  - Must check for stability to ensure proper operations
- **Can be easily checked from the transition table**
  - Any column has no stable states  $\rightarrow$  unstable
  - Ex: when  $x_1x_2=11$  in Fig. 9-9(b),  $Y$  and  $y$  are never the same



(a) Logic diagram

		$x_1 x_2$			
		00	01	11	10
$y$	0	0	1	1	0
	1	0	1	0	0

(b) Transition table




# Outline

- Asynchronous Sequential Circuits
- Analysis Procedure
- **Circuits with Latches**
- Design Procedure
- Reduction of State and Flow Tables
- Race-Free State Assignment
- Hazards
- Design Example

## **Latches in Asynchronous Circuits**

- **The traditional configuration of asynchronous circuits is using one or more feedback loops**
  - **No real delay elements**
- **It is more convenient to employ the SR latch as a memory element in asynchronous circuits**
  - **Produce an orderly pattern in the logic diagram with the memory elements clearly visible**
- **SR latch is also an asynchronous circuit**
  - **Will be analyzed first using the method for asynchronous circuits**

# SR Latch with NOR Gates

 


(a) Crossed-coupled circuit

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(After  $SR = 10$ )

(After  $SR = 01$ )

(b) Truth table

 

(c) Circuit showing feedback

		$SR$			
		00	01	11	10
$y$	0	0	0	0	1
	1	1	0	0	1

**$S=1, R=1$  ( $SR = 1$ )  
should not be used  
 $\Rightarrow SR = 0$  is  
normal mode**


$$Y = SR' + R'y$$

$$Y = S + R'y \text{ when } SR = 0 \rightarrow *$$

**should be carefully  
checked first 9-19**

(d) Transition table

# SR Latch with NAND Gates

 


(a) Crossed-coupled circuit

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(After  $SR = 10$ )

(After  $SR = 01$ )

(b) Truth table

 

(c) Circuit showing feedback

		$SR$			
		00	01	11	10
$y$	0	1	1	0	0
	1	1	1	1	0

$Y = S' + Ry$  when  $S'R' = 0$

**$S=0, R=0$  ( $S'R' = 1$ )  
should not be used  
 $\Rightarrow S'R' = 0$  is  
normal mode**

**\* should be carefully  
checked first 9-20**

(d) Transition table

# Analysis Procedure

- **Procedure to analyze an asynchronous sequential circuits with SR latches:**
  1. **Label each latch output with  $Y_i$  and its external feedback path (if any) with  $y_i$**
  2. **Derive the Boolean functions for each  $S_i$  and  $R_i$**
  3. **Check whether  $SR=0$  (NOR latch) or  $S'R'=0$  (NAND latch) is satisfied**
  4. **Evaluate  $Y=S+R'y$  (NOR latch) or  $Y=S'+Ry$  (NAND latch)**
  5. **Construct the transition table for  $Y=Y_1Y_2\cdots Y_k$**
  6. **Circle all stable states where  $Y=y$**

# Analysis Example

$$S_1 = x_1 y_2 \quad R_1 = x'_1 x'_2 \Rightarrow S_1 R_1 = x_1 y_2 x'_1 x'_2 = 0 \text{ (OK)}$$

$$S_2 = x_1 x_2 \quad R_2 = x'_2 y_1 \Rightarrow S_2 R_2 = x_1 x_2 x'_2 y_1 = 0 \text{ (OK)}$$

$$Y_1 = S_1 + R'_1 y_1$$


$$= x_1 y_2 + (x_1 + x_2) y_1$$

$$= x_1 y_2 + x_1 y_1 + x_2 y_1$$

$$Y_2 = S_2 + R'_2 y_2$$

$$= x_1 x_2 + (x_2 + y'_1) y_2$$

$$= x_1 x_2 + x_2 y_2 + y'_1 y_2$$

 

	$x_1 x_2$			
	00	01	11	10
$y_1 y_2$ 00	00	00	01	00
01	01	01	11	11
11	00	11	11	10
10	00	10	11	10

critical race !!

# Implementation Procedure

- **Procedure to implement an asynchronous sequential circuits with SR latches:**
  1. **Given a transition table that specifies the excitation function  $Y = Y_1 Y_2 \dots Y_k$ , derive a pair of maps for each  $S_i$  and  $R_i$  using the latch excitation table**
  2. **Derive the Boolean functions for each  $S_i$  and  $R_i$**   
(do not to make  $S_i$  and  $R_i$  equal to 1 in the same minterm square)
  3. **Draw the logic diagram using  $k$  latches together with the gates required to generate the S and R**  
(for NAND latch, use the complemented values in step 2)

# Implementation Example

Excitation table: list the required S and R for each possible transition from y to Y

		$x_1x_2$			
$y$		00	01	11	10
0	0	0	0	0	1
1	0	0	0	1	1

(a) Transition table  
 $Y = x_1x'_2 + x_1y$

$y$	$Y$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	1

(b) Latch excitation table

		$x_1x_2$			
$y$		00	01	11	10
0	0	0	0	0	1
1	0	0	0	X	X


(c) Map for  $S = x_1x'_2$

		$x_1x_2$			
$y$		00	01	11	10
0	0	X	X	X	0
1	0	1	1	0	0

 
(d) Map for  $R = x'_1$

$y = 1$  (outside)  $\rightarrow$  0 (inside)

$\therefore S=0, R=1$  from excitation table



(e) Circuit with NOR latch

 

(f) Circuit with NAND latch



# Debounce Circuit

- Mechanical switches are often used to generate binary signals to a digital circuit
  - It may vibrate or bounce several times before going to a final rest
  - Cause the signal to oscillate between 1 and 0
- A debounce circuit can remove the series of pulses from a contact bounce and produce a single smooth transition
  - Position A (SR=01) → bouncing (SR=11) → Position B (SR=10)  
Q = 1 (set) → Q = 1 (no change) → Q = 0 (reset)

