

# VLSI Circuits and Design

## Inverter and Dynamic View

## NMOS/PMOS Ratio

- ❑ So far we sized PMOS and NMOS so that they have matching  $R_{eq}$ 's (ratio of 3 to 3.5)
  - symmetrical VTC
  - equal high-to-low and low-to-high propagation delays
- ❑ When cascading similar inverters and if speed is the only concern, **reduce** the width of the PMOS device!
  - wide PMOS improves  $t_{pLH}$  but degrades  $t_{pHL}$  due to larger parasitic capacitance
- ❑ Define:
  - $r = R_{eqp}/R_{eqn}$  (resistance ratio of identically-sized PMOS and NMOS)
  - $\beta = (W/L)_p/(W/L)_n$

If wiring cap can be ignored, delay is minimum when

$$\beta_{opt} = \sqrt{r} \quad (\text{read text p.204 for derivation})$$

Inverter – Dynamic View.2


In slide “CMOS Inverter”, the VTC simulation on p. 20 was obtained using  $(W/L)_p/(W/L)_n = 3.4$ . For this inverter,  $V_M \sim 1.25$  V.

When we use smaller PMOS – get better speed at the cost of VTC symmetry and noise margin.

Widening PMOS of course improves  $t_{pLH}$  because it improves  $R_{eq}$  of the PMOS.

If wiring capacitance is not negligible, larger values of  $\beta$  should be used. The surprising result is that smaller device sizes (and hence smaller area) yield a faster design at the expense of VTC symmetry and noise margin.

## PMOS/NMOS Ratio Effects

 

$\beta$  of 2.4 (= 31 k $\Omega$ /13 k $\Omega$ ) gives symmetrical delay response (symmetrical VTC too)

$\beta$  of 1.6 to 1.9 gives optimal delay performance

Inverter – Dynamic View.3

From slide “MOS Transistor” p. 23,  $R_{eq}$  for PMOS and NMOS are 31 k $\Omega$  and 13 k $\Omega$ . For both transistors,  $(W/L) = 1$ .

For symmetrical characteristics, we want  $R_{pu} = R_{pd}$ . Hence we make  $(W/L)_p = 2.4(W/L)_n$  i.e.  $\beta = r = 2.4$ . From graph, delay is indeed symmetrical for this value of  $\beta$ .

In this example  $r = 31/13 = 2.4$ . Theoretically, for min delay  $\beta_{opt} = 2.4^{0.5} = 1.5$ . From plot above, min delay is actually at  $\beta = 1.9$ .

## Device Sizing for Performance

□ Divide capacitive load,  $C_L$ , into

- $C_{int}$  : intrinsic - diffusion and Miller effect (both proportional to  $W$ )
- $C_{ext}$  : extrinsic - wiring and fanout

$$t_p = 0.69R_{eq}C_{int}(1 + C_{ext}/C_{int}) = t_{p0}(1 + C_{ext}/C_{int})$$

$$t_{p0} = 0.69R_{eq}C_{int} \text{ is the intrinsic (unloaded) gate delay}$$


□ Widening both PMOS and NMOS by a factor  $S$  reduces  $R_{eq}$  by an identical factor ( $R_{eq} = R_{ref}/S$ ), but raises the **intrinsic** capacitance by the same factor ( $C_{int} = SC_{intref}$ )

$$t_p = 0.69R_{ref}C_{intref}(1 + C_{ext}/SC_{intref}) = t_{p0}(1 + C_{ext}/SC_{intref})$$

- $t_{p0}$  is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- any  $S$  sufficiently larger than  $(C_{ext}/C_{int})$  yields the best performance gains with least area impact

Making  $S$  infinitely large yields the maximum obtainable performance gain, i.e. min delay but of course area is also infinitely large too.

## Sizing Impacts on Delay

 

The majority of the improvement is already obtained for  $S = 5$ . Sizing factors larger than 10 barely yield any extra gain (and cost significantly more area).

self-loading effect  
(intrinsic capacitance dominates)

Inverter – Dynamic View.5

While sizing up an inverter reduces its delay, it also increases its input capacitance – impacting the delay of the driving gate!

## Impact of Fanout on Delay

- Extrinsic capacitance,  $C_{\text{ext}}$ , is a function of the fanout of the gate - the larger the fanout, the larger the external load.
- First determine the **input loading** effect of the inverter. Both  $C_g$  and  $C_{\text{int}}$  are proportional to gate size.
  - we can expect  $C_{\text{int}} = \gamma C_g$ .

$$t_p = t_{p0}(1 + C_{\text{ext}}/\gamma C_g) = t_{p0}(1 + f/\gamma).$$


where  $f = C_{\text{ext}}/C_g$  **effective fan-out** factor.

Delay of an inverter is a function of the ratio between its external load capacitance and its input gate capacitance.

$\gamma \approx 1$  for most submicron processes.
 
## Inverter Chain

- Real goal is to minimize the delay through an inverter chain



the delay of the  $j$ -th inverter stage is (ignore wire cap)

$$t_{p,j} = t_{p0} ( 1 + C_{g,j+1}/(\gamma C_{g,j}) ) = t_{p0} ( 1 + f_j/\gamma )$$

and  $t_p = t_{p1} + t_{p2} + \dots + t_{pN}$

so  $t_p = \sum t_{p,j} = t_{p0} \sum ( 1 + C_{g,j+1}/(\gamma C_{g,j}) )$

- If  $C_L$  is given
  - How should the inverters be sized?
  - How many stages are needed to minimize the delay?

## Sizing the Inverters in the Chain

- The optimum size of each inverter is the geometric mean of its neighbors

$$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$$

- We should size up each inverter by the same factor  $f$  wrt the preceding gate
  - each inverter has the same effective fan-out
  - each inverter has the same delay
- If  $C_{g,1}$  and  $C_L$  are given (refer text pp. 207 – 208 for derivation)

$$f = \sqrt[N]{\frac{C_L}{C_{g,1}}} = \sqrt[N]{F}$$

where  $F = C_L/C_{g,1}$  represents the overall effective fan-out of the circuit

- The minimum delay through the inverter chain is

$$t_p = N t_{p0} \left( 1 + \frac{\sqrt[N]{F}}{\gamma} \right)$$


Inverter – Dynamic View.8

Next question is, “what is the best  $N$  to minimize the delay for a given  $F$ ?”

Before that, an example of inverter chain sizing.



## Example of Inverter Chain Sizing

 

□  $C_L/C_{g,1}$  has to be evenly distributed over  $N = 3$  inverters

$$F = C_L/C_{g,1} = 8$$

$$f = \sqrt[3]{8} = 2$$

## Determining N: Optimal Number of Inverters

- What is the optimal value for N given F?
  - if the number of stages is too large, the intrinsic delay of the stages dominate
  - if the number of stages is too small, the effective fan-out of each stage dominate
- The optimum N is found by differentiating the minimum delay expression divided by the number of stages and setting the result to 0, giving

$$\gamma + \frac{\sqrt[N]{F} - \frac{\sqrt[N]{F} \ln F}{N}}{N} = 0$$

- For  $\gamma = 0$  (ignoring self-loading i.e.  $C_{int} = 0$ )
  - $N = \ln F$
  - hence the effective fan-out  $f = e = 2.7$
- For  $\gamma = 1$  (the typical case) the optimum effective fan-out (tapering factor) turns out to be close to 3.6

Inverter – Dynamic View.10

$$t_p = N t_{p0} \left( 1 + \frac{F^{1/N}}{\gamma} \right)$$

$$\begin{aligned} \frac{d}{dN} t_p &= t_{p0} + \frac{t_{p0}}{\gamma} \frac{d}{dN} N F^{1/N} \\ &= t_{p0} + \frac{t_{p0}}{\gamma} \left( F^{1/N} \frac{d}{dN} N + N \frac{d}{dN} F^{1/N} \right) \\ &= t_{p0} + \frac{t_{p0}}{\gamma} \left( F^{1/N} + N (\ln F) F^{1/N} \frac{d}{dN} \frac{1}{N} \right) \\ &= t_{p0} + \frac{t_{p0}}{\gamma} \left( F^{1/N} - N (\ln F) F^{1/N} \frac{1}{N^2} \right) \\ &= t_{p0} + \frac{t_{p0}}{\gamma} \left( F^{1/N} - \frac{1}{N} (\ln F) F^{1/N} \right) \end{aligned}$$

Set  $dt_p/dN = 0$ , we get  $\gamma + F^{1/N} - \frac{1}{N} (\ln F) F^{1/N} = 0$ .

Derivation for optimum fan-out:

$$N = \ln F$$


$$\therefore e^N = F$$

But effective fan-out  $f = F^{1/N}$ , or  $f^N = F$

$$\therefore e^N = f^N$$

$\therefore f = e$  for optimum delay.

## Optimum Effective Fan-Out

 

□ Choosing  $f$  larger than optimum has little effect on delay

- common practice to use  $f = 4$  (for  $\gamma = 1$ )
- if  $f$  is too small, then we need more stages to drive load cap – delay could be substantial

Inverter – Dynamic View.11





Rewrite  $\gamma + F^{1/N} - \frac{1}{N}(\ln F)F^{1/N} = 0$  in terms of  $f$ , where  $f = F^{1/N}$

$$\gamma + f - \frac{1}{N}(N \ln f)f = 0$$

$$\gamma + f - f \ln f = 0$$

This equation has to be solved numerically to find optimum  $f$ .

## Example of Inverter (Buffer) Staging

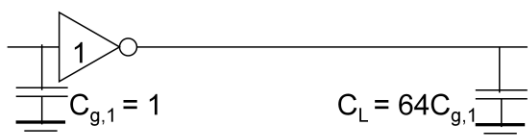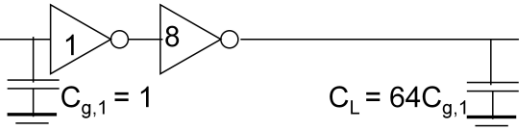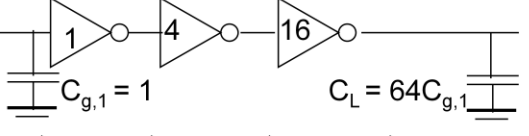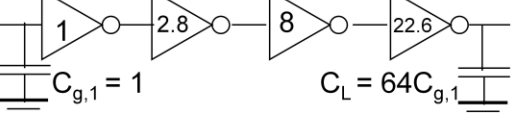	N	f	$t_p$
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64C_{g,1}</math> </p>	1	64	65
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64C_{g,1}</math> </p>	2	8	18
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64C_{g,1}</math> </p>	3	4	15
 <p> <math>C_{g,1} = 1</math> <math>C_L = 64C_{g,1}</math> </p>	4	2.8	15.3

## Impact of Buffer Staging for Large $C_L$

<b>F (<math>\gamma = 1</math>)</b>	<b>Unbuffered</b>	<b>Two Stage Chain</b>	<b>Opt. Inverter Chain</b>
10	$11t_{p0}$	$8.3t_{p0}$	$8.3t_{p0}$
100	$101t_{p0}$	$22t_{p0}$	$16.5t_{p0}$
1,000	$1001t_{p0}$	$65t_{p0}$	$24.8t_{p0}$
10,000	$10,001t_{p0}$	$202t_{p0}$	$33.1t_{p0}$

- Impressive speed-ups with optimized cascaded inverter chain for very large capacitive loads.

Inverter – Dynamic View.13

### **Exercise:**

How many stages is needed to obtain minimum delay for  $F = 1,000$ ?

How many stages is needed to obtain minimum delay for  $F = 10,000$ ?