

# VLSI Circuits and Design


## Logical Effort

# Outline

- Logical Effort
- Delay in a Logic Gate
- Multistage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary

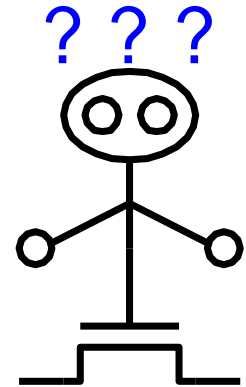
# Introduction

- Chip designers face a bewildering array of choices
  - What is the best circuit topology for a function?
  - How many stages of logic give least delay?
  - How wide should the transistors be?
- Logical effort is a method to make these decisions
  - Uses a simple model of delay
  - Allows back-of-the-envelope calculations
  - Helps make rapid comparisons between alternatives
  - Emphasizes remarkable symmetries


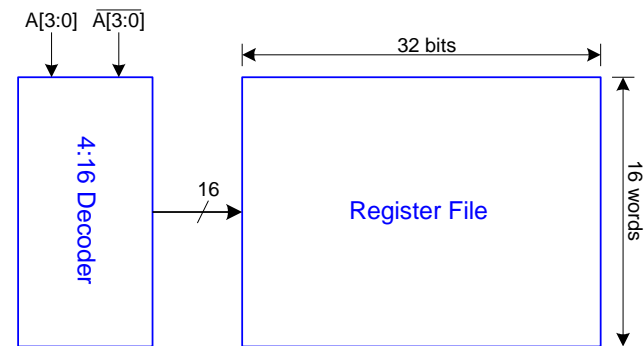
# Example

- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.
- Decoder specifications:
  - 16 word register file
  - Each word is 32 bits wide
  - Each bit presents load of 3 unit-sized transistors
  - True and complementary address inputs  $A[3:0]$
  - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
  - How many stages to use?
  - How large should each gate be?
  - How fast can decoder operate?



# Delay in a Logic Gate

- Express delays in process-independent unit
- Delay has two components:  $d = f + p$
- $f$ : *effort delay* =  $gh$  (a.k.a. stage effort)
  - Again has two components
- $g$ : *logical effort*
  - Measures relative ability of gate to deliver current
  - $g \equiv 1$  for inverter
- $h$ : *electrical effort* =  $C_{\text{out}} / C_{\text{in}}$ 
  - Ratio of output to input capacitance
  - Sometimes called fanout
- $p$ : *parasitic delay*
  - Represents delay of gate driving no load
  - Set by internal parasitic capacitance


$$d = \frac{d_{\text{abs}}}{\tau}$$
$$\tau = 3RC$$

$\approx$  3 ps in 65 nm process  
60 ps in 0.6  $\mu\text{m}$  process

# Delay Plots


$$d = f + p$$
$$= gh + p$$

- What about NOR2?

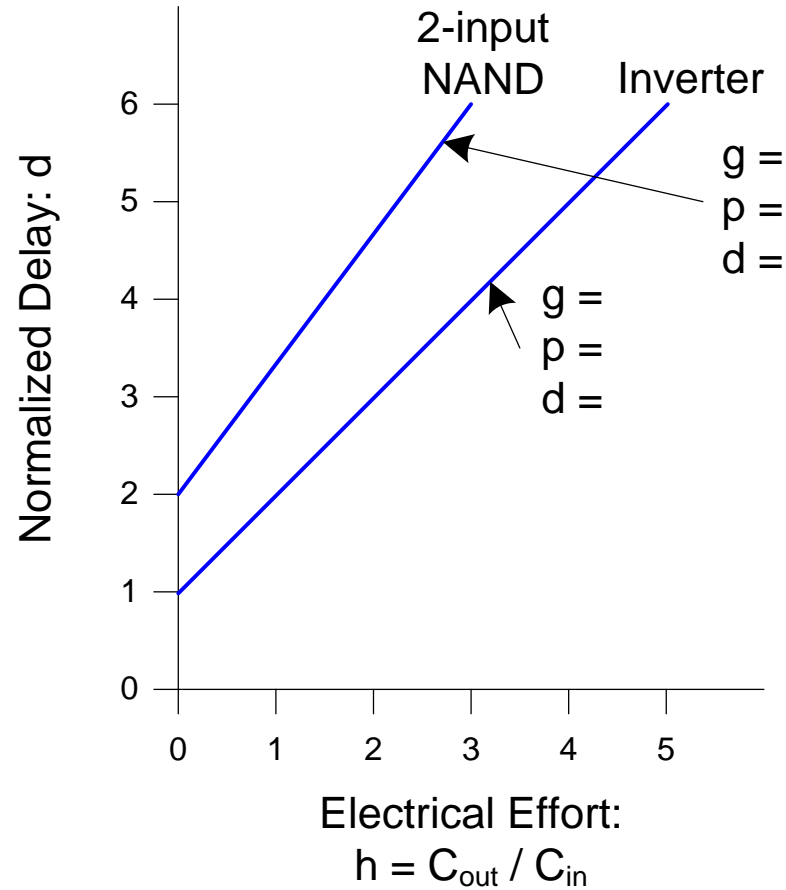

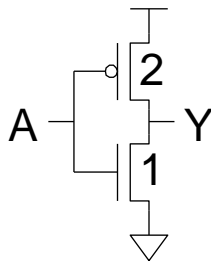
# Computing Logical Effort

- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



$$C_{in} = 3$$


$$g = 3/3$$

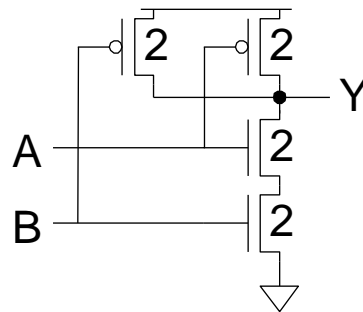

$$C_{in} = 4$$

$$g = 4/3$$

7

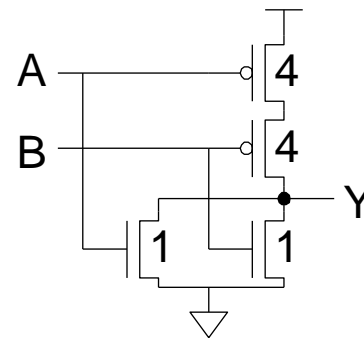

$$C_{in} = 5$$

$$g = 5/3$$

# Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	




# Catalog of Gates

- Parasitic delay of common gates
  - In multiples of  $p_{inv}$  ( $\approx 1$ )

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	
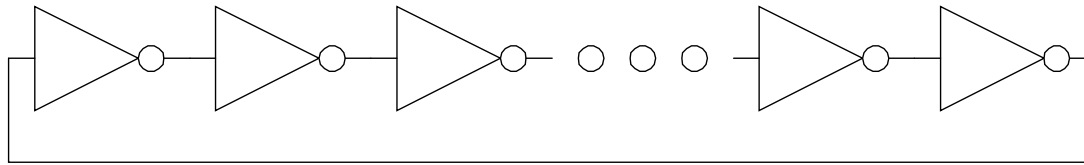
# Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort:  $g = 1$

Electrical Effort:  $h = 1$

Parasitic Delay:  $p = 1$


Stage Delay:  $d = 2$

Frequency:  $f_{osc} = 1/(2*N*d) = 1/4N$

31 stage ring oscillator in  
0.6  $\mu\text{m}$  process has  
frequency of  $\sim 200$  MHz
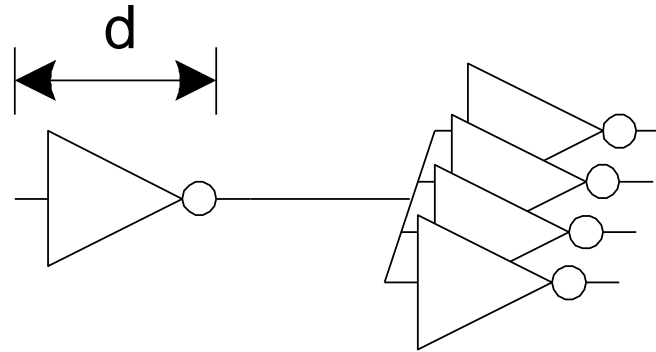
# Example: FO4 Inverter

Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g = 1$

Electrical Effort:  $h = 4$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 5$


# Multistage Logic Networks

- Logical effort generalizes to multistage networks

- *Path Logical Effort*  $G = \prod g_i$

- *Path Electrical Effort*  $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

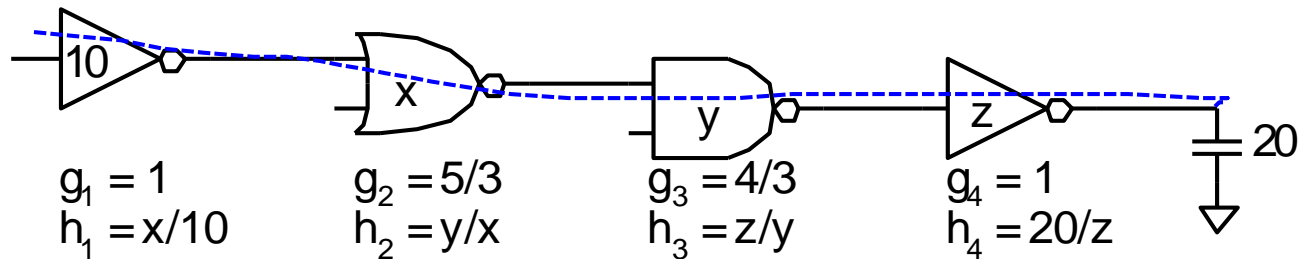- *Path Effort*  $F = \prod f_i = \prod g_i h_i$



# Multistage Logic Networks

- Logical effort generalizes to multistage networks

- *Path Logical Effort*  $G = \prod g_i$

- *Path Electrical Effort*  $H = \frac{C_{out-path}}{C_{in-path}}$

- *Path Effort*  $F = \prod f_i = \prod g_i h_i$

- Can we write  $F = GH$ ?

# Paths that Branch

- No! Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

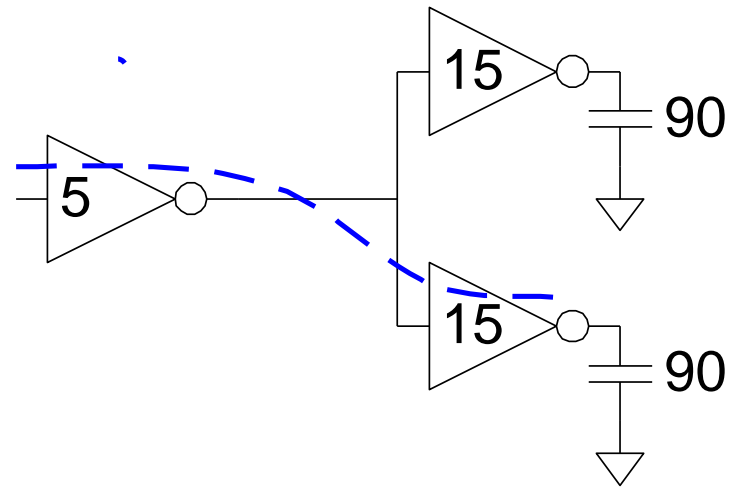

# Branching Effort

- Introduce *branching effort*
  - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
  - $F = GBH$

# Multistage Delays

- Path Effort Delay  $D_F = \sum f_i$
- Path Parasitic Delay  $P = \sum p_i$
- Path Delay  $D = \sum d_i = D_F + P$



# Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
  - Find fastest possible delay
  - Doesn't require calculating gate sizes

# Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.
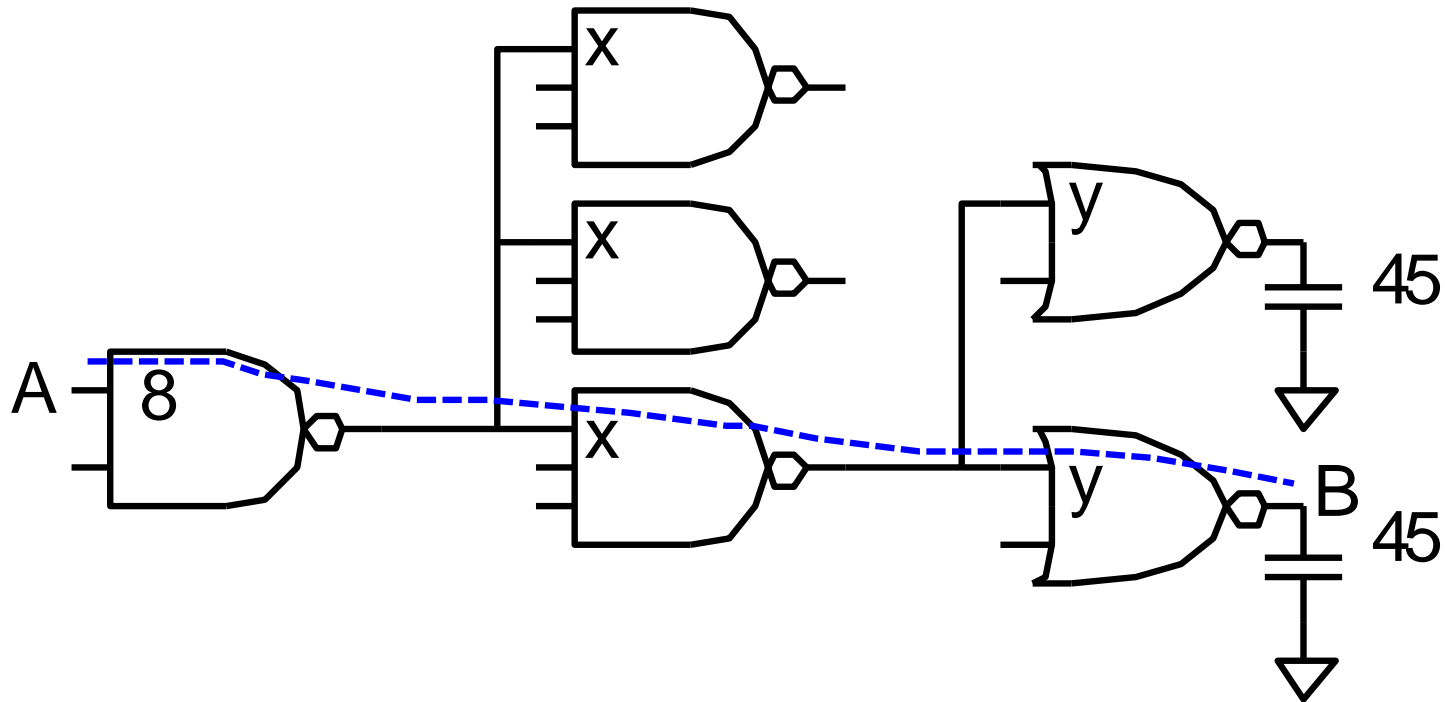
# Example: 3-stage path

- Select gate sizes  $x$  and  $y$  for least delay from A to B



# Example: 3-stage path

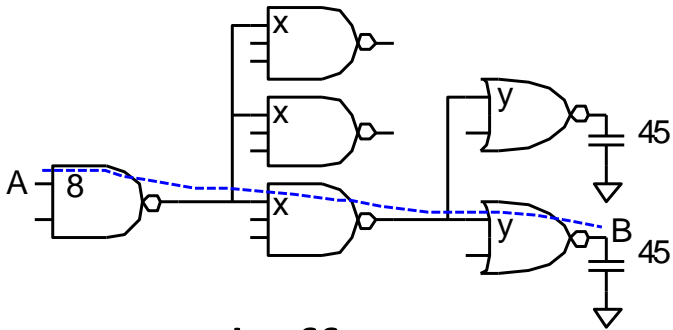

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay


$$D = 3 * 5 + 7 = 22 = 4.4 FO4$$

# Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15 * 2) * (5/3) / 5 = 10$$

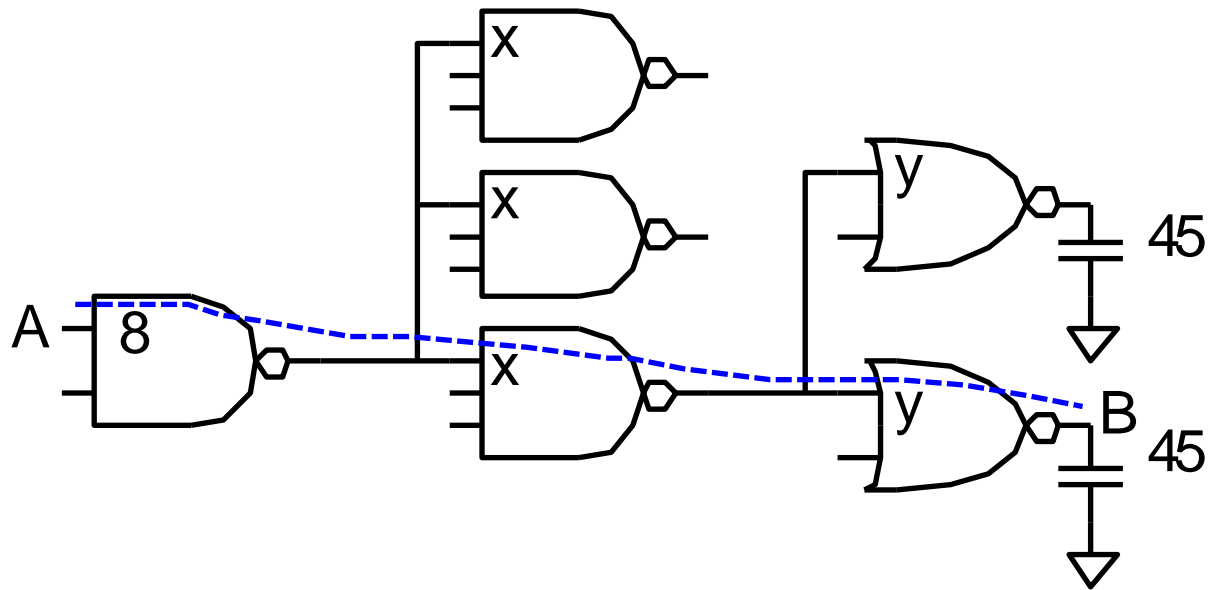


# Best Number of Stages

- How many stages should a path use?
  - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter


$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

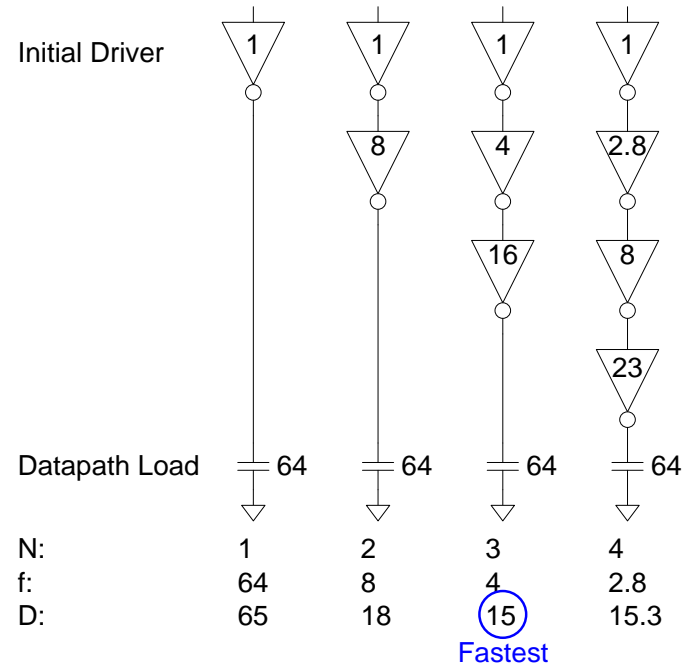
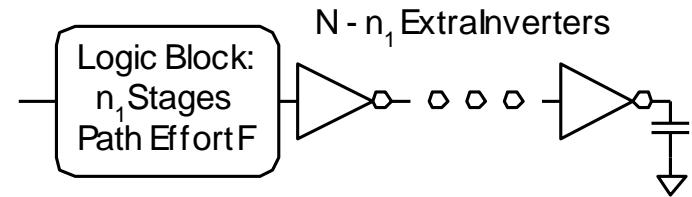
# Derivation

- Consider adding inverters to end of path
  - How many give least delay?



$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort  $\rho = F^{\frac{1}{N}}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

# Best Stage Effort

- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed-form


solution

- Neglecting parasitics ( $p_{inv} = 0$ ), we find  $\rho = 2.718$  (e)
- For  $p_{inv} = 1$ , solve numerically for  $\rho = 3.59$


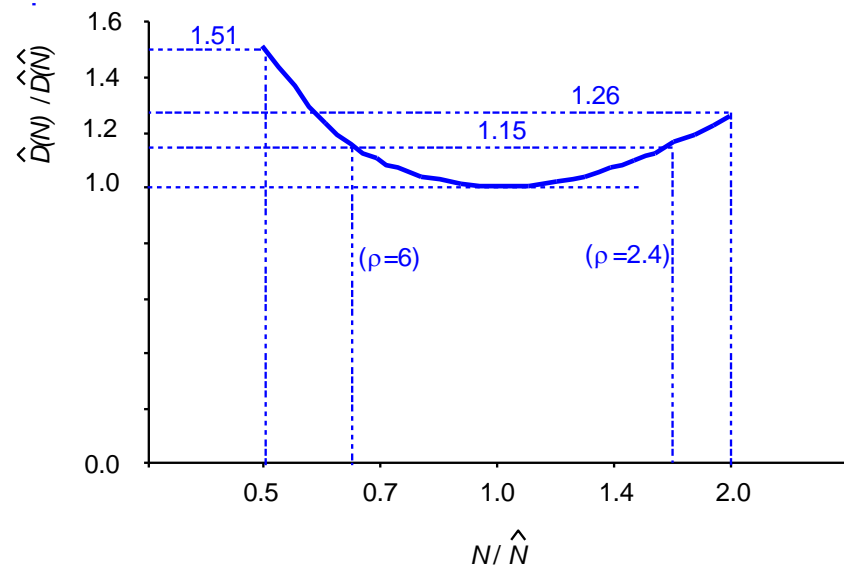
# Sensitivity Analysis


- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - We can be sloppy!
  - I like  $\rho = 4$
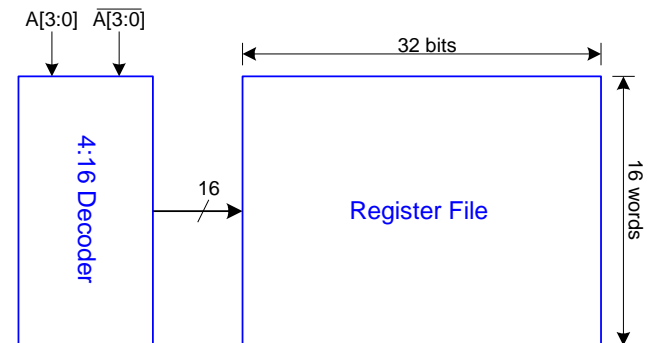
# Example, Revisited

- Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.
- Decoder specifications:
  - 16 word register file
  - Each word is 32 bits wide
  - Each bit presents load of 3 unit-sized transistors
  - True and complementary address inputs  $A[3:0]$
  - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
  - How many stages to use?
  - How large should each gate be?
  - How fast can decoder operate?



# Number of Stages

- Decoder effort is mainly electrical and branching

Electrical Effort:  $H = (32 * 3) / 10 = 9.6$

Branching Effort:  $B = 8$

- If we neglect logical effort (assume  $G = 1$ )

Path Effort:  $F = GBH = 76.8$

Number of Stages:  $N = \log_4 F = 3.1$

- Try a 3-stage design

# Gate Sizes & Delay


Logical Effort:  $G = 1 * 6/3 * 1 = 2$

Path Effort:  $F = GBH = 154$

Stage Effort:  $\hat{f} = F^{1/3} = 5.36$

Path Delay  $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

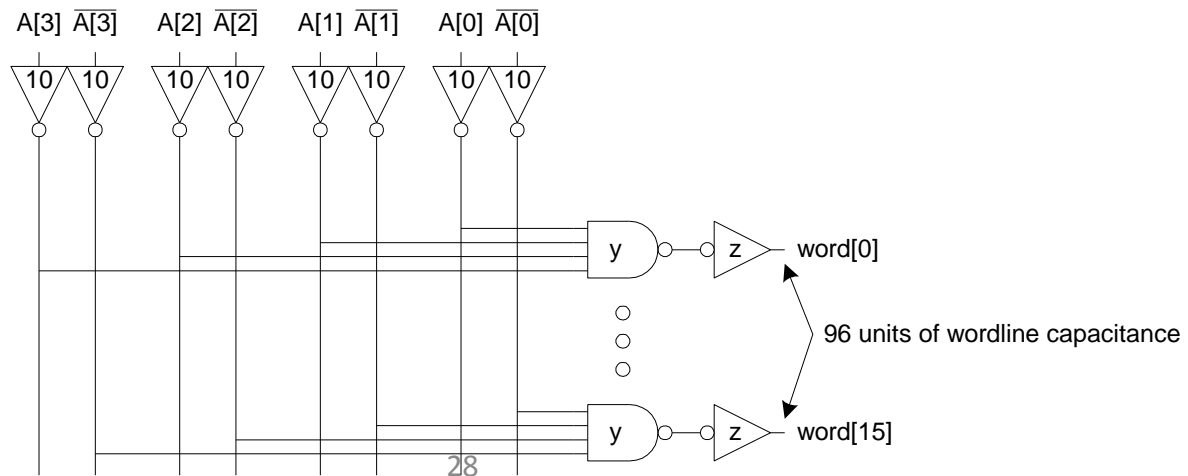Gate sizes:  $z = 96 * 1 / 5.36 = 18$      $y = 18 * 2 / 5.36 = 6.7$



# Comparison

- Compare many alternatives with a spreadsheet
- $D = N(76.8 G)^{1/N} + P$

Design	N	G	P	D
NOR4	1	3	4	234
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

# Review of Definitions

Term	Stage	Path
number of stages	1	$N$
logical effort	$g$	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	$f$	$D_F = \sum f_i$
parasitic delay	$p$	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

# Method of Logical Effort

1) Compute path effort

$$F = GBH$$

2) Estimate best number of stages

$$N = \log_4 F$$

3) Sketch path with N stages

4) Estimate least delay

$$D = NF^{\frac{1}{N}} + P$$

5) Determine best stage effort

$$\hat{f} = F^{\frac{1}{N}}$$

6) Find gate sizes

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

# Limits of Logical Effort

- Chicken and egg problem
  - Need path to compute  $G$
  - But don't know number of stages without  $G$
- Simplistic delay model
  - Neglects input rise time effects
- Interconnect
  - Iteration required in designs with wire
- Maximum speed only
  - Not minimum area/power for constrained delay



# Summary

- Logical effort is useful for thinking of delay in circuits
  - Numeric logical effort characterizes gates
  - NANDs are faster than NORs in CMOS
  - Paths are fastest when effort delays are  $\sim 4$
  - Path delay is weakly sensitive to stages, sizes
  - But using fewer stages doesn't mean faster paths
  - Delay of path is about  $\log_4 F$  FO4 inverter delays
  - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
  - But requires practice to master