
 


Lecture Six


 


V_{IL} Maximum input voltage considered as logic ‘0’.


V_{IH} Minimum input voltage considered as logic ‘1’.

V_{OH} Minimum output voltage considered as logic ‘1’.

  
V_{OL} Maximum output voltage considered as logic ‘0’.




CMOS Inverter VTC

 

 Noise Margins: Determining V_{IH} and V_{IL}



 

$$V_{IL} = V_M + \frac{V_{DD} - V_M}{g} = 1 + \frac{2.5 - 1}{-34.6} = 0.96 \text{ V}$$

$$V_{IH} = V_M - \frac{V_M}{g} = 1 - \frac{1}{-34.6} = 1.03 \text{ V}$$

$$NM_H = V_{DD} - V_{IH} = 2.5 - 0.96 = 1.54 \text{ V}$$

$$NM_L = V_{IL} = 1.03 \text{ V}$$

Slightly to large values due to the approximation

Example:-

Determine V_m if $K_n=172.5, K_p=45, V_{TN} = 0.43\text{ V}, V_{TP} = -0.4, V_{DSATN} = 0.63\text{ V}, V_{DSATP}=-1.0\text{ V}, V_{DD}=2.5\text{ V}$?

Solution:-

$$r = \frac{K_P V_{DSATP}}{K_N V_{DSATN}}$$


$$r = \frac{-45 \times (-1)}{172.5 \times 0.63} = 0.41$$

$$V_m = \frac{V_{TN} + \frac{V_{DSATN}}{2} + r(V_{DD} + V_{TP} + \frac{V_{DSATP}}{2})}{1+r}$$


$$V_m = \frac{0.43 + \frac{0.63}{2} + 0.41 \left(2.5 - 0.4 - \frac{1}{2} \right)}{1 + 0.41} = 1.0 \text{ V}$$

$$V_m \approx \frac{rV_{DD}}{1+r} = \frac{0.41 \times 1.5}{1+0.41} = 0.73 \text{ V}$$

Noise Margins

 


Example (Minimum sized transistors)

 

R_{eq} for Short Channel NMOS

Find I_{DSAT}

 
$$\begin{aligned}V_{DD} &= 2 \text{ V}; \quad V_T = 0.43 \text{ V}; \\V_{DSAT} &= 0.63 \text{ V}; \quad k_n = 115 \text{ mA/V}^2 \\W &= 0.375 \mu\text{m}; \quad L = 0.25 \mu\text{m}\end{aligned}$$




$$I_{DSAT} = k_n \frac{W}{L} \left((V_{DD} - V_T)V_{DSAT} - \frac{V_{DSAT}^2}{2} \right) = I_{DSAT} = I_D \text{ when } V_{DS} = 0 \text{ (extrapolated)}$$
 
$$I_{DSAT} = 115 \frac{0.375}{0.25} \left((2 - 0.43)0.63 - \frac{0.63^2}{2} \right) = 136 \mu\text{A}$$





Inverter - Transient Response

 


$$C_L = 2 \text{ fF}; \quad R_{eq-n} = 10 \text{ k}\Omega$$

$$t_r = 2.2RC = 2.2 \times 10 \times 10^3 \times 2 \times 10^{-15} = 44 \text{ ps}$$

$$t_{pHL} = 0.69RC = 0.69 \times 10 \times 10^3 \times 2 \times 10^{-15} = 14 \text{ ps}$$


CMOS Inverter Propagation Delay

 

$$t_{pLH} = 0.69 R_{eqp} C_L$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

Inverter Transient Response

 

$V_{DD} = 2.5V$
 $0.25\mu m$
 $W/L_n = 1.5$
 $W/L_p = 4.5$
 $R_{eqn} = 13 k\Omega (\div 1.5)$
 $R_{eqp} = 31 k\Omega (\div 4.5)$
See p. 27 for C_L
 $t_{pHL} = 36 \text{ psec}$
 $t_{pLH} = 29 \text{ psec}$
so
 $t_p = 32.5 \text{ psec}$

$$C_{LLH} = 6.1 \text{ fF}$$

$$C_{LHL} = 6.1 \text{ fF}$$


$$R_{eqn} = 13 \text{ k}\Omega / 1.5 = 8.67 \text{ k}\Omega$$

$$R_{eqp} = 31 \text{ k}\Omega / 4.5 = 6.89 \text{ k}\Omega$$

$$t_{pHL} = 0.69 \times R_{eqn} \times C_{LHL} = 0.69 \times 8.67 \times 6.1 = 36 \text{ ps}$$

$$t_{pLH} = 0.69 \times R_{eqp} \times C_{LLH} = 0.69 \times 6.89 \times 6.1 = 29 \text{ ps}$$
 
$$t_p = \frac{(t_{pHL} + t_{pLH})}{2} = \frac{36 + 29}{2} = 32.5 \text{ ps}$$




Connection and behavior of series and parallel transistors


AOI/OAI nMOS Circuits

- nMOS AOI structure

- series txs in parallel

 


$$F = \overline{a \cdot b + c \cdot d}$$

 

- nMOS OAI structure

- series of parallel txs

 

$$F = \overline{(a+e) \cdot (b+f)}$$

