



# Electrical Circuit-II

## 7<sup>th</sup> Lecture-Tutorial

### Series and Parallel AC Circuits

By:


Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

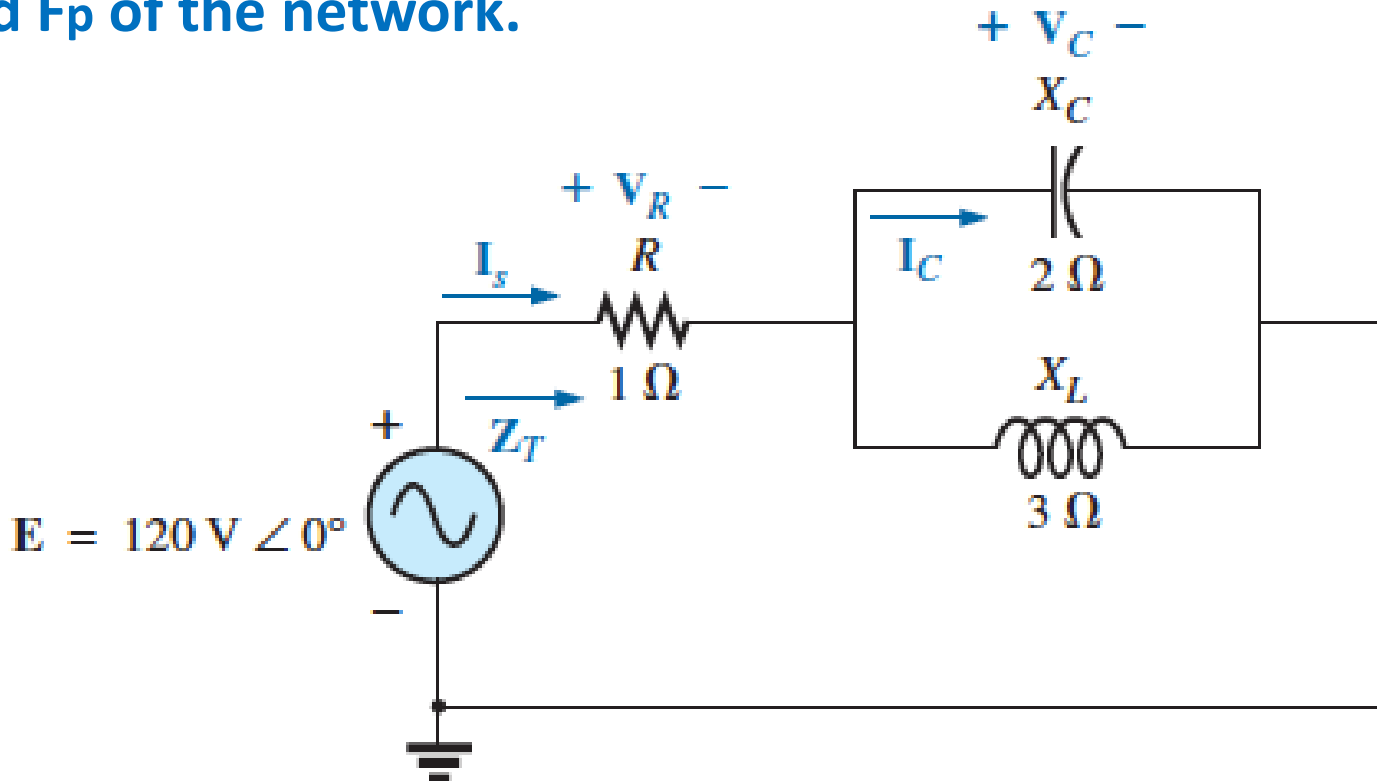**Example**

For the network calculate:

- Calculate  $Z_T$ .
- Determine  $I_s$ .
- Calculate  $V_R$  and  $V_C$ .
- Find  $I_C$ .
- Compute the power delivered.
- Find  $F_p$  of the network.



Solution

a.

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2$$

with


$$\mathbf{Z}_1 = R \angle 0^\circ = 1 \Omega \angle 0^\circ$$

$$\begin{aligned} \mathbf{Z}_2 = \mathbf{Z}_C \parallel \mathbf{Z}_L &= \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(2 \Omega \angle -90^\circ)(3 \Omega \angle 90^\circ)}{-j2 \Omega + j3 \Omega} \\ &= \frac{6 \Omega \angle 0^\circ}{j1} = \frac{6 \Omega \angle 0^\circ}{1 \angle 90^\circ} = 6 \Omega \angle -90^\circ \end{aligned}$$

and

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 1 \Omega - j6 \Omega = 6.08 \Omega \angle -80.54^\circ$$
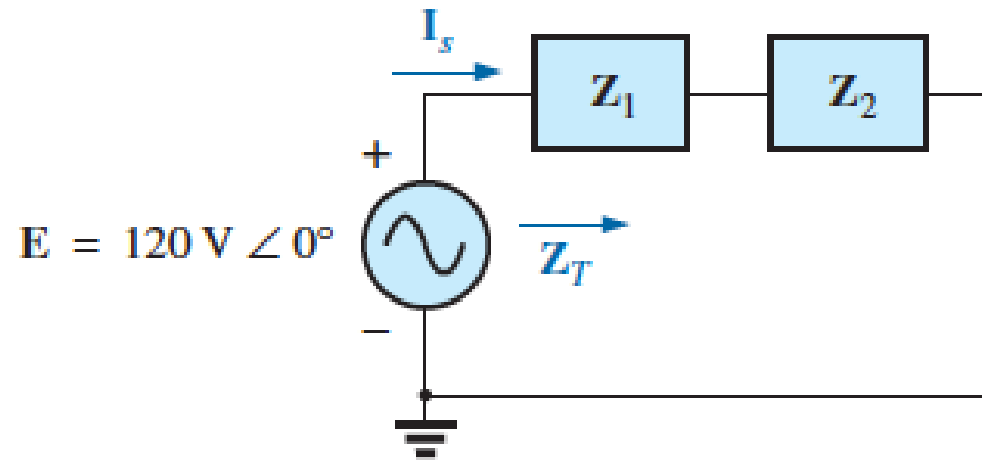
$$\text{b. } \mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{120 \text{ V} \angle 0^\circ}{6.08 \Omega \angle -80.54^\circ} = 19.74 \text{ A} \angle 80.54^\circ$$



c.  $V_R = I_s Z_1 = (19.74 \text{ A } \angle 80.54^\circ)(1 \Omega \angle 0^\circ) = \mathbf{19.74 \text{ V } \angle 80.54^\circ}$

$$V_C = I_s Z_2 = (19.74 \text{ A } \angle 80.54^\circ)(6 \Omega \angle -90^\circ) \\ = \mathbf{118.44 \text{ V } \angle -9.46^\circ}$$

d. Now that  $V_C$  is known, the current  $I_C$  can also be found using Ohm's law.

$$I_C = \frac{V_C}{Z_C} = \frac{118.44 \text{ V } \angle -9.46^\circ}{2 \Omega \angle -90^\circ} = \mathbf{59.22 \text{ A } \angle 80.54^\circ}$$


e.  $P_{\text{del}} = I_s^2 R = (19.74 \text{ A})^2(1 \Omega) = \mathbf{389.67 \text{ W}}$

f.  $F_p = \cos \theta = \cos 80.54^\circ = \mathbf{0.164 \text{ leading}}$
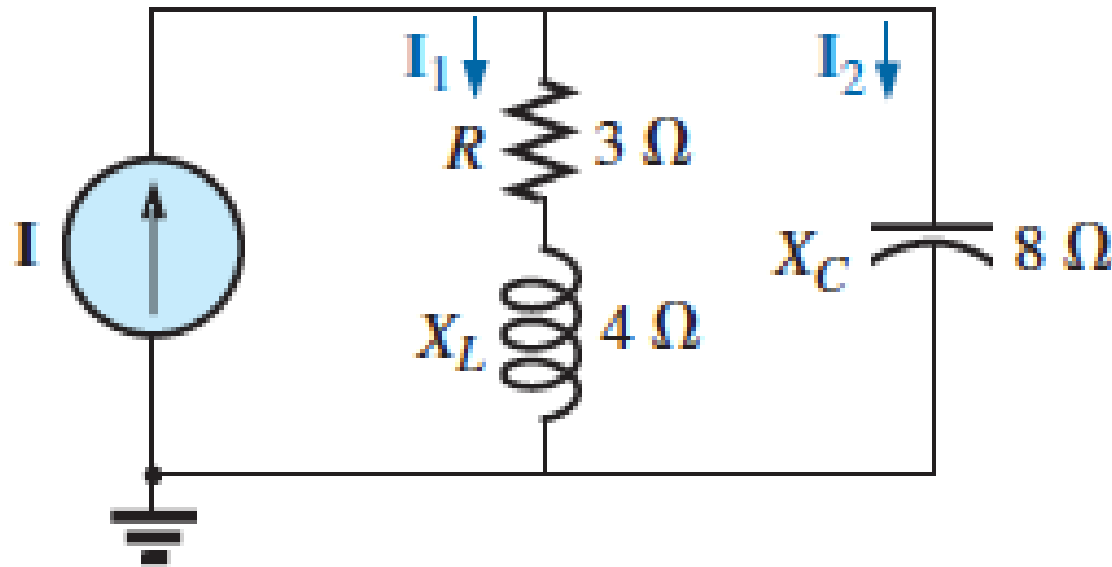
## Example

For the network calculate:

- If  $I$  is  $50 \text{ A} \angle 30^\circ$ , calculate  $I_1$  using the current divider rule.
- Repeat part (a) for  $I_2$ .
- Verify Kirchoff's current law at one node.




Solution

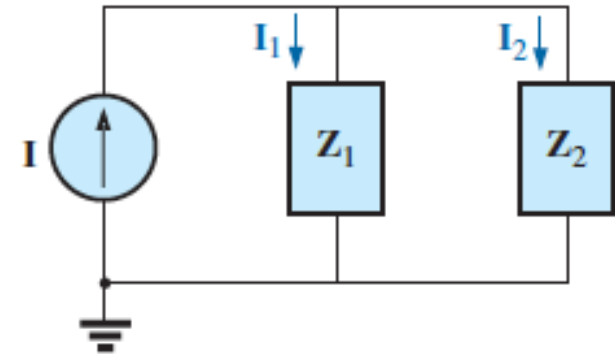a. Redrawing the circuit as

$$\mathbf{Z}_1 = R + jX_L = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$

$$\mathbf{Z}_2 = -jX_C = -j8 \Omega = 8 \Omega \angle -90^\circ$$



Using the current divider rule yields

$$\begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{Z}_2 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(8 \Omega \angle -90^\circ)(50 \text{ A} \angle 30^\circ)}{(-j8 \Omega) + (3 \Omega + j4 \Omega)} = \frac{400 \angle -60^\circ}{3 - j4} \\ &= \frac{400 \angle -60^\circ}{5 \angle -53.13^\circ} = \mathbf{80 \text{ A} \angle -6.87^\circ} \end{aligned}$$

$$\begin{aligned} \text{b. } \mathbf{I}_2 &= \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(5 \Omega \angle 53.13^\circ)(50 \text{ A} \angle 30^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{250 \angle 83.13^\circ}{5 \angle -53.13^\circ} \\ &= \mathbf{50 \text{ A} \angle 136.26^\circ} \end{aligned}$$

$$\begin{aligned} \text{c. } \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 \\ 50 \text{ A} \angle 30^\circ &= 80 \text{ A} \angle -6.87^\circ + 50 \text{ A} \angle 136.26^\circ \\ &= (79.43 - j9.57) + (-36.12 + j34.57) \\ &= 43.31 + j25.0 \\ 50 \text{ A} \angle 30^\circ &= 50 \text{ A} \angle 30^\circ \quad (\text{checks}) \end{aligned}$$

## Example

For the network calculate:

- Calculate the voltage  $V_C$  using the voltage divider rule.
- Calculate the current  $I_s$ .

## Solution


- The network is redrawn

$$Z_1 = 5 \Omega = 5 \Omega \angle 0^\circ$$

$$Z_2 = -j 12 \Omega = 12 \Omega \angle -90^\circ$$

$$Z_3 = +j 8 \Omega = 8 \Omega \angle 90^\circ$$
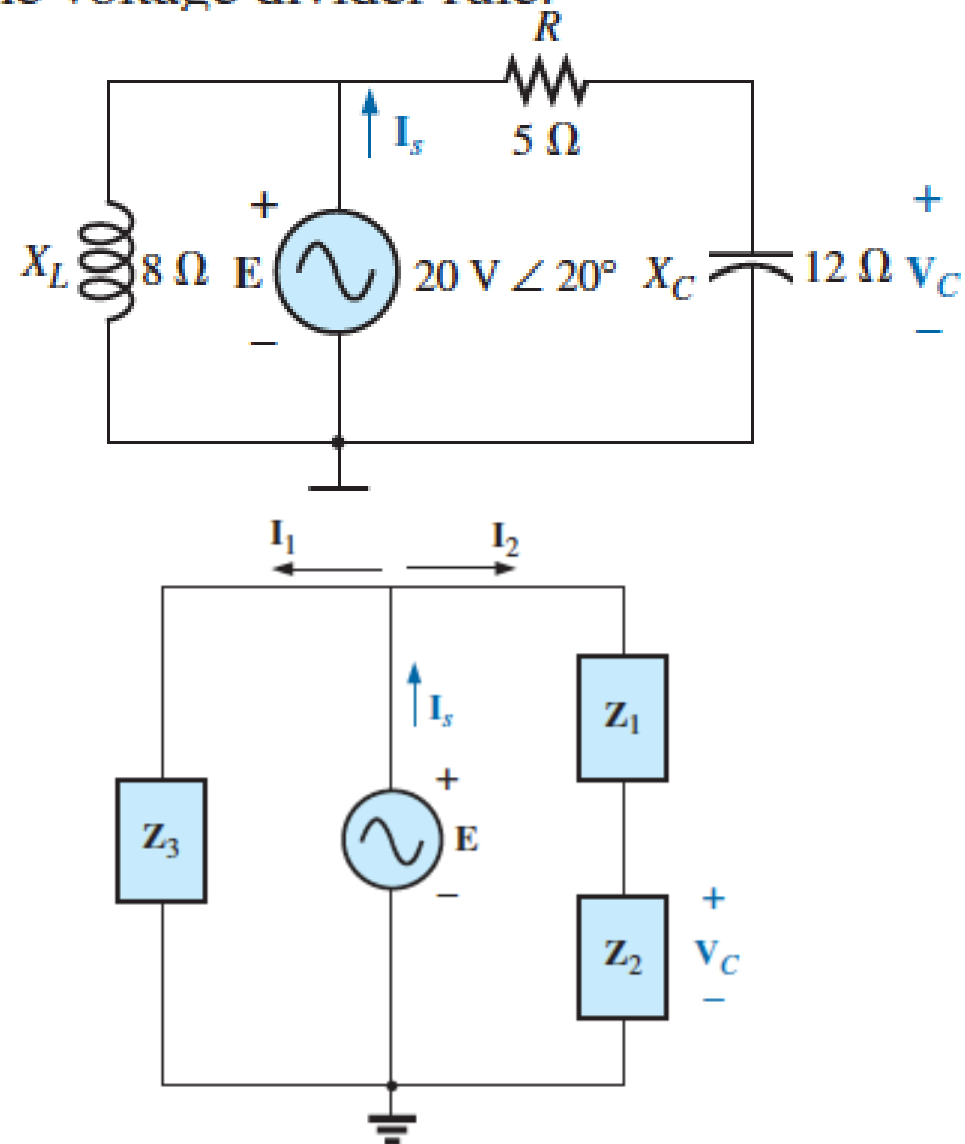
$$\begin{aligned} V_C &= \frac{Z_2 E}{Z_1 + Z_2} \\ &= \frac{(12 \Omega \angle -90^\circ)(20 \text{ V} \angle 20^\circ)}{5 \Omega - j 12 \Omega} \\ &= \frac{240 \text{ V} \angle -70^\circ}{13 \angle -67.38^\circ} \\ &= 18.46 \text{ V} \angle -2.62^\circ \end{aligned}$$



Solution

$$\text{b. } \mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_3} = \frac{20 \text{ V } \angle 20^\circ}{8 \Omega \angle 90^\circ} = 2.5 \text{ A } \angle -70^\circ$$

$$\mathbf{I}_2 = \frac{\mathbf{E}}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{20 \text{ V } \angle 20^\circ}{13 \Omega \angle -67.38^\circ} = 1.54 \text{ A } \angle 87.38^\circ$$

and

$$\begin{aligned} \mathbf{I}_s &= \mathbf{I}_1 + \mathbf{I}_2 \\ &= 2.5 \text{ A } \angle -70^\circ + 1.54 \text{ A } \angle 87.38^\circ \\ &= (0.86 - j 2.35) + (0.07 + j 1.54) \\ \mathbf{I}_s &= 0.93 - j 0.81 = 1.23 \text{ A } \angle -41.05^\circ \end{aligned}$$