



# Electrical Circuit-II

## 7<sup>th</sup> Lecture

### Series and Parallel AC Circuits


#### (Part 3)

By:


Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

# R – C Circuit

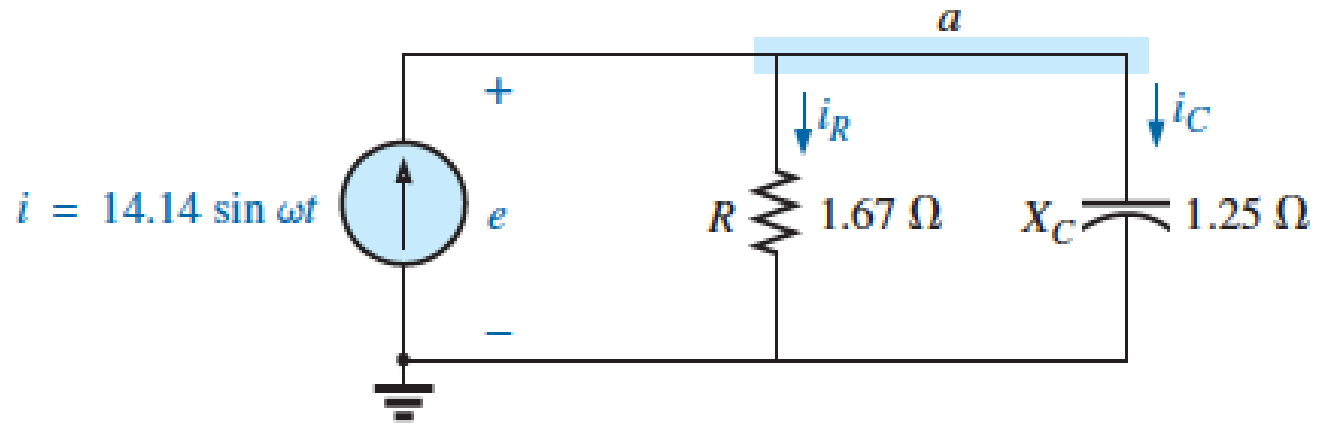

## Phasor Representation

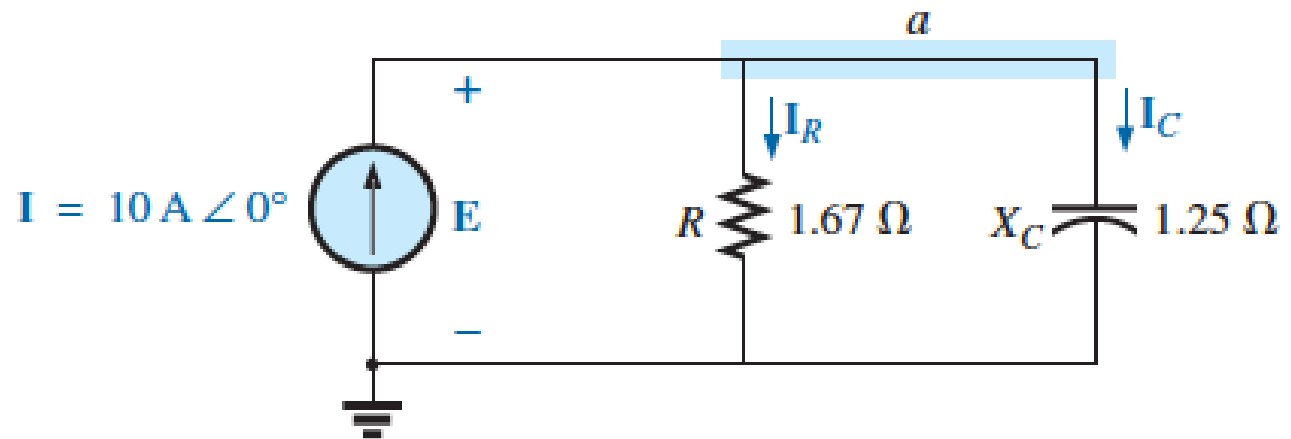


## R – C Circuit

$$\begin{aligned} \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_C = G \angle 0^\circ + B_C \angle 90^\circ = \frac{1}{1.67 \, \Omega} \angle 0^\circ + \frac{1}{1.25 \, \Omega} \angle 90^\circ \\ &= 0.6 \, \text{S} \angle 0^\circ + 0.8 \, \text{S} \angle 90^\circ = 0.6 \, \text{S} + j 0.8 \, \text{S} = \mathbf{1.0 \, \text{S} \angle 53.13^\circ} \end{aligned}$$

$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{1.0 \, \text{S} \angle 53.13^\circ} = \mathbf{1 \, \Omega \angle -53.13^\circ}$$

### Admittance diagram

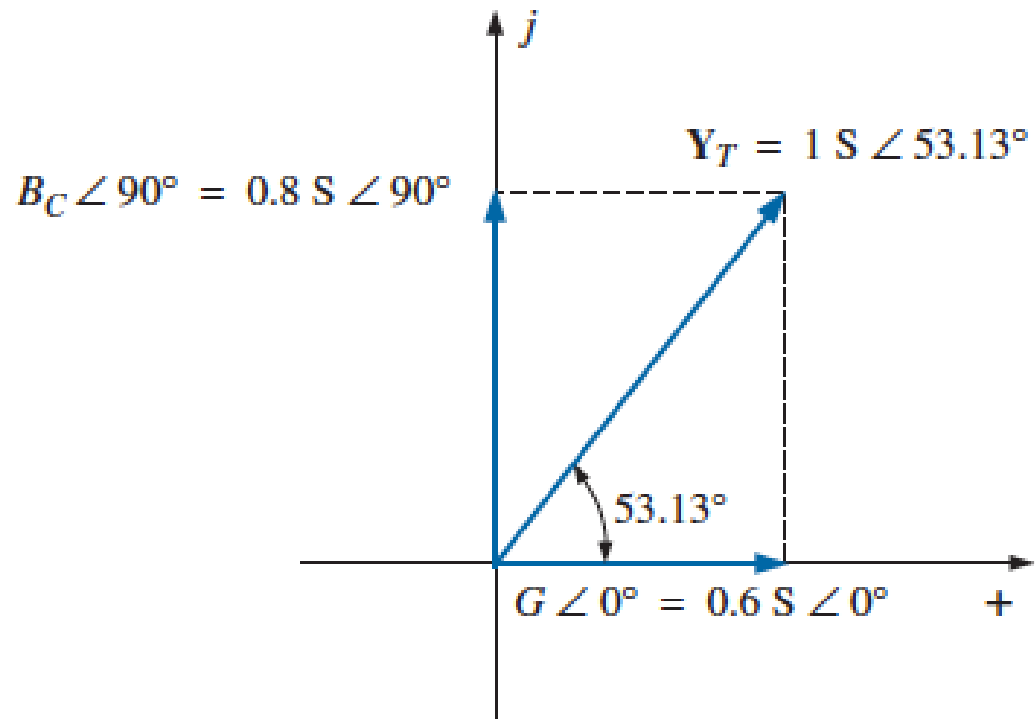

## R – C Circuit

$$\mathbf{E} = \mathbf{I}Z_T = \frac{\mathbf{I}}{\mathbf{Y}_T} = \frac{10 \text{ A } \angle 0^\circ}{1 \text{ S } \angle 53.13^\circ} = 10 \text{ V } \angle -53.13^\circ$$

$$\begin{aligned} \mathbf{I}_R &= (\mathbf{E} \angle \theta)(\mathbf{G} \angle 0^\circ) \\ &= (10 \text{ V } \angle -53.13^\circ)(0.6 \text{ S } \angle 0^\circ) = 6 \text{ A } \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= (\mathbf{E} \angle \theta)(\mathbf{B}_C \angle 90^\circ) \\ &= (10 \text{ V } \angle -53.13^\circ)(0.8 \text{ S } \angle 90^\circ) = 8 \text{ A } \angle 36.87^\circ \end{aligned}$$


*Kirchhoff's current law:* At node  $a$ ,

$$\mathbf{I} - \mathbf{I}_R - \mathbf{I}_C = 0$$

$$\mathbf{I} = \mathbf{I}_R + \mathbf{I}_C$$

or

### Phasor diagram

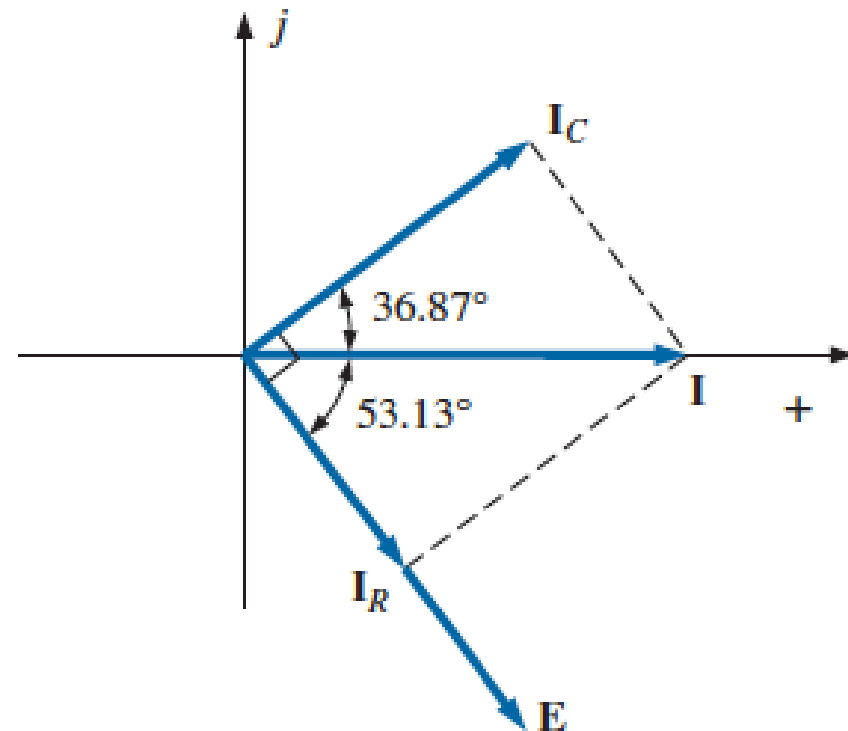


## R – C Circuit

$$e = \sqrt{2}(10) \sin(\omega t - 53.13^\circ) = 14.14 \sin(\omega t - 53.13^\circ)$$

$$i_R = \sqrt{2}(6) \sin(\omega t - 53.13^\circ) = 8.48 \sin(\omega t - 53.13^\circ)$$
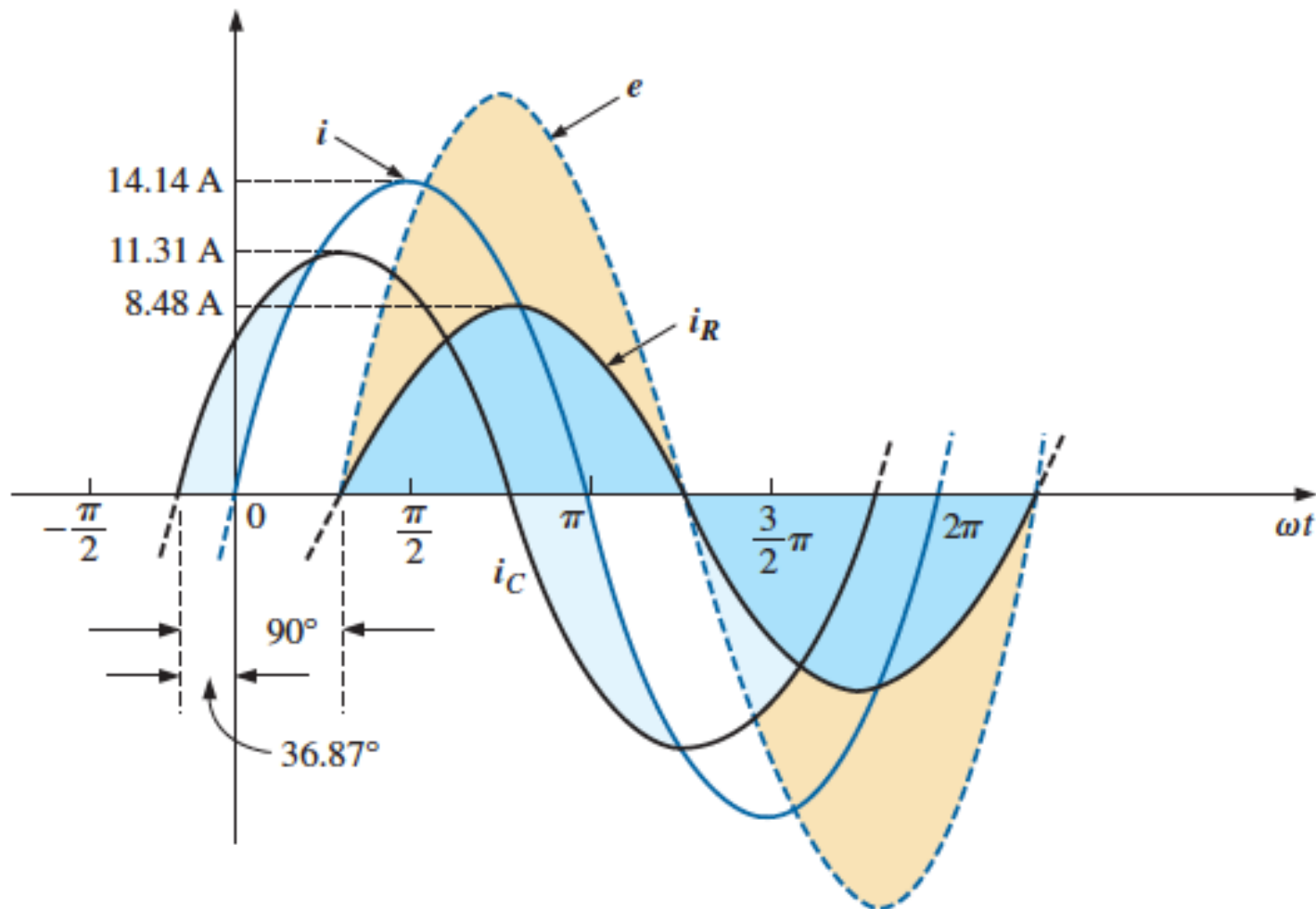
$$i_C = \sqrt{2}(8) \sin(\omega t + 36.87^\circ) = 11.31 \sin(\omega t + 36.87^\circ)$$



## R – C Circuit

*Power:*

$$P_T = EI \cos \theta = (10 \text{ V})(10 \text{ A}) \cos 53.13^\circ = (10)^2(0.6) \\ = \mathbf{60 \text{ W}}$$

or 
$$P_T = E^2 G = (10 \text{ V})^2(0.6 \text{ S}) = \mathbf{60 \text{ W}}$$

or, finally,


$$P_T = P_R + P_C = EI_R \cos \theta_R + EI_C \cos \theta_C \\ = (10 \text{ V})(6 \text{ A}) \cos 0^\circ + (10 \text{ V})(8 \text{ A}) \cos 90^\circ \\ = \mathbf{60 \text{ W}}$$

*Power factor:* The power factor of the circuit is


$$F_p = \cos 53.13^\circ = \mathbf{0.6 \text{ leading}}$$

$$F_p = \cos \theta_T = \frac{G}{Y_T} = \frac{0.6 \text{ S}}{1.0 \text{ S}} = \mathbf{0.6 \text{ leading}}$$

# R – L – C Circuit

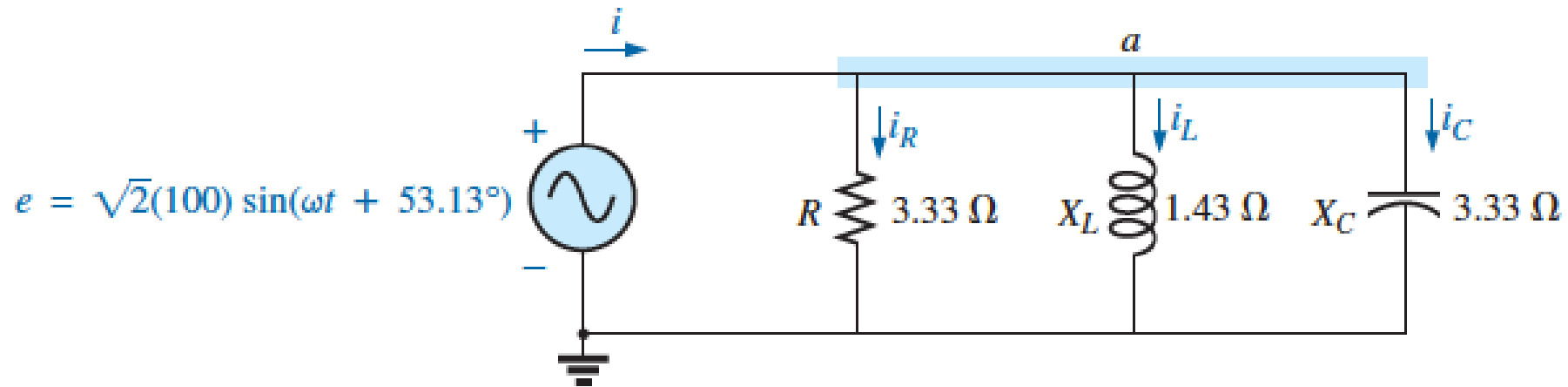

## Phasor Representation

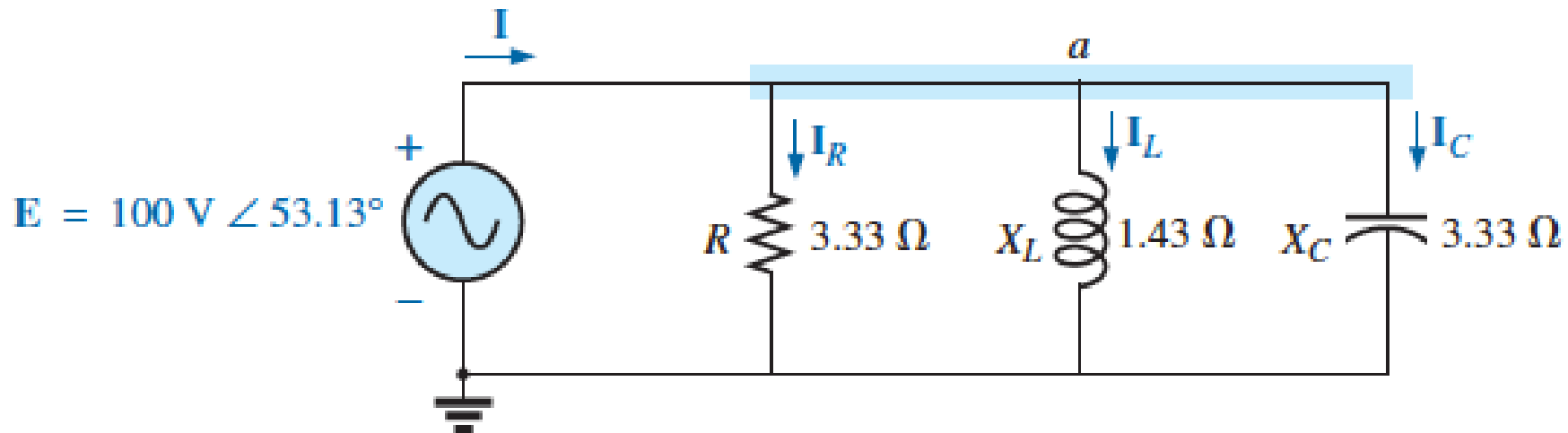


## R – L – C Circuit

$$\begin{aligned}
 \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C = G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle 90^\circ \\
 &= \frac{1}{3.33 \, \Omega} \angle 0^\circ + \frac{1}{1.43 \, \Omega} \angle -90^\circ + \frac{1}{3.33 \, \Omega} \angle 90^\circ \\
 &= 0.3 \, \text{S} \angle 0^\circ + 0.7 \, \text{S} \angle -90^\circ + 0.3 \, \text{S} \angle 90^\circ \\
 &= 0.3 \, \text{S} - j 0.7 \, \text{S} + j 0.3 \, \text{S} \\
 &= 0.3 \, \text{S} - j 0.4 \, \text{S} = 0.5 \, \text{S} \angle -53.13^\circ
 \end{aligned}$$

$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.5 \, \text{S} \angle -53.13^\circ} = 2 \, \Omega \angle 53.13^\circ$$

### Admittance diagram

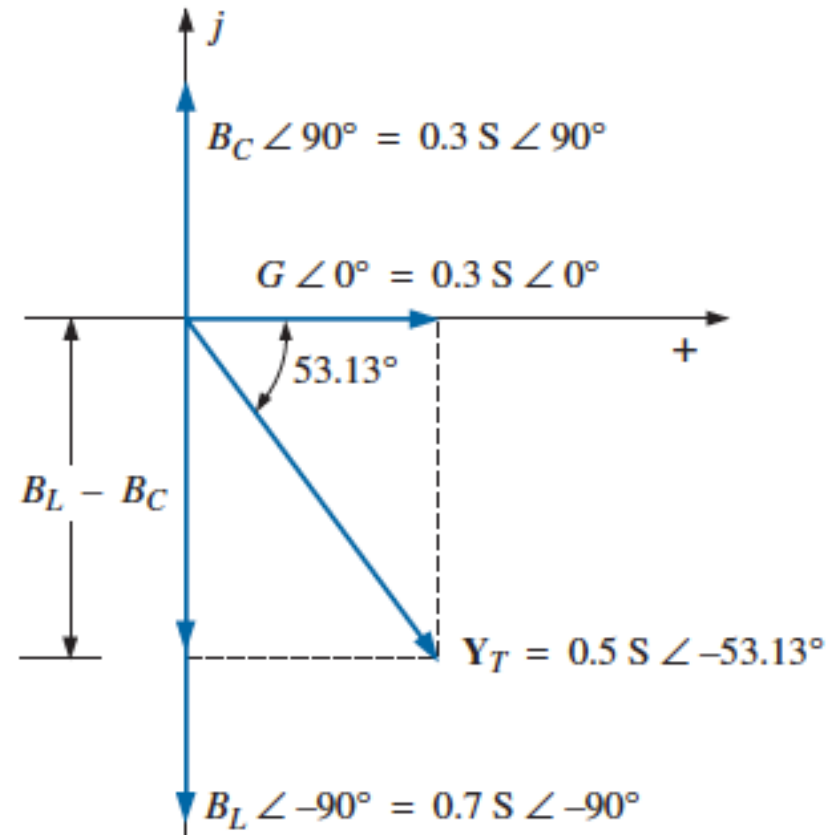



**R – L – C Circuit**

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T = (100 \text{ V } \angle 53.13^\circ)(0.5 \text{ S } \angle -53.13^\circ) = \mathbf{50 \text{ A } \angle 0^\circ}$$

$$\begin{aligned}\mathbf{I}_R &= (E \angle \theta)(G \angle 0^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle 0^\circ) = \mathbf{30 \text{ A } \angle 53.13^\circ}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_L &= (E \angle \theta)(B_L \angle -90^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.7 \text{ S } \angle -90^\circ) = \mathbf{70 \text{ A } \angle -36.87^\circ}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_C &= (E \angle \theta)(B_C \angle 90^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle +90^\circ) = \mathbf{30 \text{ A } \angle 143.13^\circ}\end{aligned}$$

*Kirchhoff's current law:* At node *a*,


$$\mathbf{I} - \mathbf{I}_R - \mathbf{I}_L - \mathbf{I}_C = 0$$

or

$$\mathbf{I} = \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C$$

# R - L - C Circuit

## Phasor diagram

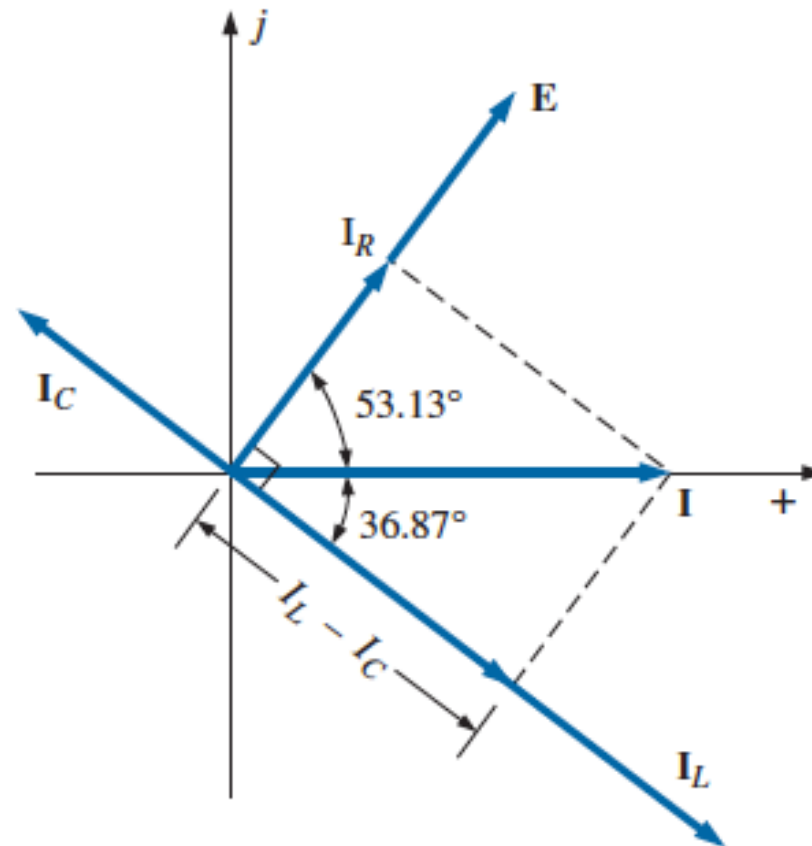


## R – L – C Circuit

$$i = \sqrt{2}(50) \sin \omega t = 70.70 \sin \omega t$$

$$i_R = \sqrt{2}(30) \sin(\omega t + 53.13^\circ) = 42.42 \sin(\omega t + 53.13^\circ)$$

$$i_L = \sqrt{2}(70) \sin(\omega t - 36.87^\circ) = 98.98 \sin(\omega t - 36.87^\circ)$$
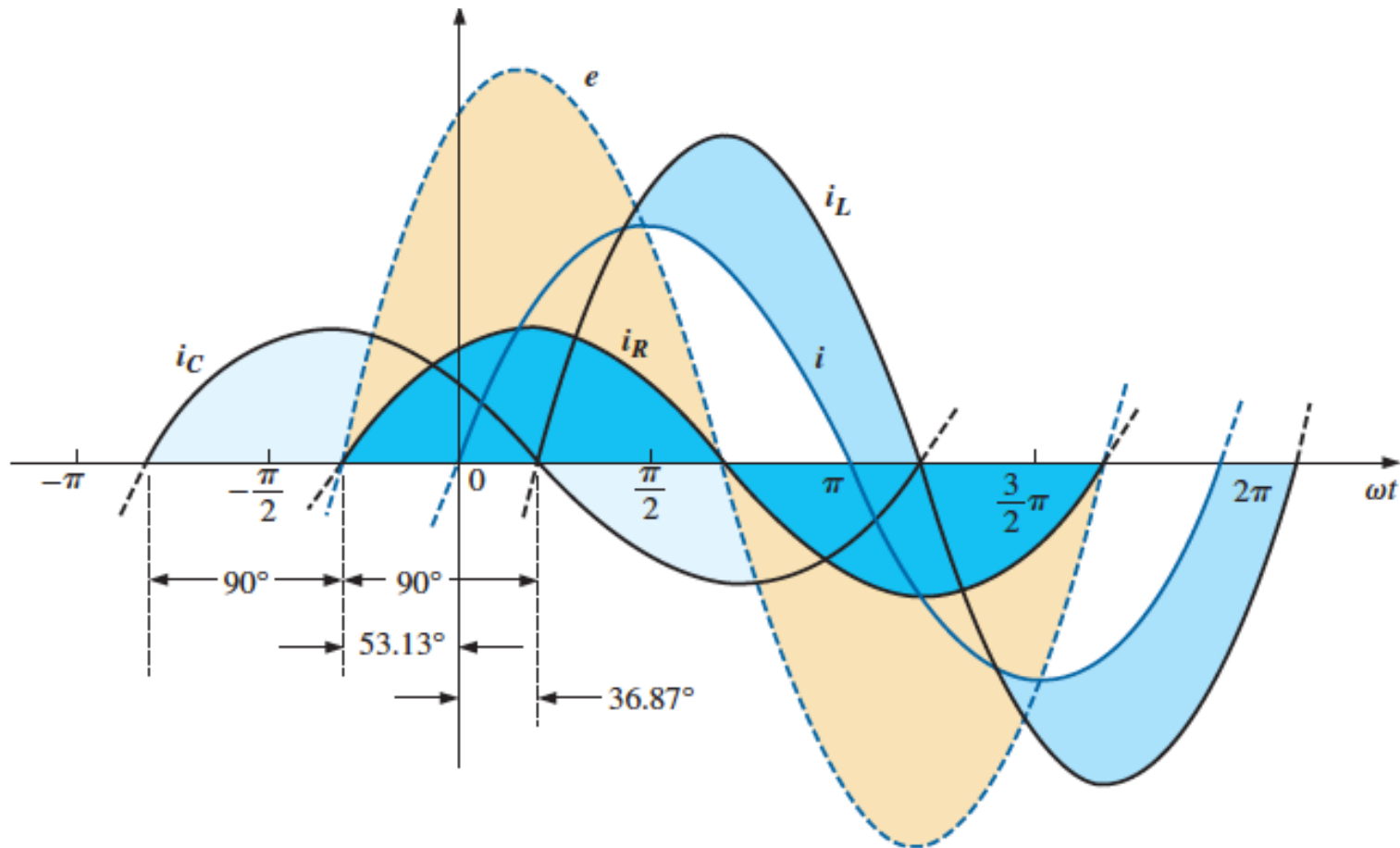
$$i_C = \sqrt{2}(30) \sin(\omega t + 143.13^\circ) = 42.42 \sin(\omega t + 143.13^\circ)$$



## R – L – C Circuit

*Power:* The total power in watts delivered to the circuit is

$$\begin{aligned}
 P_T &= EI \cos \theta = (100 \text{ V})(50 \text{ A}) \cos 53.13^\circ = (5000)(0.6) \\
 &= \mathbf{3000 \text{ W}}
 \end{aligned}$$

or

$$P_T = E^2 G = (100 \text{ V})^2 (0.3 \text{ S}) = \mathbf{3000 \text{ W}}$$

or, finally,

$$\begin{aligned}
 P_T &= P_R + P_L + P_C \\
 &= EI_R \cos \theta_R + EI_L \cos \theta_L + EI_C \cos \theta_C \\
 &= (100 \text{ V})(30 \text{ A}) \cos 0^\circ + (100 \text{ V})(70 \text{ A}) \cos 90^\circ \\
 &\qquad\qquad\qquad + (100 \text{ V})(30 \text{ A}) \cos 90^\circ \\
 &= 3000 \text{ W} + 0 + 0 \\
 &= \mathbf{3000 \text{ W}}
 \end{aligned}$$

*Power factor:* The power factor of the circuit is


$$F_p = \cos \theta_T = \cos 53.13^\circ = \mathbf{0.6 \text{ lagging}}$$

$$F_p = \cos \theta_T = \frac{G}{Y_T} = \frac{0.3 \text{ S}}{0.5 \text{ S}} = \mathbf{0.6 \text{ lagging}}$$

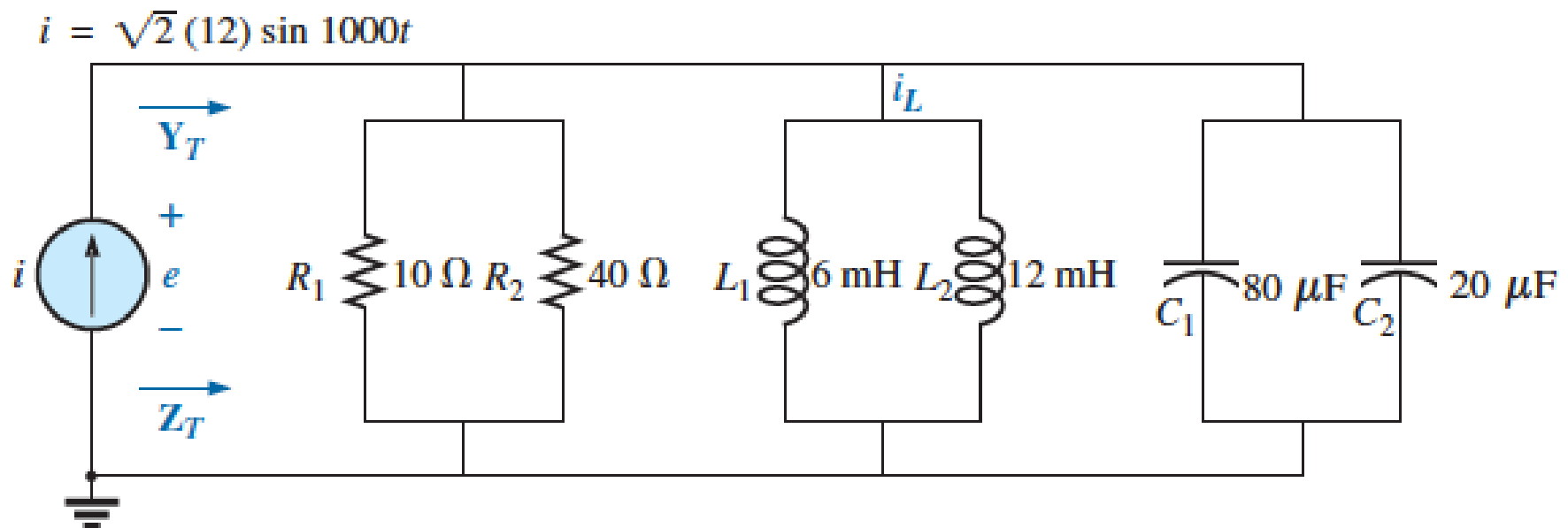**Example**

For the network calculate:

- Determine  $Y_T$  and  $Z_T$ .
- Sketch the admittance diagram.
- Find  $E$  and  $I_L$ .
- Compute the power factor of the network and the power delivered to the network.
- Determine the power delivered to the network, and compare it with the solution of part (d).



## Solutions:

- a. Combining common elements and finding the reactance of the inductor and capacitor, we obtain


$$R_T = 10 \Omega \parallel 40 \Omega = 8 \Omega$$

$$L_T = 6 \text{ mH} \parallel 12 \text{ mH} = 4 \text{ mH}$$

$$C_T = 80 \mu\text{F} + 20 \mu\text{F} = 100 \mu\text{F}$$

$$X_L = \omega L = (1000 \text{ rad/s})(4 \text{ mH}) = 4 \Omega$$
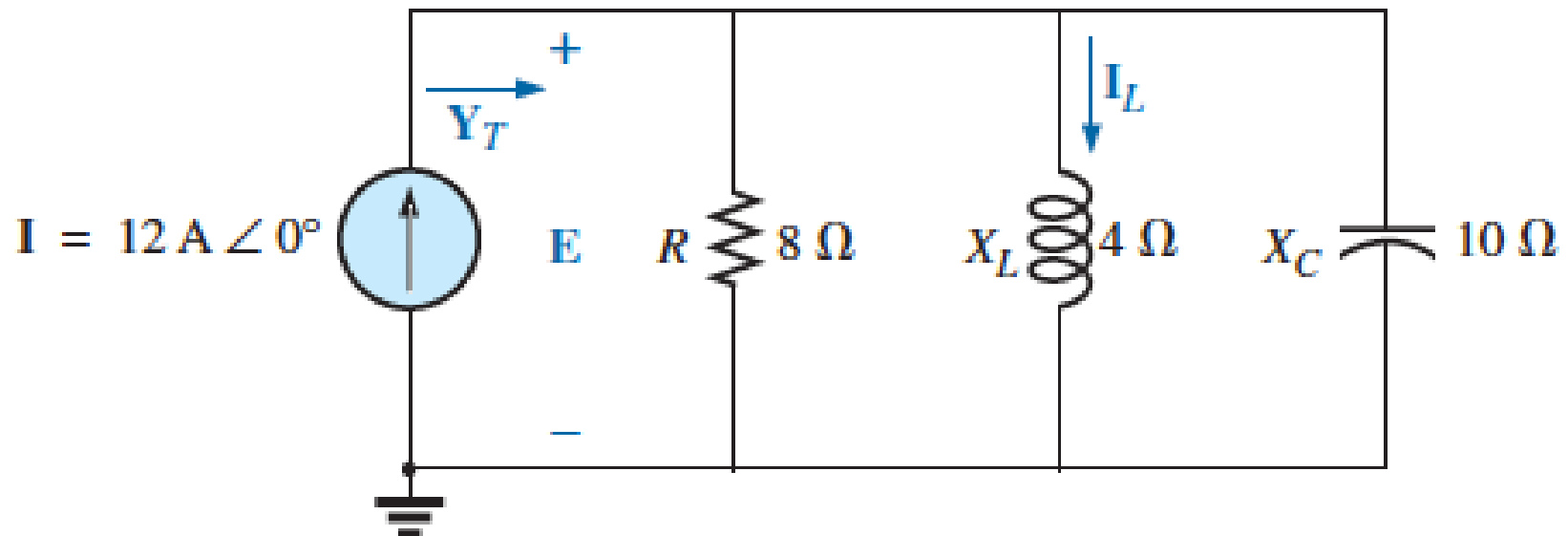
$$X_C = \frac{1}{\omega C} = \frac{1}{(1000 \text{ rad/s})(100 \mu\text{F})} = 10 \Omega$$




The network is redrawn with phasor notation.

The total admittance is

$$\begin{aligned}
 \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C \\
 &= G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle +90^\circ \\
 &= \frac{1}{8 \Omega} \angle 0^\circ + \frac{1}{4 \Omega} \angle -90^\circ + \frac{1}{10 \Omega} \angle +90^\circ \\
 &= 0.125 \text{ S} \angle 0^\circ + 0.25 \text{ S} \angle -90^\circ + 0.1 \text{ S} \angle +90^\circ \\
 &= 0.125 \text{ S} - j 0.25 \text{ S} + j 0.1 \text{ S} \\
 &= 0.125 \text{ S} - j 0.15 \text{ S} = \mathbf{0.195 \text{ S} \angle -50.194^\circ}
 \end{aligned}$$

$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.195 \text{ S}} \angle -50.194^\circ = \mathbf{5.13 \Omega \angle 50.19^\circ}$$

b.

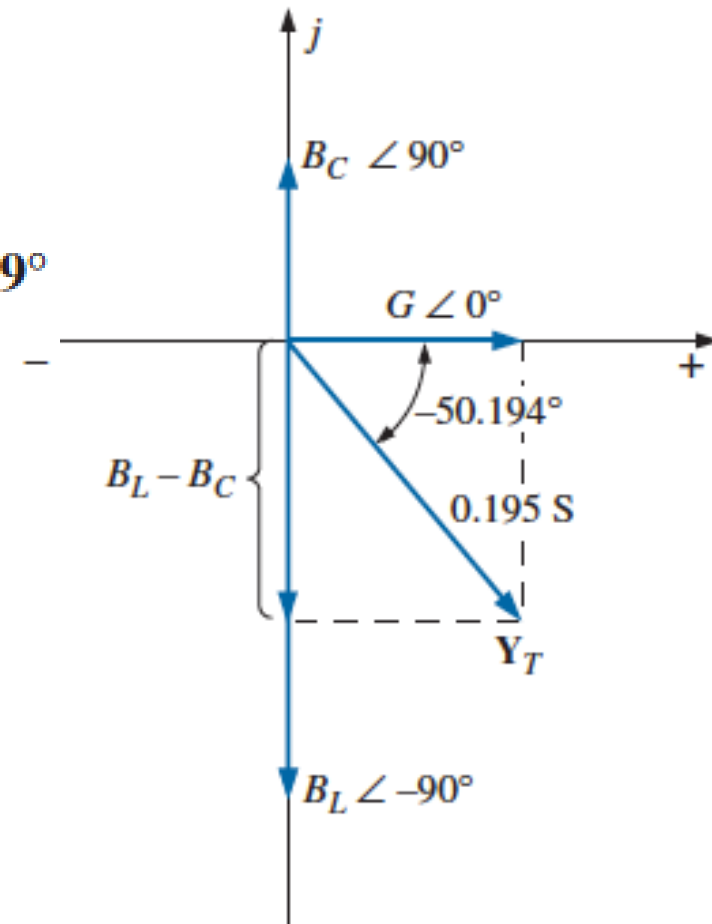

$$\text{c. } \mathbf{E} = \mathbf{IZ}_T = \frac{\mathbf{I}}{\mathbf{Y}_T} = \frac{12 \text{ A } \angle 0^\circ}{0.195 \text{ S } \angle -50.194^\circ} = \mathbf{61.54 \text{ V } \angle 50.19^\circ}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{\mathbf{Z}_L} = \frac{\mathbf{E}}{\mathbf{Z}_L} = \frac{61.538 \text{ V } \angle 50.194^\circ}{4 \Omega \angle 90^\circ} = \mathbf{15.39 \text{ A } \angle -39.81^\circ}$$

$$\text{d. } F_p = \cos \theta = \frac{G}{Y_T} = \frac{0.125 \text{ S}}{0.195 \text{ S}} = \mathbf{0.641 \text{ lagging (E leads I)}}$$

$$\begin{aligned} P &= EI \cos \theta = (61.538 \text{ V})(12 \text{ A}) \cos 50.194^\circ \\ &= \mathbf{472.75 \text{ W}} \end{aligned}$$

$$\text{e. } P = I^2 R = (12 \text{ A})^2 (3.28 \Omega) = \mathbf{472.32 \text{ W}}$$