



# Electrical Circuit-II

## 5<sup>th</sup> Lecture-Tutorial

### Series and Parallel AC Circuits

#### (Part 1)


By:

Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

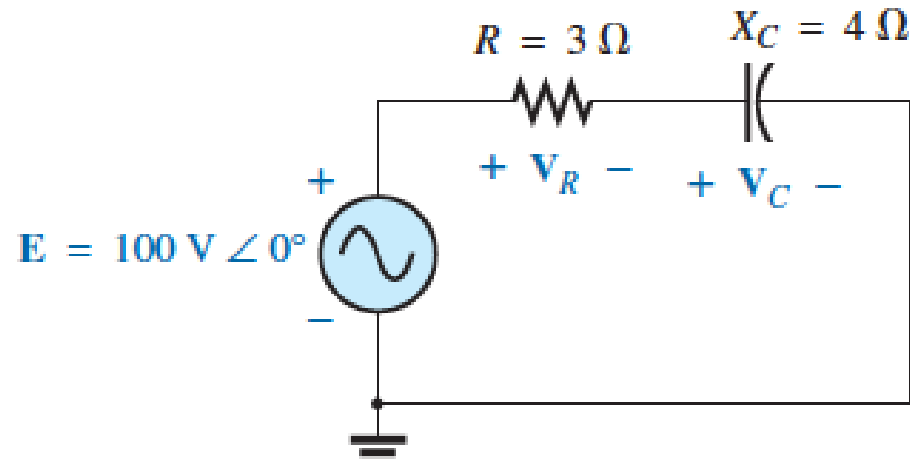**Example**

Using the voltage divider rule, find the voltage across each element of the circuit



**Solution:**

$$V_C = \frac{Z_C E}{Z_C + Z_R} = \frac{(4 \Omega \angle -90^\circ)(100 \text{ V } \angle 0^\circ)}{4 \Omega \angle -90^\circ + 3 \Omega \angle 0^\circ} = \frac{400 \angle -90^\circ}{3 - j4}$$


$$= \frac{400 \angle -90^\circ}{5 \angle -53.13^\circ} = 80 \text{ V } \angle -36.87^\circ$$

$$V_R = \frac{Z_R E}{Z_C + Z_R} = \frac{(3 \Omega \angle 0^\circ)(100 \text{ V } \angle 0^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{300 \angle 0^\circ}{5 \angle -53.13^\circ}$$

$$= 60 \text{ V } \angle +53.13^\circ$$

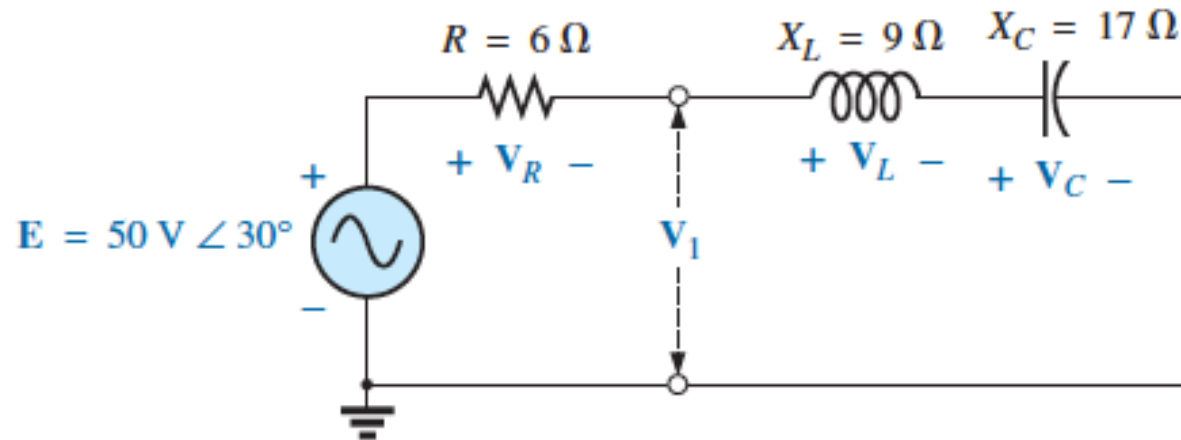**Example**

Using the voltage divider rule, find the unknown voltages  $V_R$  ,  $V_L$  ,  $V_C$  , and  $V_1$  for the circuit



**Solution:**

$$\begin{aligned}
 V_R &= \frac{Z_R E}{Z_R + Z_L + Z_C} = \frac{(6 \Omega \angle 0^\circ)(50 \text{ V} \angle 30^\circ)}{6 \Omega \angle 0^\circ + 9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ} \\
 &= \frac{300 \angle 30^\circ}{6 + j9 - j17} = \frac{300 \angle 30^\circ}{6 - j8} \\
 &= \frac{300 \angle 30^\circ}{10 \angle -53.13^\circ} = 30 \text{ V} \angle 83.13^\circ
 \end{aligned}$$

$$\begin{aligned} \mathbf{V}_L &= \frac{\mathbf{Z}_L \mathbf{E}}{\mathbf{Z}_T} = \frac{(9 \Omega \angle 90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{450 \text{ V} \angle 120^\circ}{10 \angle -53.13^\circ} \\ &= \mathbf{45 \text{ V} \angle 173.13^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_C &= \frac{\mathbf{Z}_C \mathbf{E}}{\mathbf{Z}_T} = \frac{(17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{850 \text{ V} \angle -60^\circ}{10 \angle -53^\circ} \\ &= \mathbf{85 \text{ V} \angle -6.87^\circ} \end{aligned}$$


$$\begin{aligned} \mathbf{V}_1 &= \frac{(\mathbf{Z}_L + \mathbf{Z}_C) \mathbf{E}}{\mathbf{Z}_T} = \frac{(9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} \\ &= \frac{(8 \angle -90^\circ)(50 \angle 30^\circ)}{10 \angle -53.13^\circ} \\ &= \frac{400 \angle -60^\circ}{10 \angle -53.13^\circ} = \mathbf{40 \text{ V} \angle -6.87^\circ} \end{aligned}$$

## Example

For the circuit calculate:

- Calculate  $I$ ,  $V_R$ ,  $V_L$ , and  $V_C$  in phasor form.
- Calculate the total power factor.
- Calculate the average power delivered to the circuit.
- Draw the phasor diagram.
- Obtain the phasor sum of  $V_R$ ,  $V_L$ , and  $V_C$ , and show that it equals the input voltage  $E$ .
- Find  $V_R$  and  $V_C$  using the voltage divider rule.
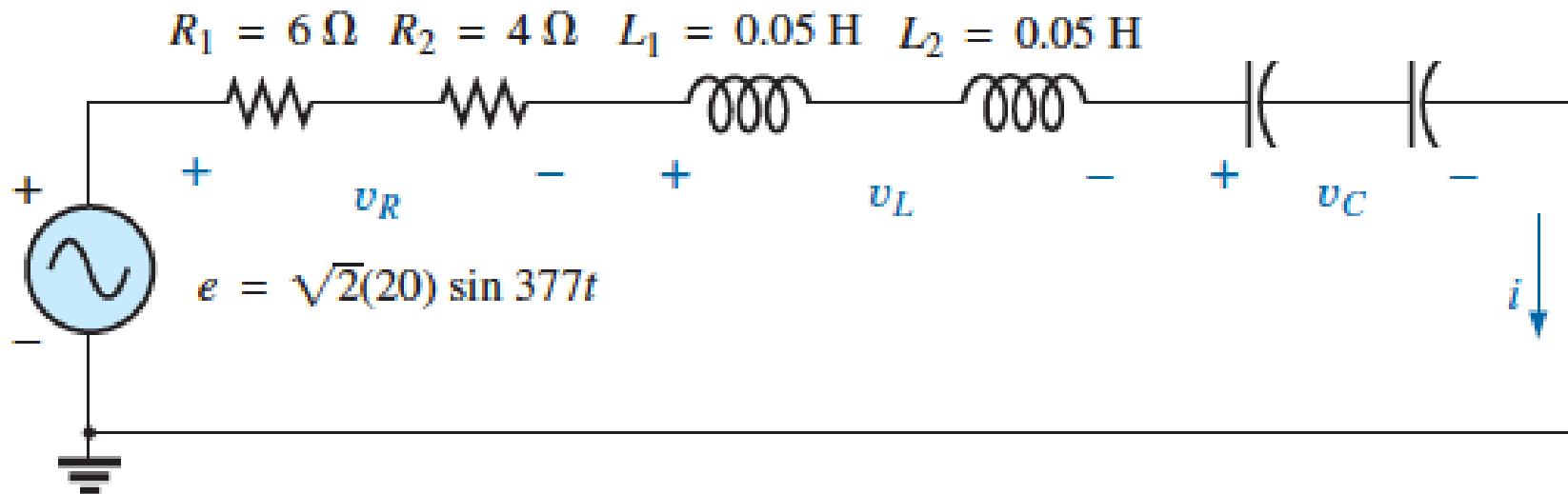
$$C_1 = 200 \mu\text{F} \quad C_2 = 200 \mu\text{F}$$



Solutions:

- a. Combining common elements and finding the reactance of the inductor and capacitor, we obtain


$$R_T = 6 \Omega + 4 \Omega = 10 \Omega$$

$$L_T = 0.05 \text{ H} + 0.05 \text{ H} = 0.1 \text{ H}$$

$$C_T = \frac{200 \mu\text{F}}{2} = 100 \mu\text{F}$$

$$X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.70 \Omega$$
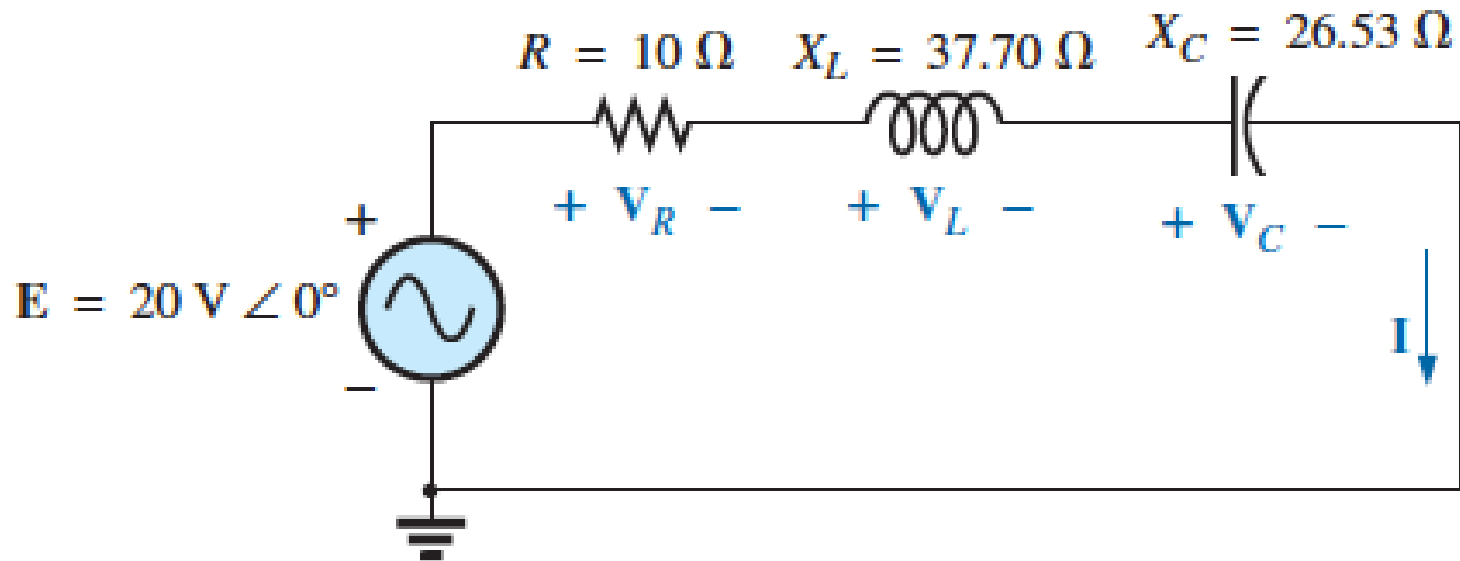
$$X_C = \frac{1}{\omega C} = \frac{1}{(377 \text{ rad/s})(100 \times 10^{-6} \text{ F})} = \frac{10^6 \Omega}{37,700} = 26.53 \Omega$$



Solutions:

$$\begin{aligned}
 \mathbf{Z}_T &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\
 &= 10 \, \Omega + j37.70 \, \Omega - j26.53 \, \Omega \\
 &= 10 \, \Omega + j11.17 \, \Omega = \mathbf{15 \, \Omega \angle 48.16^\circ}
 \end{aligned}$$

The current  $\mathbf{I}$  is

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{20 \, \text{V} \angle 0^\circ}{15 \, \Omega \angle 48.16^\circ} = \mathbf{1.33 \, \text{A} \angle -48.16^\circ}$$

The voltage across the resistor, inductor, and capacitor can be found using Ohm's law:

$$\begin{aligned}
 \mathbf{V}_R = \mathbf{IZ}_R &= (I \angle \theta)(R \angle 0^\circ) = (1.33 \, \text{A} \angle -48.16^\circ)(10 \, \Omega \angle 0^\circ) \\
 &= \mathbf{13.30 \, \text{V} \angle -48.16^\circ}
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{V}_L = \mathbf{IZ}_L &= (I \angle \theta)(X_L \angle 90^\circ) = (1.33 \, \text{A} \angle -48.16^\circ)(37.70 \, \Omega \angle 90^\circ) \\
 &= \mathbf{50.14 \, \text{V} \angle 41.84^\circ}
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{V}_C = \mathbf{IZ}_C &= (I \angle \theta)(X_C \angle -90^\circ) = (1.33 \, \text{A} \angle -48.16^\circ)(26.53 \, \Omega \angle -90^\circ) \\
 &= \mathbf{35.28 \, \text{V} \angle -138.16^\circ}
 \end{aligned}$$

Solutions:

- b. The total power factor, determined by the angle between the applied voltage  $E$  and the resulting current  $I$ , is  $48.16^\circ$ :

$$F_p = \cos \theta = \cos 48.16^\circ = \mathbf{0.667 \text{ lagging}}$$

or

$$F_p = \cos \theta = \frac{R}{Z_T} = \frac{10 \Omega}{15 \Omega} = \mathbf{0.667 \text{ lagging}}$$


- c. The total power in watts delivered to the circuit is

$$P_T = EI \cos \theta = (20 \text{ V})(1.33 \text{ A})(0.667) = \mathbf{17.74 \text{ W}}$$



Solutions:

d. The phasor diagram

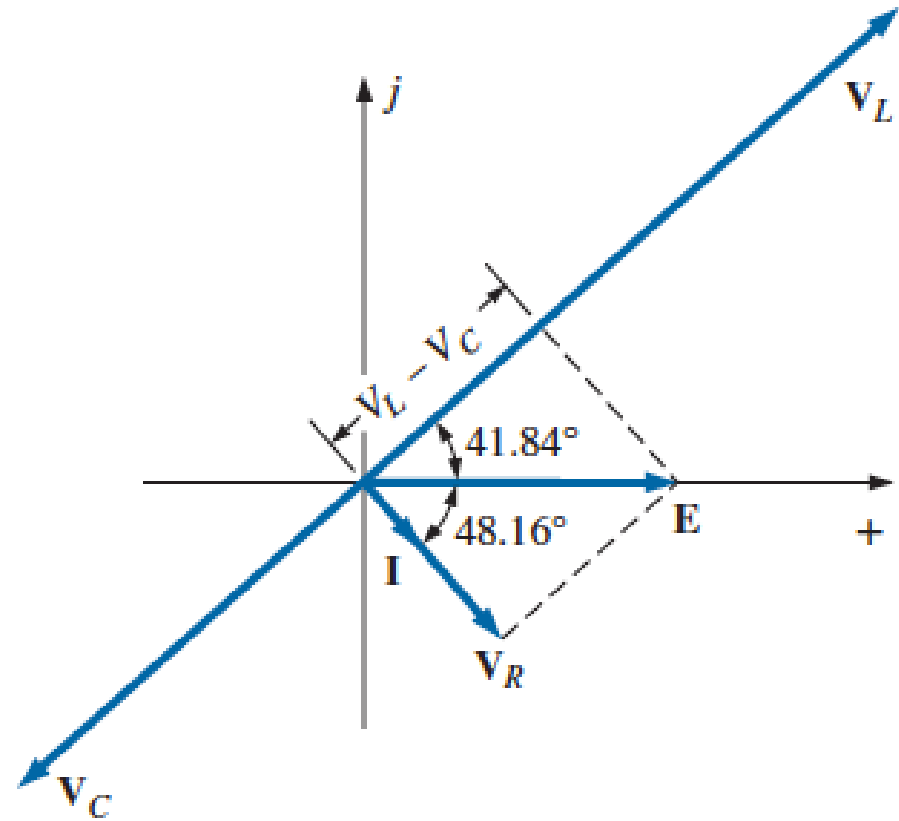

Solutions:

e. The phasor sum of  $V_R$ ,  $V_L$ , and  $V_C$  is

$$\begin{aligned} E &= V_R + V_L + V_C \\ &= 13.30 \text{ V } \angle -48.16^\circ + 50.14 \text{ V } \angle 41.84^\circ + 35.28 \text{ V } \angle -138.16^\circ \\ E &= 13.30 \text{ V } \angle -48.16^\circ + 14.86 \text{ V } \angle 41.84^\circ \end{aligned}$$

Therefore,

$$E = \sqrt{(13.30 \text{ V})^2 + (14.86 \text{ V})^2} = 20 \text{ V}$$

and  $\theta_E = 0^\circ$  (from phasor diagram)

and  $E = 20 \angle 0^\circ$

$$\begin{aligned} \text{f. } V_R &= \frac{Z_R E}{Z_T} = \frac{(10 \Omega \angle 0^\circ)(20 \text{ V } \angle 0^\circ)}{15 \Omega \angle 48.16^\circ} = \frac{200 \text{ V } \angle 0^\circ}{15 \angle 48.16^\circ} \\ &= 13.3 \text{ V } \angle -48.16^\circ \end{aligned}$$

$$\begin{aligned} V_C &= \frac{Z_C E}{Z_T} = \frac{(26.5 \Omega \angle -90^\circ)(20 \text{ V } \angle 0^\circ)}{15 \Omega \angle 48.16^\circ} = \frac{530.6 \text{ V } \angle -90^\circ}{15 \angle 48.16^\circ} \\ &= 35.37 \text{ V } \angle -138.16^\circ \end{aligned}$$