



# Electrical Circuit-II

## 5<sup>th</sup> Lecture

### Series and Parallel AC Circuits

(Part 1)

By:


Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

## Series Configuration

*The overall properties of series **AC** circuits are the same as those for **DC** circuits. For instance, the total impedance of a system is the sum of the individual impedances:*

$$Z_T = Z_1 + Z_2 + Z_3 + \cdots + Z_N$$

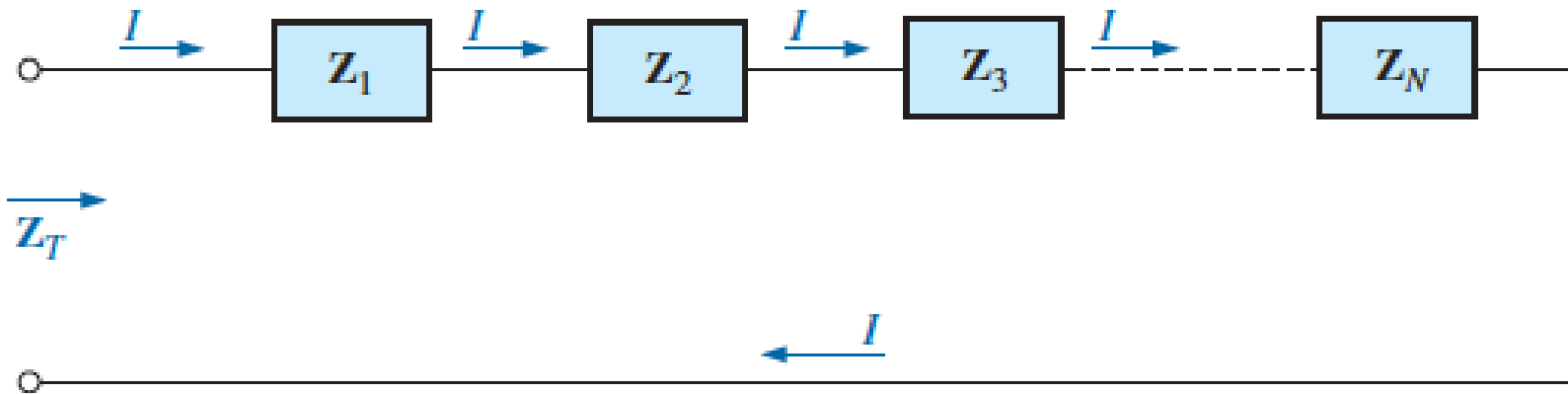


## Series Configuration

*For the representative series AC configuration having two impedances, the current is the same through each element (as it was for the series DC circuits) and is determined by Ohm's law:*

$$Z_T = Z_1 + Z_2$$

$$I = \frac{E}{Z_T}$$

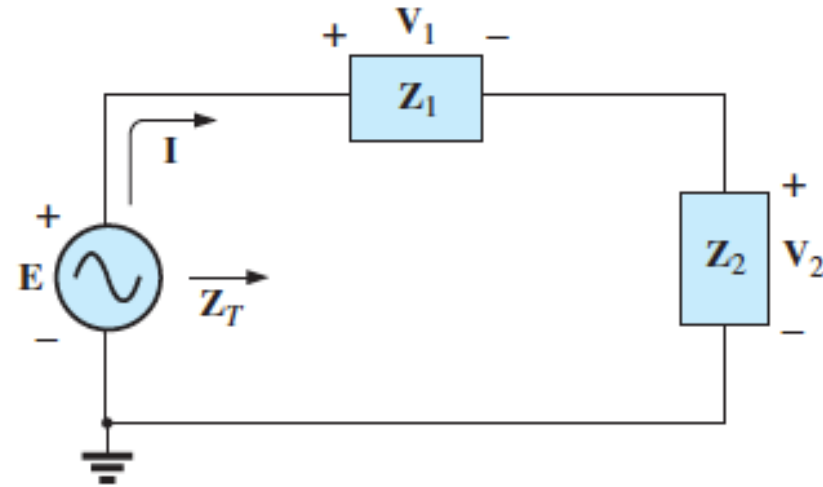

*The voltage across each element can then be found by another application of Ohm's law:*

$$V_1 = IZ_1$$

$$E - V_1 - V_2 = 0$$

$$V_2 = IZ_2$$

$$E = V_1 + V_2$$

*The power to the circuit can be determined by*

$$P = EI \cos \theta_T$$

# R – L Circuit

## Phasor Notation

$$e = 141.4 \sin \omega t \Rightarrow E = 100 \text{ V } \angle 0^\circ$$

$Z_T$

$$Z_T = Z_1 + Z_2 = 3 \Omega \angle 0^\circ + 4 \Omega \angle 90^\circ = 3 \Omega + j4 \Omega$$




and

$$Z_T = 5 \Omega \angle 53.13^\circ$$

$I$

$$I = \frac{E}{Z_T} = \frac{100 \text{ V } \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 20 \text{ A } \angle -53.13^\circ$$

## Impedance diagram

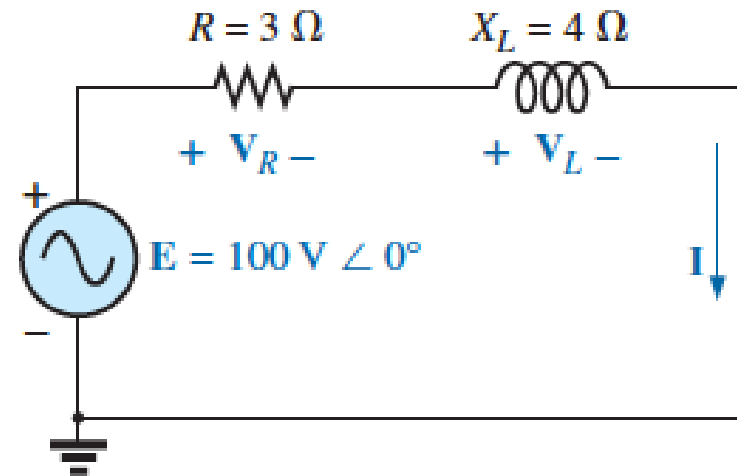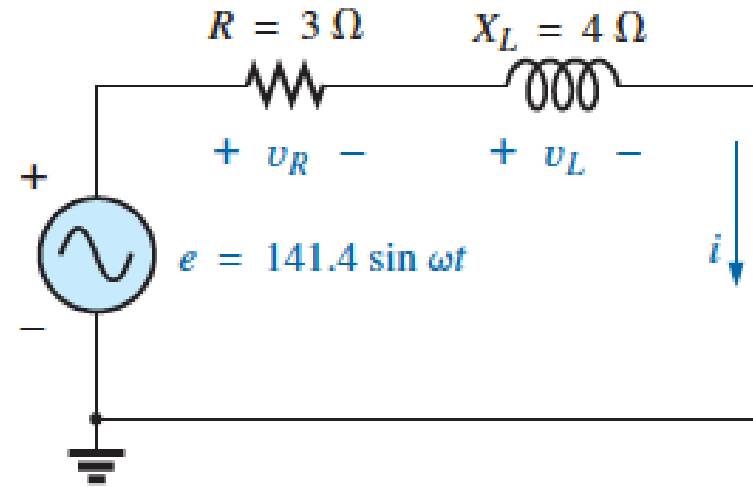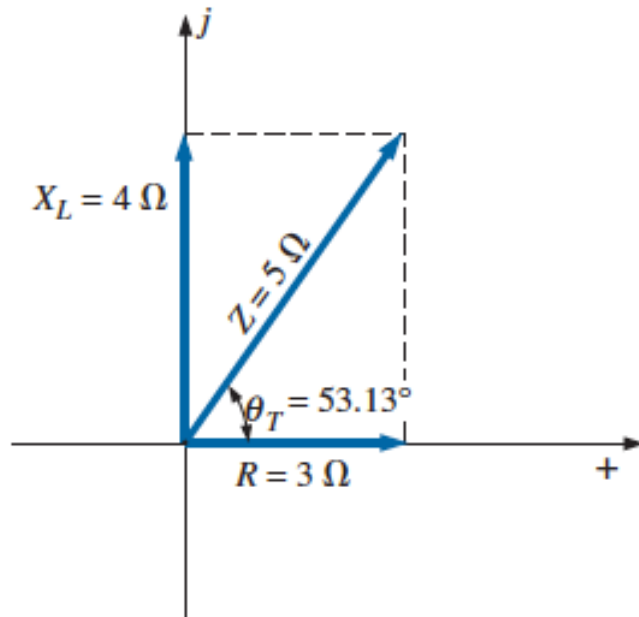

# R – L Circuit

$V_R$  and  $V_L$

*Ohm's law:*

$$\begin{aligned} V_R &= \mathbf{I}Z_R = (20 \text{ A } \angle -53.13^\circ)(3 \Omega \angle 0^\circ) \\ &= \mathbf{60 \text{ V } \angle -53.13^\circ} \end{aligned}$$

$$\begin{aligned} V_L &= \mathbf{I}Z_L = (20 \text{ A } \angle -53.13^\circ)(4 \Omega \angle 90^\circ) \\ &= \mathbf{80 \text{ V } \angle 36.87^\circ} \end{aligned}$$

*Kirchhoff's voltage law:*

$$\Sigma_C \mathbf{V} = \mathbf{E} - \mathbf{V}_R - \mathbf{V}_L = 0$$

or

$$\mathbf{E} = \mathbf{V}_R + \mathbf{V}_L$$


In rectangular form,

$$\mathbf{V}_R = 60 \text{ V } \angle -53.13^\circ = 36 \text{ V} - j48 \text{ V}$$

$$\mathbf{V}_L = 80 \text{ V } \angle +36.87^\circ = 64 \text{ V} + j48 \text{ V}$$

and
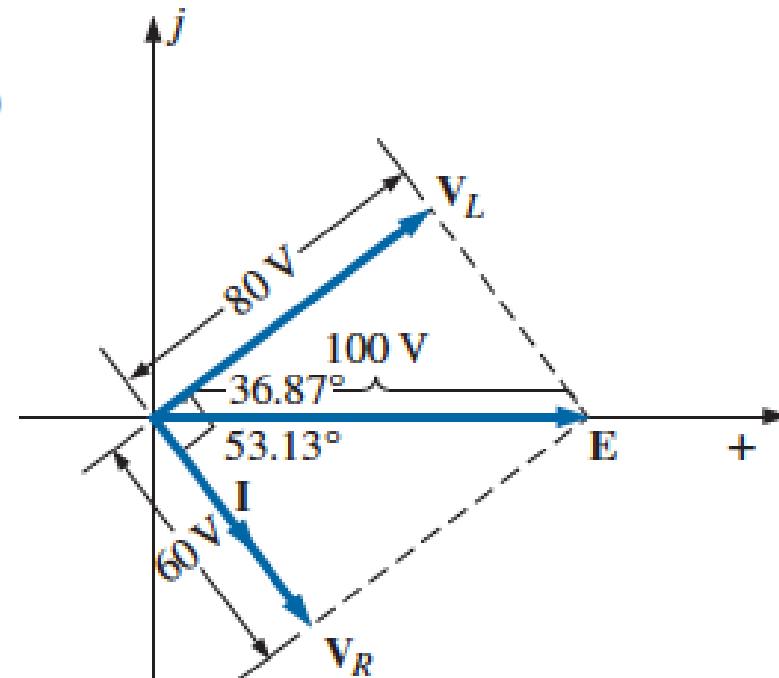
$$\begin{aligned} \mathbf{E} &= \mathbf{V}_R + \mathbf{V}_L = (36 \text{ V} - j48 \text{ V}) + (64 \text{ V} + j48 \text{ V}) = 100 \text{ V} + j0 \\ &= \mathbf{100 \text{ V } \angle 0^\circ} \end{aligned}$$



## R – L Circuit

*Power:* The total power in watts delivered to the circuit is

$$\begin{aligned} P_T &= EI \cos \theta_T \\ &= (100 \text{ V})(20 \text{ A}) \cos 53.13^\circ = (2000 \text{ W})(0.6) \\ &= \mathbf{1200 \text{ W}} \end{aligned}$$

where  $E$  and  $I$  are effective values and  $\theta_T$  is the phase angle between  $E$  and  $I$ , or

$$\begin{aligned} P_T &= I^2 R \\ &= (20 \text{ A})^2 (3 \Omega) = (400)(3) \\ &= \mathbf{1200 \text{ W}} \end{aligned}$$

where  $I$  is the effective value, or, finally,

$$\begin{aligned} P_T &= P_R + P_L = V_R I \cos \theta_R + V_L I \cos \theta_L \\ &= (60 \text{ V})(20 \text{ A}) \cos 0^\circ + (80 \text{ V})(20 \text{ A}) \cos 90^\circ \\ &= 1200 \text{ W} + 0 \\ &= \mathbf{1200 \text{ W}} \end{aligned}$$

where  $\theta_R$  is the phase angle between  $V_R$  and  $I$ , and  $\theta_L$  is the phase angle between  $V_L$  and  $I$ .

*Power factor:* The power factor  $F_p$  of the circuit is  $\cos 53.13^\circ = \mathbf{0.6}$  lagging, where  $53.13^\circ$  is the phase angle between  $E$  and  $I$ .

If we write the basic power equation  $P = EI \cos \theta$  as follows:

$$\cos \theta = \frac{P}{EI}$$

$$\begin{aligned} \cos \theta &= \frac{P}{EI} = \frac{I^2 R}{EI} \\ &= \frac{IR}{E} = \frac{R}{E/I} = \frac{R}{Z_T} \end{aligned}$$

$$F_p = \cos \theta_T = \frac{R}{Z_T}$$

# R – C Circuit

## Phasor Notation

$$i = 7.07 \sin(\omega t + 53.13^\circ)$$

$$\Rightarrow \mathbf{I} = 5 \text{ A } \angle 53.13^\circ$$

**Z<sub>T</sub>**

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2$$

$$= 6 \Omega \angle 0^\circ + 8 \Omega \angle -90^\circ$$

$$= 6 \Omega - j8 \Omega$$

and




$$\mathbf{Z}_T = 10 \Omega \angle -53.13^\circ$$

**E**

$$\mathbf{E} = \mathbf{I} \mathbf{Z}_T$$

$$= (5 \text{ A } \angle 53.13^\circ)(10 \Omega \angle -53.13^\circ)$$

$$= 50 \text{ V } \angle 0^\circ$$

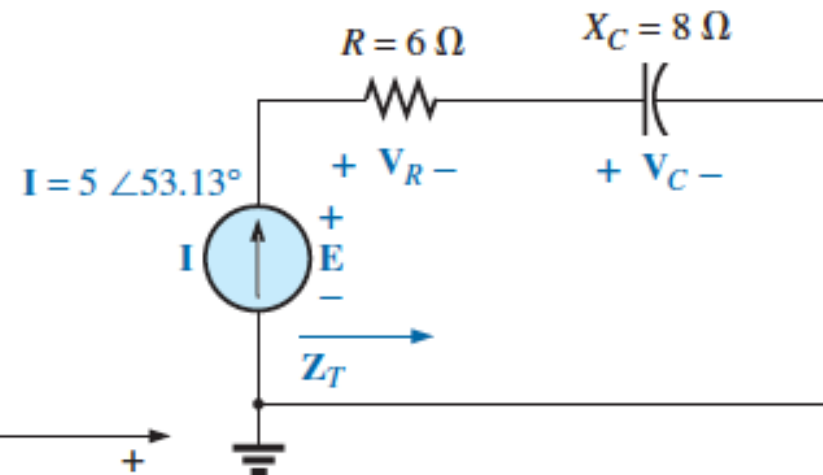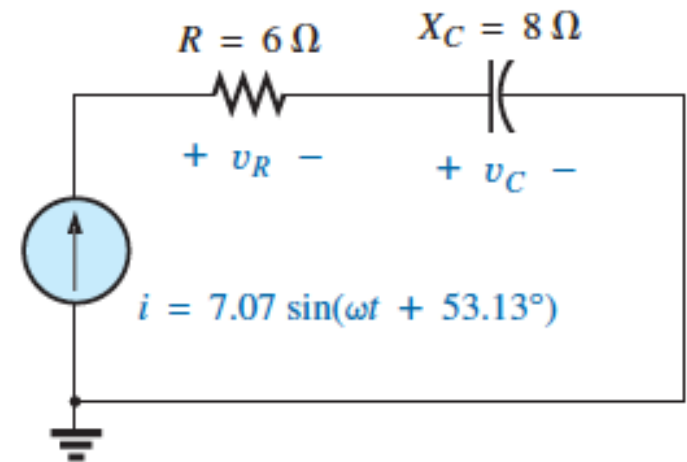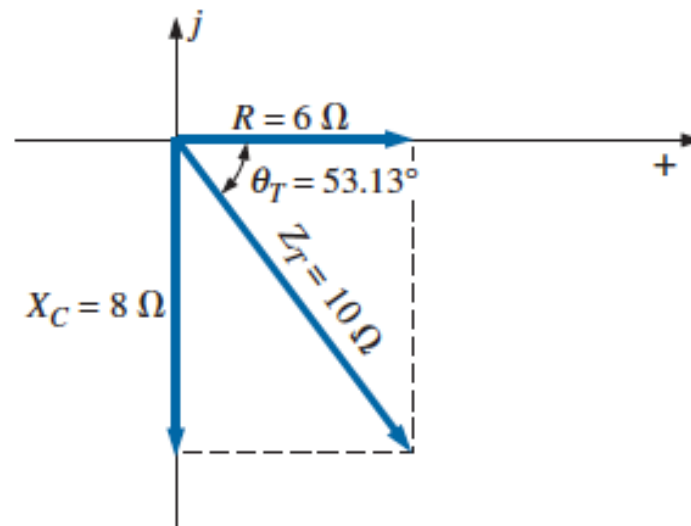**Impedance diagram**

# R – C Circuit

## $V_R$ and $V_C$

$$\begin{aligned} V_R &= IZ_R = (I \angle \theta)(R \angle 0^\circ) = (5 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) \\ &= 30 \text{ V } \angle 53.13^\circ \end{aligned}$$

$$\begin{aligned} V_C &= IZ_C = (I \angle \theta)(X_C \angle -90^\circ) = (5 \text{ A } \angle 53.13^\circ)(8 \Omega \angle -90^\circ) \\ &= 40 \text{ V } \angle -36.87^\circ \end{aligned}$$

*Kirchhoff's voltage law:*


$$\Sigma_C V = E - V_R - V_C = 0$$

or

$$E = V_R + V_C$$

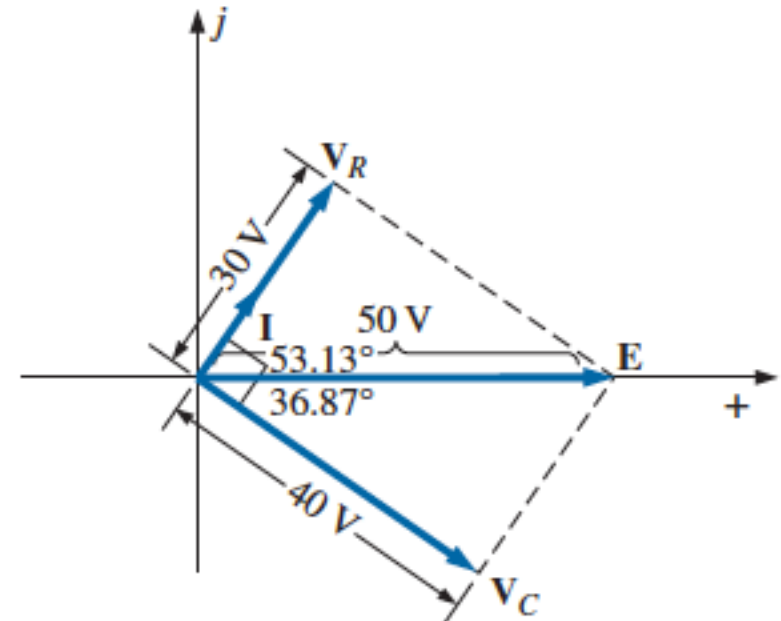**which can be verified by vector algebra as demonstrated for the *R-L* circuit.**

**Phasor diagram:** Note on the phasor diagram that the current  $I$  is in phase with the voltage across the resistor and leads the voltage across the capacitor by  $90^\circ$ .






# R – C Circuit

*Time domain:* In the time domain,

$$e = \sqrt{2}(50) \sin \omega t = 70.70 \sin \omega t$$

$$v_R = \sqrt{2}(30) \sin(\omega t + 53.13^\circ) = 42.42 \sin(\omega t + 53.13^\circ)$$
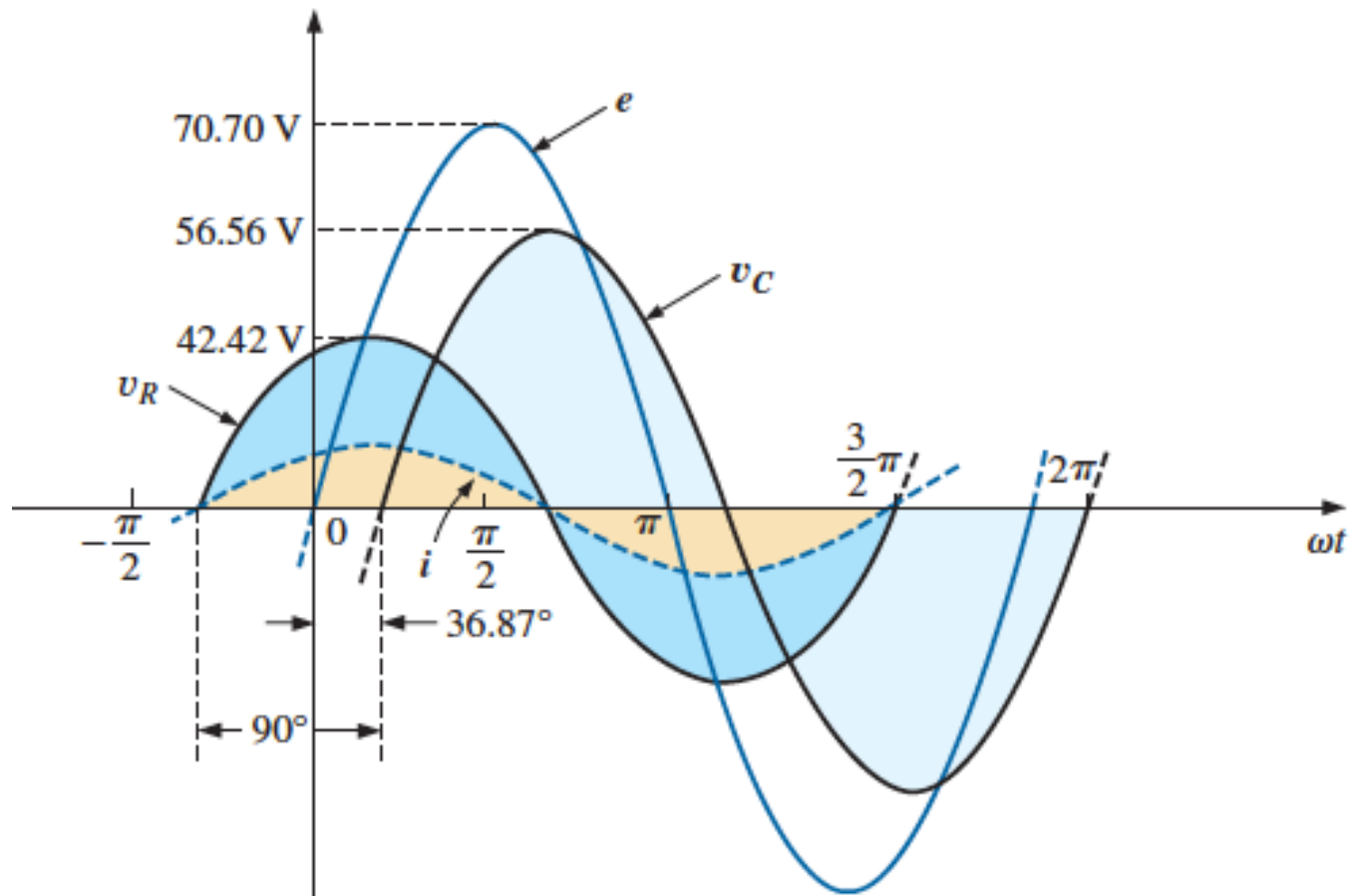
$$v_C = \sqrt{2}(40) \sin(\omega t - 36.87^\circ) = 56.56 \sin(\omega t - 36.87^\circ)$$



## R – C Circuit

*Power:* The total power in watts delivered to the circuit is

$$\begin{aligned} P_T &= EI \cos \theta_T = (50 \text{ V})(5 \text{ A}) \cos 53.13^\circ \\ &= (250)(0.6) = \mathbf{150 \text{ W}} \end{aligned}$$

or

$$\begin{aligned} P_T &= I^2 R = (5 \text{ A})^2 (6 \Omega) = (25)(6) \\ &= \mathbf{150 \text{ W}} \end{aligned}$$

or, finally,

$$\begin{aligned} P_T &= P_R + P_C = V_R I \cos \theta_R + V_C I \cos \theta_C \\ &= (30 \text{ V})(5 \text{ A}) \cos 0^\circ + (40 \text{ V})(5 \text{ A}) \cos 90^\circ \\ &= 150 \text{ W} + 0 \\ &= \mathbf{150 \text{ W}} \end{aligned}$$

*Power factor:* The power factor of the circuit is

$$F_p = \cos \theta = \cos 53.13^\circ = \mathbf{0.6 \text{ leading}}$$

Using Eq. (15.9), we obtain

$$\begin{aligned} F_p &= \cos \theta = \frac{R}{Z_T} = \frac{6 \Omega}{10 \Omega} \\ &= \mathbf{0.6 \text{ leading}} \end{aligned}$$

# R - L - C Circuit

Phasor Notation  $E = 50 \text{ V} \angle 0^\circ$




$Z_T$

$$\begin{aligned} Z_T &= Z_1 + Z_2 + Z_3 \\ &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 3 \Omega + j7 \Omega - j3 \Omega \\ &= 3 \Omega + j4 \Omega \end{aligned}$$

$$Z_T = 5 \Omega \angle 53.13^\circ$$

$$\begin{aligned} I &= \frac{E}{Z_T} = \frac{50 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} \\ &= 10 \text{ A} \angle -53.13^\circ \end{aligned}$$

Impedance diagram

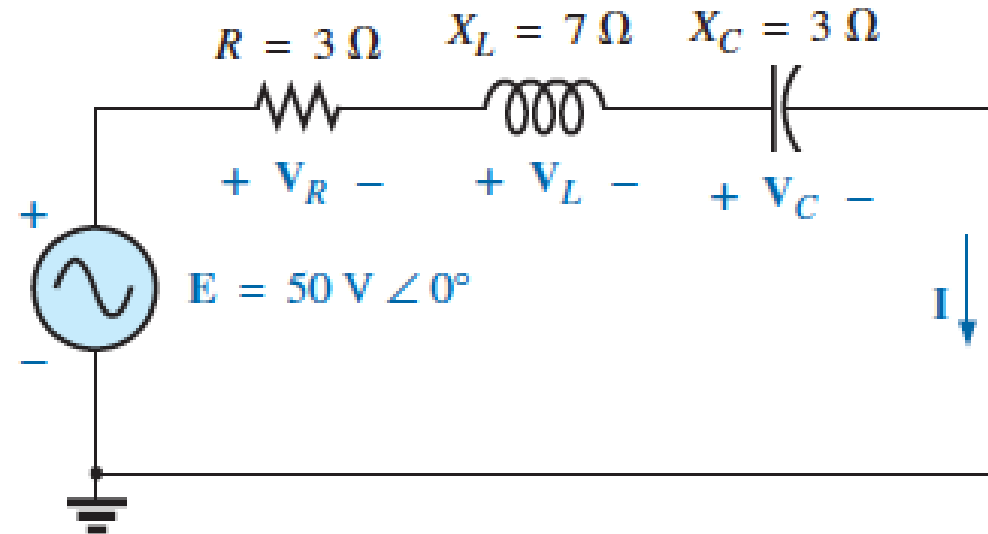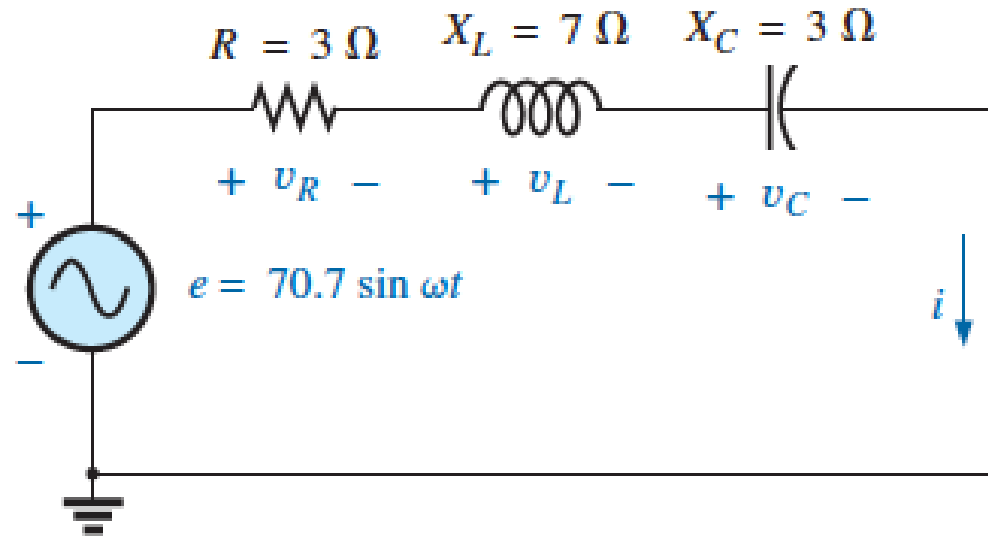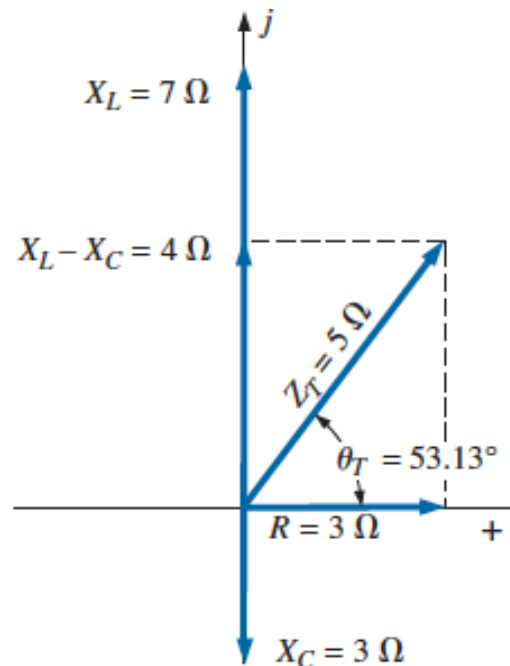

# R – L – C Circuit

$V_R$ ,  $V_L$ , and  $V_C$

$$\begin{aligned} V_R &= IZ_R = (I \angle \theta)(R \angle 0^\circ) = (10 \text{ A} \angle -53.13^\circ)(3 \Omega \angle 0^\circ) \\ &= 30 \text{ V} \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} V_L &= IZ_L = (I \angle \theta)(X_L \angle 90^\circ) = (10 \text{ A} \angle -53.13^\circ)(7 \Omega \angle 90^\circ) \\ &= 70 \text{ V} \angle 36.87^\circ \end{aligned}$$

$$\begin{aligned} V_C &= IZ_C = (I \angle \theta)(X_C \angle -90^\circ) = (10 \text{ A} \angle -53.13^\circ)(3 \Omega \angle -90^\circ) \\ &= 30 \text{ V} \angle -143.13^\circ \end{aligned}$$


*Kirchhoff's voltage law:*

$$\Sigma_C V = E - V_R - V_L - V_C = 0$$

or

$$E = V_R + V_L + V_C$$

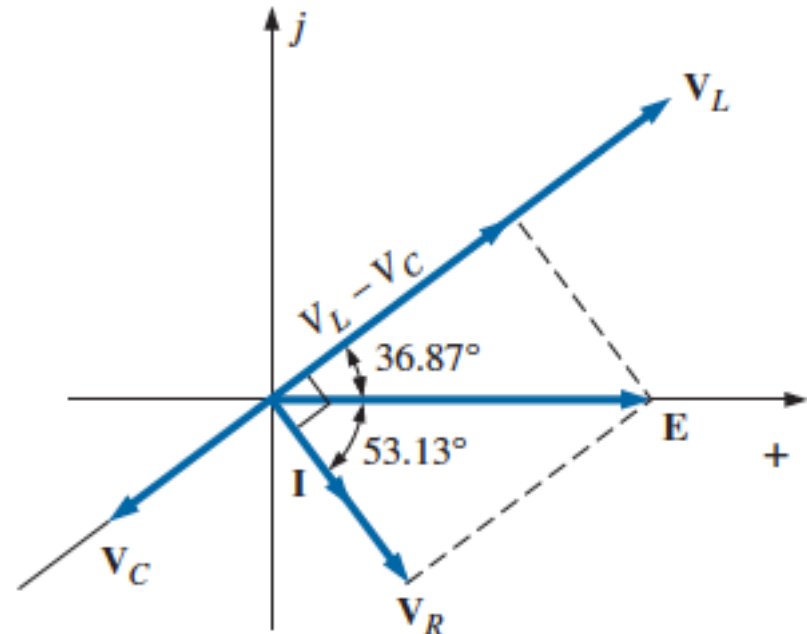**Phasor diagram:** The phasor diagram indicates that the current **I** is **in phase** with the voltage across the **resistor**, **lags** the voltage across the **inductor** by  $90^\circ$ , and **leads** the voltage across the **capacitor** by  $90^\circ$ .



# R – L – C Circuit


*Time domain:*

$$i = \sqrt{2}(10) \sin(\omega t - 53.13^\circ) = 14.14 \sin(\omega t - 53.13^\circ)$$

$$v_R = \sqrt{2}(30) \sin(\omega t - 53.13^\circ) = 42.42 \sin(\omega t - 53.13^\circ)$$

$$v_L = \sqrt{2}(70) \sin(\omega t + 36.87^\circ) = 98.98 \sin(\omega t + 36.87^\circ)$$
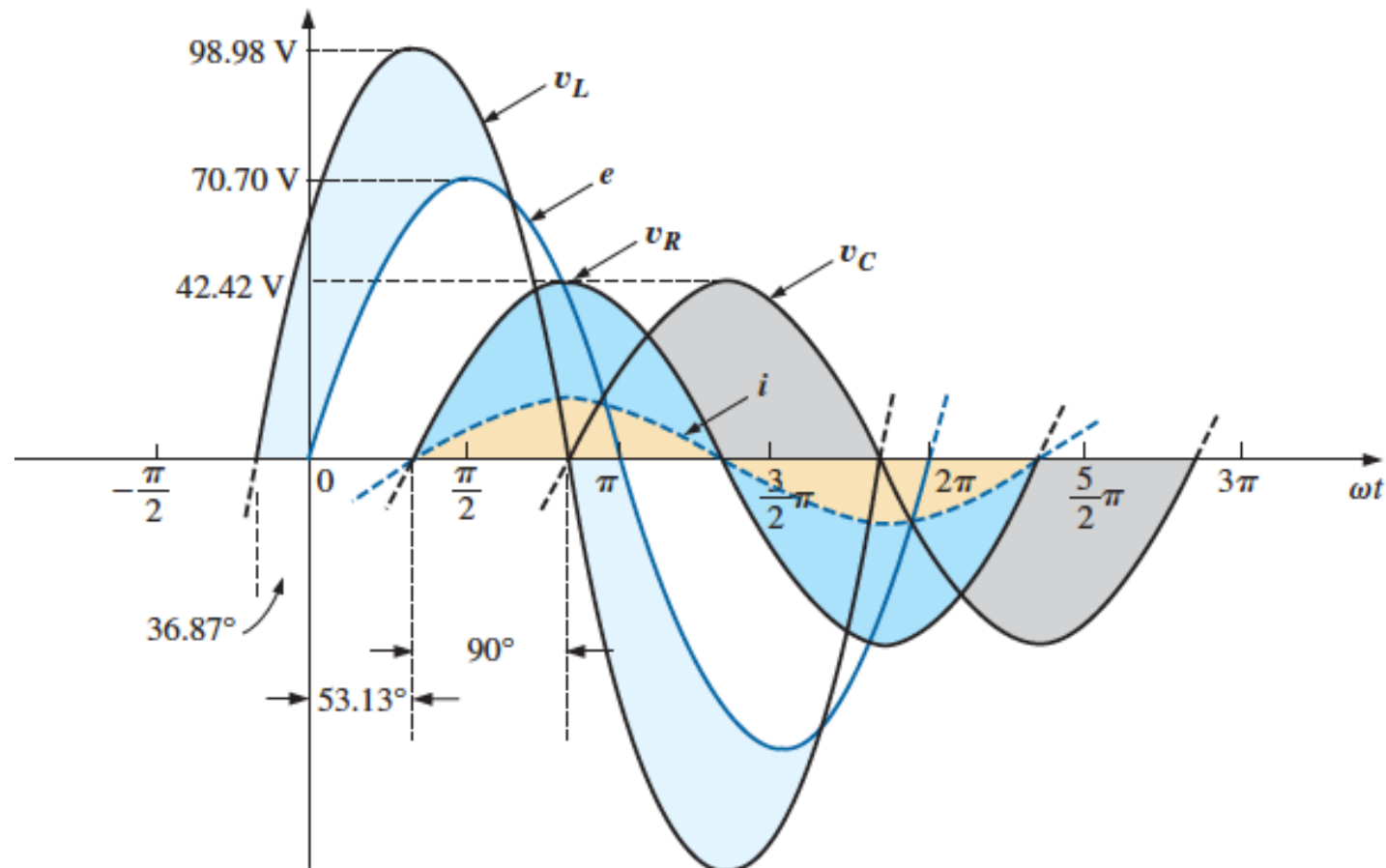
$$v_C = \sqrt{2}(30) \sin(\omega t - 143.13^\circ) = 42.42 \sin(\omega t - 143.13^\circ)$$



## R – L – C Circuit

*Power:* The total power in watts delivered to the circuit is

$$P_T = EI \cos \theta_T = (50 \text{ V})(10 \text{ A}) \cos 53.13^\circ = (500)(0.6) = \mathbf{300 \text{ W}}$$

or 
$$P_T = I^2R = (10 \text{ A})^2(3 \ \Omega) = (100)(3) = \mathbf{300 \text{ W}}$$

or

$$\begin{aligned} P_T &= P_R + P_L + P_C \\ &= V_R I \cos \theta_R + V_L I \cos \theta_L + V_C I \cos \theta_C \\ &= (30 \text{ V})(10 \text{ A}) \cos 0^\circ + (70 \text{ V})(10 \text{ A}) \cos 90^\circ + (30 \text{ V})(10 \text{ A}) \cos 90^\circ \\ &= (30 \text{ V})(10 \text{ A}) + 0 + 0 = \mathbf{300 \text{ W}} \end{aligned}$$

*Power factor:* The power factor of the circuit is

$$F_p = \cos \theta_T = \cos 53.13^\circ = \mathbf{0.6 \text{ lagging}}$$

or

$$F_p = \cos \theta = \frac{R}{Z_T} = \frac{3 \ \Omega}{5 \ \Omega} = \mathbf{0.6 \text{ lagging}}$$