



# Electrical Circuit-I

## 10<sup>th</sup> Lecture-Tutorial

### MESH ANALYSIS

By:

Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

**Example (6)**

**Write the mesh equations for the network in Fig. 6, and find the current  $I_2$  through the  $7\ \Omega$  resistor**

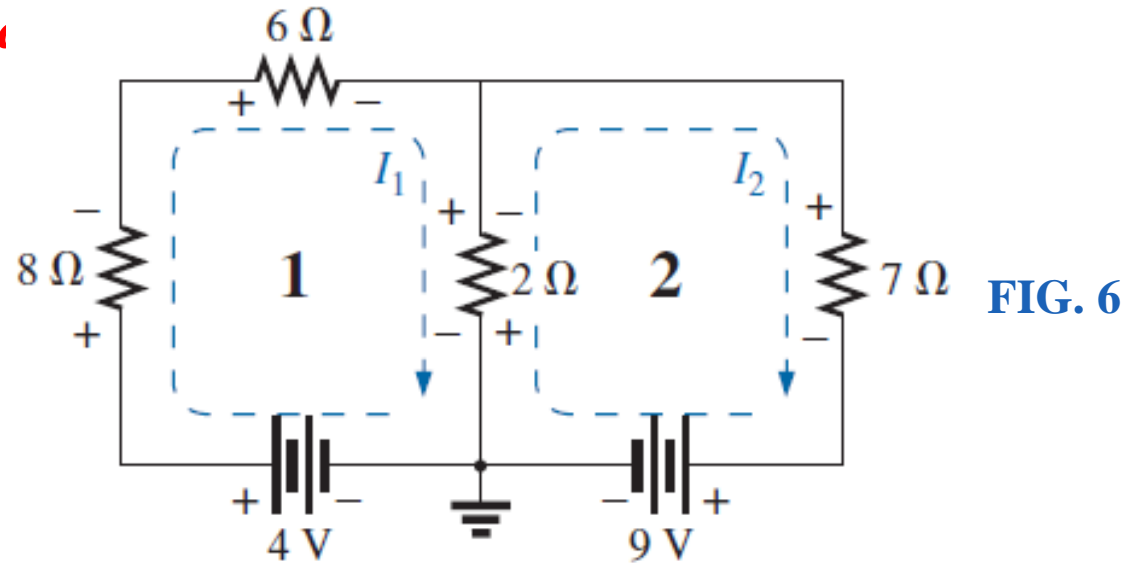


FIG. 6

**Solution:**

**Step 1:**

**Step 1:** As indicated in Fig. 6, each assigned loop current has a clockwise direction.

**Steps 2 to 4:**

$$I_1: (8\ \Omega + 6\ \Omega + 2\ \Omega)I_1 - (2\ \Omega)I_2 = 4\ \text{V}$$

$$I_2: (7\ \Omega + 2\ \Omega)I_2 - (2\ \Omega)I_1 = -9\ \text{V}$$

and


$$\begin{aligned} 16I_1 - 2I_2 &= 4 \\ -2I_1 + 9I_2 &= -9 \end{aligned}$$

which, for determinants, are

$$\begin{aligned} \text{and } I_2 = I_{7\Omega} &= \frac{\begin{vmatrix} 16 & 4 \\ -2 & -9 \end{vmatrix}}{\begin{vmatrix} 16 & -2 \\ -2 & 9 \end{vmatrix}} = \frac{-144 + 8}{144 - 4} = \frac{-136}{140} \\ &= -0.97\ \text{A} \end{aligned}$$

**Example (7)**

**Write the mesh equations for the network in Fig. 7**

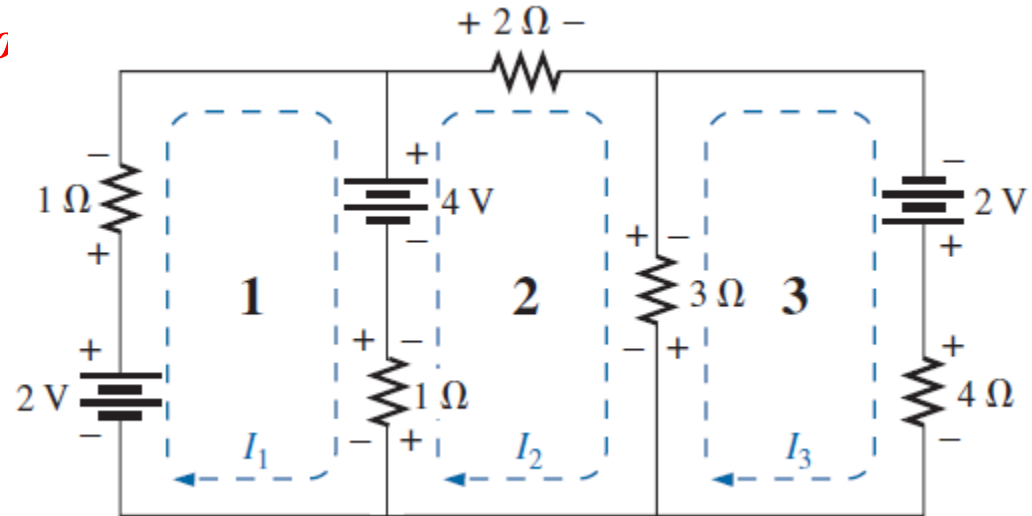

**FIG. 7**

**Solution:**

**Each window is assigned a loop current in the clockwise direction:**

$I_1$  does not pass through an element mutual with  $I_3$ .

$$\begin{aligned}
 I_1: & \quad (1\ \Omega + 1\ \Omega)I_1 - (1\ \Omega)I_2 + 0 = 2\ \text{V} - 4\ \text{V} \\
 I_2: & \quad (1\ \Omega + 2\ \Omega + 3\ \Omega)I_2 - (1\ \Omega)I_1 - (3\ \Omega)I_3 = 4\ \text{V} \\
 I_3: & \quad (3\ \Omega + 4\ \Omega)I_3 - (3\ \Omega)I_2 + 0 = 2\ \text{V}
 \end{aligned}$$

$I_3$  does not pass through an element mutual with  $I_1$ .

Summing terms yields :

$$\begin{aligned}
 2I_1 - I_2 + 0 &= -2 \\
 6I_2 - I_1 - 3I_3 &= 4 \\
 7I_3 - 3I_2 + 0 &= 2
 \end{aligned}$$

**Example (8)**

**Write the mesh equations for the network in Fig. 8 and find the current  $I_3$  through the  $10\ \Omega$  resistor**

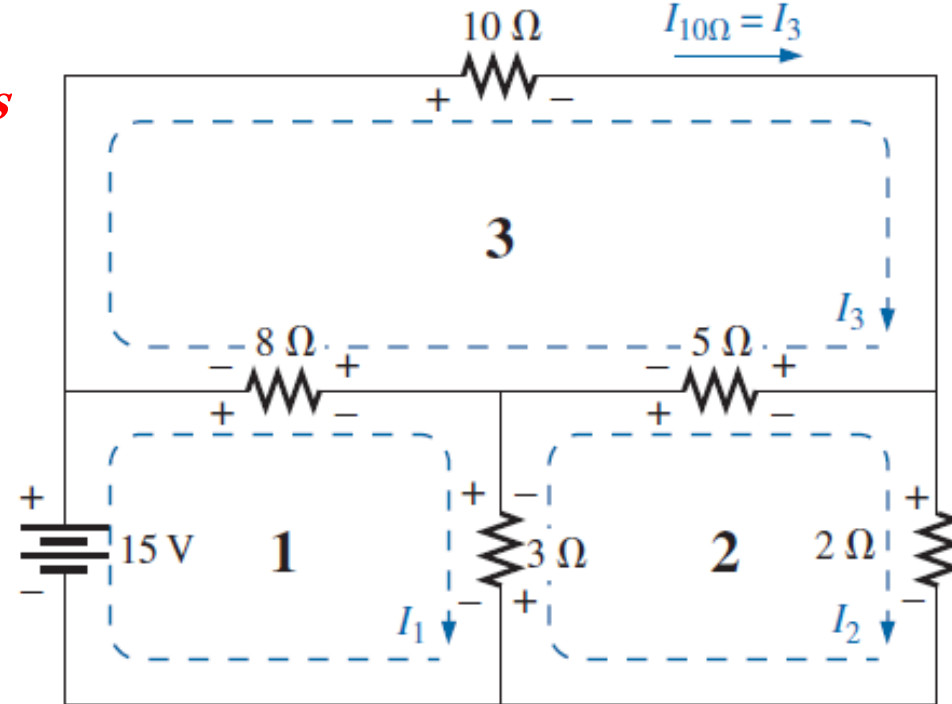


FIG. 8

**Solution:**

$$\begin{aligned}
 I_1: \quad & (8\ \Omega + 3\ \Omega)I_1 - (8\ \Omega)I_3 - (3\ \Omega)I_2 = 15\ \text{V} \\
 I_2: \quad & (3\ \Omega + 5\ \Omega + 2\ \Omega)I_2 - (3\ \Omega)I_1 - (5\ \Omega)I_3 = 0 \\
 I_3: \quad & (8\ \Omega + 10\ \Omega + 5\ \Omega)I_3 - (8\ \Omega)I_1 - (5\ \Omega)I_2 = 0
 \end{aligned}$$

$$\begin{aligned}
 \text{or} \quad & \underline{11I_1 - 8I_3 - 3I_2 = 15\ \text{V}} \\
 & 10I_2 - 3I_1 - 5I_3 = 0 \\
 & \underline{23I_3 - 8I_1 - 5I_2 = 0} \\
 & 11I_1 - 3I_2 - 8I_3 = 15\ \text{V} \\
 & -3I_1 + 10I_2 - 5I_3 = 0 \\
 & \underline{-8I_1 - 5I_2 + 23I_3 = 0}
 \end{aligned}$$

$$\text{and } I_3 = I_{10\Omega} = \frac{\begin{vmatrix} 11 & -3 & 15 \\ -3 & 10 & 0 \\ -8 & -5 & 0 \end{vmatrix}}{\begin{vmatrix} 11 & -3 & -8 \\ -3 & 10 & -5 \\ -8 & -5 & 23 \end{vmatrix}} = 1.22\ \text{A}$$