



# Electrical Circuit-I

## 11<sup>th</sup> Lecture

### NODAL ANALYSIS

By:

Dr. Ali Abu-Rghaif

Ref: Robert L. Boylestad, "*Introductory Circuit Analysis*", Pearson Prentice Hall, Eleventh Edition, 2007

- *the number of nodes for which the voltage must be determined using nodal analysis is 1 less than the total number of nodes.*

*(N - 1) nodal voltages that need to be determined*

- *the number of equations required to solve for all the nodal voltages of a network is 1 less than the total number of independent nodes.*


*(N - 1) independent equations be written to find the nodal voltages*

**Nodal Analysis Procedure**

- 1) Determine the number of nodes within the network.*
- 2) Pick a reference node, and label each remaining node with a subscripted value of voltage:  $V_1$ ,  $V_2$ , and so on.*
- 3) Apply Kirchhoff's current law at each node except the reference. Assume that all unknown currents leave the node for each application of Kirchhoff's current law. In other words, for each node, don't be influenced by the direction that an unknown current for another node may have had. Each node is to be treated as a separate entity, independent of the application of Kirchhoff's current law to the other nodes.*
- 4) Solve the resulting equations for the nodal voltages.*

**Example (1)**

**Apply nodal analysis to the network in Fig. 1-1**

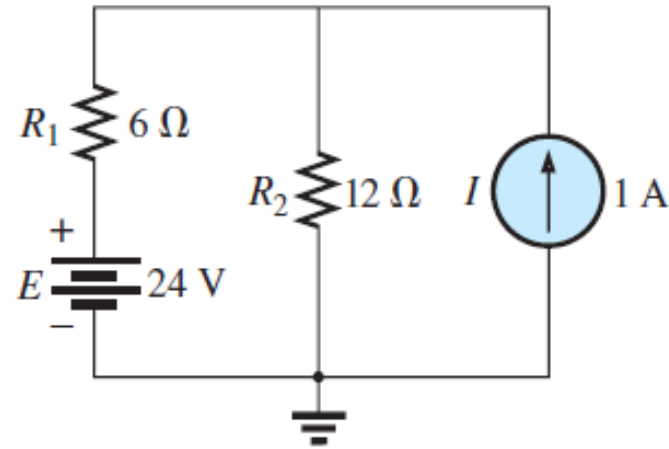


**FIG. 1-1**

**Solution:**

**Step 1 and 2:**

**The network has two nodes, as shown in Fig. 1-2. The lower node is defined as the reference node at ground potential (zero volts), and the other node as  $V_1$ , the voltage from node 1 to ground.**

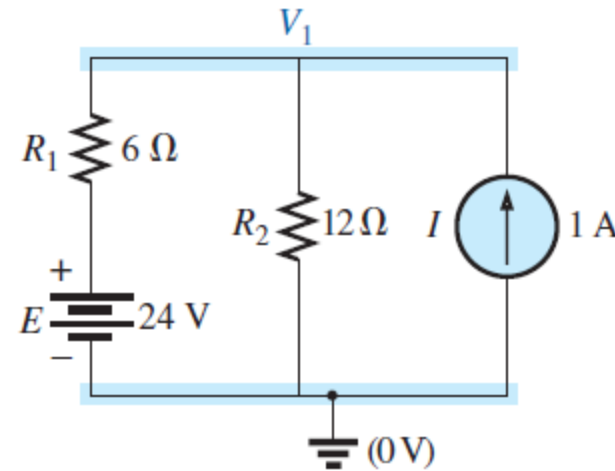

**FIG. 1-2**

**Step 3:**

**$I_1$  and  $I_2$  are defined as leaving the node in Fig. 1-3, and Kirchhoff's current law is applied as follows:**

$$I = I_1 + I_2$$


**The current  $I_2$  is related to the nodal voltage  $V_1$  by Ohm's law:**

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1}{R_2}$$

**The current  $I_1$  is also determined by Ohm's law as follows:**

$$I_1 = \frac{V_{R_1}}{R_1}$$

$$V_{R_1} = V_1 - E$$

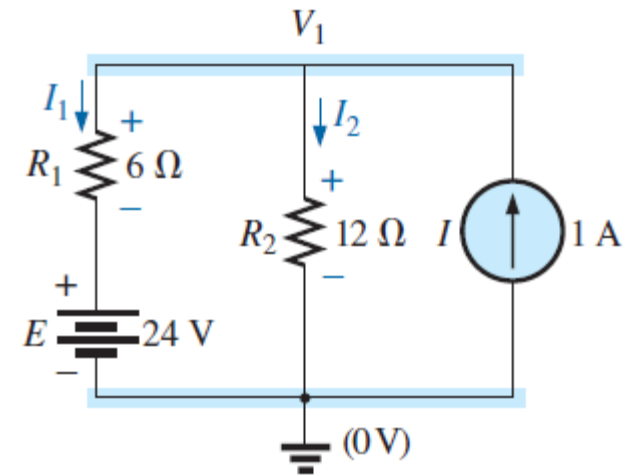

**FIG. 1-3**

**Substituting into the Kirchhoff's current law equation.**  $I = \frac{V_1 - E}{R_1} + \frac{V_1}{R_2}$

$$I = \frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} = V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{E}{R_1}$$

$$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E}{R_1} + 1$$

$$V_1 \left( \frac{1}{6 \Omega} + \frac{1}{12 \Omega} \right) = \frac{24 \text{ V}}{6 \Omega} + 1 \text{ A} = 4 \text{ A} + 1 \text{ A}$$

$$V_1 \left( \frac{1}{4 \Omega} \right) = 5 \text{ A}$$

$$V_1 = 20 \text{ V}$$

**The currents  $I_1$  and  $I_2$  can then be determined using the preceding equations:**


$$I_1 = \frac{V_1 - E}{R_1} = \frac{20 \text{ V} - 24 \text{ V}}{6 \Omega} = \frac{-4 \text{ V}}{6 \Omega}$$

$$= -0.67 \text{ A}$$

$$I_2 = \frac{V_1}{R_2} = \frac{20 \text{ V}}{12 \Omega} = 1.67 \text{ A}$$

**Example (2)**

**Apply nodal analysis to the network in Fig. 2-1**

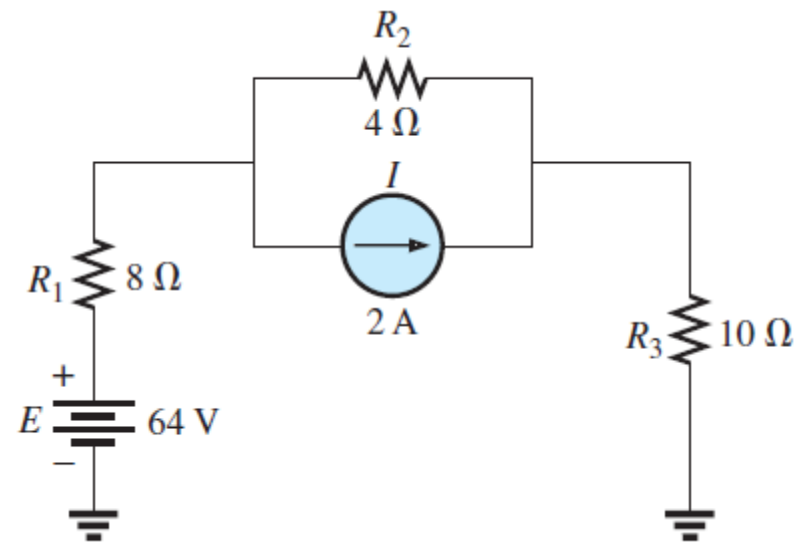


**FIG. 2-1**

**Solution:**

**Step 1 and 2:**

**The network has three nodes, as defined in Fig. 2-2, with the bottom node again defined as the reference node (at ground potential, or zero volts), and the other nodes as V1 and V2.**

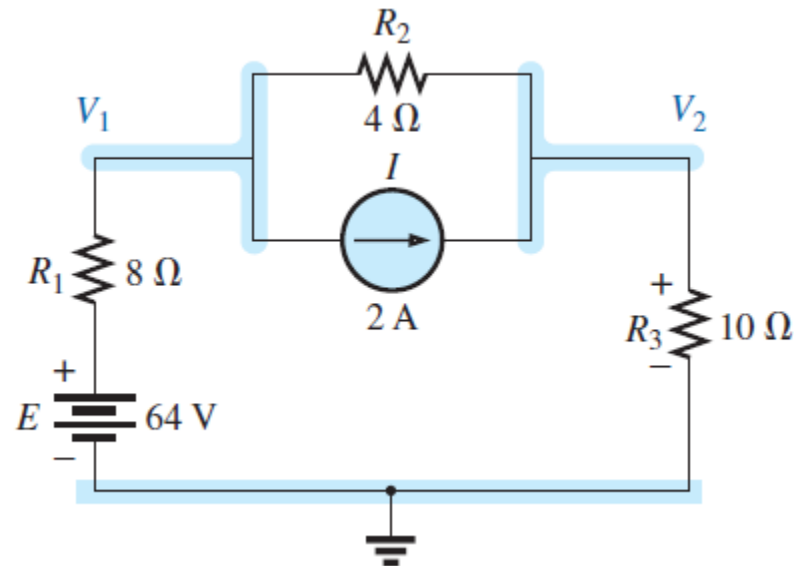

**FIG. 2-2**

**Step 3:**

For node **V1**, the currents are defined as shown in **Fig. 2-3** and Kirchoff's current law is applied::

$$0 = I_1 + I_2 + I$$

with

$$I_1 = \frac{V_1 - E}{R_1}$$

and

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{V_1 - V_2}{R_2}$$

so that

$$\frac{V_1 - E}{R_1} + \frac{V_1 - V_2}{R_2} + I = 0$$

or


$$\frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + I = 0$$

and

$$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \left( \frac{1}{R_2} \right) = -I + \frac{E}{R_1}$$

Substituting values:

$$V_1 \left( \frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left( \frac{1}{4 \Omega} \right) = -2 \text{ A} + \frac{64 \text{ V}}{8 \Omega} = 6 \text{ A}$$

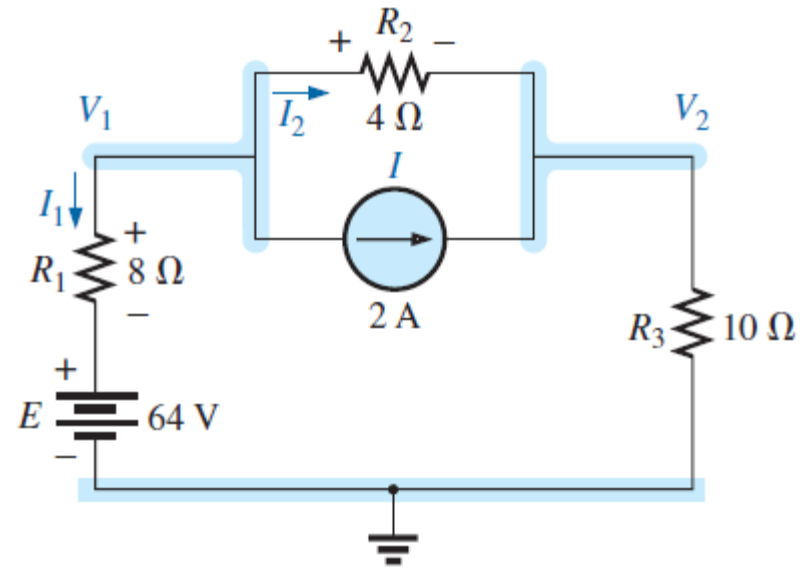

**FIG. 2-3**

For node **V2** the currents are defined as shown in **Fig. 2-4**, and Kirchoff's current law is applied:

$$I = I_2 + I_3$$

with

$$I = \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3}$$

or


$$I = \frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_3}$$

and

$$V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - V_1 \left( \frac{1}{R_2} \right) = I$$

Substituting values:

$$V_2 \left( \frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) - V_1 \left( \frac{1}{4 \Omega} \right) = 2 \text{ A}$$

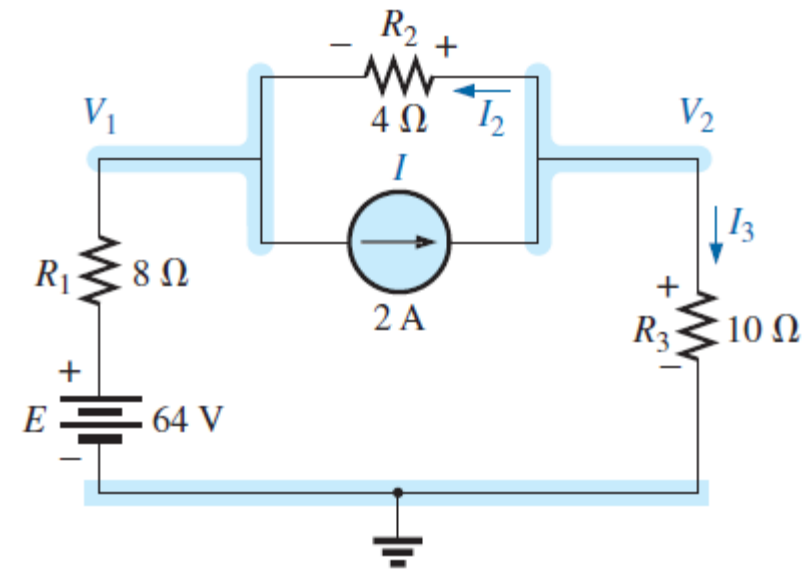

**FIG. 2-4**

**Step 4:**

*The result is two equations and two unknowns:*

$$V_1 \left( \frac{1}{8 \Omega} + \frac{1}{4 \Omega} \right) - V_2 \left( \frac{1}{4 \Omega} \right) = 6 \text{ A}$$

$$-V_1 \left( \frac{1}{4 \Omega} \right) + V_2 \left( \frac{1}{4 \Omega} + \frac{1}{10 \Omega} \right) = 2 \text{ A}$$


---



*which become:*

$$\begin{aligned}0.375V_1 - 0.25V_2 &= 6 \\ -0.25V_1 + 0.35V_2 &= 2\end{aligned}$$

*Using determinants:*

$$\begin{aligned}V_1 &= 37.82 \text{ V} \\ V_2 &= 32.73 \text{ V}\end{aligned}$$

*Since **E** is greater than **V1**, the current **I1** flows from ground to **V1** and is equal to:*

$$I_{R_1} = \frac{E - V_1}{R_1} = \frac{64 \text{ V} - 37.82 \text{ V}}{8 \Omega} = 3.27 \text{ A}$$

*The positive value for **V2** results in a current **IR3** from node **V2** to ground equal to:*


$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{V_2}{R_3} = \frac{32.73 \text{ V}}{10 \Omega} = 3.27 \text{ A}$$

*Since **V1** is greater than **V2**, the current **IR2** flows from **V1** to **V2** and is equal to:*

$$I_{R_2} = \frac{V_1 - V_2}{R_2} = \frac{37.82 \text{ V} - 32.73 \text{ V}}{4 \Omega} = 1.27 \text{ A}$$

**Example (3)**

**Determine the nodal voltages for the network in Fig. 3-1**

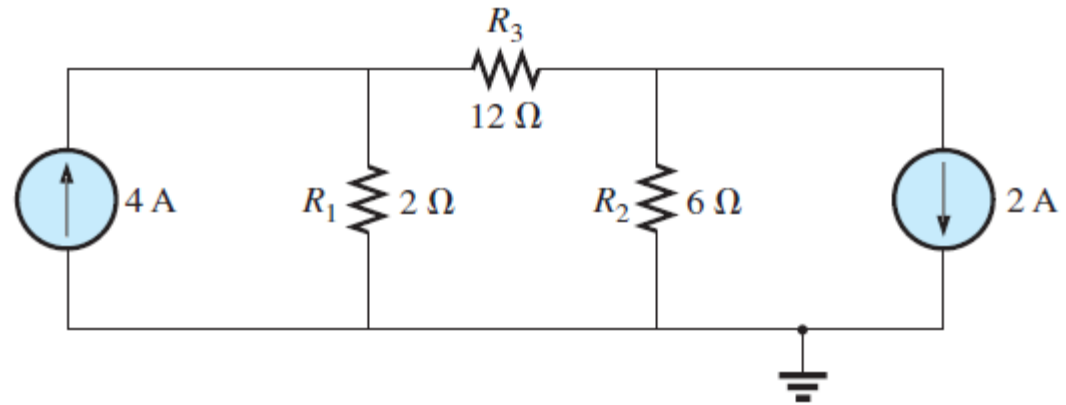


**FIG. 3-1**

**Solution:**

**Step 1 and 2:**

**As indicated in Fig. 3-2**

**FIG. 3-2**

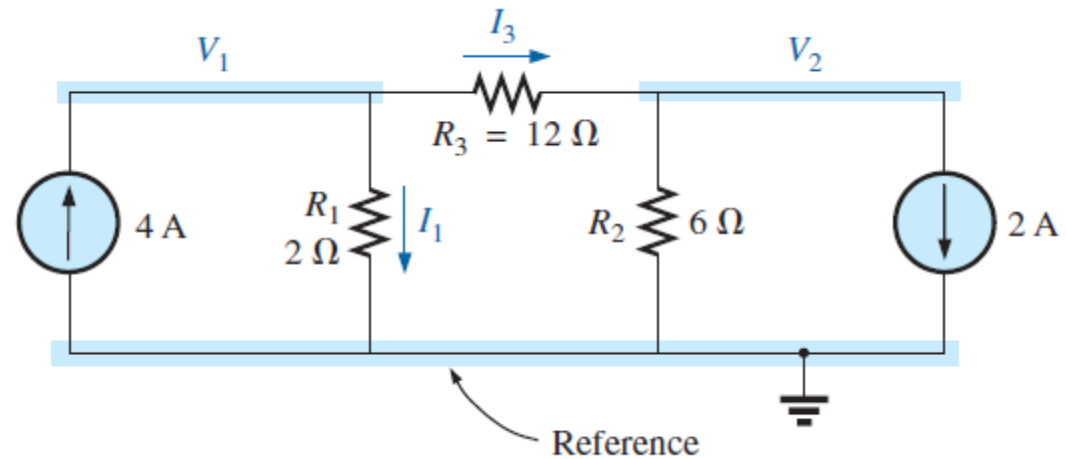

**Step 3:**

**Included in Fig. 3-2 for the node V1. Applying Kirchhoff's current law:**

$$4 \text{ A} = I_1 + I_3$$


$$4 \text{ A} = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_3} = \frac{V_1}{2 \Omega} + \frac{V_1 - V_2}{12 \Omega}$$

*Expanding and rearranging:*

$$V_1 \left( \frac{1}{2 \Omega} + \frac{1}{12 \Omega} \right) - V_2 \left( \frac{1}{12 \Omega} \right) = 4 \text{ A}$$

*For node **V2**, the currents are defined as in **Fig. 3-3**.*

**FIG. 3-3**

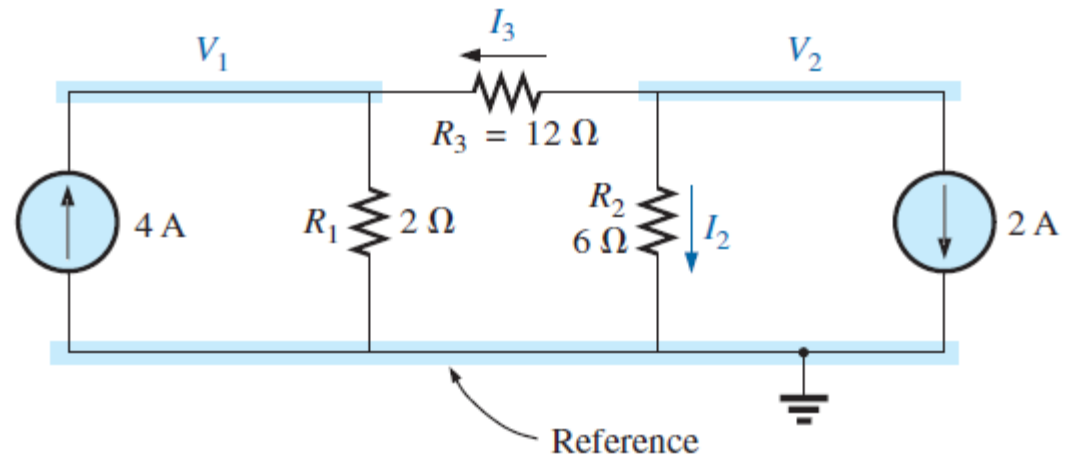

*Applying Kirchhoff's current law:*

$$0 = I_3 + I_2 + 2 \text{ A}$$

$$\frac{V_2 - V_1}{R_3} + \frac{V_2}{R_2} + 2 \text{ A} = 0 \longrightarrow \frac{V_2 - V_1}{12 \Omega} + \frac{V_2}{6 \Omega} + 2 \text{ A} = 0$$

*Expanding and rearranging:*

$$V_2 \left( \frac{1}{12 \Omega} + \frac{1}{6 \Omega} \right) - V_1 \left( \frac{1}{12 \Omega} \right) = -2 \text{ A}$$

**Step 4:**

*The result is two equations and two unknowns:*

$$\left. \begin{aligned} V_1 \left( \frac{1}{2 \Omega} + \frac{1}{12 \Omega} \right) - V_2 \left( \frac{1}{12 \Omega} \right) &= +4 \text{ A} \\ V_2 \left( \frac{1}{12 \Omega} + \frac{1}{6 \Omega} \right) - V_1 \left( \frac{1}{12 \Omega} \right) &= -2 \text{ A} \end{aligned} \right\} \Rightarrow \left. \begin{aligned} \frac{7}{12} V_1 - \frac{1}{12} V_2 &= +4 \\ -\frac{1}{12} V_1 + \frac{3}{12} V_2 &= -2 \end{aligned} \right\} \begin{aligned} 7V_1 - V_2 &= 48 \\ -1V_1 + 3V_2 &= -24 \end{aligned}$$

$$V_1 = \frac{\begin{vmatrix} 48 & -1 \\ -24 & 3 \end{vmatrix}}{\begin{vmatrix} 7 & -1 \\ -1 & 3 \end{vmatrix}} = \frac{120}{20} = +6 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 7 & 48 \\ -1 & -24 \end{vmatrix}}{20} = \frac{-120}{20} = -6 \text{ V}$$

*Since **V1** is greater than **V2**, the current through **R3** passes from **V1** to **V2**.*

*Its value is*

$$I_{R_3} = \frac{V_1 - V_2}{R_3} = \frac{6 \text{ V} - (-6 \text{ V})}{12 \Omega} = \frac{12 \text{ V}}{12 \Omega} = 1 \text{ A}$$

*The fact that **V1** is positive results in a current **IR1** from **V1** to ground equal to*

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_1}{R_1} = \frac{6 \text{ V}}{2 \Omega} = 3 \text{ A}$$

*Finally, since **V2** is negative, the current **IR2** flows from ground to **V2** and is equal to*

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_2}{R_2} = \frac{6 \text{ V}}{6 \Omega} = 1 \text{ A}$$