



Electrical Circuit-I

2nd Lecture

Ohm's Law

By:

Dr. Ali Abu-Rghaif

Ref: Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

Ohm's Law

States that the voltage (**v**) across a resistor is directly proportional to the current (**i**) flowing through the resistor.

That is :

$$v \propto i$$

Ohm define the constant of proportionality for a resistor to be the resistor (**R**)

$$V = I R$$

volts, V

R: is measured in the unit of Ohms, designated (Ω)

and

$$I = \frac{V}{R} = \frac{E}{R}$$

amperes, A


$$R = \frac{V}{I} = \frac{E}{I}$$

ohms, Ω


Ohm's Law

The three quantities **V**, **I**, **R** are defined by the simple circuit


(**Basic circuit**)

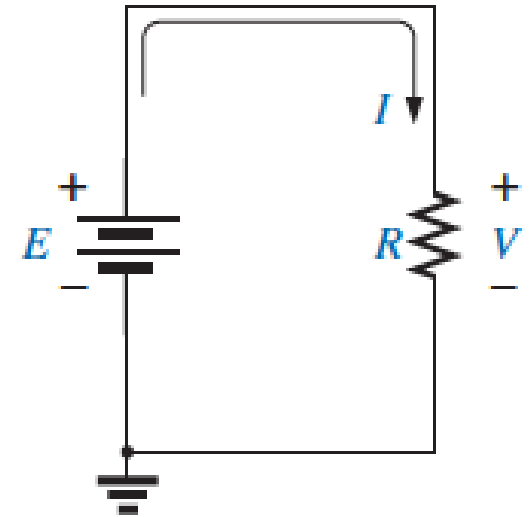

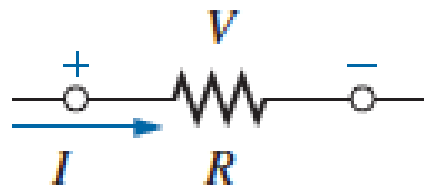- *the symbol E is applied to all sources of voltage*
- *the symbol V is applied to all voltage drops across components of the network.*
- *For any resistor, in any network, the direction of current through a resistor will define the polarity of the voltage drop across the resistor*



(a)

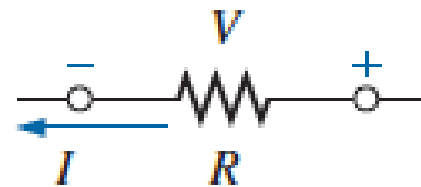

(b)

Example (1)

Determine the **current** resulting from the application of a **9 V** battery across a network with a resistance of **2.2 Ω**.

Solution:

$$I = \frac{V_R}{R} = \frac{E}{R} = \frac{9 \text{ V}}{2.2 \text{ } \Omega} = 4.09 \text{ A}$$

Example (2)

Calculate the resistance of a **60 W** bulb if a current of **500 mA** results from an applied voltage of **120 V**.

Solution:


$$R = \frac{V_R}{I} = \frac{E}{I} = \frac{120 \text{ V}}{500 \times 10^{-3} \text{ A}} = 240 \text{ } \Omega$$

Example (3)

Calculate the voltage that must be applied across the soldering iron to establish a current of **1.5 A** through the iron if its internal resistance is **80 Ω**.

Solution:


$$E = V_R = IR = (1.5 \text{ A})(80 \Omega) = 120 \text{ V}$$

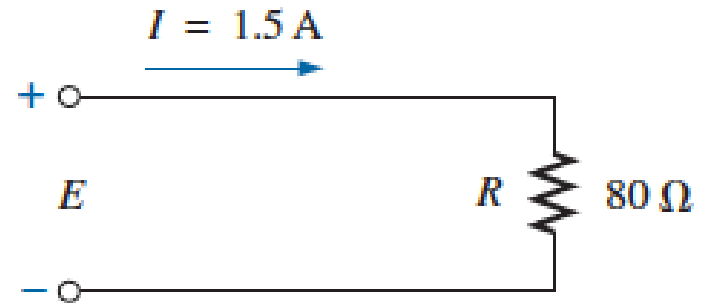**Example (4)**

Calculate the current through the **2 kΩ** resistor if the voltage drop across it is **16 V**.

Solution:
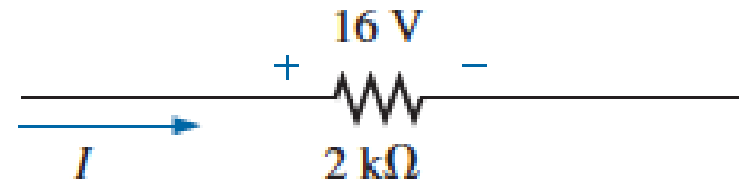
$$I = \frac{V}{R} = \frac{16 \text{ V}}{2 \times 10^3 \Omega} = 8 \text{ mA}$$



Plotting Ohm's Law


$$R_{dc} = \frac{V}{I}$$

If we write Ohm's law in the following manner and relate it to the basic straight-line equation

$$I = \frac{1}{R} \cdot E + 0$$

↓ ↓ ↓ ↓

$$y = m \cdot x + b$$

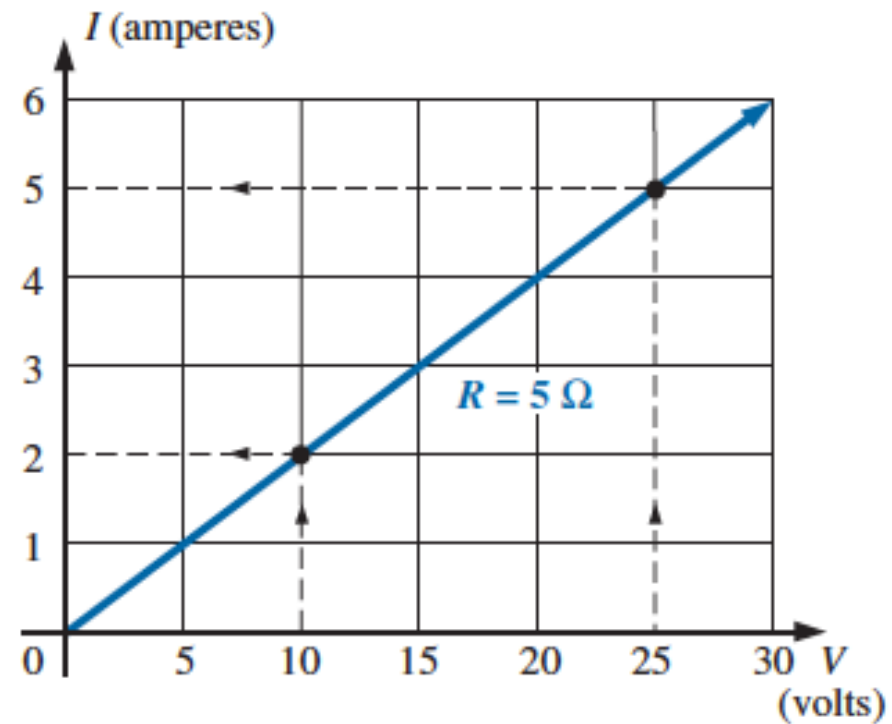


Plotting Ohm's Law

we find that the slope is equal to 1 divided by the resistance value, as indicated by the following:

$$m = \text{slope} = \frac{\Delta y}{\Delta x} = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$
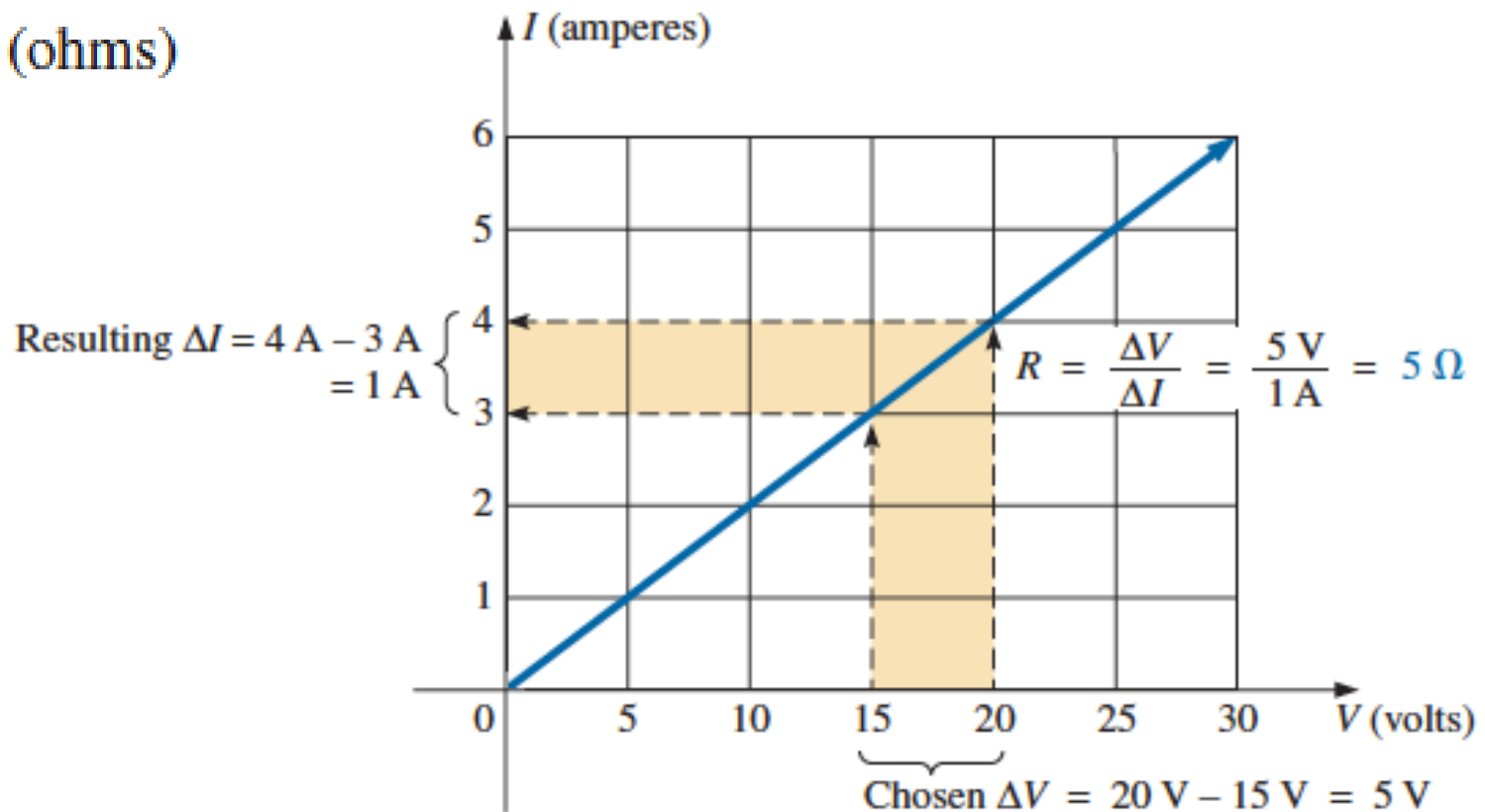
$$R = \frac{\Delta V}{\Delta I} \quad (\text{ohms})$$



Example (5)

Determine the resistance associated with the curve in the figure below ? And compare results


Solution:

At $V = 6 \text{ V}$, $I = 3 \text{ mA}$, and

$$R_{dc} = \frac{V}{I} = \frac{6 \text{ V}}{3 \text{ mA}} = 2 \text{ k}\Omega$$

For the interval between 6 V and 8 V ,
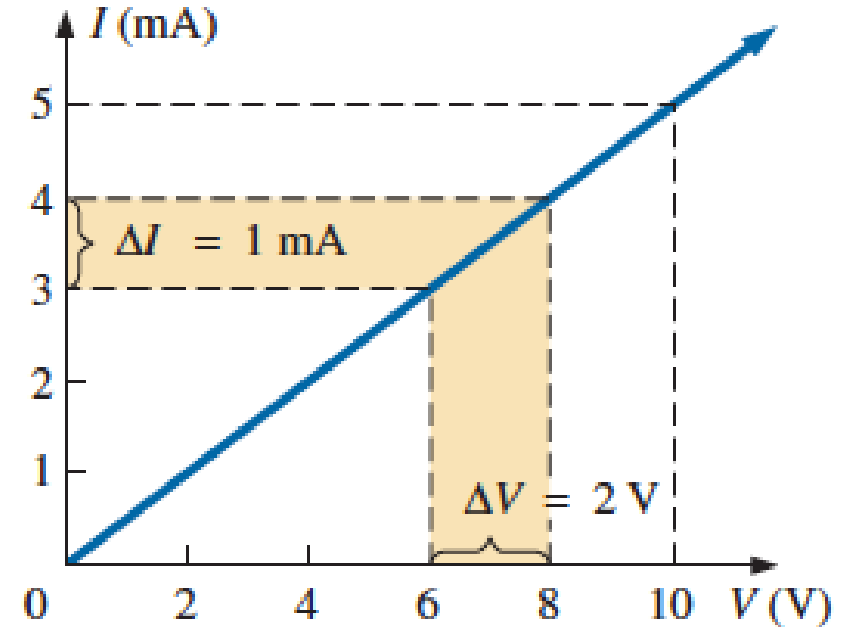
$$R = \frac{\Delta V}{\Delta I} = \frac{2 \text{ V}}{1 \text{ mA}} = 2 \text{ k}\Omega$$




The results are equivalent.

Short Circuit

Is a circuit element with resistance approaching **zero**

$$R = 0 \text{ (for a short circuit)}$$

$$V = I R = 0$$

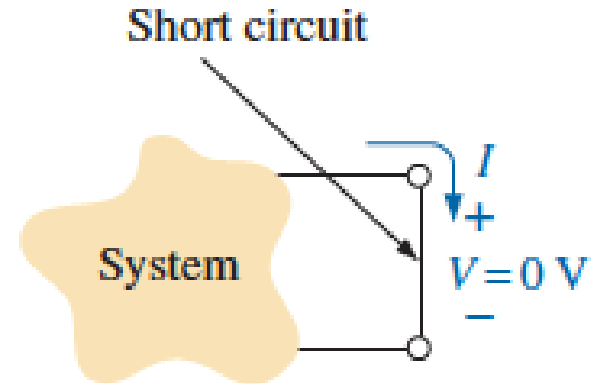


Open Circuit

Is a circuit element with resistance approaching **infinity**

$$R = \infty \text{ (for an open circuit)}$$
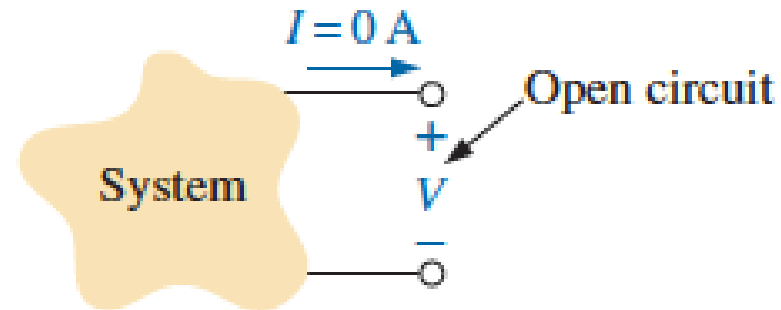
$$I = \lim_{R \rightarrow \infty} \frac{V}{R} = 0$$



Conductance

Is the ability of an element to conduct electric current; it is measured in **Mho's (Ω)** or **Siemens (S)**

$$G = \frac{1}{R} = \frac{I}{V}$$

The SI unit of G

$$1 \text{ S} = 1 \text{ Ω} = 1 \text{ A/V}$$

Power

The power dissipated by resistor can be expressed in term of (**P**)

$$P = VI = I^2R = \frac{V^2}{R}$$

We should note two things:


- The power dissipated in a resistor is nonlinear function of either current or voltage.
- Since R is positive quantities, the power dissipated in a resistor is always positive. Thus, a resistor always absorbs power from the circuit.

Branch

Branch represents a single element such as a voltage source or a resistor

Node

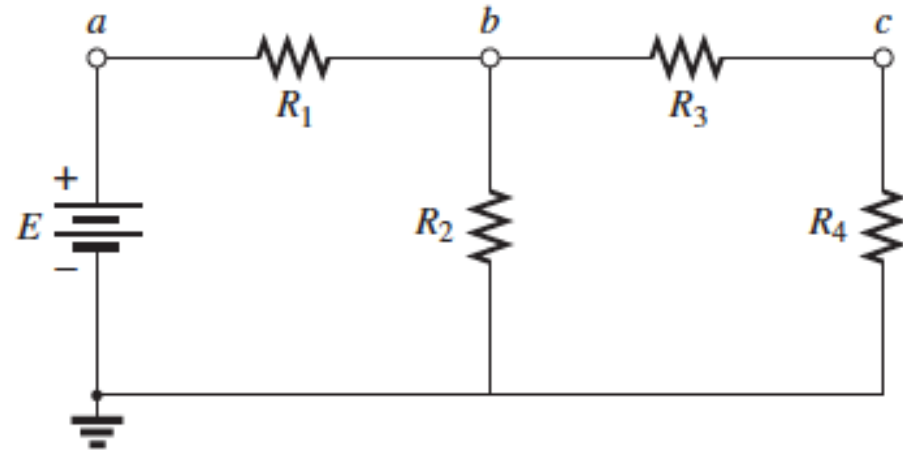Node is the point of connection between two or more branches.



Loop

Loop is any closed path in a circuit.

A network with (b) branches, (n) nodes, and (ℓ) independent loops will satisfy the fundamental theorem of network topology:

$$b = \ell + n - 1$$