



# Electrical Circuit-I

## 3<sup>rd</sup> Lecture

### Series dc Circuits

By:


Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007
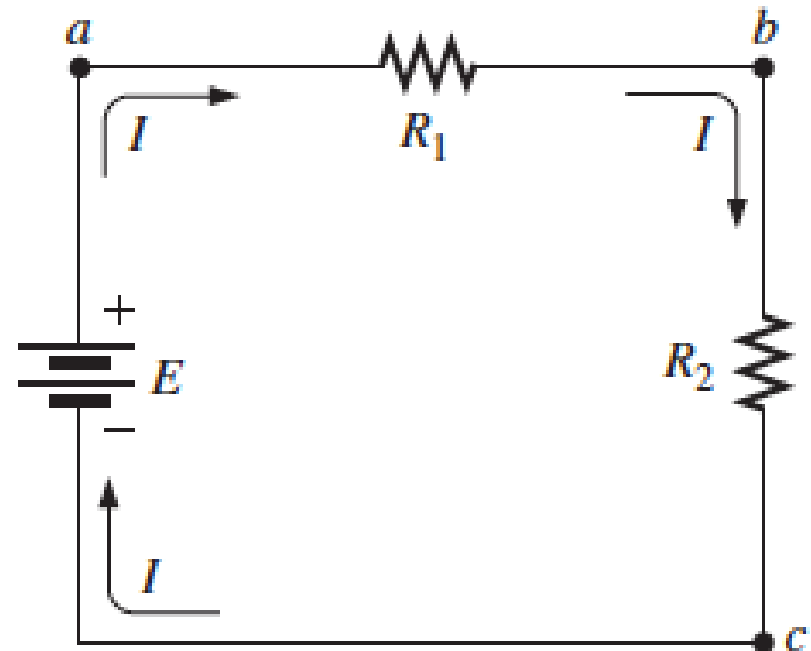
# Series Circuits

*A circuit consists of any number of elements joined at terminal point, providing at least one closed path through which charge can flow.*


*The circuit of Fig. below, has three elements joined at three terminal points (a, b, c) to provide a closed path for the current **I**.*



**The current is the same through series elements**
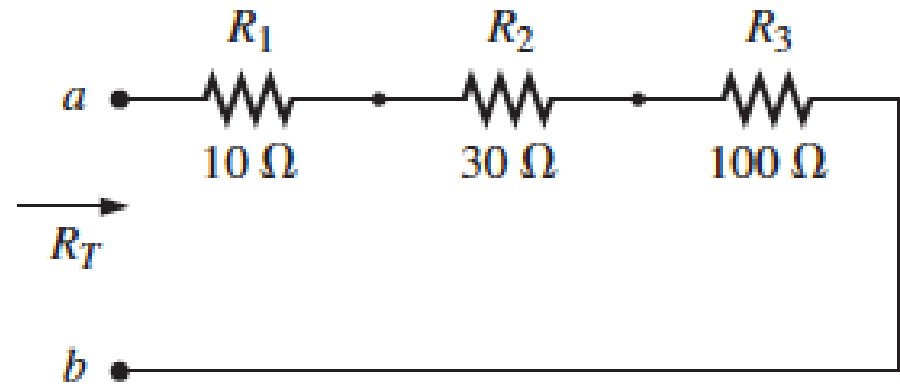
# Series Resistors

*The total resistance of a series configuration is the sum of the resistance levels..*



$$R_T = R_1 + R_2 + R_3 + R_4 + \dots + R_N$$

*For the special case where resistors are the same values can be modified as follows:*

$$R_T = NR$$

*The current is the same at every point in a series circuit, and can be determined using Ohm's law:*

$$I_s = \frac{E}{R_T}$$

# Series Resistors

*The voltage across each resistor with the total resistance, using ohm's law:*

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3, \dots V_N = IR_N$$

*The power delivered to each resistor can then be determined using any one of three equations as listed below (shown for resistor  $R_1$  only):*

$$P_1 = V_1 I_1 = I_1^2 R_1 = \frac{V_1^2}{R_1} \quad (\text{watts, W})$$

*The power delivered by the supply can be determined using*

$$P_E = EI_s \quad (\text{watts, W})$$

*The power applied by the dc supply must equal that dissipated by the resistive elements.*

$$P_E = P_{R_1} + P_{R_2} + P_{R_3}$$

**Example (1)**


Determine the total resistance for the series resistors?

**Solution:**

$$R_T = R_1 + R_2 + R_3 + R_4$$

$$R_T = 20 \Omega + 220 \Omega + 1.2 \text{ k}\Omega + 5.6 \text{ k}\Omega$$

$$R_T = 7040 \Omega = 7.04 \text{ k}\Omega$$

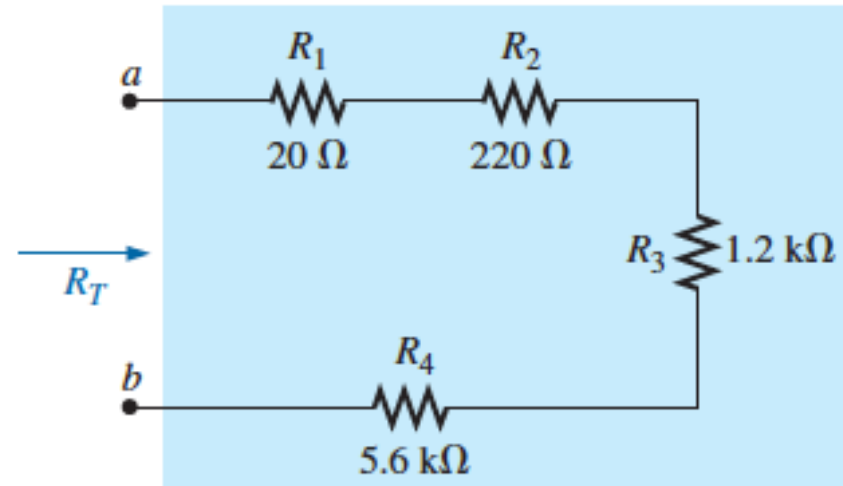
**Example (2)**

Find the total resistance of the series resistors

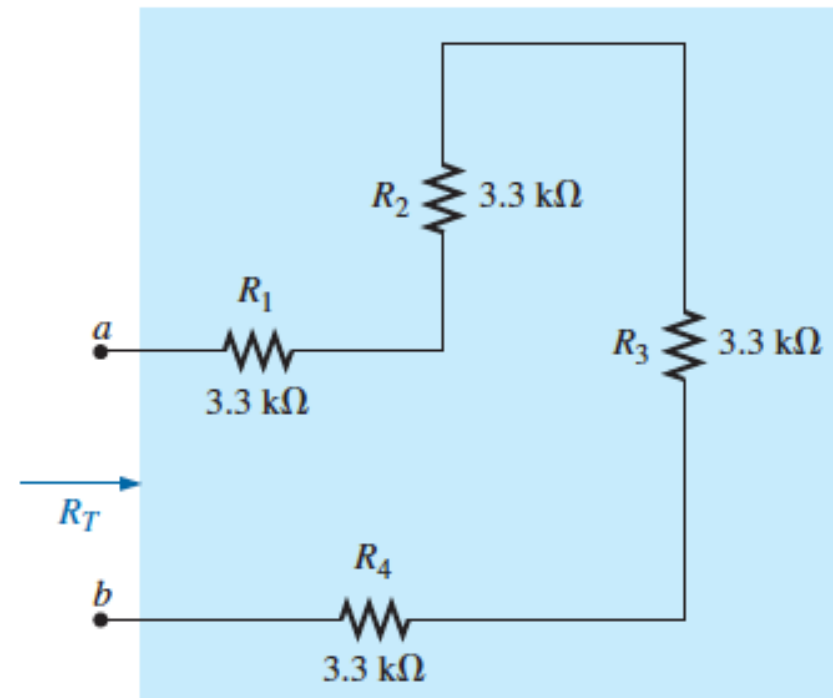**Solution:**

$$R_T = NR$$

$$= (4)(3.3 \text{ k}\Omega) = 13.2 \text{ k}\Omega$$



**Example (3)**

For the series circuit:

- Find the total resistance  $R_T$ .
- Calculate the resulting source current  $I$ .
- Determine the **voltage** across each resistor.
- Calculate the power dissipated by  $R_1$ ,  $R_2$ ,  $R_3$
- Determine the power **delivered** by the source, and compare it to the **sum** of the power levels of part (d)

**Solution:**

$$\text{a. } R_T = R_1 + R_2 + R_3$$

$$= 2 \Omega + 1 \Omega + 5 \Omega$$


$$R_T = 8 \Omega$$

$$\text{b. } I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{8 \Omega} = 2.5 \text{ A}$$

$$\text{c. } V_1 = I_1 R_1 = I_s R_1 = (2.5 \text{ A})(2 \Omega) = 5 \text{ V}$$

$$V_2 = I_2 R_2 = I_s R_2 = (2.5 \text{ A})(1 \Omega) = 2.5 \text{ V}$$
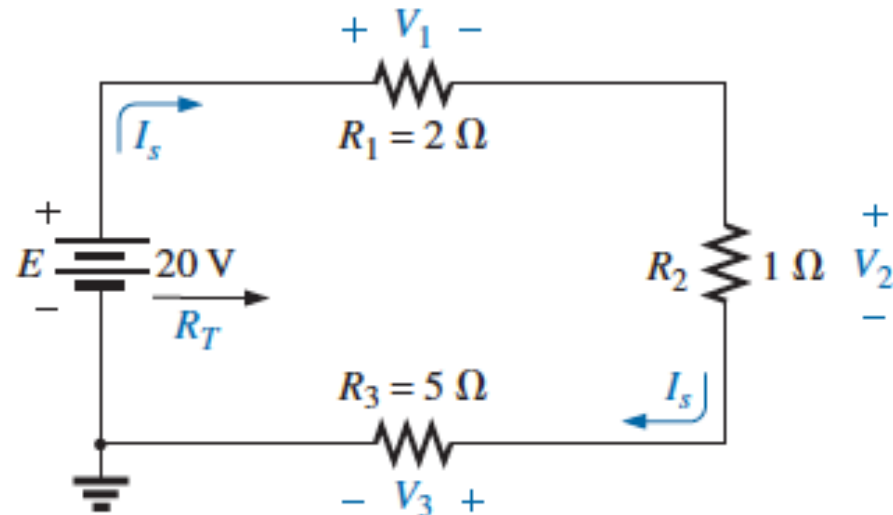
$$V_3 = I_3 R_3 = I_s R_3 = (2.5 \text{ A})(5 \Omega) = 12.5 \text{ V}$$



**Example (3)**

For the series circuit:

- d. Calculate the power dissipated by  $R_1$ ,  $R_2$ ,  $R_3$
- e. Determine the power **delivered** by the source, and compare it to the **sum** of the power levels of part (d)

**Solution:**

$$\begin{aligned} \text{d. } P_1 &= V_1 I &= (5V)(2.5 A) &= 12.5 W \\ P_2 &= I^2 R_2 &= (2.5 A)^2 (1\Omega) &= 6.25 W \\ P_3 &= V_3^2 / R_3 &= (12.5 V)^2 / (5\Omega) &= 31.25 W \end{aligned}$$

$$\begin{aligned} \text{e. } P_E &= EI &= (20V)(2.5A) &= 50 W \\ P_{del} &= P_1 + P_2 + P_3 \\ 50 W &= 12.5 W + 6.25 W + 31.5 W \\ 50 W &= 50 W && \text{(checks)} \end{aligned}$$

**Example (4)**

For the series circuit:

- Find the **total** resistance  $R_T$ .
- Determine the **source** current  $I_S$ .
- Find the **voltage** across resistor  $R_2$ .

**Solution:**

a.

$$\begin{aligned} R_T &= R_2 + NR \\ &= 4 \Omega + (3)(7 \Omega) \\ &= 4 \Omega + 21 \Omega \end{aligned}$$

$$R_T = 25 \Omega$$


b.

$$I_s = \frac{E}{R_T} = \frac{50 \text{ V}}{25 \Omega} = 2 \text{ A}$$

c.

$$V_2 = I_2 R_2 = I_s R_2 = (2 \text{ A})(4 \Omega)$$

$$V_2 = 8 \text{ V}$$

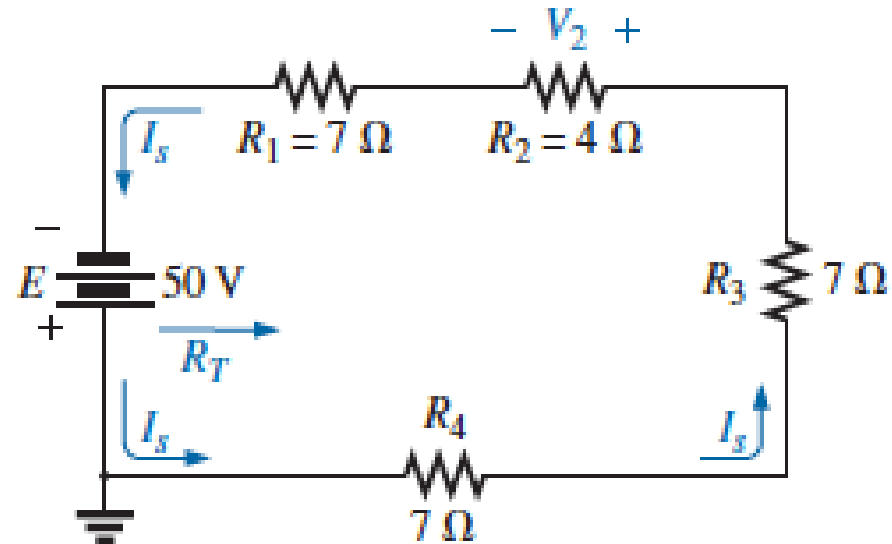



# Kirchhoff's Voltage Law (KVL)

**KVL** states that the algebraic sum of the potential rises and drops around a closed path (or closed loop) is **zero**.

**A closed loop**: is any continuous path that leaves a point in one direction and return to that same point from another direction without leaving the circuit.

As shown in the circuit below, we can trace a continuous path that leaves point **a** through **R<sub>1</sub>** and returns through **E** without leaving the circuit. Therefore, **abcda** is a closed loop. For us to be able to apply **KVL**, the summation of potential rises and drops must be made in one direction around the closed loop.

In symbolic form it can be written as


$$\sum_{\text{C}} V = 0$$

(Kirchhoff's voltage law in symbolic form)

Writing out the sequence with the voltages and the signs results in the following:

$$+E - V_1 - V_2 = 0$$

$$E = V_1 + V_2$$

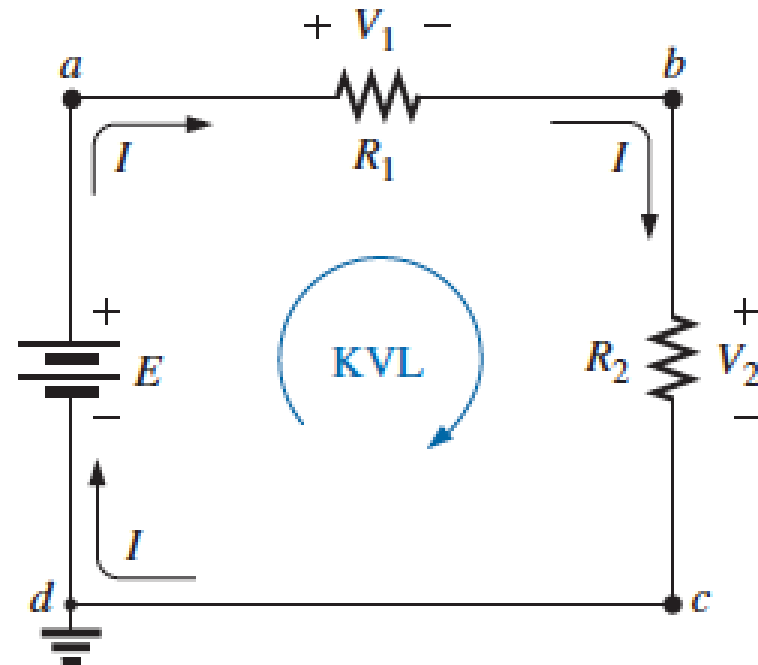

# Kirchhoff's Voltage Law (KVL)

*The applied voltage of a series dc circuit will equal the sum of the voltage drops of the circuit.*

*Kirchhoff's voltage law can also be written in the following form:*

$$\sum_{\odot} V_{\text{rises}} = \sum_{\odot} V_{\text{drops}}$$

*revealing that*

*the sum of the voltage rises around a closed path will always equal the sum of the voltage drops.*

*To demonstrate that the direction that you take around the loop has no effect on the results, let's take the counter-clockwise path and compare results.*

*The resulting sequence appears as*

$$-E + V_2 + V_1 = 0$$


$$E = V_1 + V_2$$

**Example (5)**

Use Kirchhoff's voltage law to determine the unknown voltage for the circuit

**Solution:**

$$\begin{aligned}
 +E_1 - V_1 - V_2 - E_2 &= 0 \\
 V_1 &= E_1 - V_2 - E_2 \\
 &= 16\text{ V} - 4.2\text{ V} - 9\text{ V} \\
 V_1 &= 2.8\text{ V}
 \end{aligned}$$

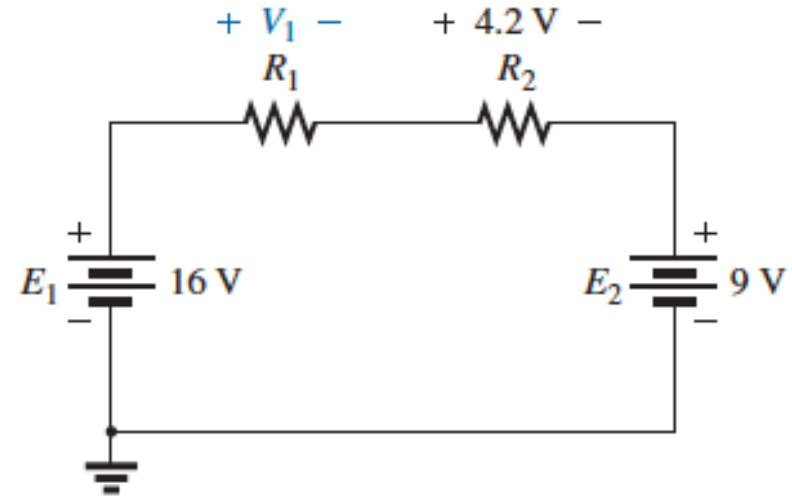**Example (6)**


Use Kirchhoff's voltage law to determine the unknown voltage for the circuit

**Solution:**

$$\begin{aligned}
 +E - V_1 - V_x &= 0 \\
 V_x &= E - V_1 = 32\text{ V} - 12\text{ V} = 20\text{ V}
 \end{aligned}$$

For the clockwise path, including resistor  $R_3$ , the following results:
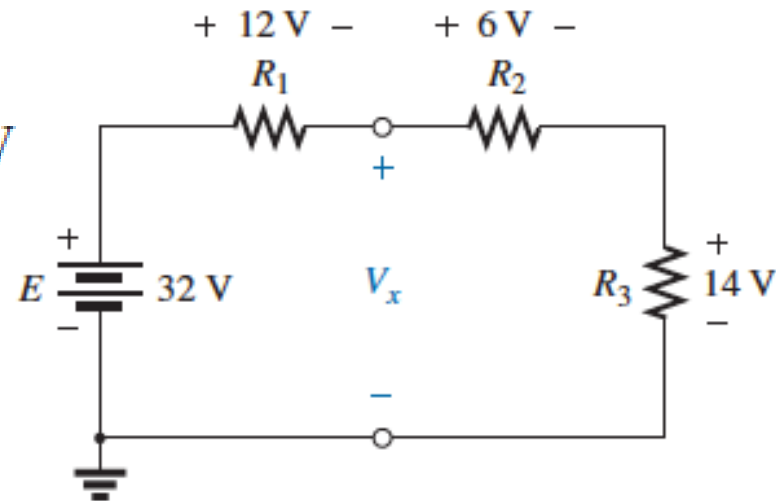
$$\begin{aligned}
 +V_x - V_2 - V_3 &= 0 \\
 V_x &= V_2 + V_3 \\
 &= 6\text{ V} + 14\text{ V} \\
 V_x &= 20\text{ V}
 \end{aligned}$$



**Example (7)**


Use Kirchhoff's voltage law to determine the unknown voltage for the circuit

**Solution:**

$$+60 \text{ V} - 40 \text{ V} - V_x + 30 \text{ V} = 0$$

$$V_x = 60 \text{ V} + 30 \text{ V} - 40 \text{ V} = 90 \text{ V} - 40 \text{ V}$$

$$V_x = 50 \text{ V}$$

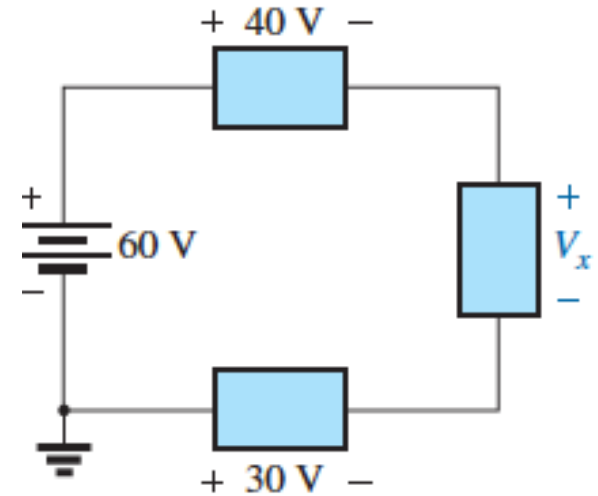**Example (8)**


Use Kirchhoff's voltage law to find the voltage  $V_x$  for the circuit

**Solution:**

$$-6 \text{ V} - 14 \text{ V} - V_x + 2 \text{ V} = 0$$

$$V_x = -20 \text{ V} + 2 \text{ V}$$


$$V_x = -18 \text{ V}$$

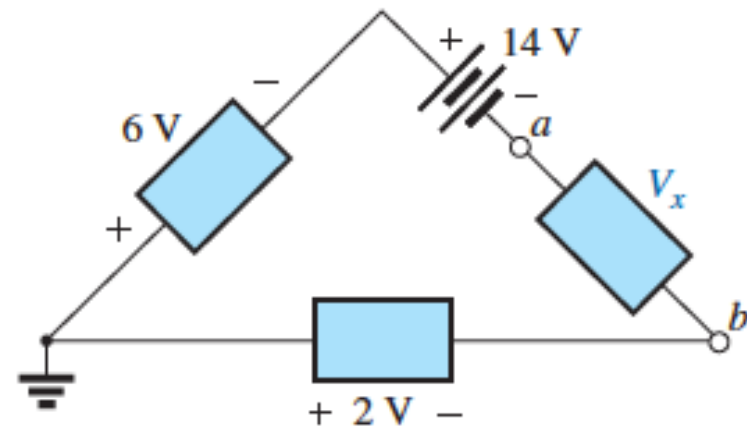

**Example (9)**

For the series circuit:

- Determine  $V_2$  using Kirchhoff's voltage law.
- Determine current  $I_2$ .
- Find  $R_1$  and  $R_3$ .

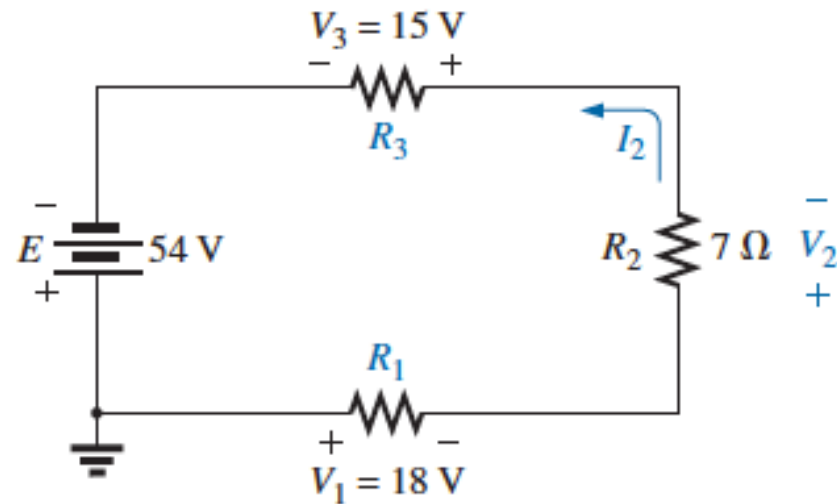**Solution:**

- Applying Kirchhoff's voltage law in the clockwise direction

$$-E + V_3 + V_2 + V_1 = 0$$

and  $E = V_1 + V_2 + V_3$  (as expected)

so that  $V_2 = E - V_1 - V_3 = 54 \text{ V} - 18 \text{ V} - 15 \text{ V}$

and  $V_2 = 21 \text{ V}$

- $I_2 = \frac{V_2}{R_2} = \frac{21 \text{ V}}{7 \Omega}$

$$I_2 = 3 \text{ A}$$

- $R_1 = \frac{V_1}{I_1} = \frac{18 \text{ V}}{3 \text{ A}} = 6 \Omega$

with  $R_3 = \frac{V_3}{I_3} = \frac{15 \text{ V}}{3 \text{ A}} = 5 \Omega$

# Voltage Divider Rule (VDR)

*The voltage divider rule (VDR) permits the determination of the voltage across a series resistor without first having to determine the current of the circuit.*

*The rule itself can be derived by analysing the simple series circuit shown:*


$$R_T = R_1 + R_2$$

$$I_s = I_1 = I_2 = \frac{E}{R_T}$$

*Apply Ohm's law to each resistor:*

$$V_1 = I_1 R_1 = \left( \frac{E}{R_T} \right) R_1 = R_1 \frac{E}{R_T}$$
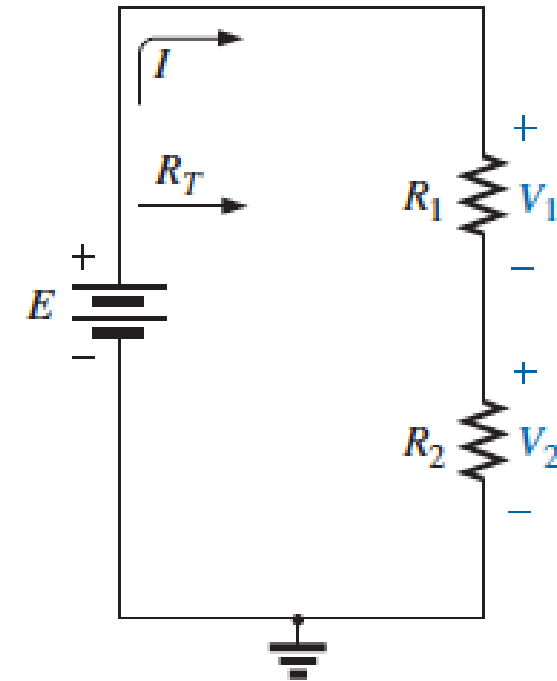
$$V_2 = I_2 R_2 = \left( \frac{E}{R_T} \right) R_2 = R_2 \frac{E}{R_T}$$



*The resulting format for V1 and V2 is*

$$V_x = R_x \frac{E}{R_T}$$

# Voltage Divider Rule (VDR)

where  $V_x$  is the voltage across the resistor  $R_x$ ,  $E$  is the impressed voltage across the series elements, and  $R_T$  is the total resistance of the series circuit.

$$V_x = R_x \frac{E}{R_T}$$

*The voltage divider rule states that:*

*the voltage across a resistor in a series circuit is equal to the value of that resistor times the total applied voltage divided by the total resistance of the series configuration.*

**Example (10)**

Using the voltage divider rule, determine voltages  $V_1$  and  $V_3$  for the series circuit?


**Solution:**

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega \end{aligned}$$

$$R_T = 15 \text{ k}\Omega$$

$$V_1 = R_1 \frac{E}{R_T} = 2 \text{ k}\Omega \left( \frac{45 \text{ V}}{15 \text{ k}\Omega} \right) = 6 \text{ V}$$
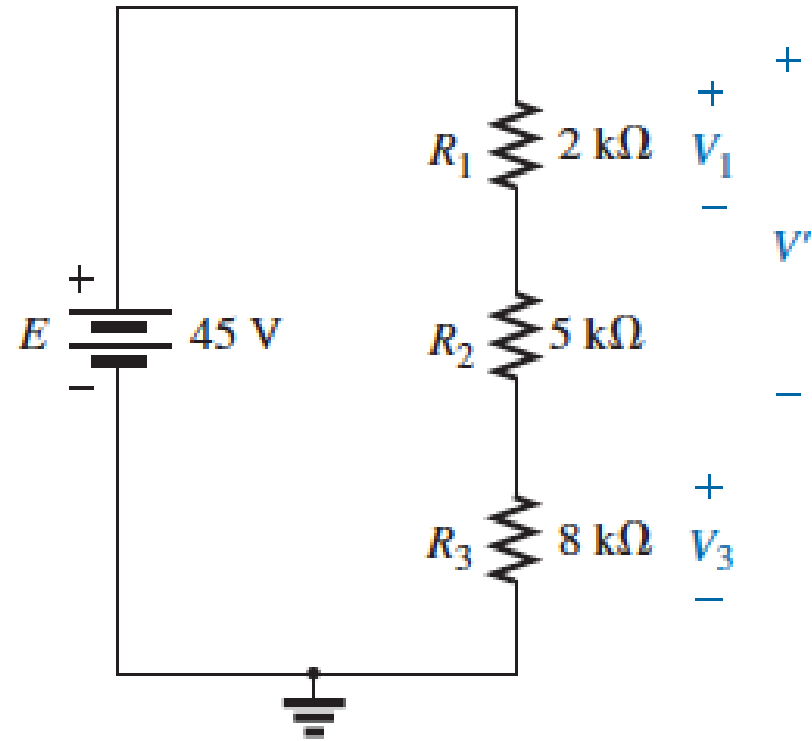
$$V_3 = R_3 \frac{E}{R_T} = 8 \text{ k}\Omega \left( \frac{45 \text{ V}}{15 \text{ k}\Omega} \right) = 24 \text{ V}$$





**Example (11)**

For the series circuit:

- Without making any calculations, how much larger would you expect the voltage across  $R_2$  to be compared to that across  $R_1$ ?
- Find the voltage  $V_1$  using only the voltage divider rule.
- Using the conclusion of part (a), determine the voltage across  $R_2$ .
- Use the voltage divider rule to determine the voltage across  $R_2$ , and compare your answer to your conclusion in part (c).
- How does the sum of  $V_1$  and  $V_2$  compare to the applied voltage?

**Solution:**

a. Since resistor  $R_2$  is three times  $R_1$ , it is expected that  $V_2 = 3V_1$ .

$$b. V_1 = R_1 \frac{E}{R_T} = 20 \Omega \left( \frac{64 \text{ V}}{20 \Omega + 60 \Omega} \right) = 20 \Omega \left( \frac{64 \text{ V}}{80 \Omega} \right) = 16 \text{ V}$$

$$c. V_2 = 3V_1 = 3(16 \text{ V}) = 48 \text{ V}$$

$$d. V_2 = R_2 \frac{E}{R_T} = (60 \Omega) \left( \frac{64 \text{ V}}{80 \Omega} \right) = 48 \text{ V}$$

The results are an exact match.

$$e. E = V_1 + V_2$$

$$64 \text{ V} = 16 \text{ V} + 48 \text{ V} = 64 \text{ V} \quad (\text{checks})$$

