



# Electrical Circuit-I

## 4<sup>th</sup> Lecture

### Parallel dc Circuits

By:

Dr. Ali Abu-Rghaif


**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

# Parallel Circuits




*The term parallel is used so often to describe a physical arrangement between two elements that most individuals are aware of its general characteristics. In general,*

*two elements, branches, or circuits are in parallel if they have two points in common.*

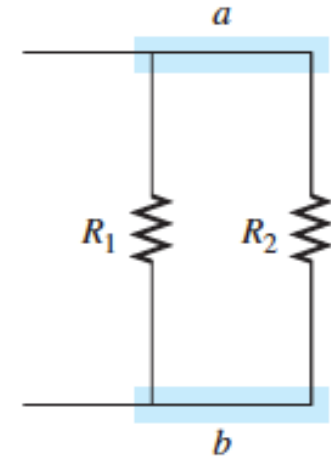*For instance, in figure below, the two resistors are in parallel because they are connected at points a and b.*




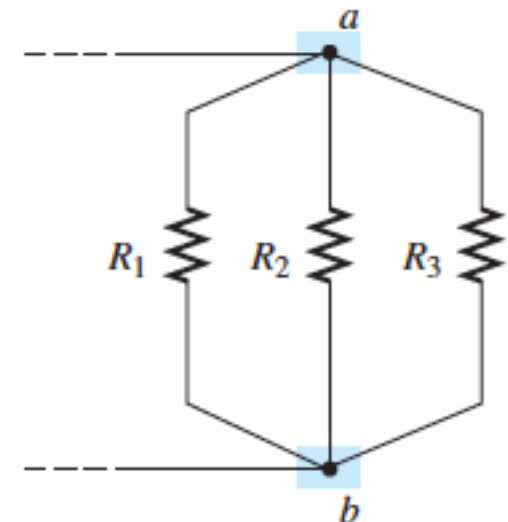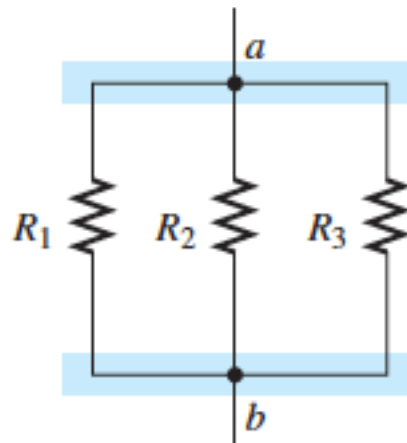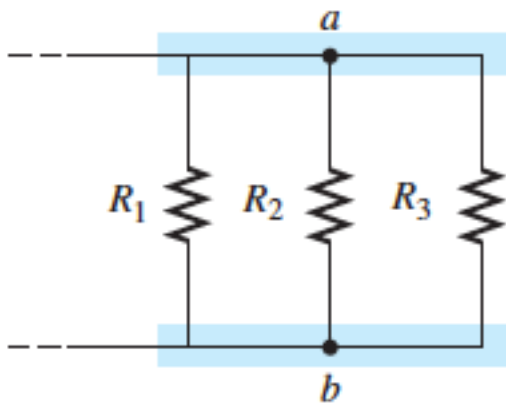*the parallel combination can appear in a number of ways, as shown in below. In each case, the three resistors are in parallel. They all have points a and b in common.*


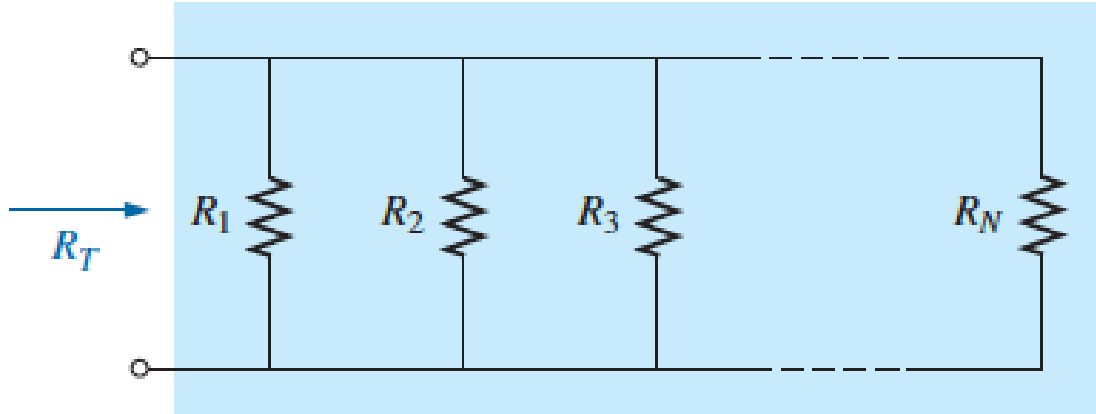
# Total Conductance and Resistance

*For resistors in parallel as shown, the total resistance is determined from the following equation:*



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots + \frac{1}{R_N}$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots + \frac{1}{R_N}}$$

*Since  $G = 1/R$ , the equation can also be written in terms of conductance levels as follows:*

$$G_T = G_1 + G_2 + G_3 + \cdots + G_N$$

*(Siemens, S)*

**Example (1)**


Determine the total conductance and resistance for the parallel network?

**Solution:**

$$G_1 = \frac{1}{R_1} = \frac{1}{3 \Omega} = 0.333 \text{ S}, \quad G_2 = \frac{1}{R_2} = \frac{1}{6 \Omega} = 0.167 \text{ S}$$

$$G_T = G_1 + G_2 = 0.333 \text{ S} + 0.167 \text{ S} = 0.5 \text{ S}$$


$$R_T = \frac{1}{G_T} = \frac{1}{0.5 \text{ S}} = 2 \Omega$$

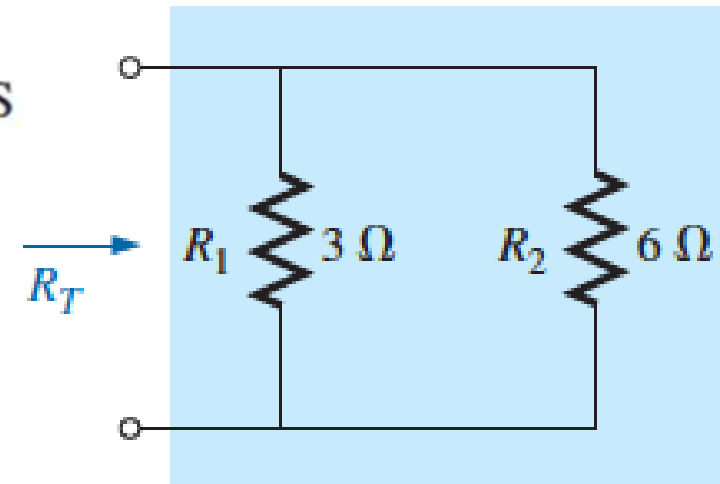**Example (2)**

Find the total resistance of the parallel resistors

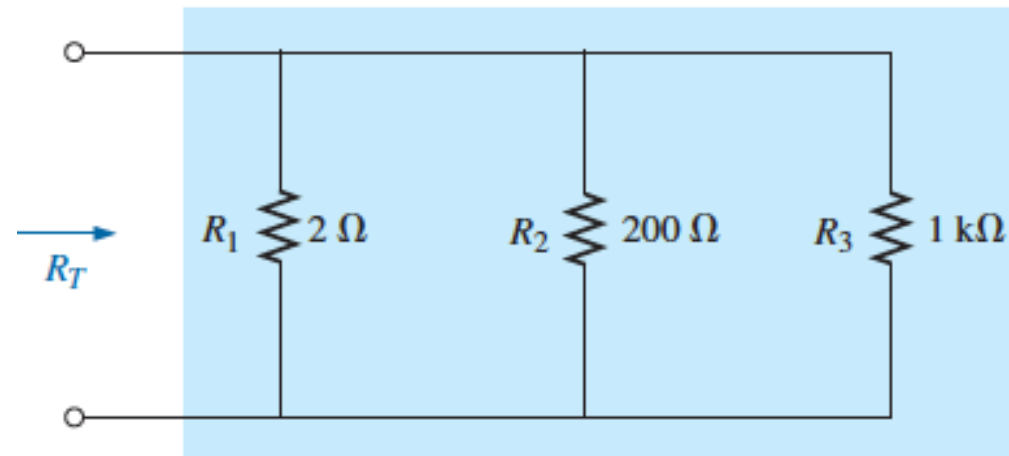
**Solution:**

$$\begin{aligned} R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \\ &= \frac{1}{\frac{1}{2 \Omega} + \frac{1}{200 \Omega} + \frac{1}{1 \text{ k}\Omega}} \\ &= \frac{1}{0.5 \text{ S} + 0.005 \text{ S} + 0.001 \text{ S}} \\ &= \frac{1}{0.506 \text{ S}} = 1.98 \Omega \end{aligned}$$




**Example (3)**

Find the total resistance of the configuration?

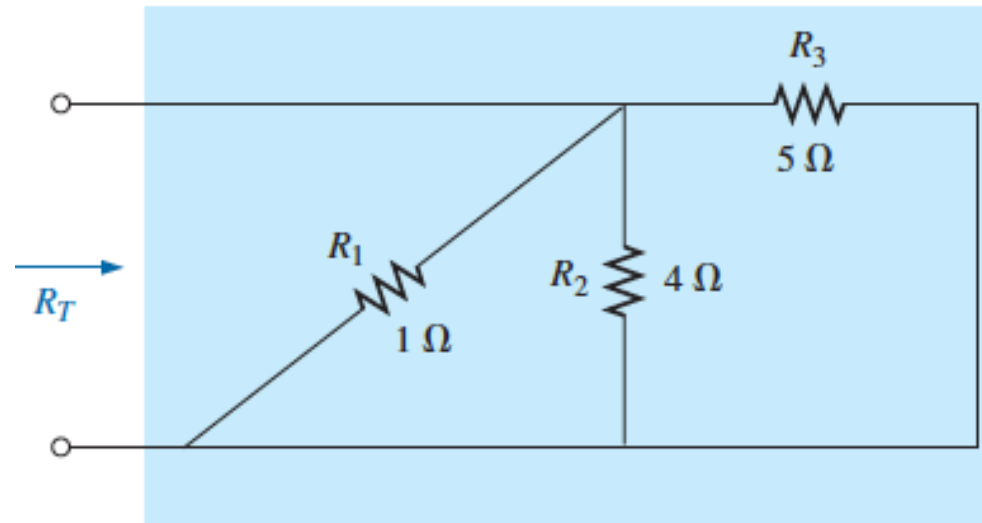**Solution:**

First the network is redrawn as shown

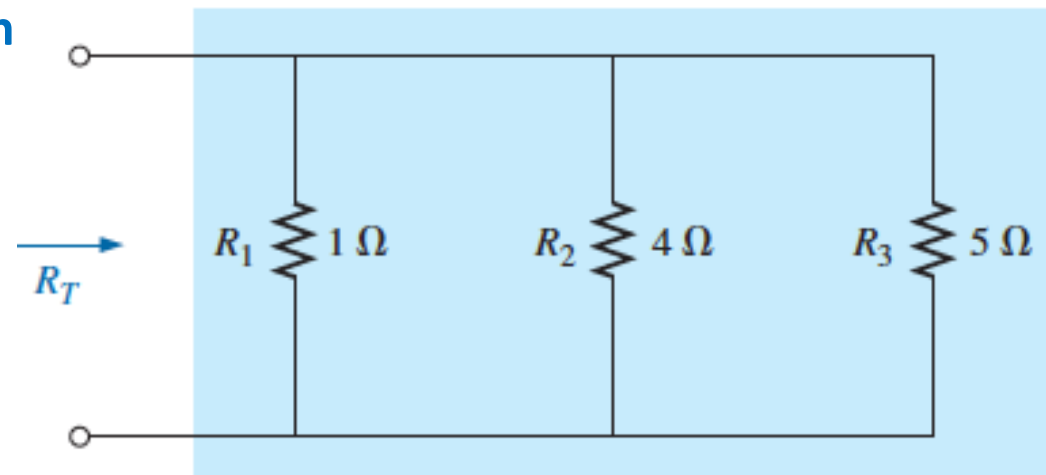

$$\begin{aligned}
 R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \\
 &= \frac{1}{\frac{1}{1\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{5\ \Omega}} \\
 &= \frac{1}{1\ \text{S} + 0.25\ \text{S} + 0.2\ \text{S}} \\
 &= \frac{1}{1.45\ \text{S}} \cong \mathbf{0.69\ \Omega}
 \end{aligned}$$

# Parallel Resistors

- *The total resistance of parallel resistors is always less than the value of the smallest resistor.*
- *If the smallest resistor of a parallel combination is much smaller than the other parallel resistors, the total resistance will be very close to the smallest resistor value.*
- *The total resistance of parallel resistors will always drop as new resistors are added in parallel, irrespective of their value.*

*For equal resistors in parallel, the equation for the total resistance becomes significantly easier to apply. For N equal resistors in parallel,*

*In other words,*


*the total resistance of N parallel resistors of equal value is the resistance of one resistor divided by the number (N) of parallel resistors.*

$$\begin{aligned}
 R_T &= \frac{1}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R_N}} \\
 &= \frac{1}{N\left(\frac{1}{R}\right)} = \frac{1}{\frac{N}{R}}
 \end{aligned}$$

$$\boxed{R_T = \frac{R}{N}}$$

**Example (4)**

- a. What is the effect of adding another resistor of **100 Ω** in parallel with the parallel resistors of **Example (1)** as shown below?
- b. What is the effect of adding a parallel **1 Ω** resistor to the configuration?

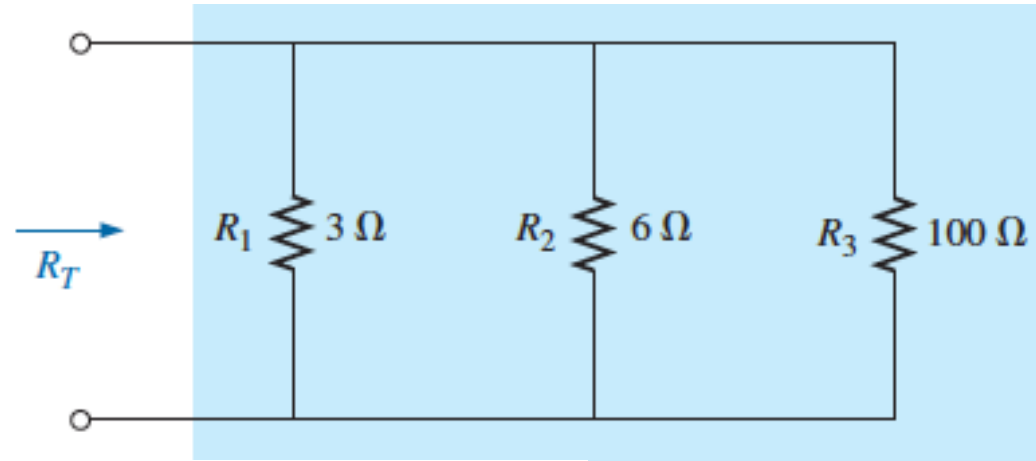**Solution:**

$$\begin{aligned} \text{a. } R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} + \frac{1}{100\ \Omega}} \\ &= \frac{1}{0.333\ \text{S} + 0.167\ \text{S} + 0.010\ \text{S}} = \frac{1}{0.510\ \text{S}} = \mathbf{1.96\ \Omega} \end{aligned}$$


$$\begin{aligned} \text{b. } R_T &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} + \frac{1}{100\ \Omega} + \frac{1}{1\ \Omega}} \\ &= \frac{1}{0.333\ \text{S} + 0.167\ \text{S} + 0.010\ \text{S} + 1\ \text{S}} = \frac{1}{1.51\ \text{S}} = \mathbf{0.66\ \Omega} \end{aligned}$$

**Example (5)**



Find the total resistance of the parallel resistors?

**Solution:**

$$R_T = \frac{R}{N} = \frac{12 \Omega}{3} = 4 \Omega$$

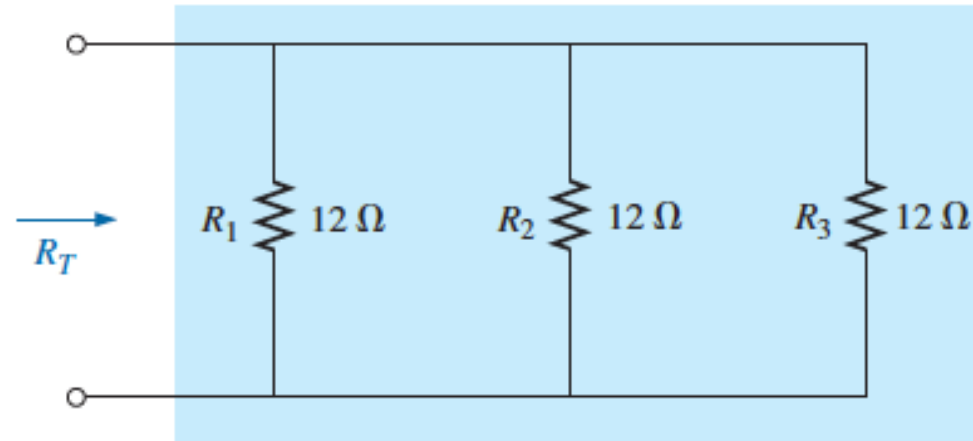**Example (6)**

Find the total resistance of the parallel resistors?

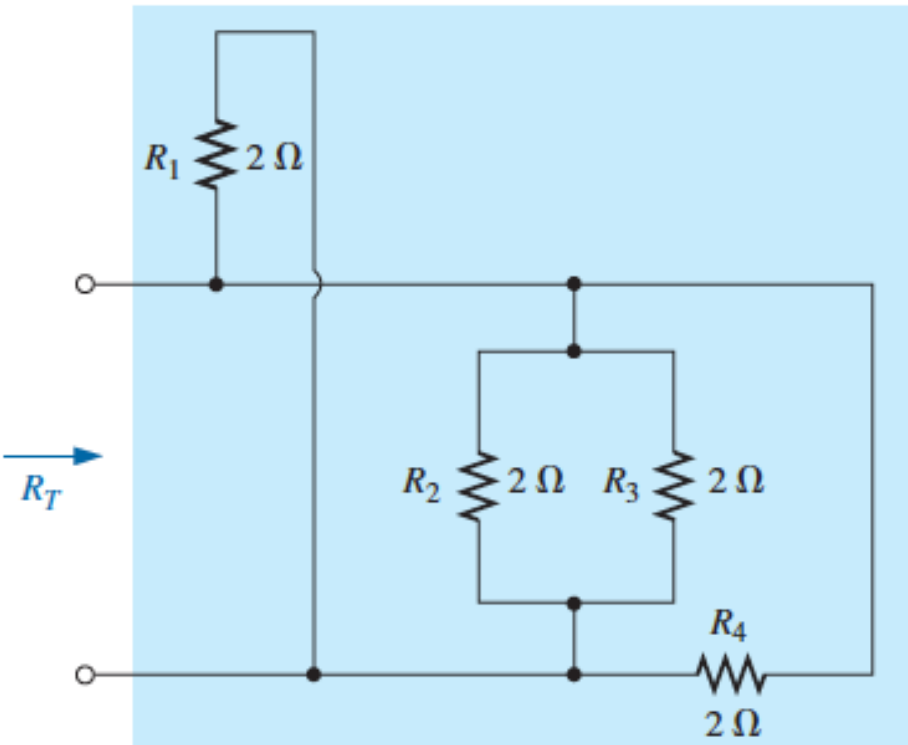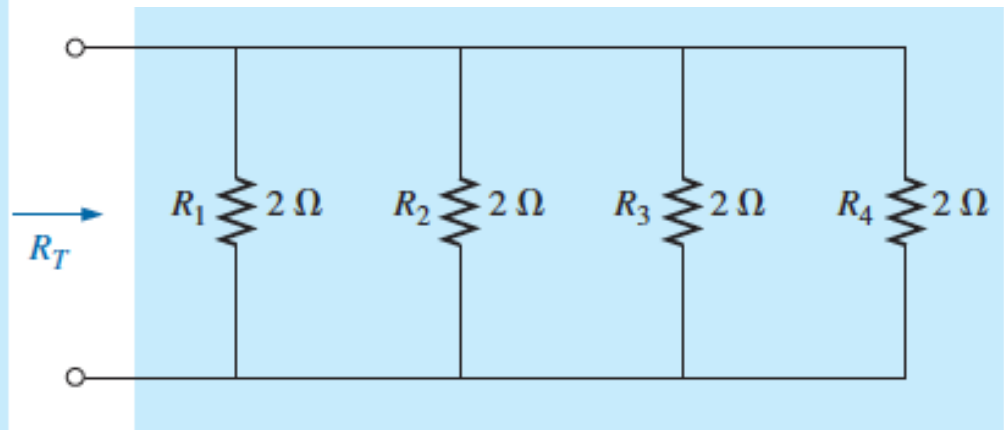**Solution:**

$$R_T = \frac{R}{N} = \frac{2 \Omega}{4} = 0.5 \Omega$$



# Two Parallel Resistors

*For two parallel resistors, the total resistance is determined by:*

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

*Multiplying the top and bottom of each term of the right side of the equation by the other resistor results in:*

$$\begin{aligned}\frac{1}{R_T} &= \left(\frac{R_2}{R_2}\right)\frac{1}{R_1} + \left(\frac{R_1}{R_1}\right)\frac{1}{R_2} = \frac{R_2}{R_1R_2} + \frac{R_1}{R_1R_2} \\ \frac{1}{R_T} &= \frac{R_2 + R_1}{R_1R_2}\end{aligned}$$

$$R_T = \frac{R_1R_2}{R_1 + R_2}$$


*In words, the equation states that*

*the total resistance of two parallel resistors is simply the product of their values divided by their sum.*

**Example (7)**

Determine the total resistance for the parallel combination

In **example (3)**?

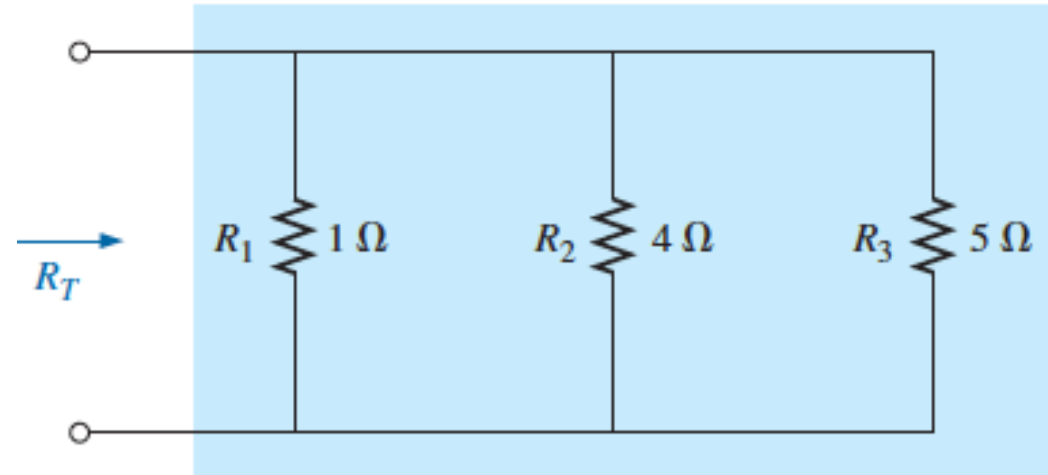
**Solution:**

First the **1 Ω** and **4 Ω** resistors are combined, resulting in the reduced network to figure below:

$$R'_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(1\ \Omega)(4\ \Omega)}{1\ \Omega + 4\ \Omega} = \frac{4}{5}\ \Omega = 0.8$$


Then the equivalent value is applied again to find the total resistance:
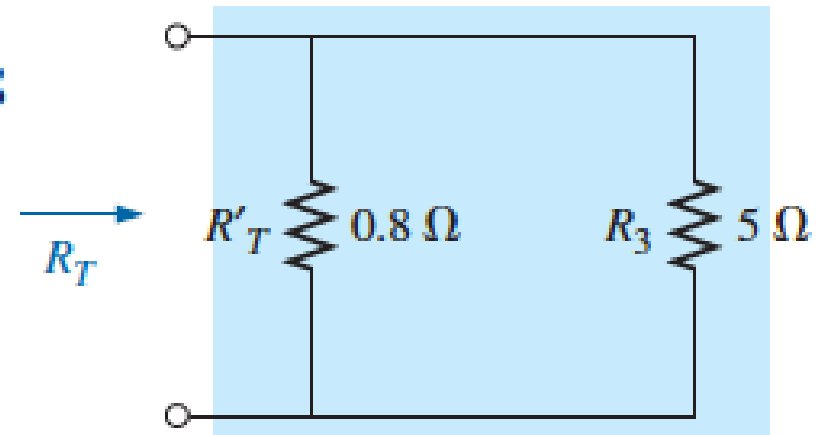
$$R_T = \frac{R'_T R_3}{R'_T + R_3} = \frac{(0.8\ \Omega)(5\ \Omega)}{0.8\ \Omega + 5\ \Omega} = \frac{4}{5.8}\ \Omega = 0.69\ \Omega$$




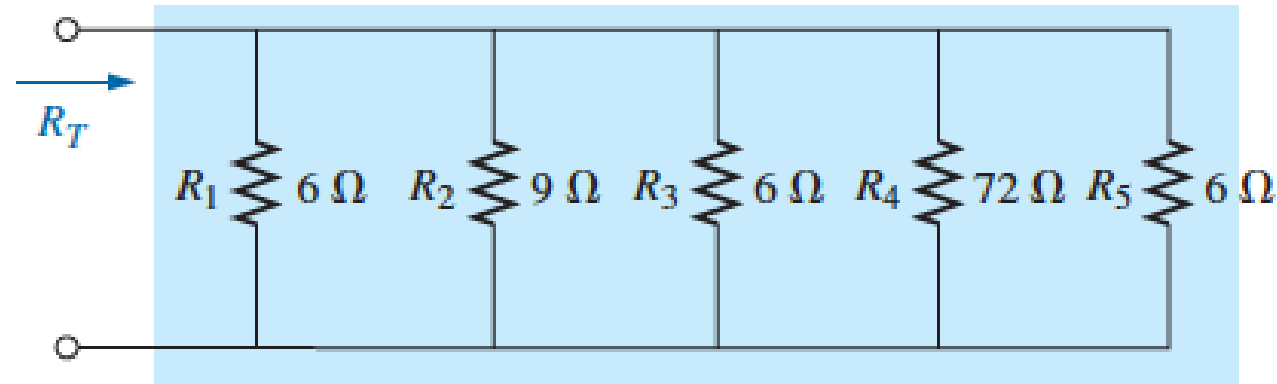**Example (8)**

Determine the total resistance for the parallel combination?



**Solution:**

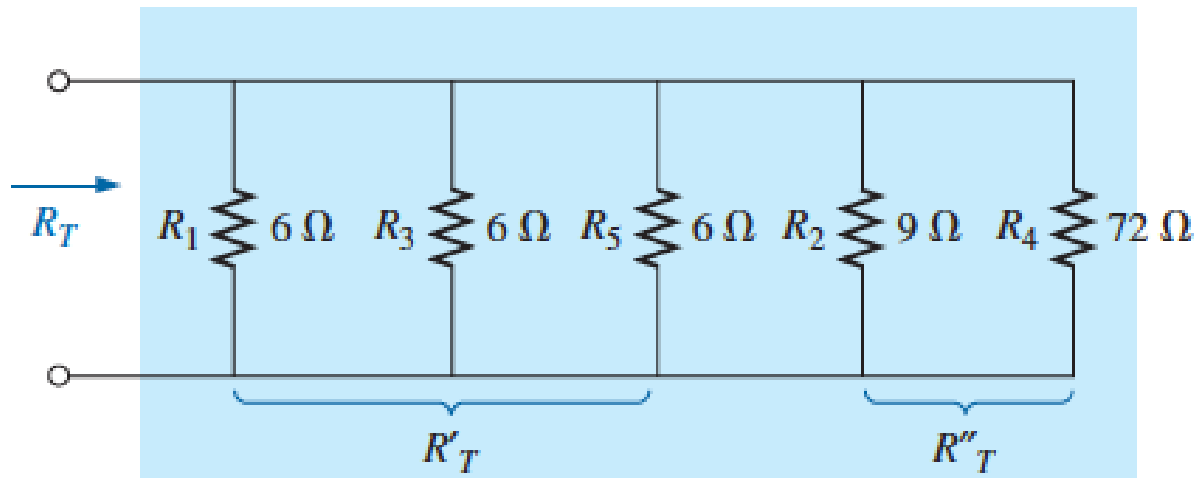

$$R'_T = \frac{R}{N} = \frac{6\ \Omega}{3} = 2\ \Omega$$

$$R''_T = \frac{R_2 R_4}{R_2 + R_4} = \frac{(9\ \Omega)(72\ \Omega)}{9\ \Omega + 72\ \Omega} = \frac{648}{81}\ \Omega = 8\ \Omega$$

$$R_T = \frac{R'_T R''_T}{R'_T + R''_T} = \frac{(2\ \Omega)(8\ \Omega)}{2\ \Omega + 8\ \Omega} = \frac{16}{10}\ \Omega = 1.6\ \Omega$$

# Kirchhoff's Current Law (KCL)

**KCL** states that the algebraic sum of the currents entering and leaving a junction (or region) of a network is **zero**.

**The law can also be stated in the following way:**


**The sum of the currents entering a junction (or region) of a network must equal the sum of the currents leaving the same junction (or region).**

$$\Sigma I_i = \Sigma I_o$$

(Kirchhoff's current law in symbolic form)

for example, the shaded area can enclose an entire system or a complex network, or it can simply provide a connection point (junction) for the displayed currents. In each case, the current entering must equal that leaving
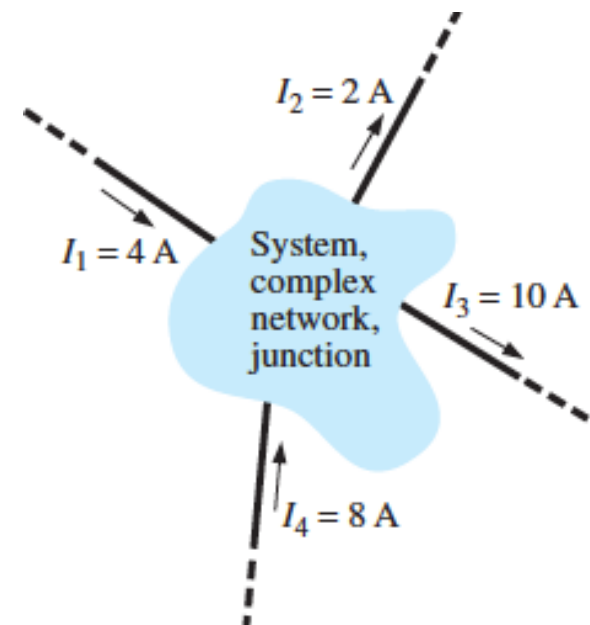
$$\begin{aligned}\Sigma I_i &= \Sigma I_o \\ I_1 + I_4 &= I_2 + I_3 \\ 4 \text{ A} + 8 \text{ A} &= 2 \text{ A} + 10 \text{ A} \\ 12 \text{ A} &= 12 \text{ A} \quad (\text{checks})\end{aligned}$$



**Example (9)**

Determine currents  $I_3$  and  $I_4$  using Kirchhoff's current law.


**Solution:**

At node a:

$$\sum I_i = \sum I_o$$

$$I_1 + I_2 = I_3$$
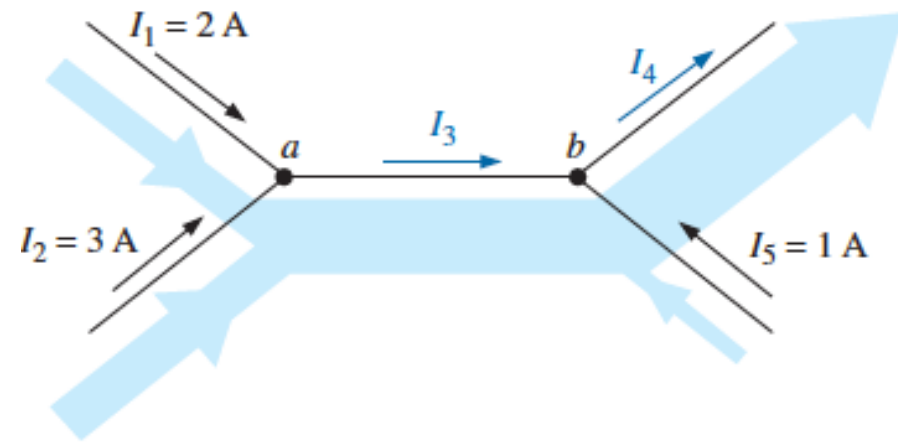
$$2 \text{ A} + 3 \text{ A} = I_3 = 5 \text{ A}$$



At node b, using the result just obtained:

$$\sum I_i = \sum I_o$$

$$I_3 + I_5 = I_4$$

$$5 \text{ A} + 1 \text{ A} = I_4 = 6 \text{ A}$$

**Example (10)**

Determine currents  $I_1$ ,  $I_3$ ,  $I_4$ , and  $I_5$  for the network using Kirchoff's current law.

**Solution:**


At node a:

$$\sum I_i = \sum I_o$$

$$I = I_1 + I_2$$

$$5 \text{ A} = I_1 + 4 \text{ A}$$
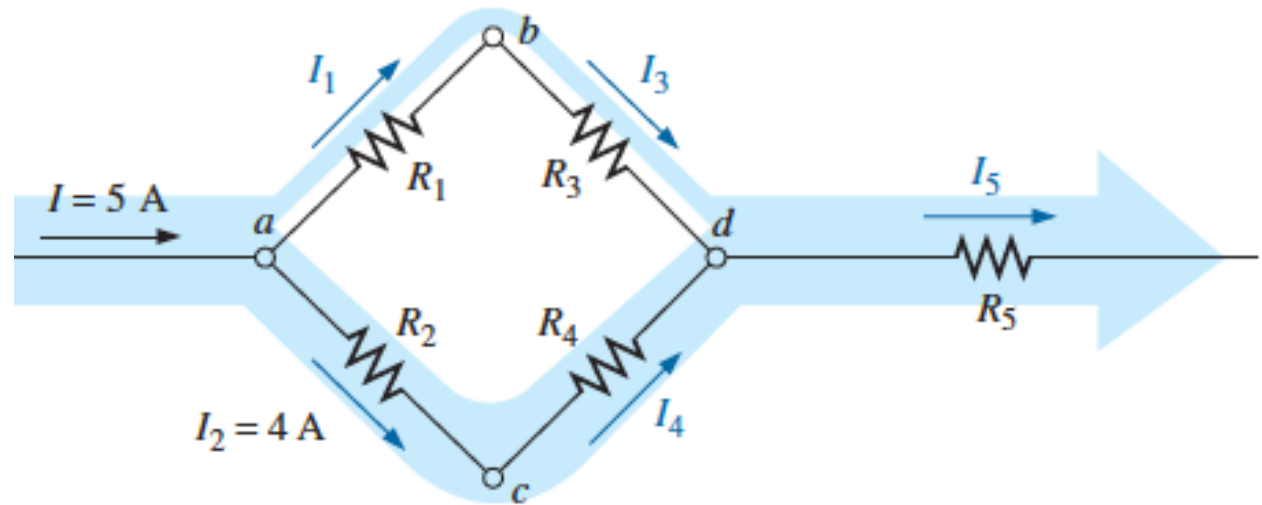
$$I_1 = 5 \text{ A} - 4 \text{ A} = 1 \text{ A}$$



At node b:

$$\sum I_i = \sum I_o$$

$$I_1 = I_3$$

$$I_3 = I_1 = 1 \text{ A}$$

At node c:

$$\sum I_i = \sum I_o$$

$$I_2 = I_4$$

$$I_4 = I_2 = 4 \text{ A}$$

At node d:

$$\sum I_i = \sum I_o$$

$$I_3 + I_4 = I_5$$

$$1 \text{ A} + 4 \text{ A} = I_5 = 5 \text{ A}$$

**Example (11)**

Determine currents  $I_3$  and  $I_5$  for the network using Kirchhoff's current law.

**Solution:**

At node a:

$$\sum I_i = \sum I_o$$

$$I_1 + I_2 = I_3$$

$$4 \text{ A} + 3 \text{ A} = I_3 = 7 \text{ A}$$


At node b:

$$\sum I_i = \sum I_o$$

$$I_3 = I_4 + I_5$$

$$7 \text{ A} = 1 \text{ A} + I_5$$

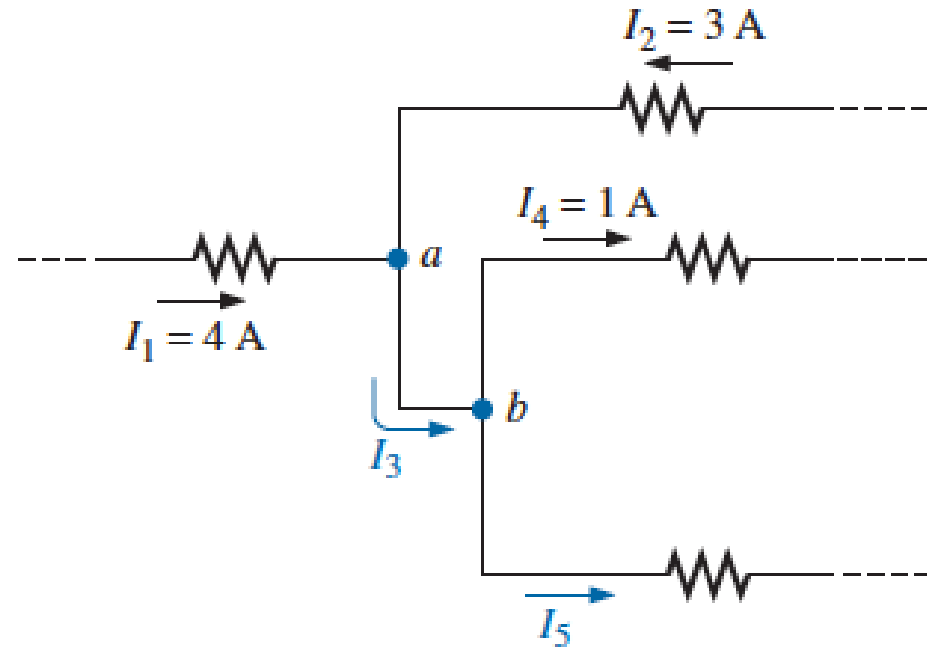
$$I_5 = 7 \text{ A} - 1 \text{ A} = 6 \text{ A}$$



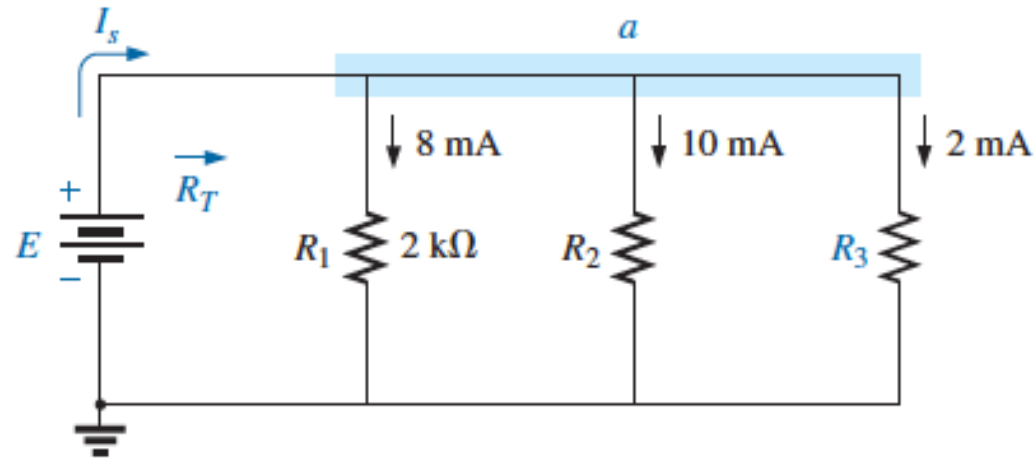**Example (12)**

For the parallel dc network:

- Determine the source current  $I_s$
- Find the source voltage  $E$
- Determine  $R_3$
- Calculate  $R_T$



**Solution:**

a:

$$\sum I_i = \sum I_o$$

$$I_s = I_1 + I_2 + I_3$$

$$I_s = 8 \text{ mA} + 10 \text{ mA} + 2 \text{ mA} = 20 \text{ mA}$$

b:


$$E = V_1 = I_1 R_1 = (8 \text{ mA})(2 \text{ k}\Omega) = 16 \text{ V}$$

c:

$$R_3 = \frac{V_3}{I_3} = \frac{E}{I_3} = \frac{16 \text{ V}}{2 \text{ mA}} = 8 \text{ k}\Omega$$

d:
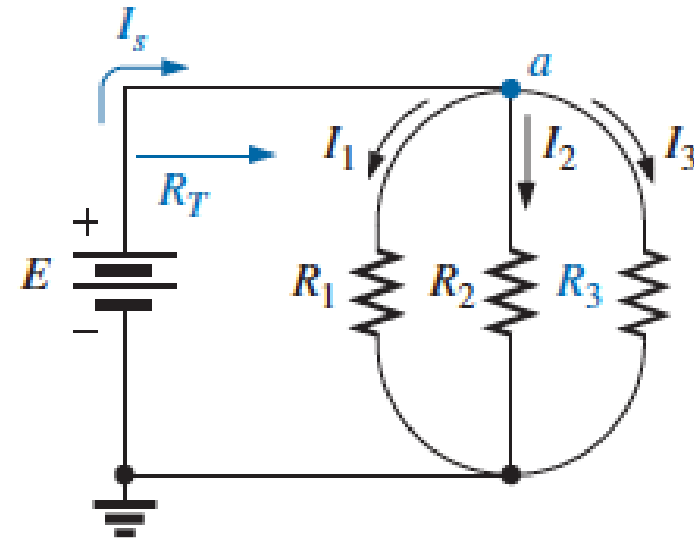
$$R_T = \frac{E}{I_s} = \frac{16 \text{ V}}{20 \text{ mA}} = 0.8 \text{ k}\Omega$$





# Current Divider Rule (CDR)

*We now introduce the equally powerful current divider rule (CDR) for finding the current through a resistor in a parallel circuit.*

- *For two parallel elements of equal value, the current will divide equally.*
- *For parallel elements with different values, the smaller the resistance, the greater the share of input current.*
- *For parallel elements of different values, the current will split with a ratio equal to the inverse of their resistor values.*

*The current through any branch of a parallel resistive network is equal to the total resistance of the parallel network divided by the resistor of interest and multiplied by the total current entering the parallel configuration.*


$$I_x = \frac{R_T}{R_x} I_T$$

# Current Divider Rule (CDR)

The current  $I_T$  splits between the  $N$  parallel resistors and then gathers itself together again at the bottom of the configuration

The current  $I_T$  can then be determined using Ohm's law:

$$I_T = \frac{V}{R_T}$$

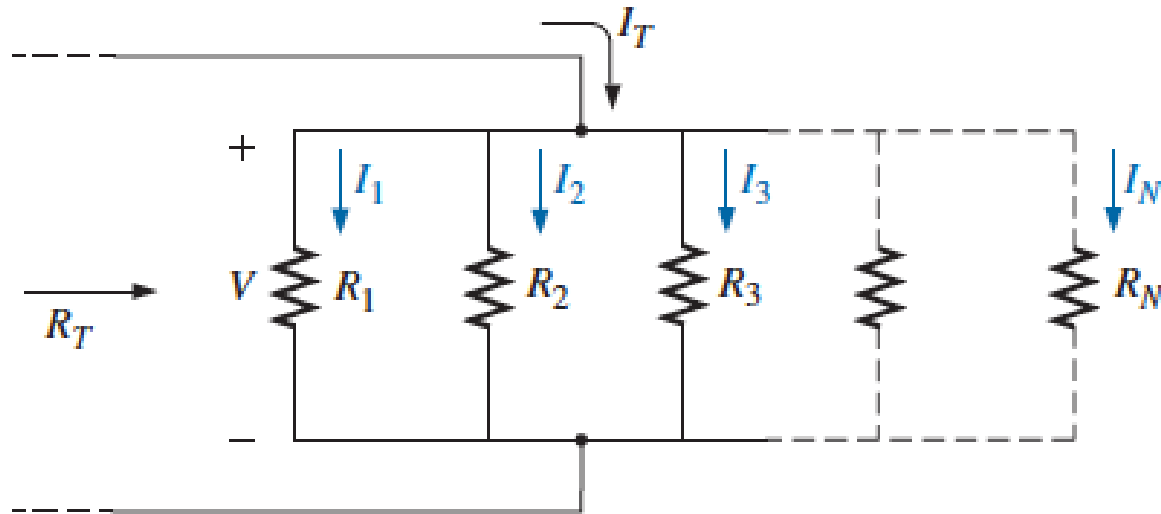

Since the voltage  $V$  is the same across parallel elements, the following is true:

$$V = I_1 R_1 = I_2 R_2 = I_3 R_3 = \dots = I_x R_x$$


where the product  $I_x R_x$  refers to any combination in the series.

Substituting for  $V$  in the above equation for  $I_T$ , we have

$$I_T = \frac{I_x R_x}{R_T}$$

Current Divider Rule:

$$I_x = \frac{R_T}{R_x} I_T$$

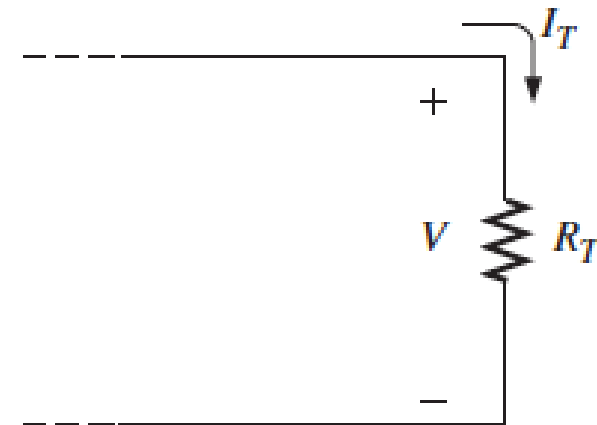

**Example (13)**

For the parallel network, determine current  $I_1$ , Using the current divider rule?

**Solution:**

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


$$= \frac{1}{\frac{1}{1 \text{ k}\Omega} + \frac{1}{10 \text{ k}\Omega} + \frac{1}{22 \text{ k}\Omega}}$$

$$= \frac{1}{1 \times 10^{-3} + 100 \times 10^{-6} + 45.46 \times 10^{-6}}$$

$$= \frac{1}{1.145 \times 10^{-3}} = \mathbf{873.01 \Omega}$$

$$I_1 = \frac{R_T}{R_1} I_T$$
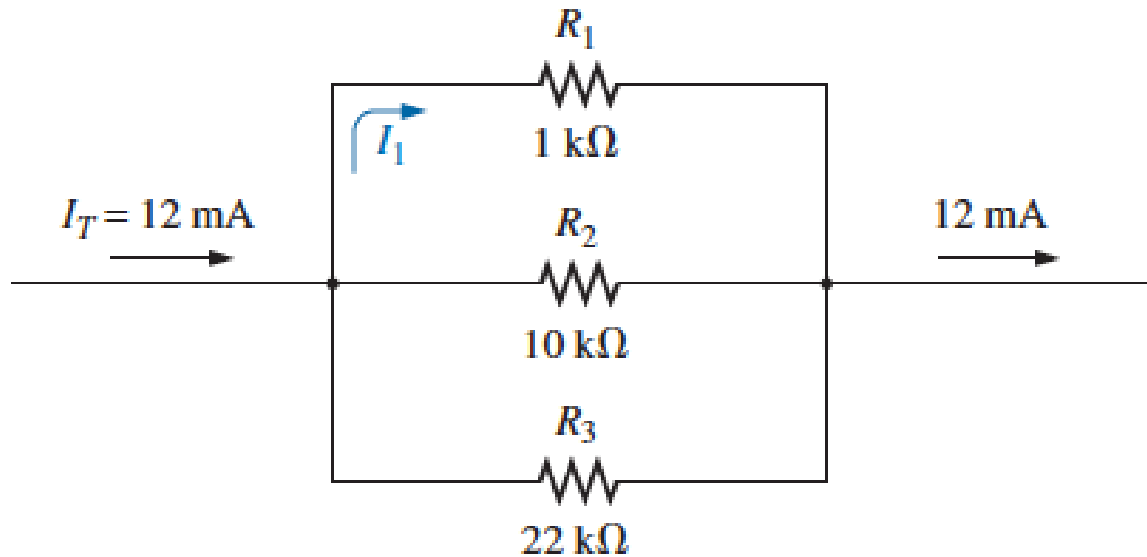
$$= \frac{(873.01 \Omega)}{1 \text{ k}\Omega} (12 \text{ mA}) = (0.873)(12 \text{ mA}) = \mathbf{10.48 \text{ mA}}$$



# Special Case: Two Parallel Resistors

*For the case of two parallel resistors as shown below, the total resistance is determined by*


$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

*Substituting  $R_T$  into Eq. for current  $I_1$  results in*

$$I_1 = \frac{R_T}{R_1} I_T = \left( \frac{R_1 R_2}{R_1 + R_2} \right) \frac{I_T}{R_1}$$

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I_T$$
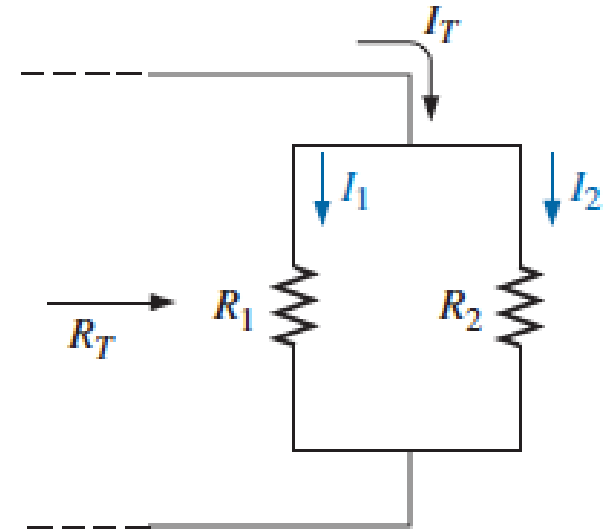
$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I_T$$



*for two parallel resistors, the current through one is equal to the other resistor times the total entering current divided by the sum of the two resistors.*

**Example (14)**

Determine current  $I_2$  for the network using the current divider rule.

**Solution:**

$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I_T$$


$$= \left( \frac{4 \text{ k}\Omega}{4 \text{ k}\Omega + 8 \text{ k}\Omega} \right) 6 \text{ A} = (0.333)(6 \text{ A}) = 2 \text{ A}$$

**or**

$$I_2 = \frac{R_T}{R_2} I_T$$





$$R_T = 4 \text{ k}\Omega \parallel 8 \text{ k}\Omega = \frac{(4 \text{ k}\Omega)(8 \text{ k}\Omega)}{4 \text{ k}\Omega + 8 \text{ k}\Omega} = 2.667 \text{ k}\Omega$$

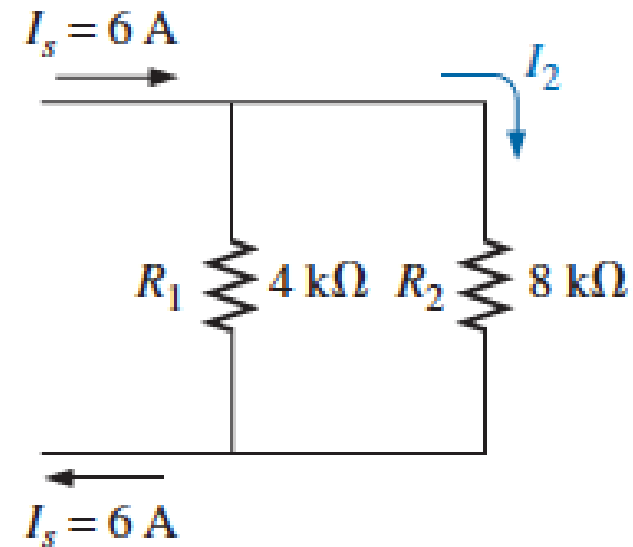
$$I_2 = \left( \frac{2.667 \text{ k}\Omega}{8 \text{ k}\Omega} \right) 6 \text{ A} = (0.333)(6 \text{ A}) = 2 \text{ A}$$


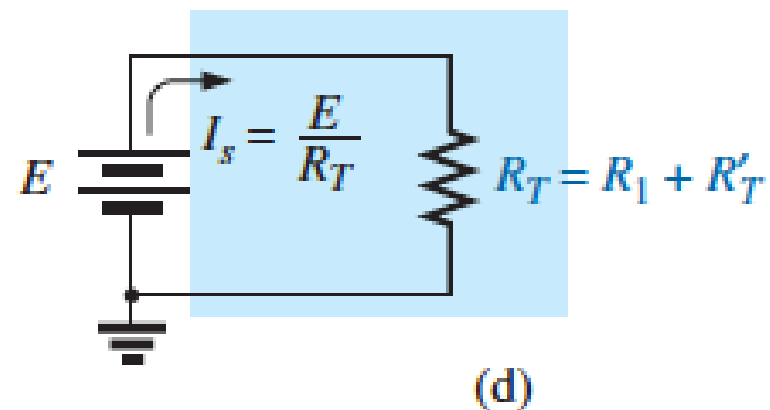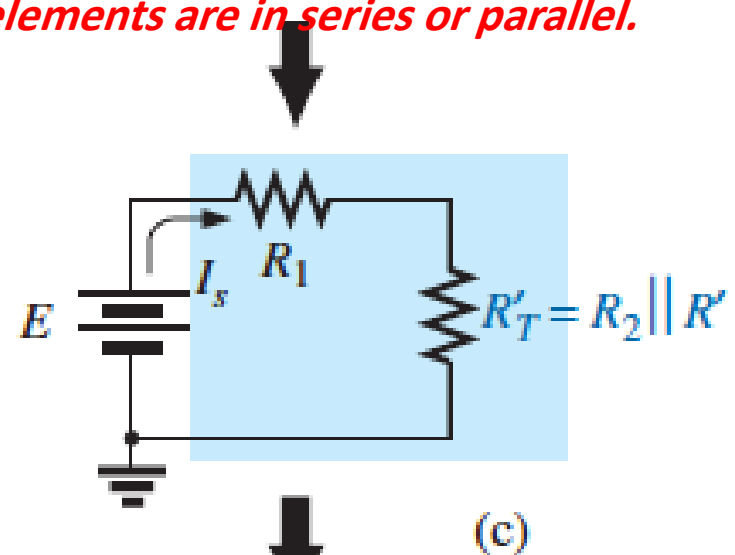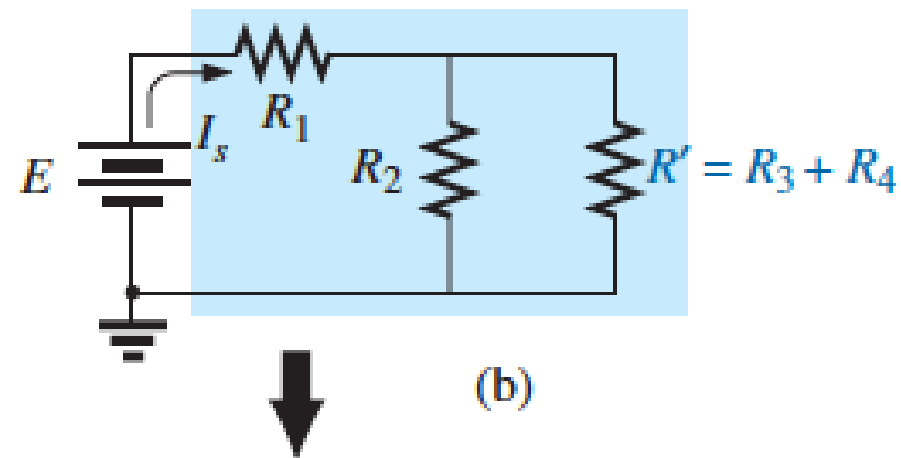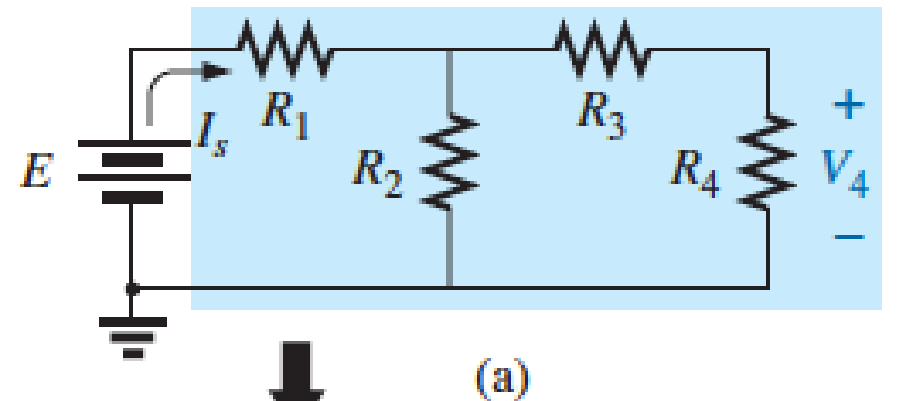
# Series-Parallel Network

- A series-parallel configuration is one that is formed by a combination of series and parallel elements.
- A complex configuration is one in which none of the elements are in series or parallel.



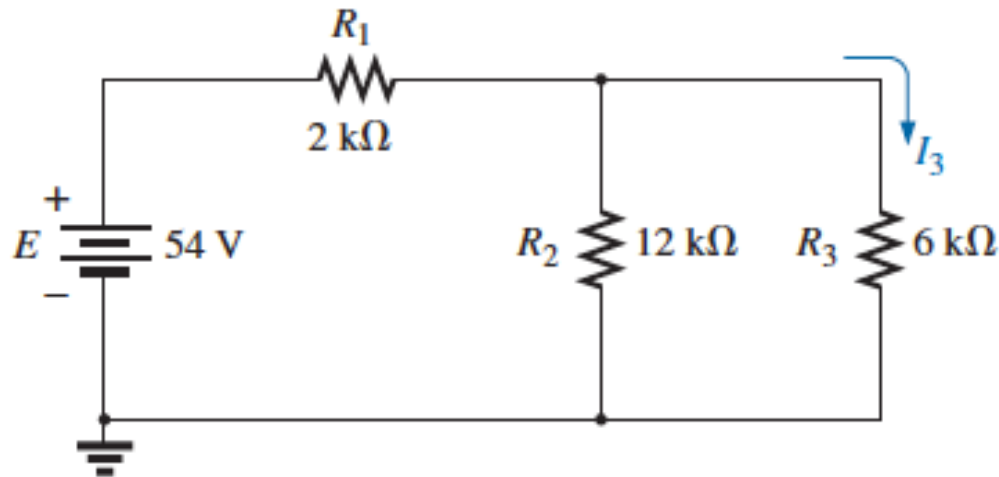**Example (15)**Find current  $I_3$  for the series-parallel network?**Solution:**


$$R' = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(12 \text{ k}\Omega)(6 \text{ k}\Omega)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = 4 \text{ k}\Omega$$

$$R_T = R_1 + R' = 2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$I_s = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}\Omega} = 9 \text{ mA}$$

$$I_1 = I_s = 9 \text{ mA}$$
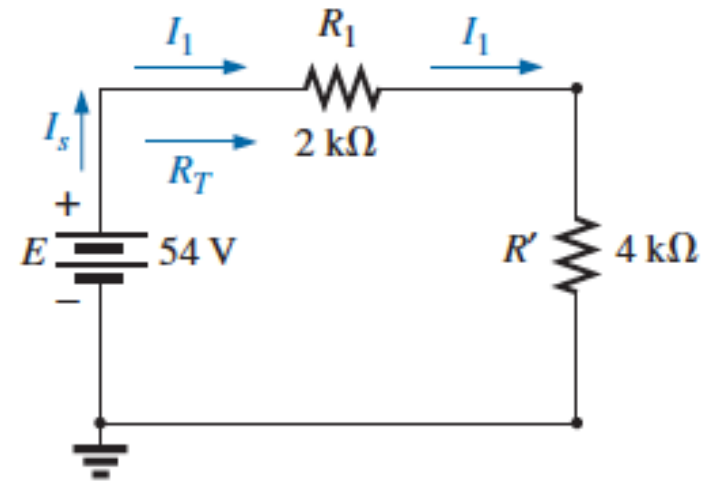
$$I_3 = \left( \frac{R_2}{R_2 + R_3} \right) I_1 = \left( \frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 6 \text{ k}\Omega} \right) 9 \text{ mA} = 6 \text{ mA}$$



**Example (16)**

For the network, determine currents  $I_4$  and  $I_s$  and voltage  $V_2$ .

**Solution:**

$$I_4 = \frac{V_4}{R_4} = \frac{E}{R_4} = \frac{12 \text{ V}}{8.2 \text{ k}\Omega} = 1.46 \text{ mA}$$

$$R' = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

$$= \frac{(18 \text{ k}\Omega)(2 \text{ k}\Omega)}{18 \text{ k}\Omega + 2 \text{ k}\Omega} = 1.8 \text{ k}\Omega$$

$$V_2 = \left( \frac{R'}{R' + R_1} \right) E =$$

$$= \left( \frac{1.8 \text{ k}\Omega}{1.8 \text{ k}\Omega + 6.8 \text{ k}\Omega} \right) 12 \text{ V} = 2.51 \text{ V}$$

$$I_1 = \frac{E}{R_1 + R'} = \frac{12 \text{ V}}{6.8 \text{ k}\Omega + 1.8 \text{ k}\Omega} = 1.40 \text{ mA}$$

$$I_s = I_1 + I_4 = 1.40 \text{ mA} + 1.46 \text{ mA} = 2.86 \text{ mA}$$

