



# Electrical Circuit-I

## 5<sup>th</sup> Lecture

### $\Delta$ - Y & Y - $\Delta$ Conversions

By:


Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

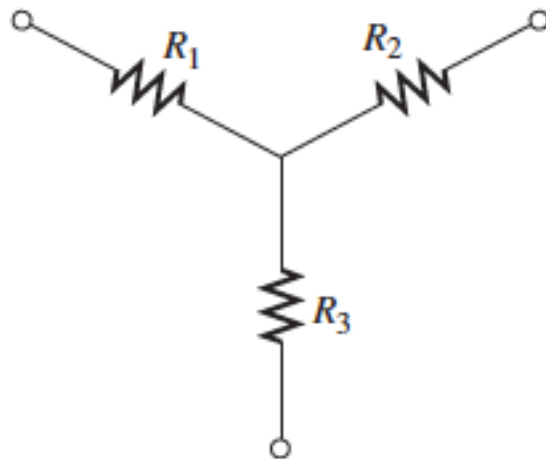
# $\Delta$ - Y & Y - $\Delta$ Conversions

*Circuit configurations are often encountered in which the resistors do not appear to be in series or parallel. Under these conditions, it may be necessary to convert the circuit from one form to another to solve for any unknown quantities if mesh or nodal analysis is not applied.*

*Two circuit configurations that often account for these difficulties are the wye (Y) and delta ( $\Delta$ ) configurations depicted below*



“ Y ”

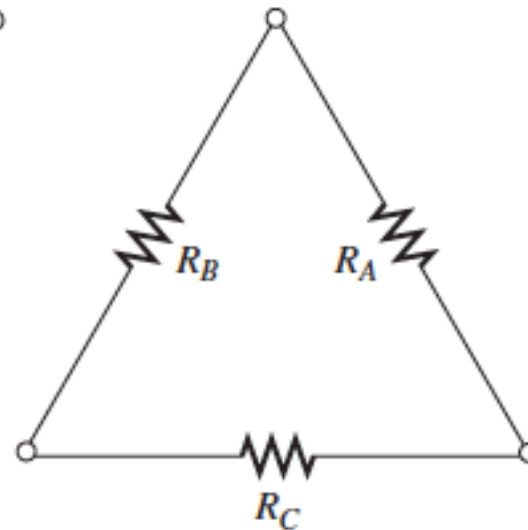

“  $\Delta$  ”


**The purpose of this section is to develop the equations for converting from  $\Delta$  to Y, or vice versa.**

# Delta to Star

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$
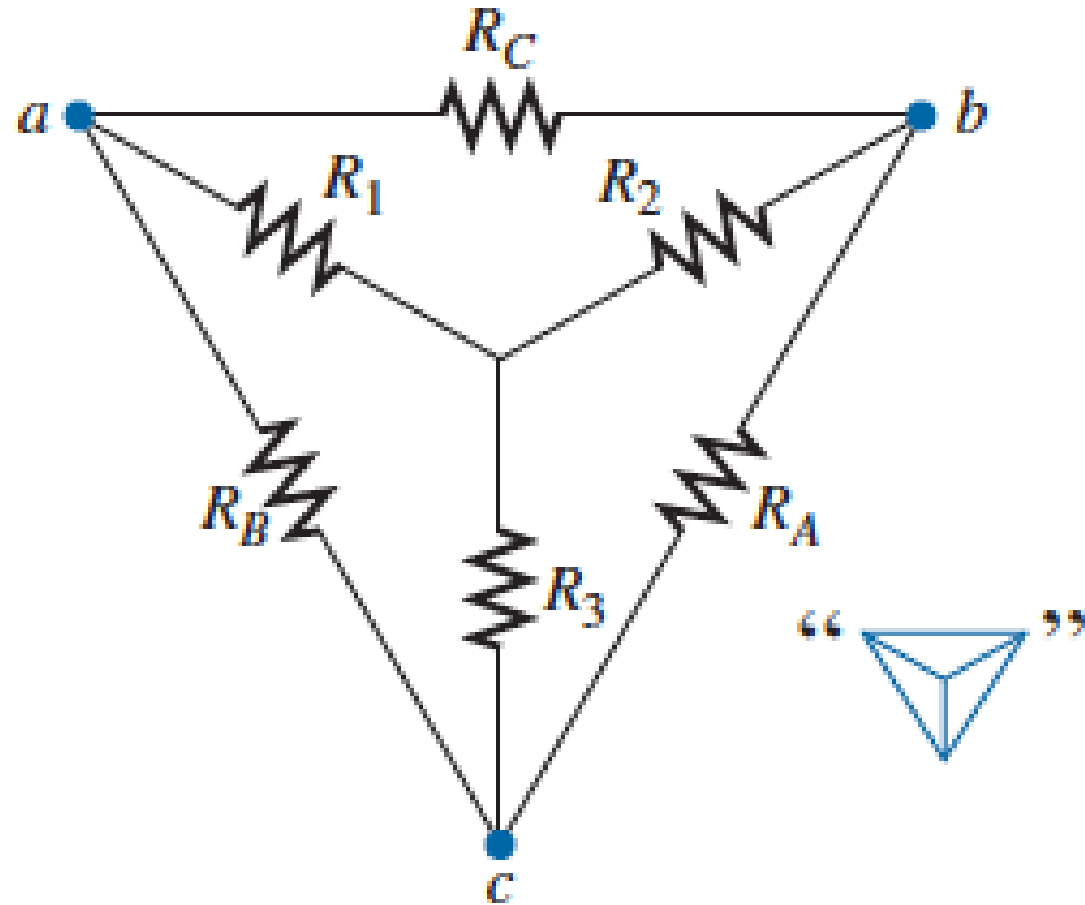
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$




*Note that each resistor of the Y is equal to the product of the resistors in the two closest branches of the  $\Delta$  divided by the sum of the resistors in the  $\Delta$ .*

# Star to Delta

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$
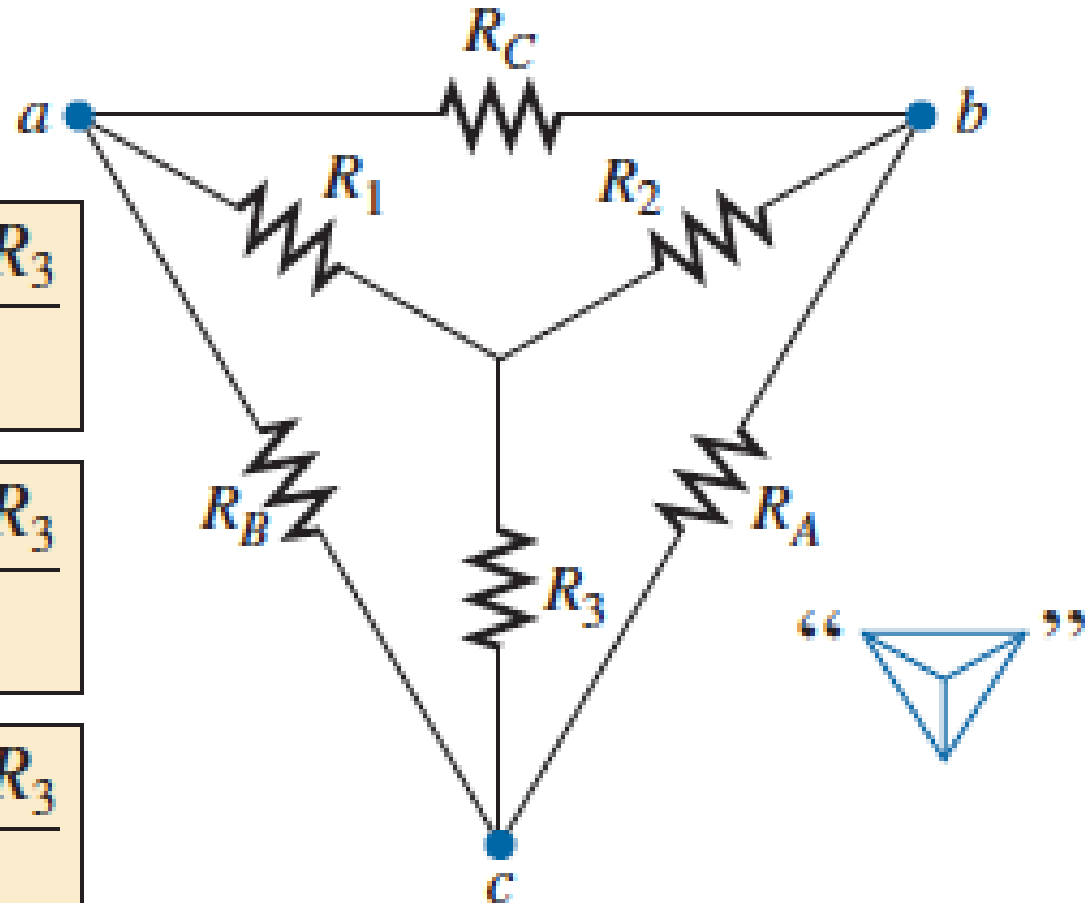
$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$



*Note that the value of each resistor of the  $\Delta$  is equal to the sum of the possible product combinations of the resistances of the Y divided by the resistance of the Y farthest from the resistor to be determined.*

# Star $\longleftrightarrow$ Delta

Let us consider what would occur if all the values of a  $\Delta$  or Y were the same.  
If  $R_A = R_B = R_C$ ,

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{R_A R_A}{R_A + R_A + R_A} = \frac{R_A^2}{3R_A} = \frac{R_A}{3}$$


and, following the same procedure,

$$R_1 = \frac{R_A}{3} \quad R_2 = \frac{R_A}{3}$$

In general, therefore,



$$R_Y = \frac{R_\Delta}{3}$$

$$R_\Delta = 3R_Y$$

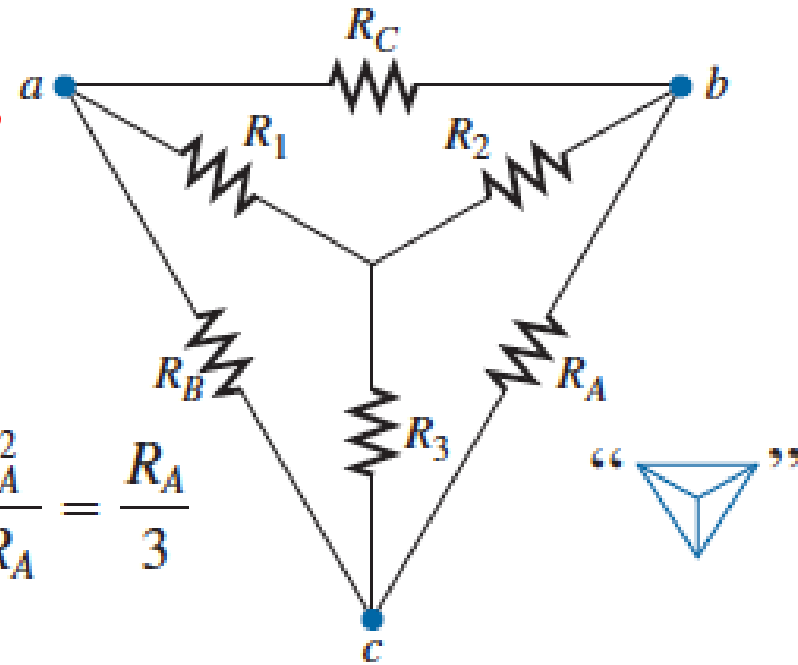

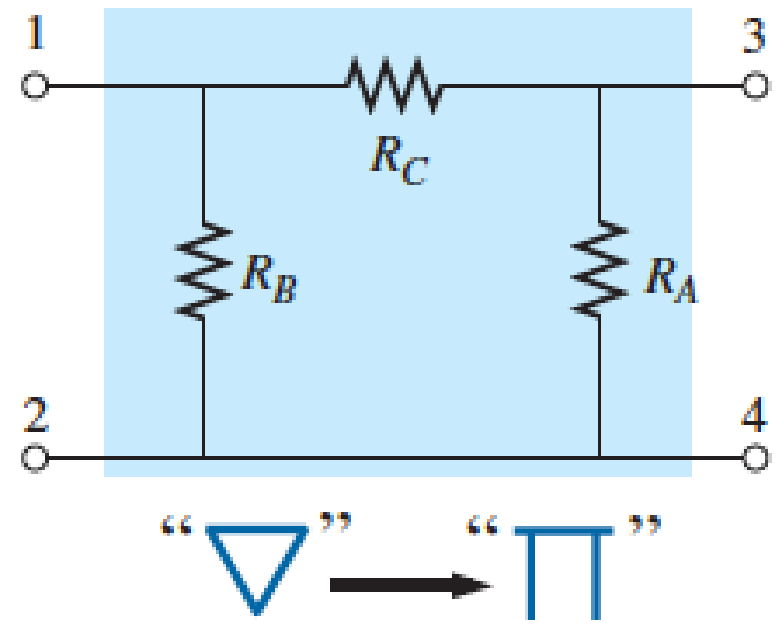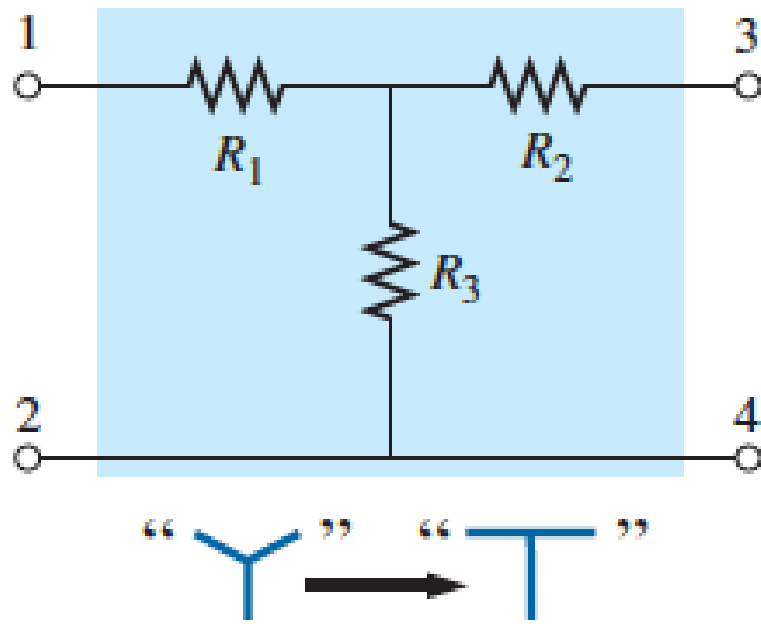
# Star $\longleftrightarrow$ Delta

The  $Y$  and the  $\Delta$  often appear as shown below. They are then referred to as a tee ( $T$ ) and a pi ( $\pi$ ) network, respectively. The equations used to convert from one form to the other are exactly the same as those developed for the  $Y$  and  $\Delta$  transformation.



**Example (1)**

Convert the Δ in Fig. to a Y

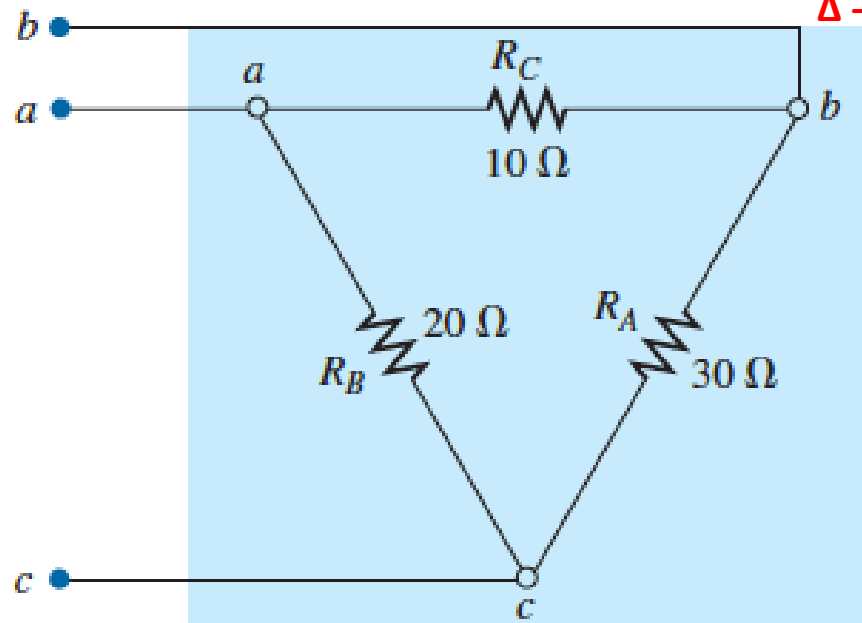


**Solution:**

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(20\ \Omega)(10\ \Omega)}{30\ \Omega + 20\ \Omega + 10\ \Omega} = \frac{200\ \Omega}{60} = 3\frac{1}{3}\ \Omega$$


$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(30\ \Omega)(10\ \Omega)}{60\ \Omega} = \frac{300\ \Omega}{60} = 5\ \Omega$$
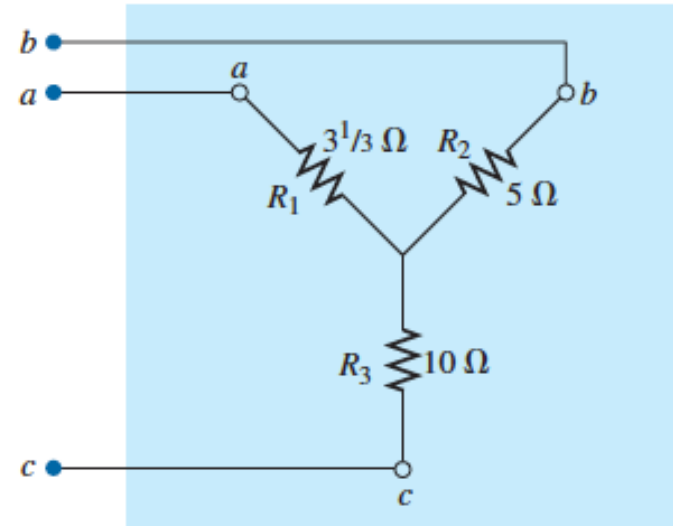
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(20\ \Omega)(30\ \Omega)}{60\ \Omega} = \frac{600\ \Omega}{60} = 10\ \Omega$$



**Example (2)**

**Convert the Y in Fig. to a Δ**

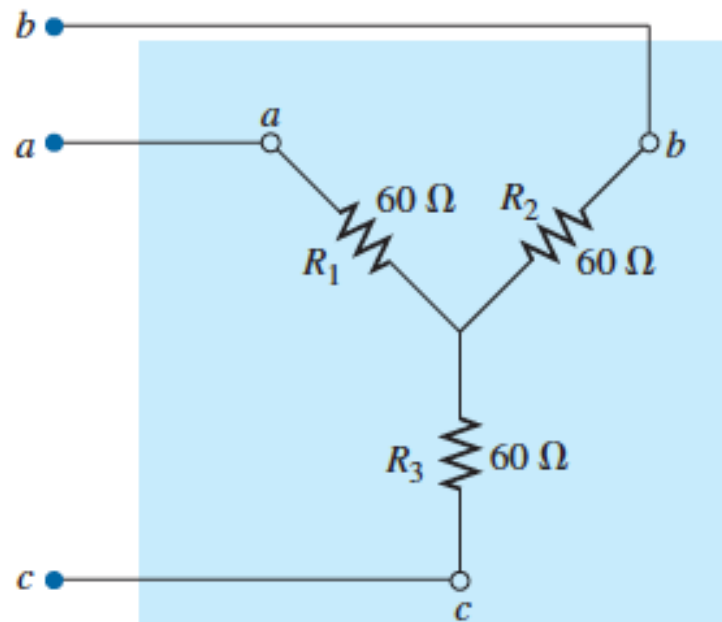


**Solution:**

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$
$$= \frac{(60\ \Omega)(60\ \Omega) + (60\ \Omega)(60\ \Omega) + (60\ \Omega)(60\ \Omega)}{60\ \Omega}$$
$$= \frac{3600\ \Omega + 3600\ \Omega + 3600\ \Omega}{60} = \frac{10,800\ \Omega}{60}$$

$R_A = 180\ \Omega$  **However, the three resistors for the Y are equal**

$$R_\Delta = 3R_Y = 3(60\ \Omega) = 180\ \Omega$$

$$R_B = R_C = 180\ \Omega$$

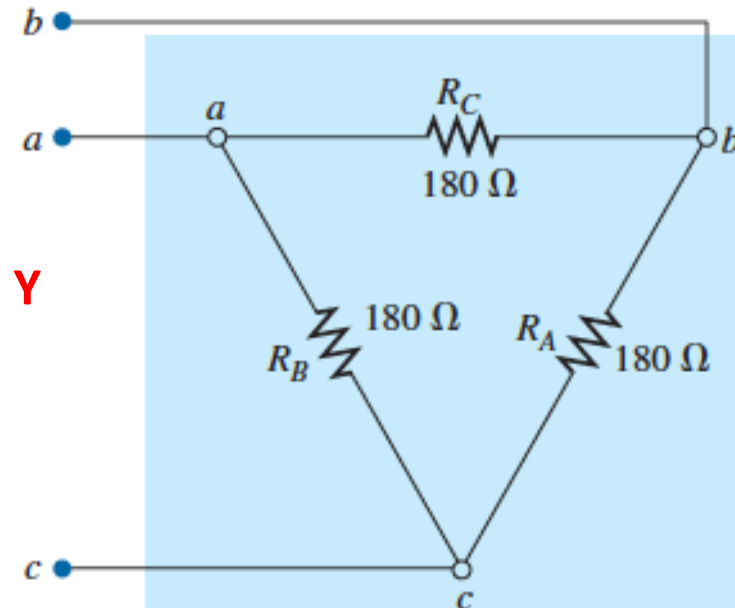




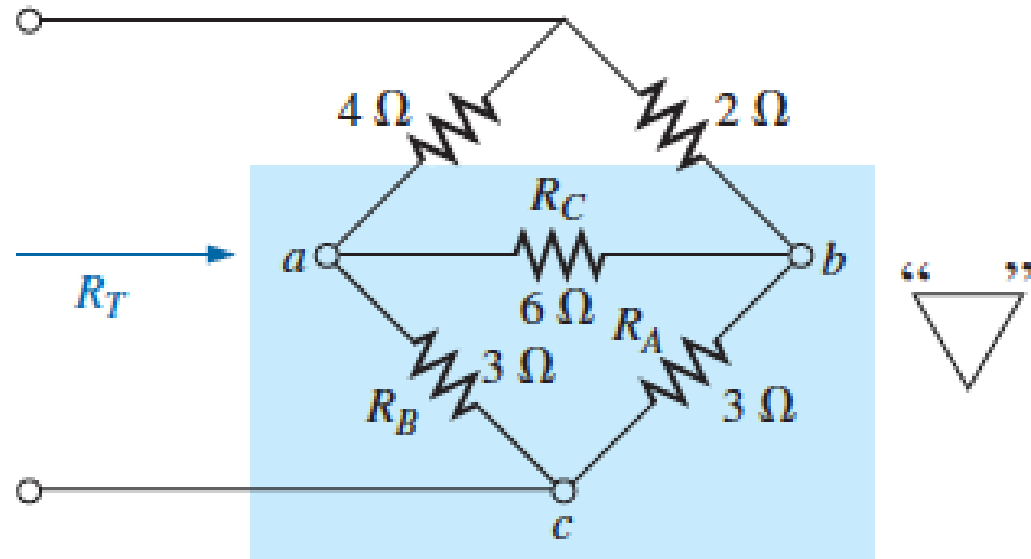**Example (3)**

Find the total resistance of the network, where:

$R_A = 3\Omega, R_B = 3\Omega, \text{ and } R_C = 6\Omega ?$




**Solution:**

Two resistors of the Δ were equal; therefore, two resistors of the Y will be equal.

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3\Omega)(6\Omega)}{3\Omega + 3\Omega + 6\Omega} = \frac{18\Omega}{12} = 1.5\Omega \leftarrow$$
$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3\Omega)(6\Omega)}{12\Omega} = \frac{18\Omega}{12} = 1.5\Omega \leftarrow$$
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3\Omega)(3\Omega)}{12\Omega} = \frac{9\Omega}{12} = 0.75\Omega$$

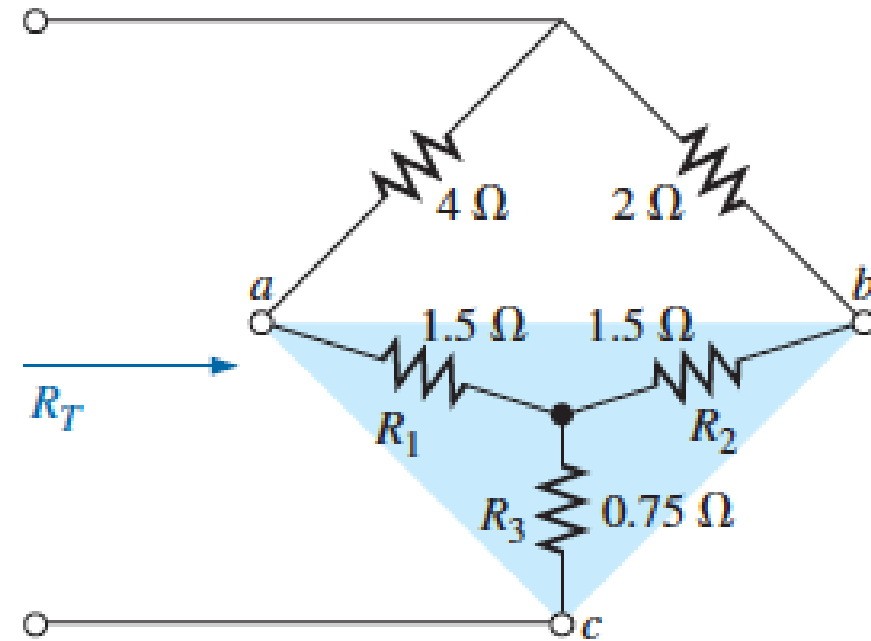**Example (3)**

Replacing the  $\Delta$  by the Y, as shown



$$\begin{aligned} R_T &= 0.75 \Omega + \frac{(4 \Omega + 1.5 \Omega)(2 \Omega + 1.5 \Omega)}{(4 \Omega + 1.5 \Omega) + (2 \Omega + 1.5 \Omega)} \\ &= 0.75 \Omega + \frac{(5.5 \Omega)(3.5 \Omega)}{5.5 \Omega + 3.5 \Omega} \\ &= 0.75 \Omega + 2.139 \Omega \\ R_T &= 2.89 \Omega \end{aligned}$$


### Example (4)

Find the total resistance of the network,

#### Solution:

Since all the resistors of the  $\Delta$  or  $Y$  are the same


a. Converting the  $\Delta$  to a  $Y$ :

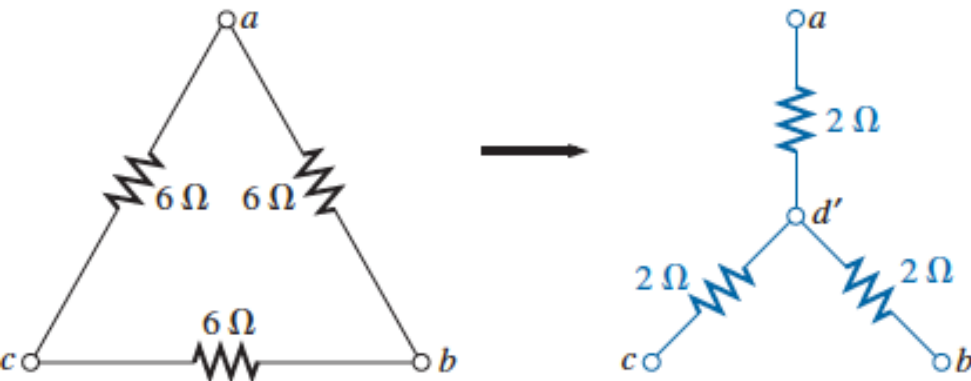


$$R_Y = \frac{R_{\Delta}}{3} = \frac{6 \Omega}{3} = 2 \Omega$$

$$R_T = 2 \left[ \frac{(2 \Omega)(9 \Omega)}{2 \Omega + 9 \Omega} \right] = 3.27 \Omega$$
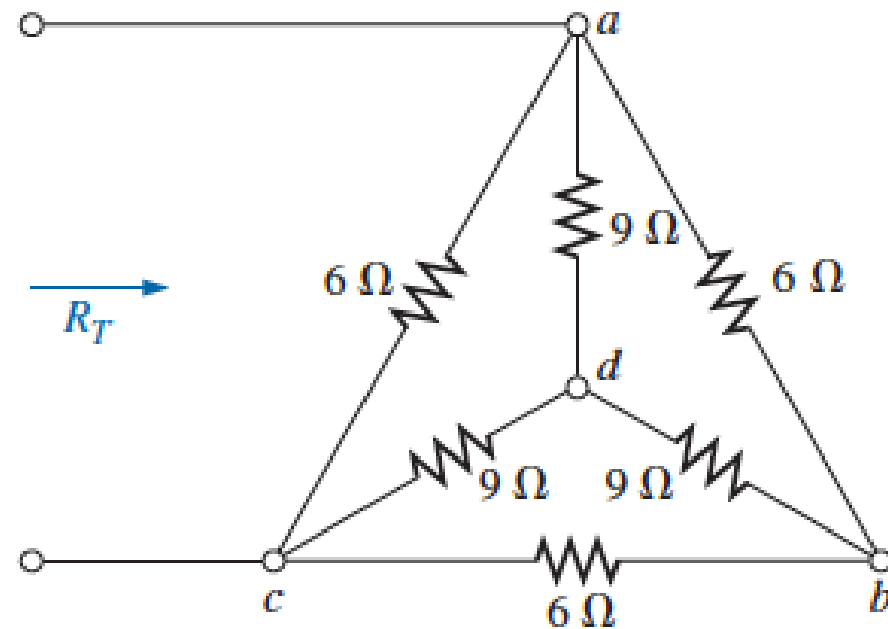
### $\Delta - Y$ & $Y - \Delta$ Conversions



The network then appears as shown

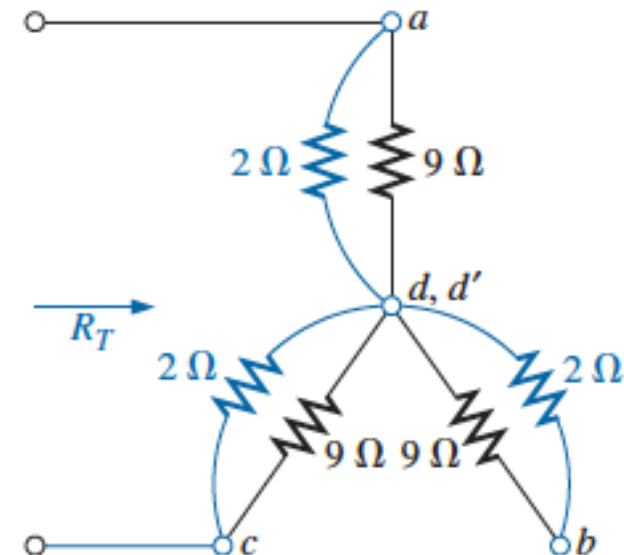

**Example (4)**

**b. Converting the Y to a Δ :**

$$R_{\Delta} = 3R_Y = (3)(9 \Omega) = 27 \Omega$$
$$R'_T = \frac{(6 \Omega)(27 \Omega)}{6 \Omega + 27 \Omega} = \frac{162 \Omega}{33} = 4.91 \Omega$$
$$R_T = \frac{R'_T(R'_T + R'_T)}{R'_T + (R'_T + R'_T)} = \frac{R'_T 2R'_T}{3R'_T} = \frac{2R'_T}{3}$$
$$= \frac{2(4.91 \Omega)}{3} = 3.27 \Omega$$

