



# Electrical Circuit-I

## 7<sup>th</sup> Lecture

### Superposition Theorem

By:

Dr. Ali Abu-Rghaif

**Ref:** Robert L. Boylestad, *INTRODUCTORY CIRCUIT ANALYSIS*, Pearson Prentice Hall, Eleventh Edition, 2007

# Superposition Theorem

*The superposition theorem is unquestionably one of the most powerful in this field. It has such widespread application that people often apply it without recognizing that their maneuvers are valid only because of this theorem.*

*In general, the theorem can be used to do the following:*

➤ *The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.*


*In other words, this theorem allows us to find a solution for a current or voltage using only one source at a time.*

➤ *when removing a voltage source from a network schematic, replace it with a direct connection (short circuit) of zero ohms. Any internal resistance associated with the source must remain in the network.*

➤ *when removing a current source from a network schematic, replace it by an open circuit of infinite ohms. Any internal resistance associated with the source must remain in the network.*
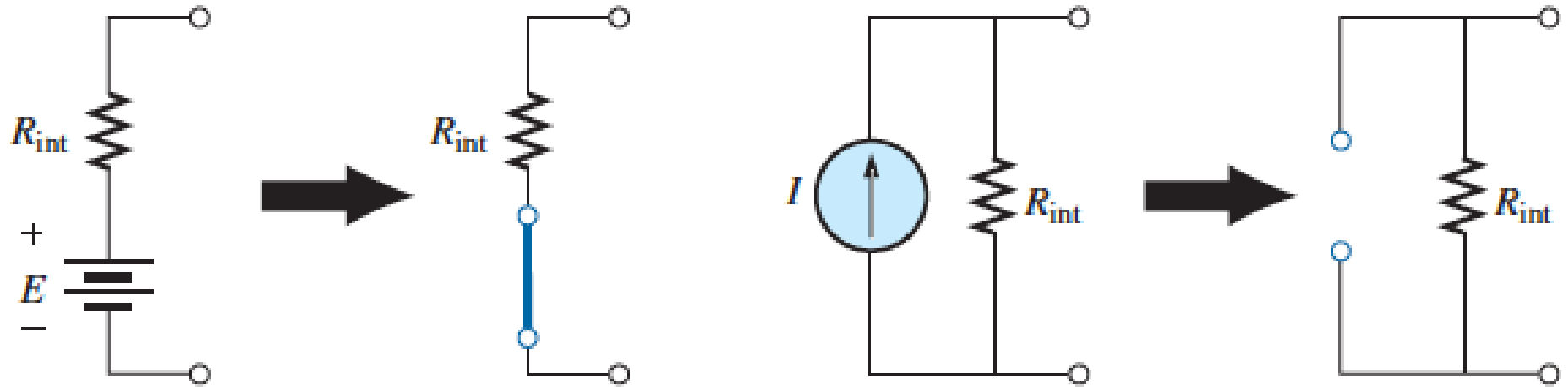
# Superposition Theorem

*The above statements are illustrated below:*



*Since the effect of each source will be determined independently, the number of networks to be analysed will equal the number of sources.*

### **Example (1)**

Using the superposition theorem, determine current  $I_1$  for the network



**Solution:**

First let us determine the effects of the voltage source by setting the current source to zero amperes as shown

$$I'_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{30 \text{ V}}{6 \Omega} = 5 \text{ A}$$

Now for the contribution due to the current source. Setting the voltage source to zero volts results as shown

### **Superposition Theorem**

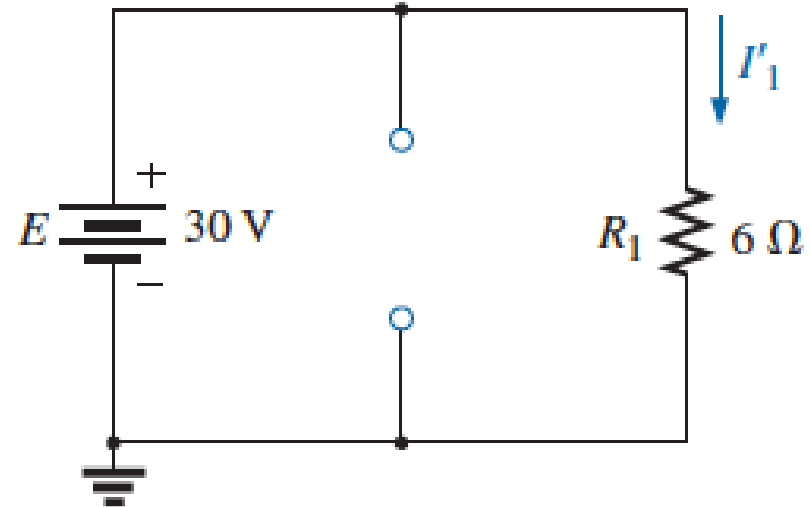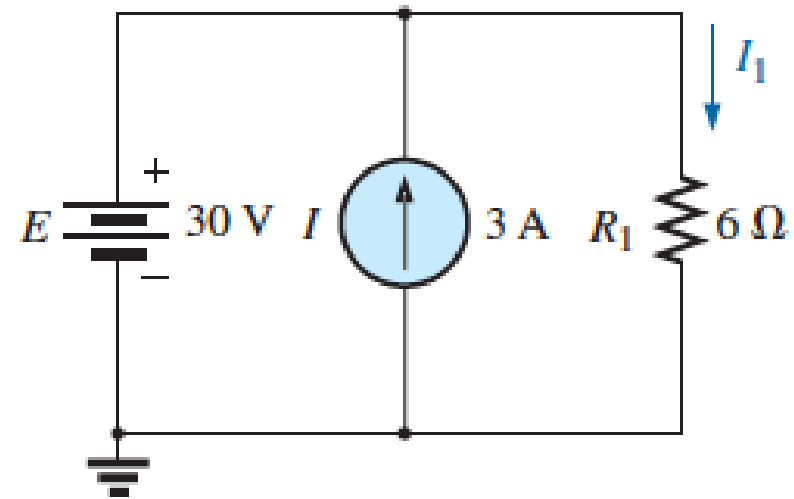

## Example (1)

### Solution:



Now for the contribution due to the current source. Setting the voltage source to zero volts results as shown

$$I''_1 = \frac{R_{sc}I}{R_{sc} + R_1} = \frac{(0 \Omega)I}{0 \Omega + 6 \Omega} = 0 \text{ A}$$

Since  $I'_1$  and  $I''_1$  have the same defined direction the total current is defined by

$$I_1 = I'_1 + I''_1 = 5 \text{ A} + 0 \text{ A} = 5 \text{ A}$$

### Superposition Theorem

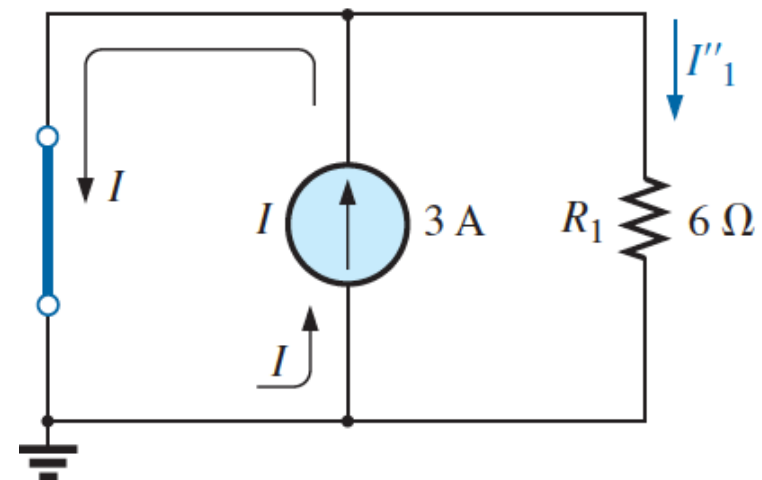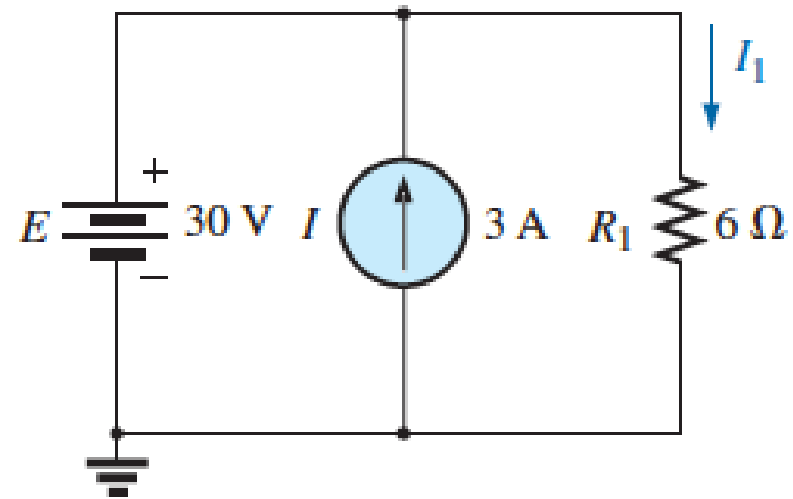



## Superposition Theorem

### Example (2)

Using the superposition theorem, determine the current through the **12  $\Omega$**  resistor

### Solution:

1)  $E_2 = 0$

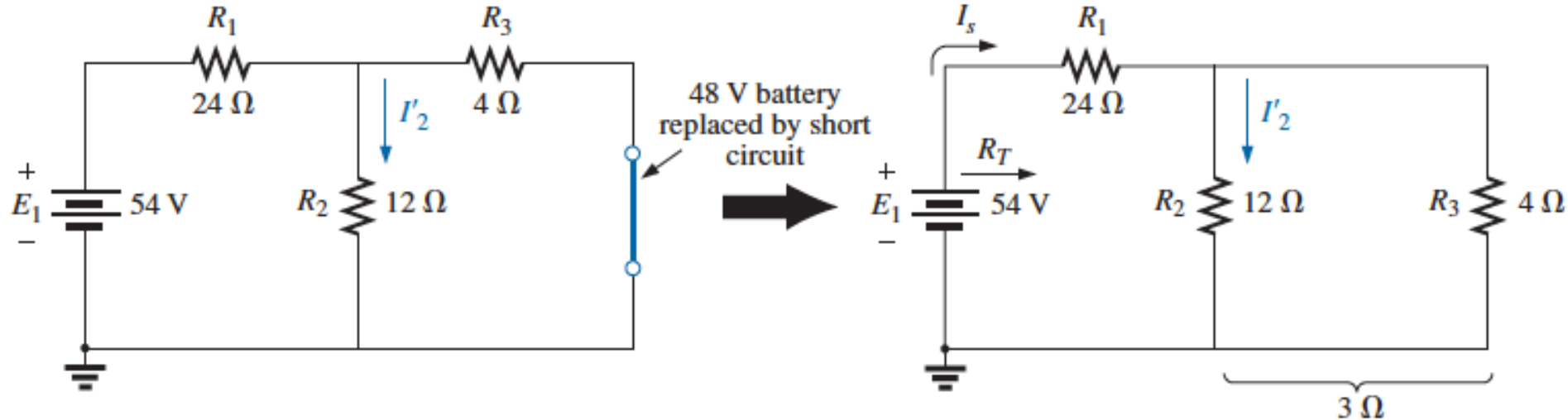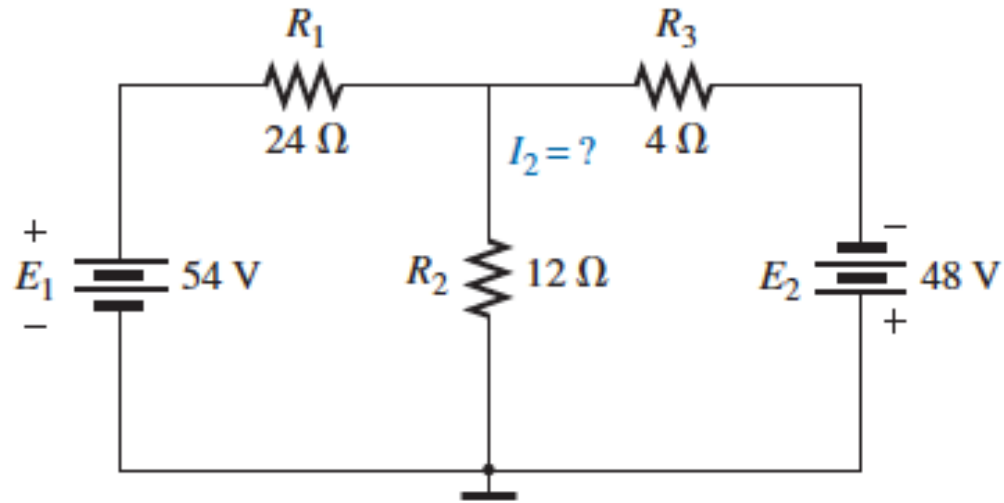


The total resistance seen by the source is therefore

$$R_T = R_1 + R_2 \parallel R_3 = 24 \Omega + 12 \Omega \parallel 4 \Omega = 24 \Omega + 3 \Omega = 27 \Omega$$

$$I_s = \frac{E_1}{R_T} = \frac{54 \text{ V}}{27 \Omega} = 2 \text{ A} \quad \longrightarrow \quad I'_2 = \frac{R_3 I_s}{R_3 + R_2} = \frac{(4 \Omega)(2 \text{ A})}{4 \Omega + 12 \Omega} = 0.5 \text{ A}$$

Example (2)

2)  $E_1 = 0$

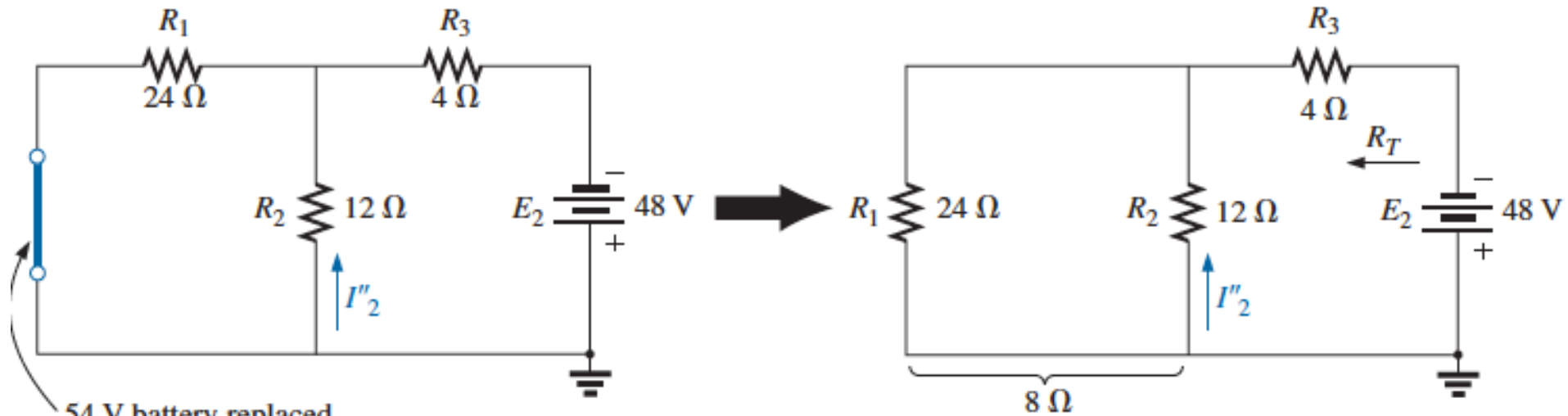


54 V battery replaced by short circuit

The total resistance seen by the source is therefore

$$R_T = R_3 + R_2 \parallel R_1 = 4 \Omega + 12 \Omega \parallel 24 \Omega = 4 \Omega + 8 \Omega = 12 \Omega$$

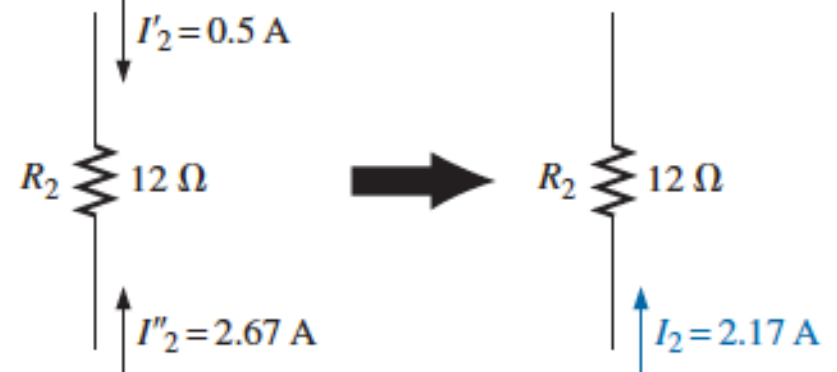
$$I_s = \frac{E_2}{R_T} = \frac{48 \text{ V}}{12 \Omega} = 4 \text{ A} \quad \longrightarrow \quad I''_2 = \frac{R_1(I_s)}{R_1 + R_2} = \frac{(24 \Omega)(4 \text{ A})}{24 \Omega + 12 \Omega} = 2.67 \text{ A}$$



$$I_2 = I''_2 - I'_2 = 2.67 \text{ A} - 0.5 \text{ A} = 2.17 \text{ A}$$

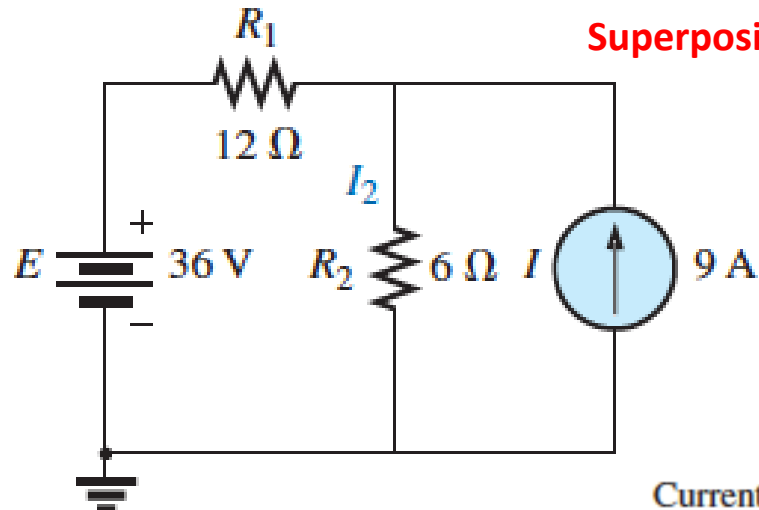**Example (3)**

Using the superposition theorem, determine the current through resistor  $R_2$  for the network



**Solution:**


1)  $I = 0$

$$I'_2 = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{36 \text{ V}}{12 \Omega + 6 \Omega} = \frac{36 \text{ V}}{18 \Omega} = 2 \text{ A}$$


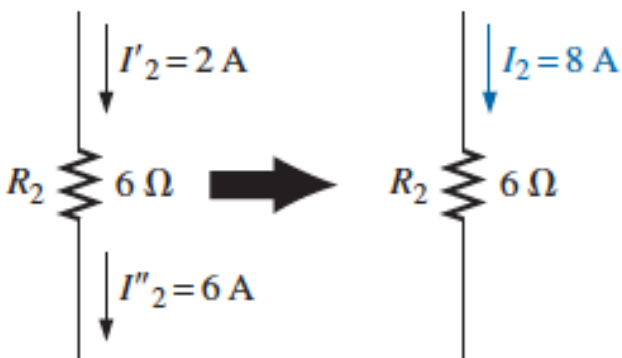
2)  $E = 0$

$$I''_2 = \frac{R_1(I)}{R_1 + R_2} = \frac{(12 \Omega)(9 \text{ A})}{12 \Omega + 6 \Omega} = 6 \text{ A}$$

$$I_2 = I'_2 + I''_2 = 2 \text{ A} + 6 \text{ A} = 8 \text{ A}$$



Current source replaced by open circuit

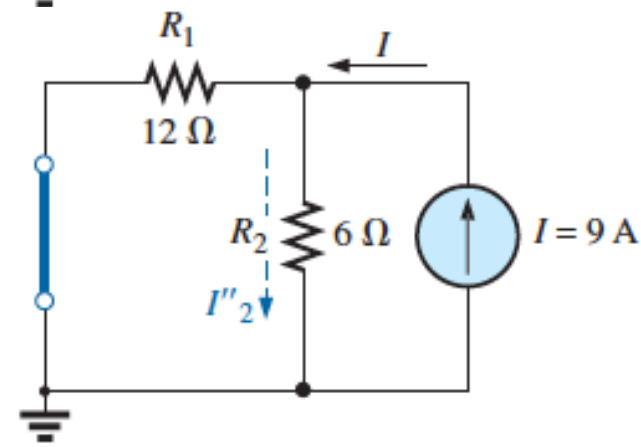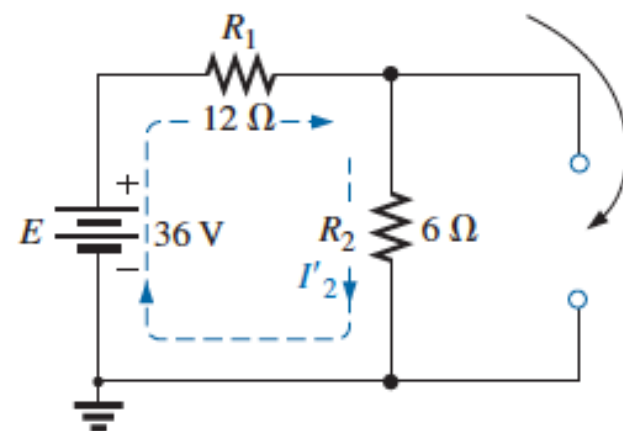





**Example (4)**

Using the principle of superposition, find the current  $I_2$  through the  $12\text{ k}\Omega$  resistor

**Solution:**



1)  $E = 0$

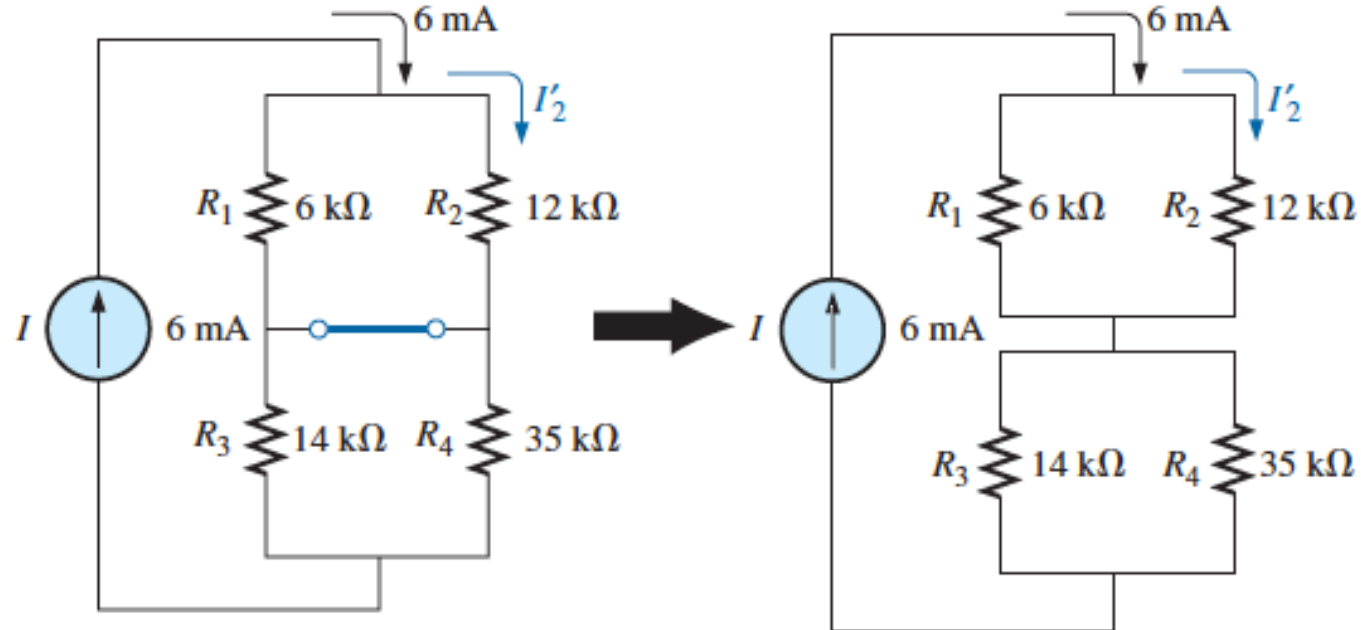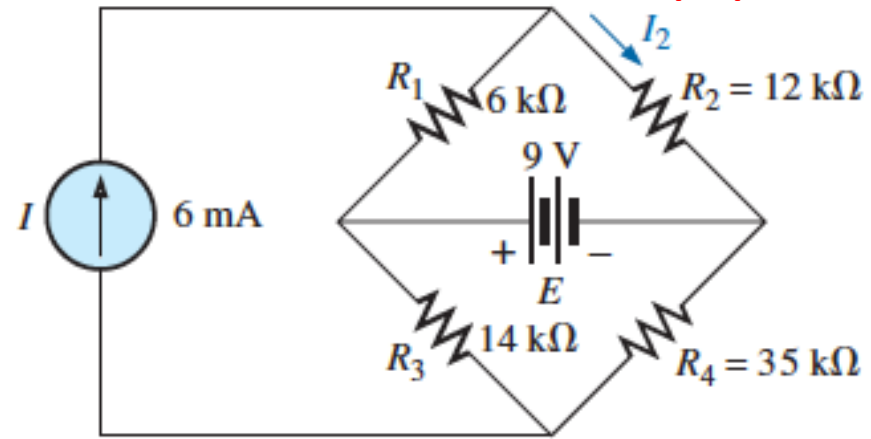

$$I'_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(6\text{ k}\Omega)(6\text{ mA})}{6\text{ k}\Omega + 12\text{ k}\Omega} = 2\text{ mA}$$

### Example (4)

2)  $I = 0$

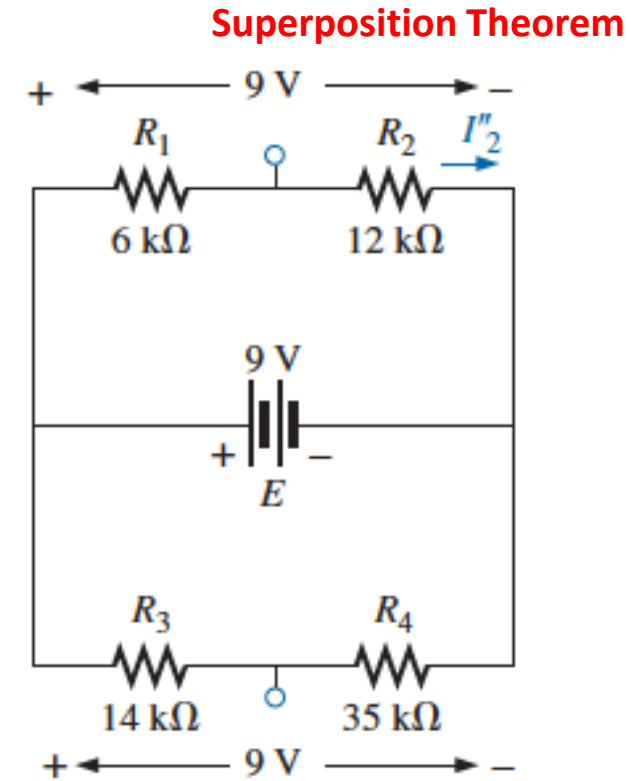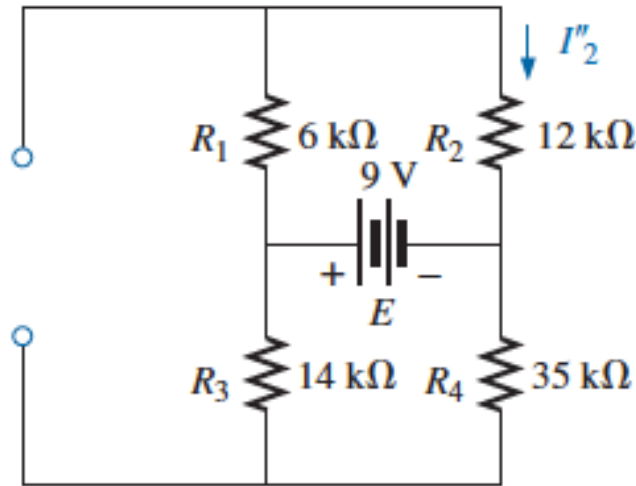

$$I''_2 = \frac{E}{R_1 + R_2} = \frac{9\text{ V}}{6\text{ k}\Omega + 12\text{ k}\Omega} = 0.5\text{ mA}$$

*Since  $I'_2$  and  $I''_2$  have the same direction through  $R_2$ , the desired current is the sum of the two:*

$$\begin{aligned} I_2 &= I'_2 + I''_2 \\ &= 2\text{ mA} + 0.5\text{ mA} \\ &= 2.5\text{ mA} \end{aligned}$$



**Example (5)**

Find the current through the **2 Ω** resistor of the network

**Solution:**

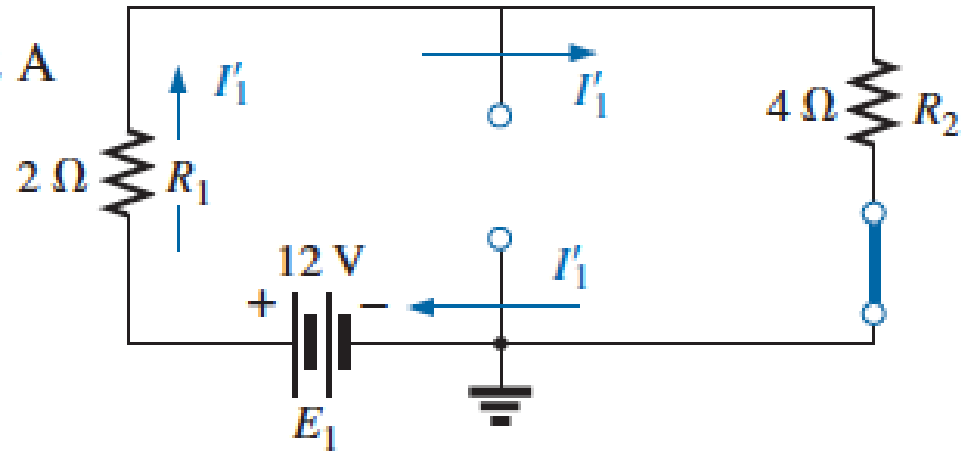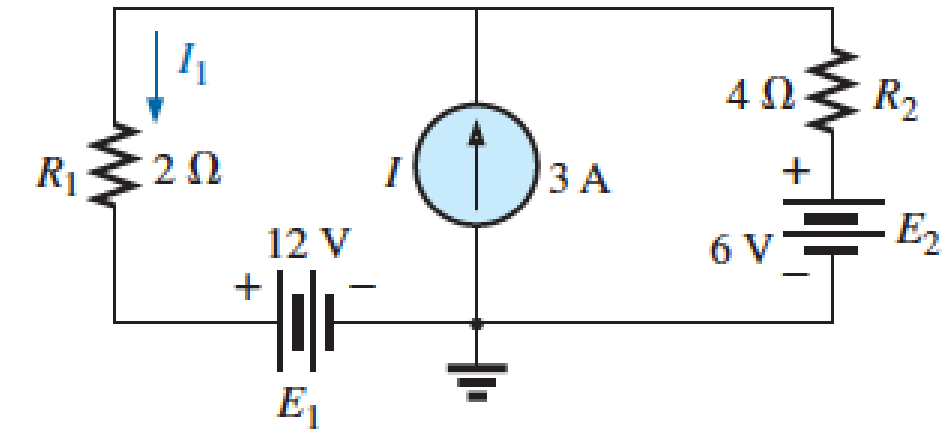
1)  $I = 0$  and  $E_2 = 0$

$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12 \text{ V}}{2 \Omega + 4 \Omega} = \frac{12 \text{ V}}{6 \Omega} = 2 \text{ A}$$



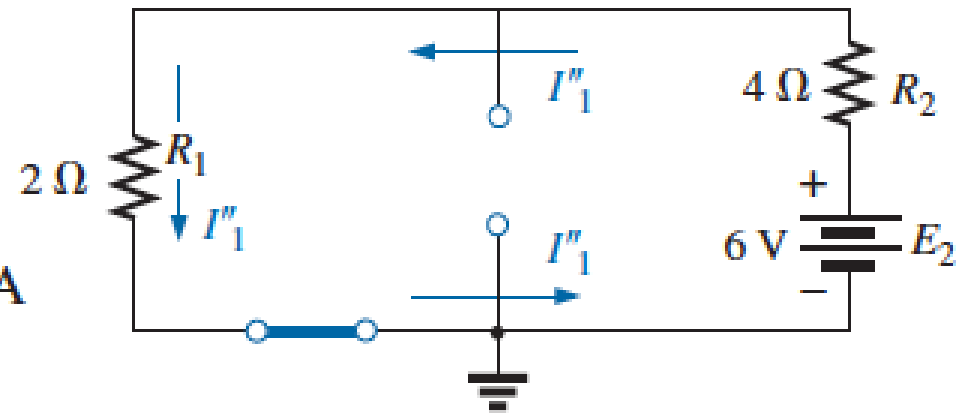2)  $I = 0$  and  $E_1 = 0$


$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6 \text{ V}}{2 \Omega + 4 \Omega} = \frac{6 \text{ V}}{6 \Omega} = 1 \text{ A}$$



**Example (5)**

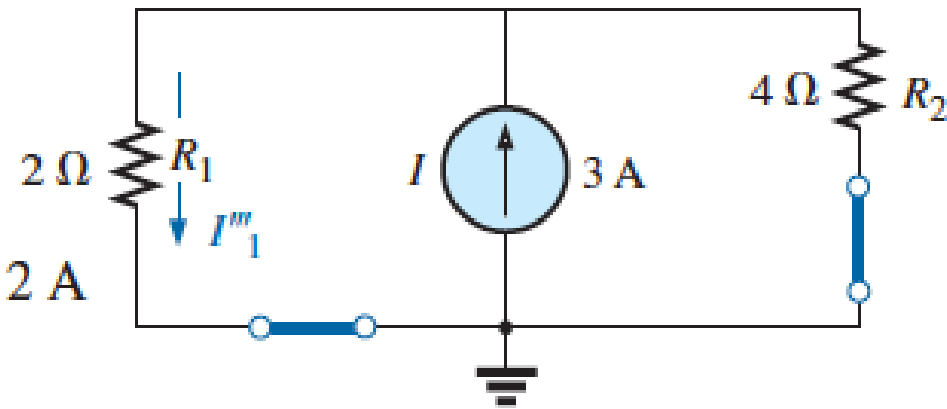3)  $E_1 = 0$  and  $E_2 = 0$

$$I'''_1 = \frac{R_2 I}{R_1 + R_2} = \frac{(4 \Omega)(3 \text{ A})}{2 \Omega + 4 \Omega} = \frac{12 \text{ A}}{6} = 2 \text{ A}$$



**The total current through the 2 Ω resistor**

Same direction as  $I_1$  in Fig. 9.18

Opposite direction to  $I_1$  in Fig. 9.18

$$I_1 = \overbrace{I''_1 + I'''_1} - I'_1 = 1 \text{ A} + 2 \text{ A} - 2 \text{ A} = 1 \text{ A}$$

