

## Chapter 3: Zener Diodes Circuits

The Zener model to be employed for the “on” state will be as shown in Figure a. For the “off” state as defined by a voltage less than  $V_Z$  but greater than 0 V with the polarity indicated in Figure 3.1-b, the Zener equivalent is the open circuit that appears in the same figure

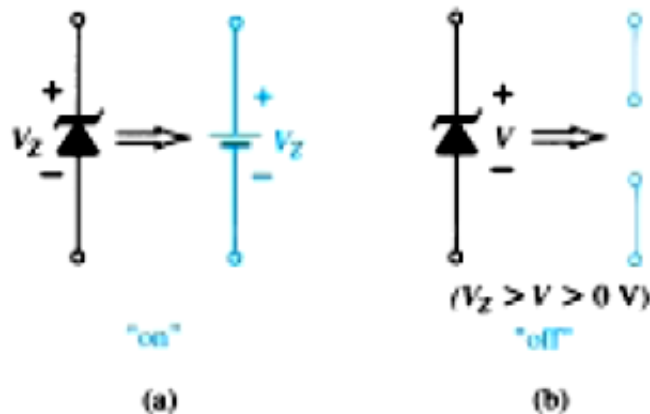


Figure 3.1 : Zener diode equivalents for the (a) “on” and (b) “off” states.

The simplest Zener diode circuit appears in Figure 3.2.


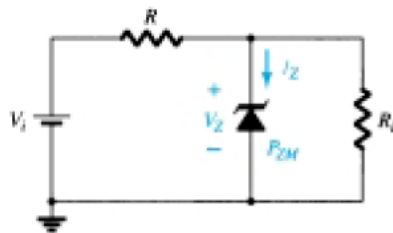


Figure 3.2: Basic Zener diode regulator.

### 3.1 Fixed $V_i$ and $R_L$

The analysis can fundamentally be broken down into two steps:

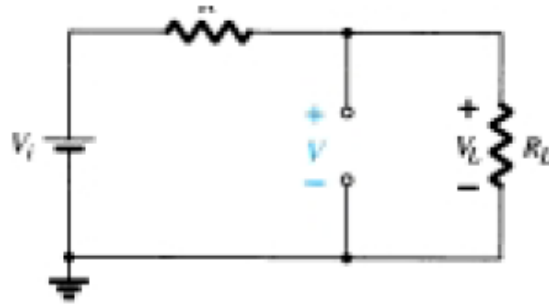
1. Determine the state of the Zener diode by removing it from the network and calculating the voltage across the resulting open circuit, as shown below:



Using voltage divider rule:

$$V = V_L = \frac{R_L V_i}{R + R_L}$$

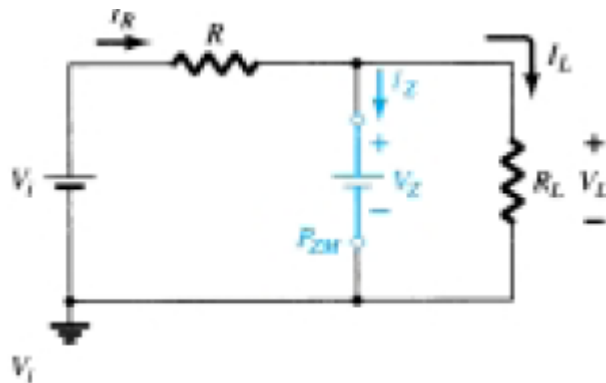- If  $V \geq V_Z$ , the Zener diode is “on” and the equivalent model of Figure a can be substituted.
  - If  $V < V_Z$ , the diode is “off” and the open-circuit equivalence of Figure b is substituted.
2. Substitute the appropriate equivalent circuit (Figure a or b) and solve for the desired unknowns.
- If the diode is ON:



Then

$$V_L = V_Z$$

Apply KCL to find  $I_Z$ :

$$I_R = I_Z + I_L$$

$$I_Z = I_R - I_L$$

Where,

$$I_L = \frac{V_L}{R_L} \quad \text{and} \quad I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$


The power dissipated by the Zener diode is determined by

$$P_Z = V_Z I_Z$$

Which must be less than the  $P_{ZM}$  (Maximum Zener Power) specified for the device.

**Example 1:** (a) For the Zener diode network of Figure 3.3, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ .

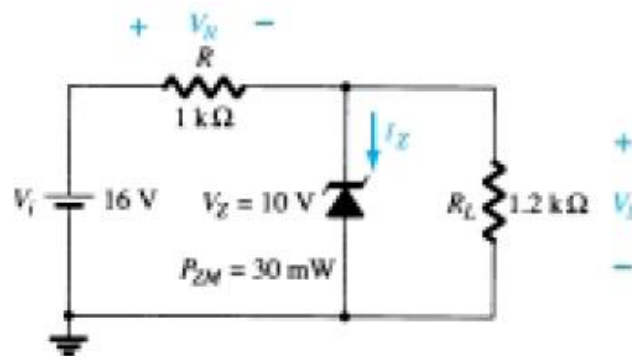(b) Repeat part (a) with  $R_L = 3 \text{ k}\Omega$ .




**Solution:**

**Part (a):**

$$V = \frac{R_L V_i}{R + R_L} = \frac{1.2 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 8.73 \text{ V}$$

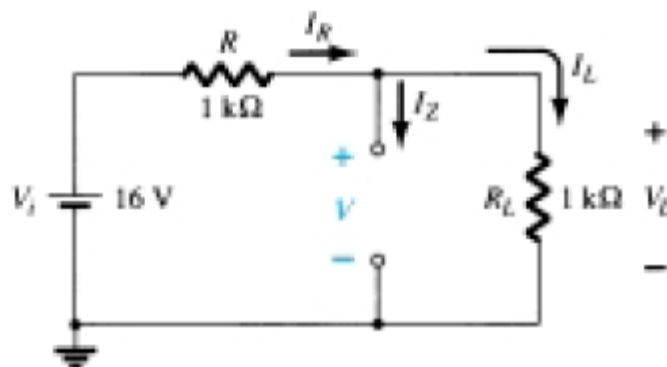**Since  $V < V_Z$ ; the diode is OFF and the resultant circuit will be**



$$V_L = V = 8.73 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 8.73 \text{ V} = 7.27 \text{ V}$$


$$I_Z = 0 \text{ A}$$

$$P_Z = V_Z I_Z = V_Z (0 \text{ A}) = 0 \text{ W}$$

**Part (b):**

$$V = \frac{R_L V_i}{R + R_L} = \frac{3 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 12 \text{ V}$$

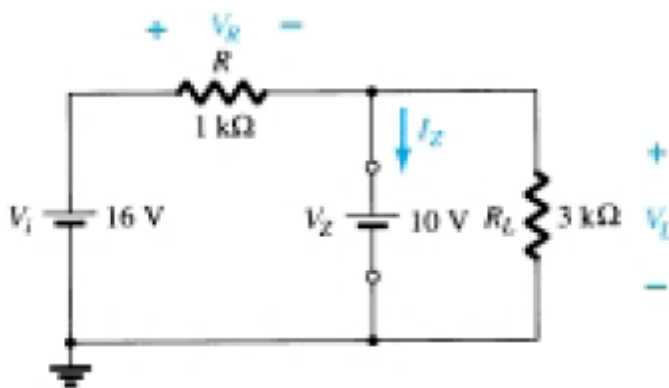**Since  $V > V_Z$ ; the diode is ON and the resultant circuit will be**



$$V_L = V_Z = 10 \text{ V}$$

$$V_R = V_i - V_L = 16 \text{ V} - 10 \text{ V} = 6 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{10 \text{ V}}{3 \text{ k}\Omega} = 3.33 \text{ mA}$$

$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$

$$I_Z = I_R - I_L \text{ [Eq. (2.18)]}$$

$$= 6 \text{ mA} - 3.33 \text{ mA}$$

$$= 2.67 \text{ mA}$$

The power dissipated,


$$P_Z = V_Z I_Z = (10 \text{ V})(2.67 \text{ mA}) = 26.7 \text{ mW}$$

which is less than the specified  $P_{ZM} = 30 \text{ mW}$ .
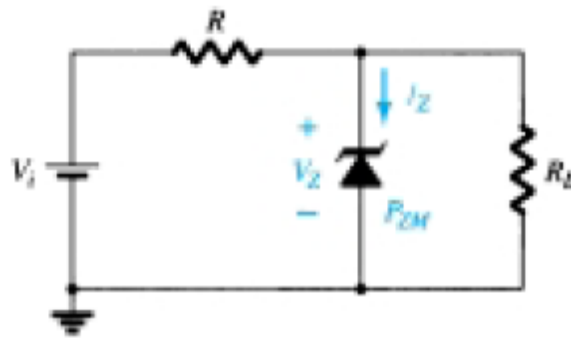
### 3.2 Fixed $V_i$ , Variable $R_L$

Due to the offset voltage  $V_Z$ , there is a **specific range of resistor values (and therefore load current) which will ensure that the Zener is in the “on” state**. Too small a load resistance  $R_L$  will result in a voltage  $V_L$  across the load resistor less than  $V_Z$ , and the Zener device will be in the “off” state.

To determine the minimum load resistance of the regulator in the figure below that will turn the Zener diode on, simply calculate the value of  $R_L$  that will result in a load voltage  $V_L = V_Z$ . That is:



$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

Then the minimum load resistance is :

$$R_{L_{\min}} = \frac{R V_Z}{V_i - V_Z}$$

It means any load resistance greater than  $R_{L_{\min}}$  will make the **diode ON**.

$$I_{L_{\max}} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L_{\min}}}$$

Once the diode is in the “on” state, the voltage across  $R$  remains fixed at

$$V_R = V_i - V_Z$$

and  $I_R$  remains fixed at

$$I_R = \frac{V_R}{R}$$

Then the Zener current:

$$I_Z = I_R - I_L$$

Resulting in a minimum  $I_Z$  when  $I_L$  is a maximum and a maximum  $I_Z$  when  $I_L$  is a minimum value since  $I_R$  is constant.

Since  $I_Z$  is limited to  $I_{ZM}$  as provided on the data sheet, it does affect the range of  $R_L$  and therefore  $I_L$ . Substituting  $I_{ZM}$  for  $I_Z$  establishes the minimum  $I_L$  as


$$I_{L_{\min}} = I_R - I_{ZM}$$

and the maximum load resistance as

$$R_{L_{\max}} = \frac{V_Z}{I_{L_{\min}}}$$

Example: (a) For the circuit shown below, determine the range of  $R_L$  and  $I_L$  that will result in  $V_{R_L}$  being maintained at 10 V.

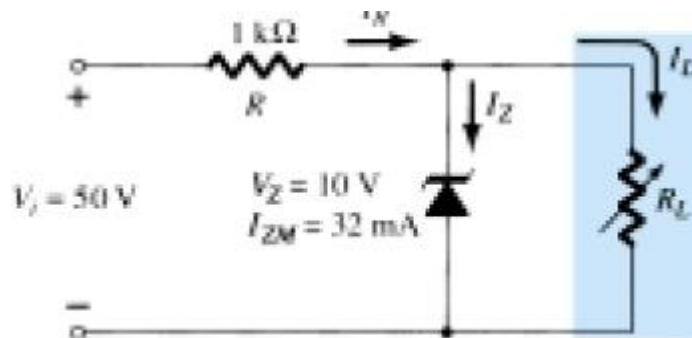(b) Determine the maximum wattage rating of the diode.



### $I_{ZM}$ = Maximum Zener Diode

**Solution:**

(a)

$$R_{L_{\min}} = \frac{RV_Z}{V_1 - V_Z} = \frac{(1 \text{ k}\Omega)(10 \text{ V})}{50 \text{ V} - 10 \text{ V}} = \frac{10 \text{ k}\Omega}{40} = 250 \text{ }\Omega$$


$$V_R = V_I - V_Z = 50 \text{ V} - 10 \text{ V} = 40 \text{ V}$$

$$I_R = \frac{V_R}{R} = \frac{40 \text{ V}}{1 \text{ k}\Omega} = 40 \text{ mA}$$


$$I_{L_{\min}} = I_R - I_{ZM} = 40 \text{ mA} - 32 \text{ mA} = 8 \text{ mA}$$

$$R_{L_{\max}} = \frac{V_Z}{I_{L_{\min}}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

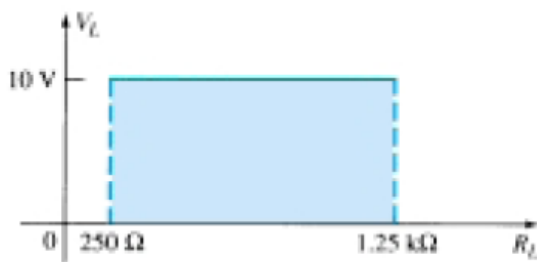A plot between  $V_L$  and  $R_L$  and  $I_L$  and  $R_L$  is shown below:



(a)

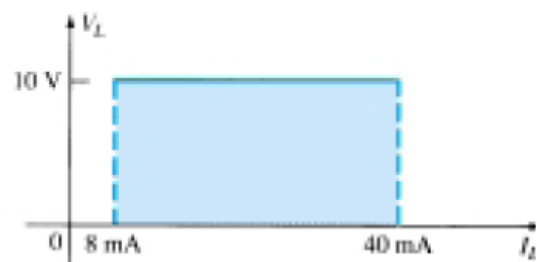

(b)

$$\begin{aligned} \text{(b) } P_{\max} &= V_Z I_{ZM} \\ &= (10 \text{ V})(32 \text{ mA}) = 320 \text{ mW} \end{aligned}$$

### 3.3 Fixed $R_L$ , Variable $V_i$

The voltage  $V_i$  must be sufficiently large to turn the Zener diode on. The minimum turn-on voltage  $V_i = V_{i_{\min}}$  is determined by:

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$V_{i_{\min}} = \frac{(R_L + R) V_Z}{R_L}$$

The maximum value of  $V_i$  is limited by the maximum Zener current  $I_{ZM}$ .

Since  $I_{ZM} = I_R - I_L$ ,


$$I_{R_{\max}} = I_{ZM} + I_L$$

Since  $I_L$  is fixed at  $V_Z/R_L$  and  $I_{ZM}$  is the maximum value of  $I_Z$ , the maximum  $V_i$  is defined by

$$V_{i_{\max}} = V_{R_{\max}} + V_Z$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z$$

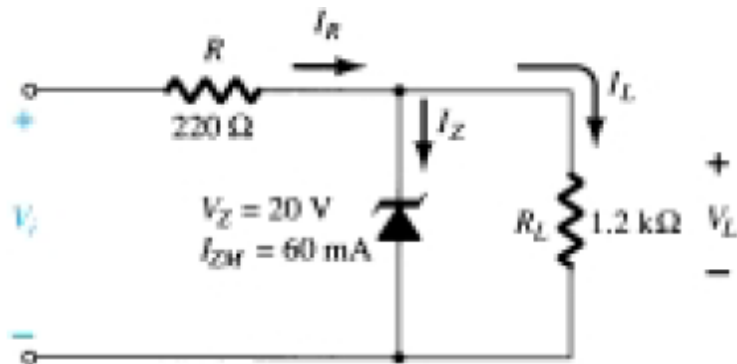**Example:** Determine the range of values of  $V_i$  that will maintain the Zener diode of the figure below in the “ON” state.



**Solution:**


$$V_{i_{\min}} = \frac{(R_L + R)V_Z}{R_L} = \frac{(1200 \Omega + 220 \Omega)(20 \text{ V})}{1200 \Omega} = 23.67 \text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20 \text{ V}}{1.2 \text{ k}\Omega} = 16.67 \text{ mA}$$

$$I_{R_{\max}} = I_{ZM} + I_L = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$


$$\begin{aligned} V_{i_{\max}} &= I_{R_{\max}} R + V_Z \\ &= (76.67 \text{ mA})(0.22 \text{ k}\Omega) + 20 \text{ V} \\ &= 16.87 \text{ V} + 20 \text{ V} \\ &= 36.87 \text{ V} \end{aligned}$$

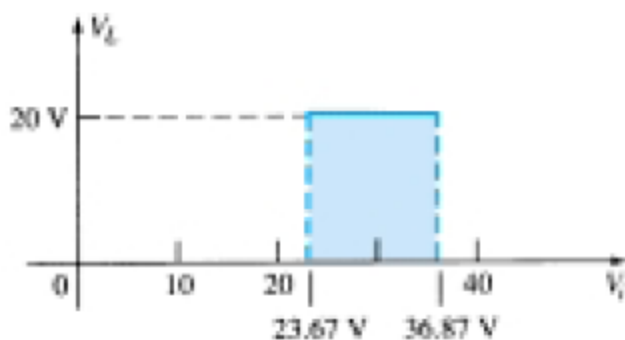A plot of  $V_L$  versus  $V_i$  is provided in the figure below:






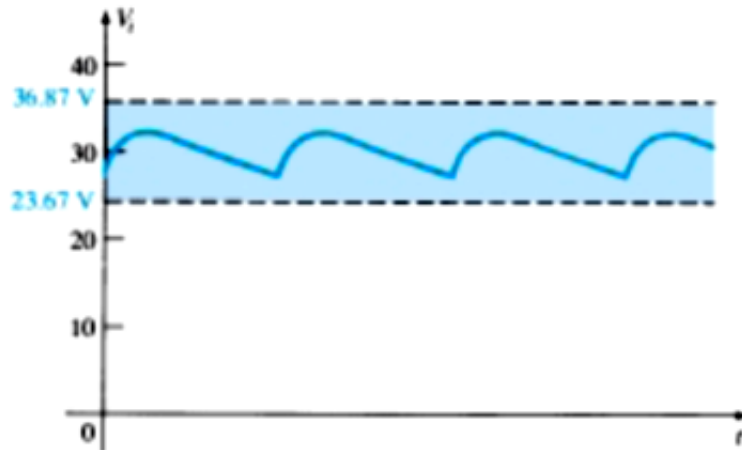
- The results of this example with a fixed  $RL$  reveals that, the output voltage will remain fixed at 20 V for a range of input voltage that extends from 23.67 to 36.87 V.
- In fact, the input could appear as shown the figure below and the output would remain constant at 20 V.



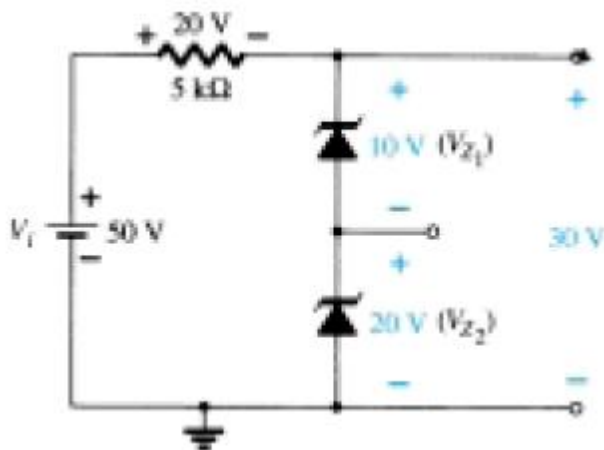- Two reference levels can be obtained using two Zener diodes as shown in the figure below, if the input voltage  $>V_{Z1}+V_{Z2}$ , both diodes are in ON state.



- Back to back Zener diodes can be used to get the output as illustrated in the figures below:

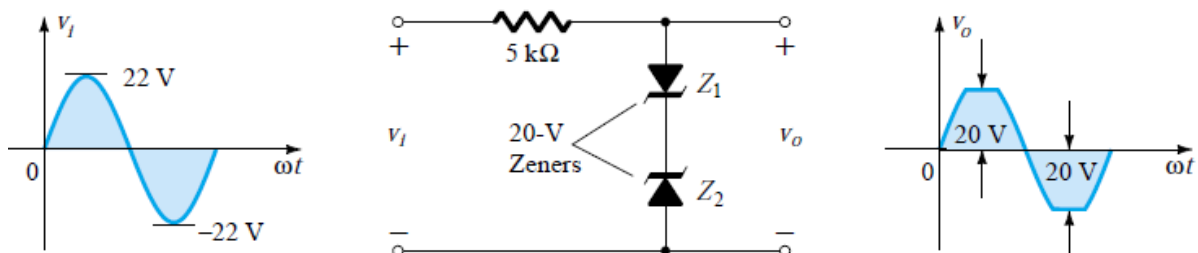

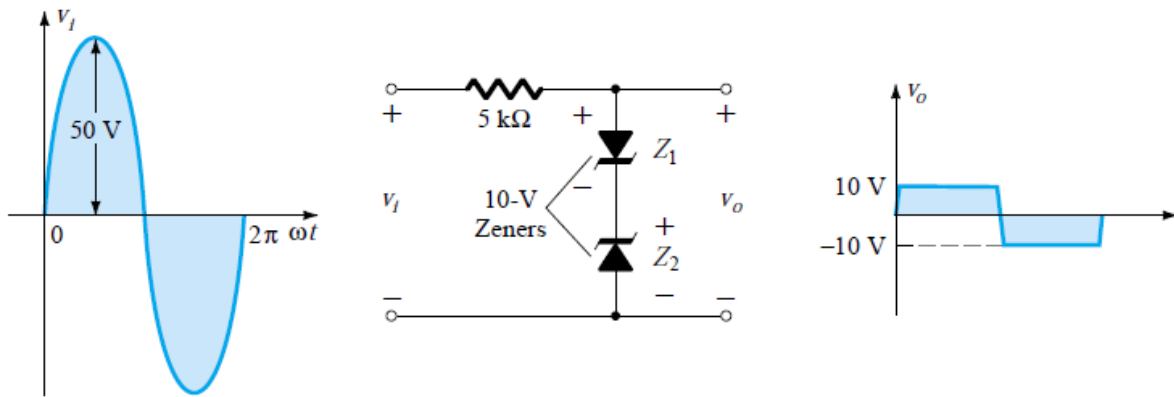


Figure: Output voltage and diode current waveforms: (a) small  $C$ ; (b) large  $C$ .