

**University Of Diyala
College Of Engineering
Computer Engineering Department**



Digital System Design II

Dr. Yasir Amer Al-Zubaidi

Third stage

2021


Design of Digital Sequential Circuits Using New Methods

Microprogramming Overview

- **Data path and Control**
- **Microoperations**
- **Sequencing and control**

Datapath and Control

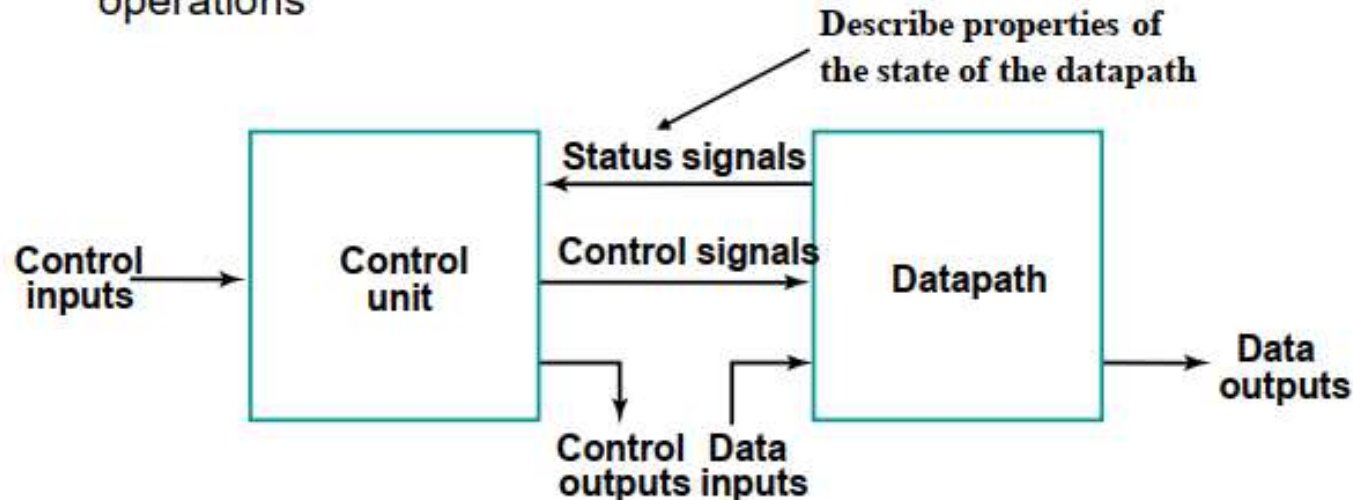- Datapath - performs data transfer and processing operations
- Control Unit - Determines the enabling and sequencing of the operations



- The control unit receives:
 - External control inputs
 - Status signals
- The control unit sends:
 - Control signals
 - Control outputs

Overview


- Datapath and control
- **Microoperations**
 - Register transfer operations
 - Microoperations - arithmetic, logic, and shift
 - Register cell design
 - Serial transfers and microoperations
- Sequencing and control

Register Transfer Operations

- Register Transfer Operations – the movement and processing of data stored in registers
- Three basic components:
 - A set of registers (operands)
 - Transfer operations
 - Control of operations
- Elementary operations -- called *microoperations*
 - load, count, shift, add, bitwise "OR", etc.

Register Notation

 
- Letters and numbers – register (e.g. R2, PC, IR)
- Parentheses () – range of register bits (e.g. R1(1), PC(7:0), AR(L))



- Arrow (\leftarrow) – data transfer (ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$)
- Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$)
- Comma – separates parallel operations

Conditional Transfer

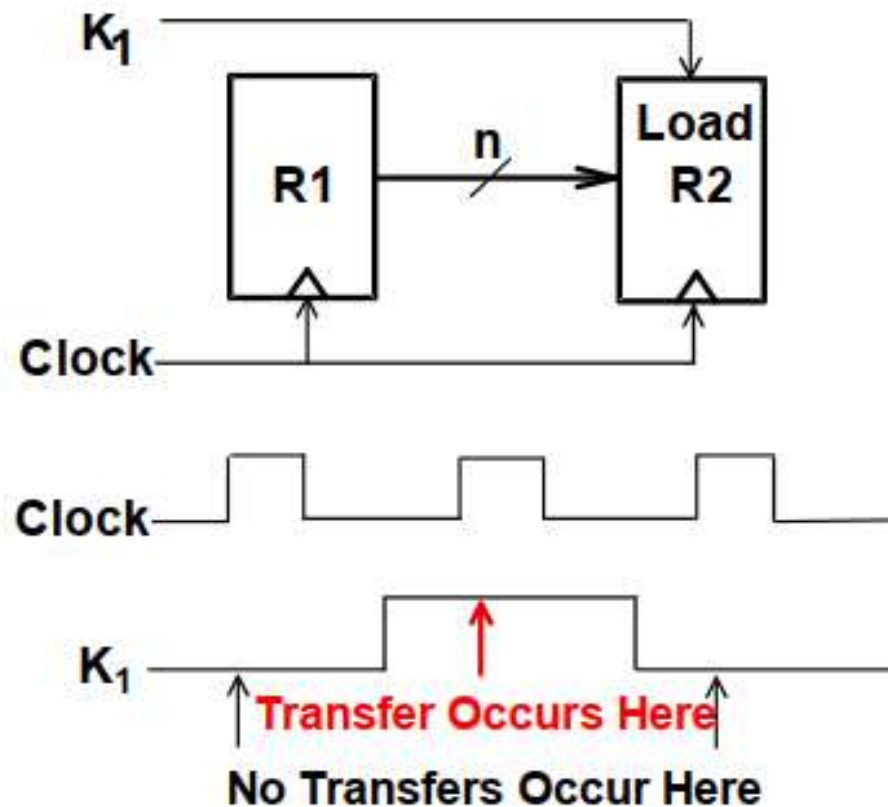- If $(K_1 = 1)$ then $(R2 \leftarrow R1)$
 $\Leftrightarrow K_1: (R2 \leftarrow R1)$
where K_1 is a control expression specifying a conditional execution of the microoperation.



Microoperations

- Logical groupings:
 - Transfer - move data from one set of registers to another
 - Arithmetic - perform arithmetic on data in registers
 - Logic - manipulate data or use bitwise logical operations
 - Shift - shift data in registers

Arithmetic operations

+ Addition
– Subtraction
* Multiplication
/ Division

Logical operations

∨ Logical OR
∧ Logical AND
⊕ Logical Exclusive OR
– Not

Example Microoperations

- $R1 \leftarrow R1 + R2$
 - Add the content of R1 to the content of R2 and place the result in R1.
- $PC \leftarrow R1 * R6$
- $R1 \leftarrow R1 \oplus R2$
- $(K1 + K2): R1 \leftarrow R1 \vee R3$
 - On condition $K1$ OR $K2$, the content of R1 is Logic bitwise Ored with the content of R3 and the result placed in R1.
 - NOTE: "+" (as in $K_1 + K_2$) means "OR." In $R1 \leftarrow R1 + R2$, + means "plus."

Arithmetic Microoperations

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	Ones Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
$R1 \leftarrow R1 + 1$	Increment (count up)
$R1 \leftarrow R1 - 1$	Decrement (count down)

- Any register may be specified for source 1, source 2, or destination.
- These simple microoperations operate on the whole word

Logical Microoperations

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)

Shift Microoperations

- Let R2 = 11001001

Symbolic Designation	Description	R1 content
$R1 \leftarrow sl R2$	Shift Left	10010010
$R1 \leftarrow sr R2$	Shift Right	01100100

- **Note:** These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic)

University Of Diyala
College Of Engineering
Computer Engineering Department



Digital System Design II


Dr. Yasir Al-Zubaidi

Third stage

2019

Multiplexer-Based Single Register Transfers

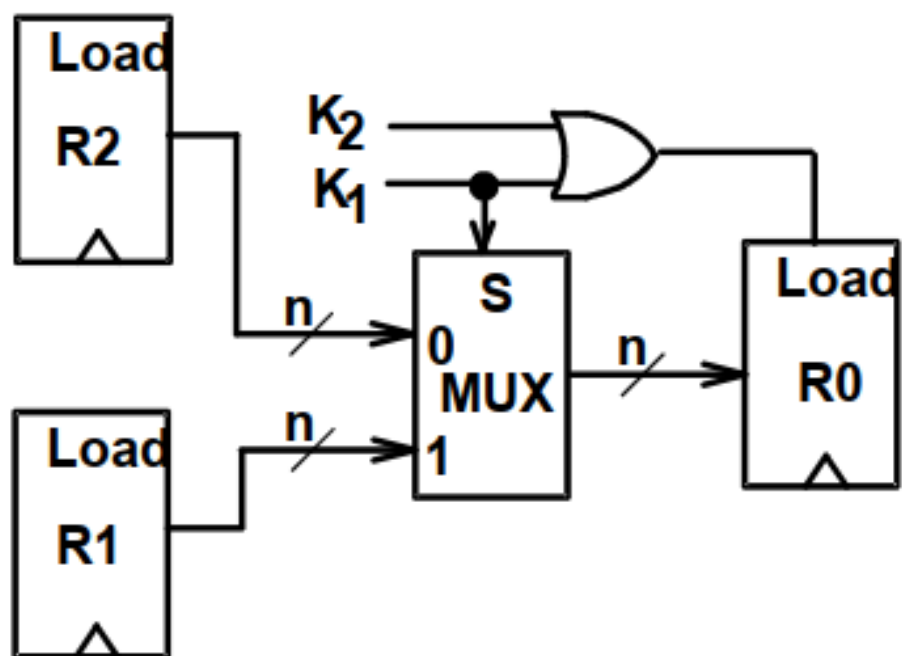- MUX connected to register outputs produce flexible transfer structures
- Transfers: $K1: \underline{R0} \leftarrow R1$
 $K2 \ K1: R0 \leftarrow R2$




Register Design

- Assume: a register consists of identical cells
- Register design can be approached as follows:
 - Design a representative cell for the register
 - Make copies of the cell and connect together to form the register
 - Applying appropriate “boundary conditions” to cells that need to be different and contract if appropriate
- Register cell design is the first step of the above process

Approach I: Multiplexer-based

- An n-input multiplexer with a variety of sources and functions
- Load enable by OR of control signals K_0, K_1, \dots, K_{n-1} (for 00...0, no load)
- Use encoder + multiplexer to select sources and/or transfer functions

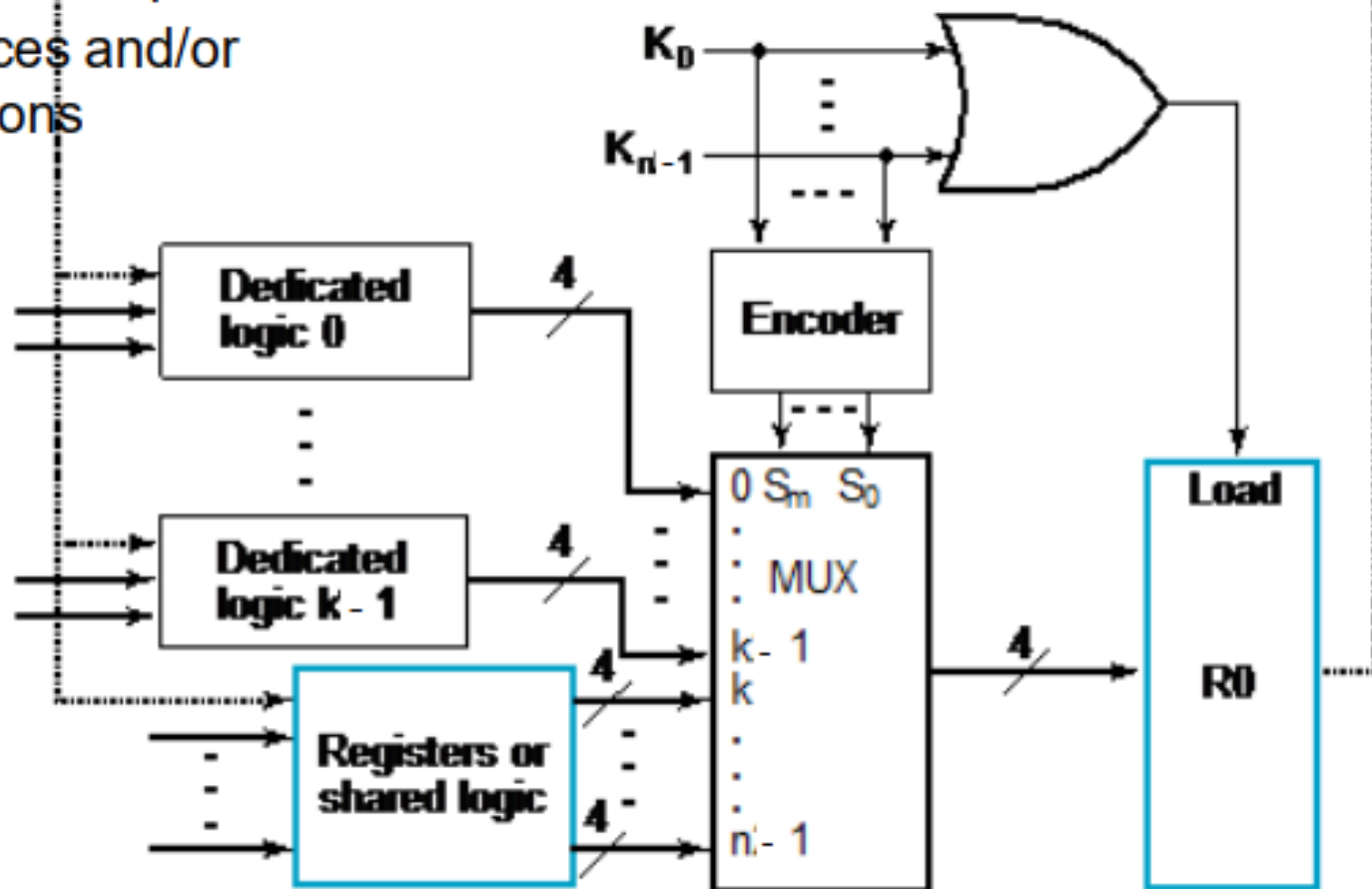

Example 1: Register Cell Design

- Register A (m-bits) Specification:
 - Data input: B; Control inputs (CX, CY): (0,0), (0,1) (1,0)
 - Register transfers:
 - CX: $A \leftarrow B \vee A$; CY : $A \leftarrow B \oplus A$; Hold state: (0,0)
- Load Control: Load = CX + CY
- Since all control combinations appear as if encoded (0,0), (0,1), (1,0), can use multiplexer without encoder:

$$S_1 = CX$$

$$S_0 = CY$$

$$I_0 = A_i$$


$$I_1 = A_i \leftarrow B_i \oplus A_i$$

$$I_2 = A_i \leftarrow B_i \vee A_i$$

Hold A

CY = 1

CX = 1

 

Approach II: Sequential Circuit Design

- Find a state diagram or state table
- For optimization:
 - Use K-maps for up to 4 to 6 variables
 - Otherwise, use computer-aided or manual optimization

Example 1 Again

- State Table for D_i :

	Hold	$A_i \vee B_i$		$A_i \oplus B_i$	
A_i	$CX = 0$ $CY = 0$	$CX = 1$ $CY = 0$ $B_i = 0$	$CX = 1$ $CY = 0$ $B_i = 1$	$CX = 0$ $CY = 1$ $B_i = 0$	$CX = 0$ $CY = 1$ $B_i = 1$
0	0	0	1	0	1
1	1	1	1	1	0

- Four variables (CX, CY, A, B) should give a total of 16 state table entries
- By using:
 - Combinations of variable names and values
 - Don't care conditions (for $CX = CY = 1$)only 12 entries are required to represent the 16 entries

Example 1 Again (Contd.)

- K-map - Use variable ordering CX , CY , A_i , B_i and assume a D flip-flop

				A_i
D_i	0	0	1	1
	0	1	0	1
	X	X	X	X
CX	0	1	1	1
				B_i

The Karnaugh map shows the function D_i with variables CX , CY , A_i , and B_i . The map is a 4x4 grid. The top row is labeled D_i and the right side is labeled CY . The bottom row is labeled CX . The columns are labeled A_i and B_i . The values in the cells are: (0,0)=0, (0,1)=0, (0,2)=1, (0,3)=1; (1,0)=0, (1,1)=1, (1,2)=0, (1,3)=1; (2,0)=X, (2,1)=X, (2,2)=X, (2,3)=X; (3,0)=0, (3,1)=1, (3,2)=1, (3,3)=1. Blue groupings are shown: a 2x2 square at the top right, a 2x2 square at the bottom right, a 2x2 square at the bottom left, a 2x2 square at the top left, a 2x2 square at the middle left, and a 2x2 square at the middle right.

Example 1 Again (Contd.)

- The resulting SOP equation:

$$\begin{aligned}D_i &= CX B_i + CY \bar{A}_i B_i + A_i \bar{B}_i + \bar{C} \bar{Y} A_i \\ &= CX B_i + \bar{A}_i (CY B_i) + A_i (\bar{C} \bar{Y} B_i) \\ &= CX B_i + A_i \oplus (CY B_i)\end{aligned}$$


The gate input cost per cell = 13

- The gate input cost per cell for the previous version is:
 - Per cell: 19
 - Shared decoder logic: 8
- Cost gain by sequential design > 6 per cell
- Also, no Enable on the flip-flop makes it cost less

Serial Transfers and Microoperations

- Serial Transfers
 - Used for “narrow” transfer paths
 - Example 1: Telephone or cable line
 - Parallel-to-Serial conversion at source
 - Serial-to-Parallel conversion at destination

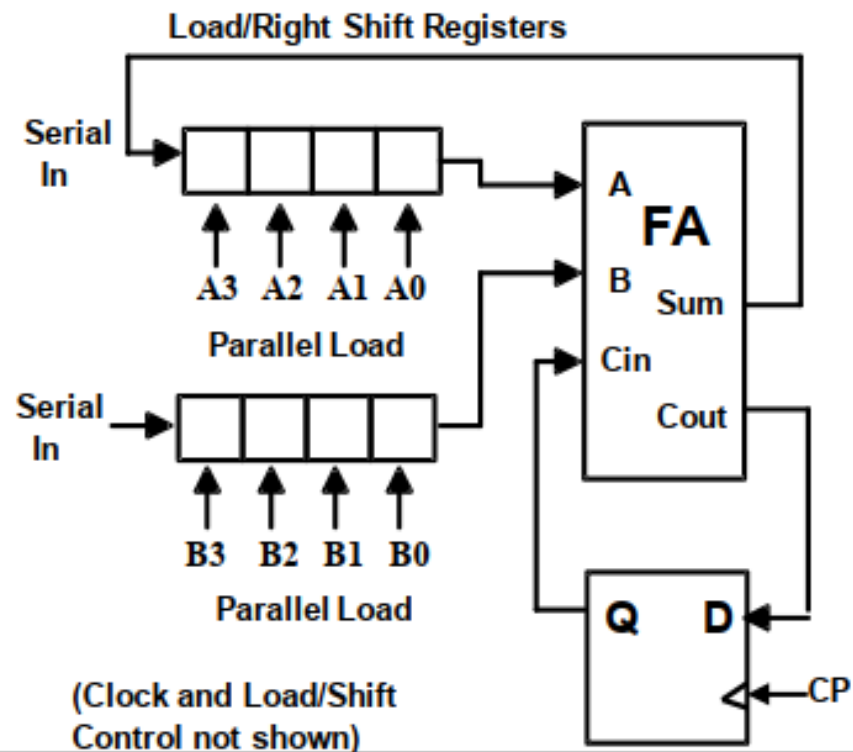- Serial microoperations
 - Example 1: Addition
 - A low cost way
 - Loss in performance



Overview

- Datapath and control
- Microoperations
- Sequencing and control
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

Control Unit Types

- Two distinct classes:
 - Programmable
 - Non-programmable.
- A programmable control unit:
 - An external memory array for storing instructions and control information
 - A program counter (PC) register points to the next instruction to be executed
 - Decision logic for determining the sequence of operations and logic to interpret the instructions
- A non-programmable control unit: does not fetch instructions from a memory and is not responsible for sequencing instructions

Algorithmic State Machines


- The function of a sequential circuit can be represented by a state table or a state diagram.

- An Algorithmic State Machine (ASM) is a flowchart-like way to specify state diagrams for sequential logic and, optionally, actions performed in a datapath.
 - A flowchart is a way of showing actions and control flow in an algorithm.
 - An ASM explicitly specifies a sequence of actions and their timing relationships
 - An ASM chart directly leads to a hardware realization

- Primitives:
 1. State Box (a rectangle)
 2. Decision Box
 - I. Scalar (a diamond)
 - II. Vector (a hexagon)
 3. Conditional Output Box (an oval)


State Box

 - A rectangle with:
 - The symbolic name for the state
 - An optional state code
 - Containing register transfer operations, and outputs activated within or while leaving the state
- The symbolic name for the state marked outside the upper left top
- An optional state code, if assigned, outside the upper right top




Decision Box

 - **Scalar** : A diamond with:
 - One input path (entry point).
 - One input condition that is tested.
 - A TRUE/FALSE exit path (logic 1/0).




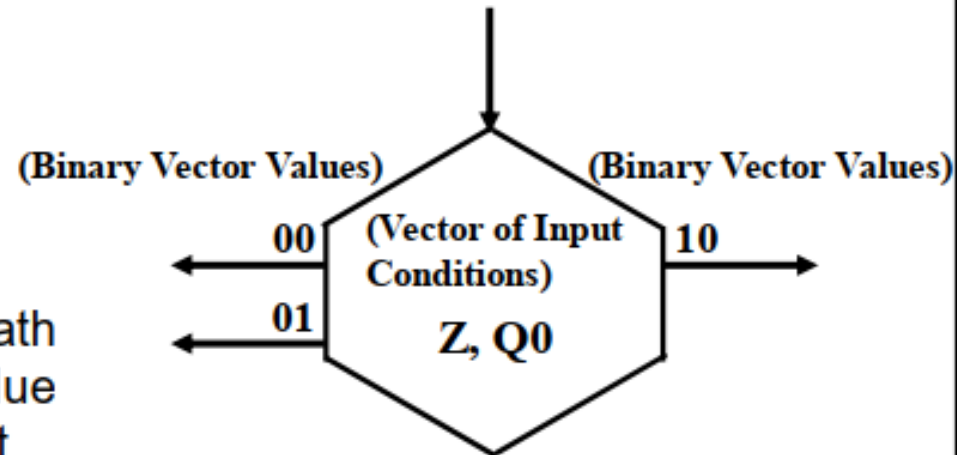- **Vector**: A hexagon with:
 - One input path (entry point).
 - A vector of input conditions tested.
 - Up to 2^n output paths. The path taken has a binary vector value that matches the vector input condition




Conditional Output Box

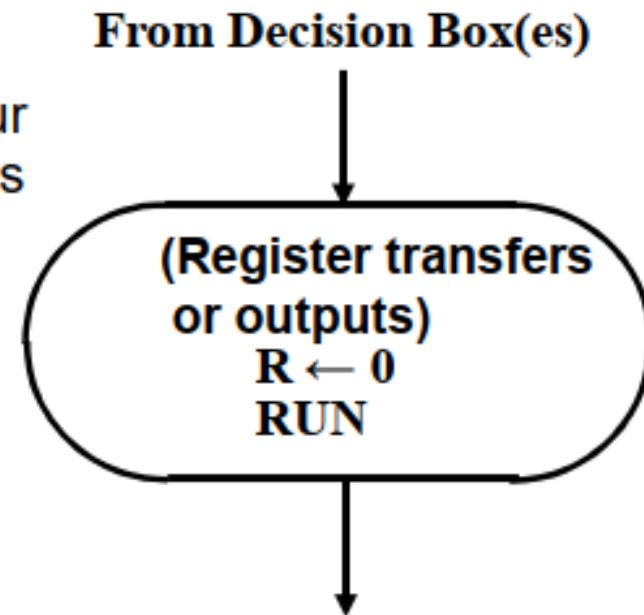- An oval with:
 - One input path from a decision box(es)
 - One output path
 - Register transfers or outputs that occur only if the conditional path to the box is taken.
- Transfers and outputs
 - in a state box are Moore type - dependent only on state
 - in a conditional output box are Mealy type - dependent on both state and inputs



Connecting Boxes Together

 
- By connecting boxes together, we see the power of expression.



- What are the:
 - Inputs? start
 - Outputs? Avail, Init
 - Conditional Outputs?
 - Transfers? $A \leftarrow 0$, $PC \leftarrow 0$
 - Conditional Transfers? INIT, transfer: $PC \leftarrow 0$



ASM Blocks

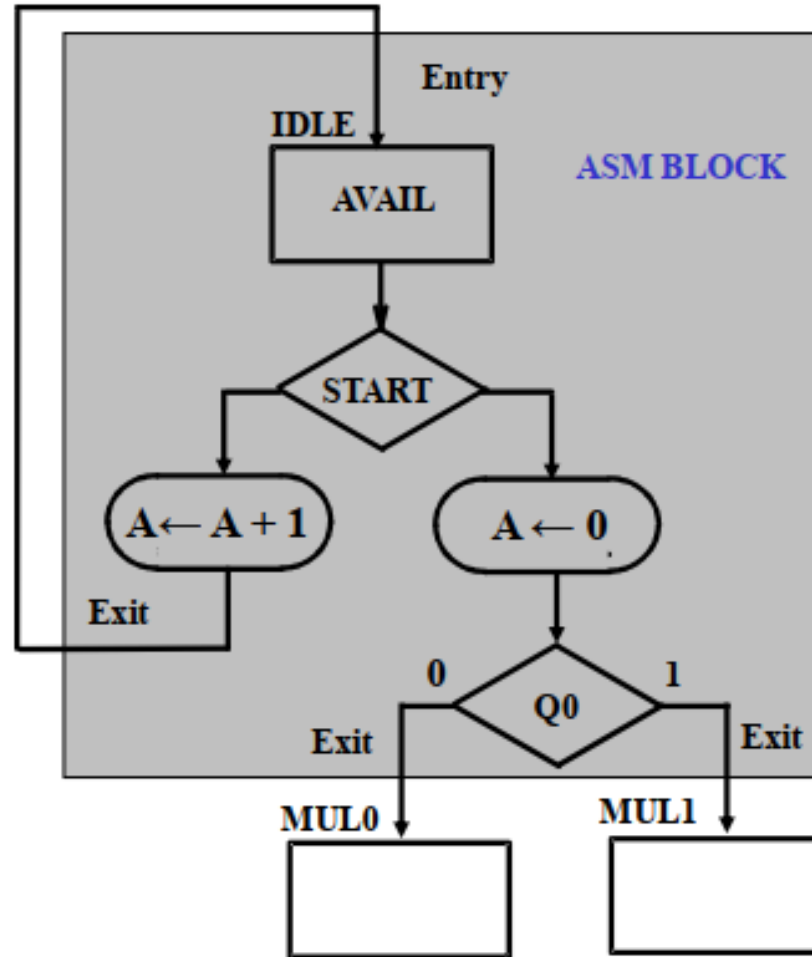- One state box along with all decision and conditional output boxes connected to it, called an **ASM Block**. i.e., the ASM Block includes all items on the path from the current state to the same or other states.




ASM Timing

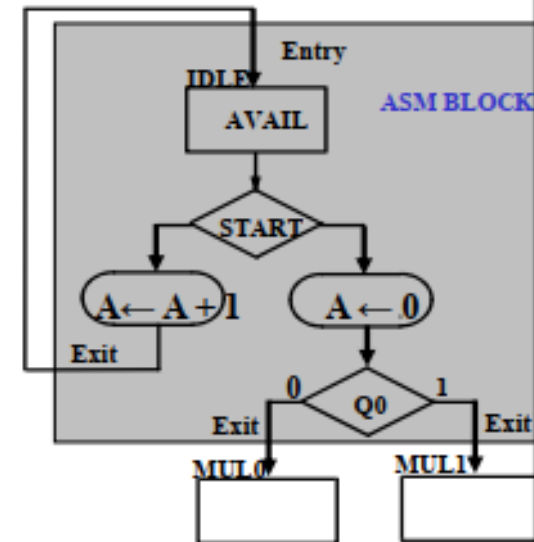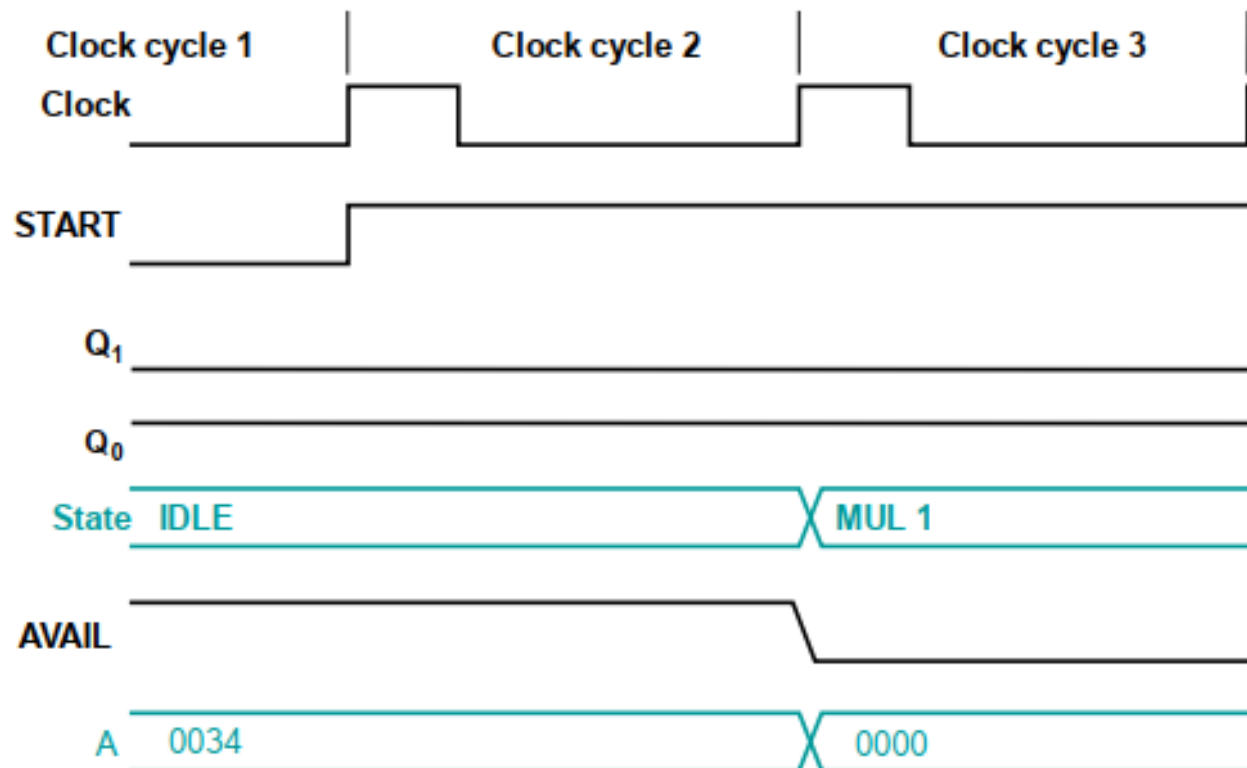- Outputs appear while in the state
- Register transfers and conditional outputs occur at the clock while exiting the state - New value occur in the next state!



Multiply Overview

 - Binary multiplication is just a *bunch* of left shifts and adds




Multiplier Example

- Example: (101 x 011) Base 2
- Partial products are:
101 x 0, 101 x 1, and 101 x 1


				1	0	1	multiplicand	
			x	0	1	1	multiplier	
				<hr/>				
				1	0	1		
				1	0	1		
			0	0	0			
			<hr/>					
	0	0	1	1	1	1		

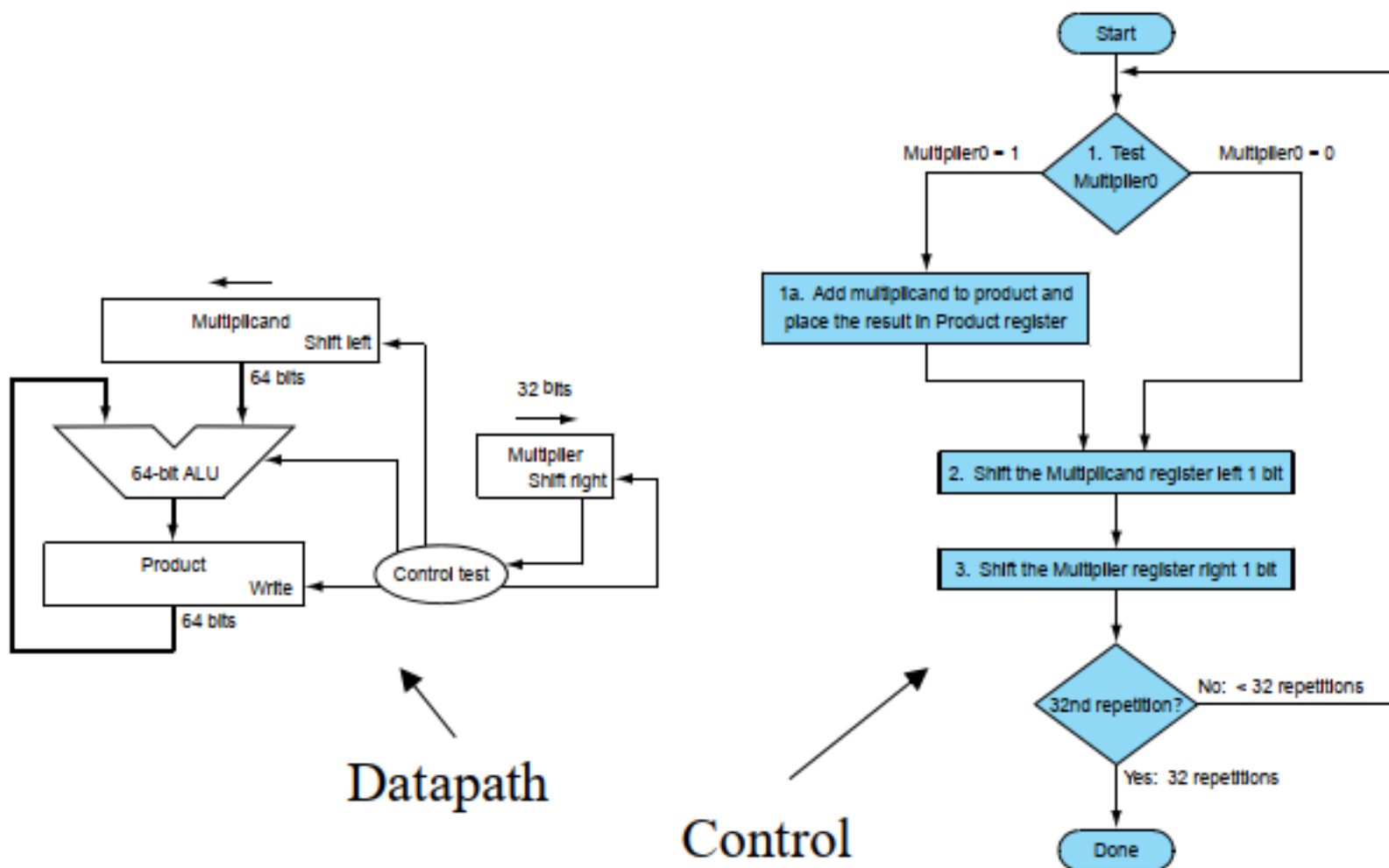Multiplication: Implementation (version 1)




Unsigned shift-add multiplier (version 1)

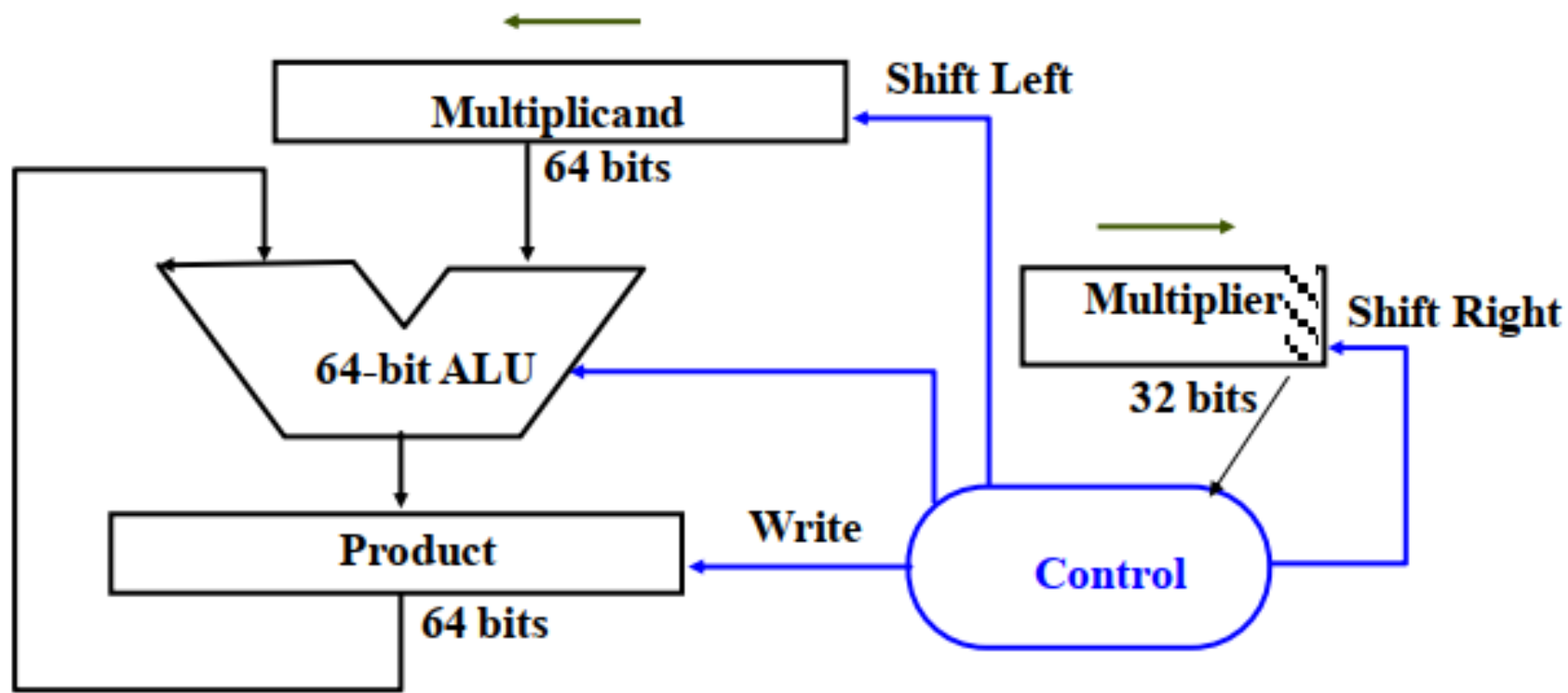- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

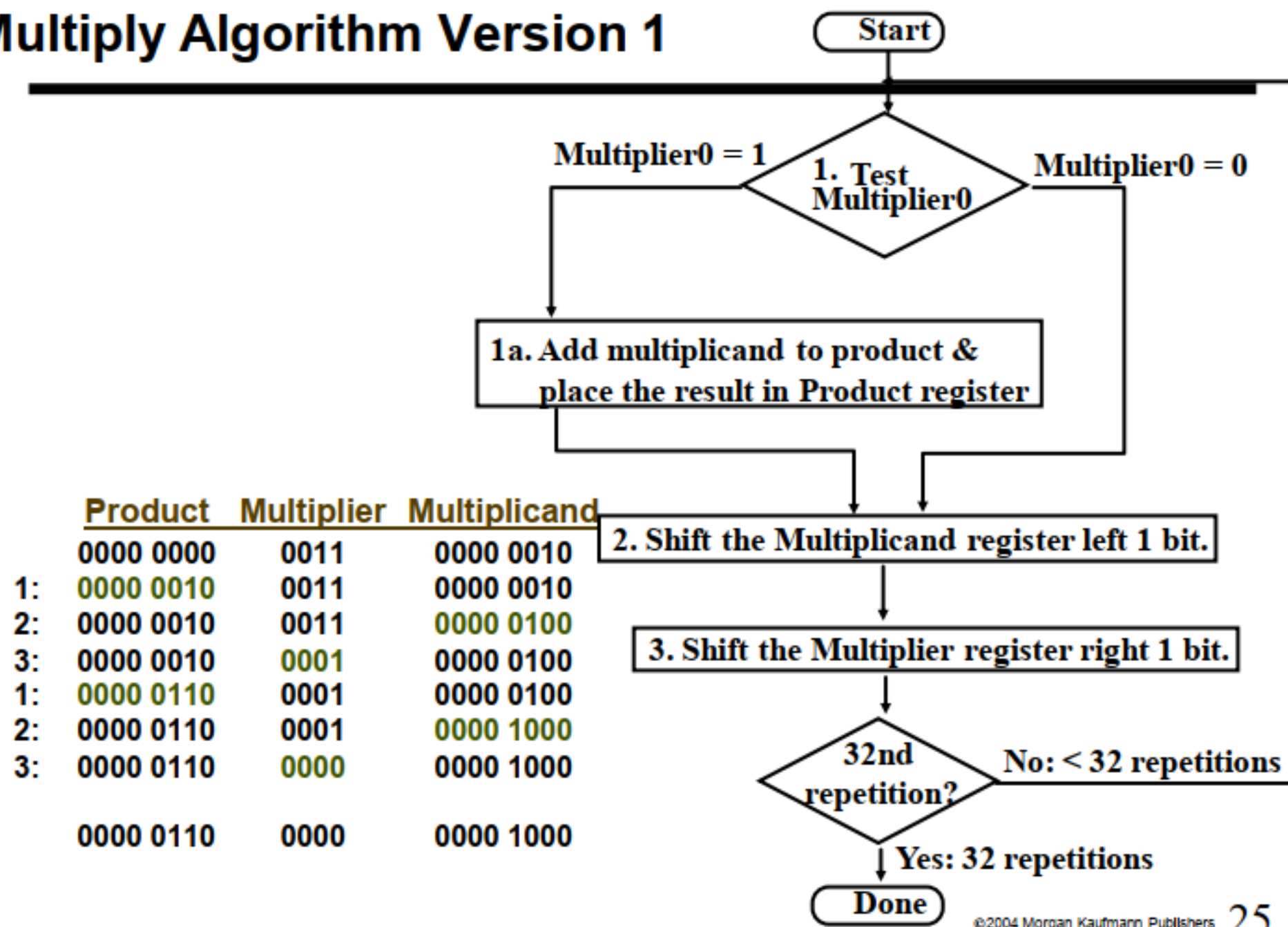


	Product	Multiplier	Multiplicand
	0000 0000	0011	0000 0010
1:	0000 0010	0011	0000 0010
2:	0000 0010	0011	0000 0100
3:	0000 0010	0001	0000 0100
1:	0000 0110	0001	0000 0100
2:	0000 0110	0001	0000 1000
3:	0000 0110	0000	0000 1000
	0000 0110	0000	0000 1000

Observations on Multiply Version 1


- 1 clock per cycle $\Rightarrow \approx 100$ clocks per multiply because of 32 repetitions, 3 steps in one repetition
 - Ratio of add/sub to multiply is from 5:1 to 100:1
 - Slow
- 0's inserted in the rightmost bit of multiplicand as shifting left
 - \Rightarrow least significant bits of product never changed once formed
- 1/2 bits in multiplicand always 0
 - MSB are 0s at the beginning
 - 0 is inserted in LSB as multiplicand shifting left
 - \Rightarrow 64-bit multiplicand register is wasted
 - \Rightarrow 64-bit adder is wasted
- **Instead of shifting multiplicand to left, let's shift product to right**

MULTIPLY HARDWARE Version 2

 - 32-bit Multiplicand reg, 32 -bit ALU, 64-bit Product reg, 32-bit Multiplier reg




Multiply Algorithm Version 2

 

	<u>Product</u>	<u>Multiplier</u>	<u>Multiplicand</u>
	0000 0000	0011	0010
1:	0010 0000	0011	0010
2:	0001 0000	0011	0010
3:	0001 0000	0001	0010
1:	0011 0000	0001	0010
2:	0001 1000	0001	0010
3:	0001 1000	0000	0010
1:	0001 1000	0000	0010
2:	0000 1100	0000	0010
3:	0000 1100	0000	0010
1:	0000 1100	0000	0010
2:	0000 0110	0000	0010
3:	0000 0110	0000	0010
	0000 0110	0000	0010

Still more wasted space in Version2!

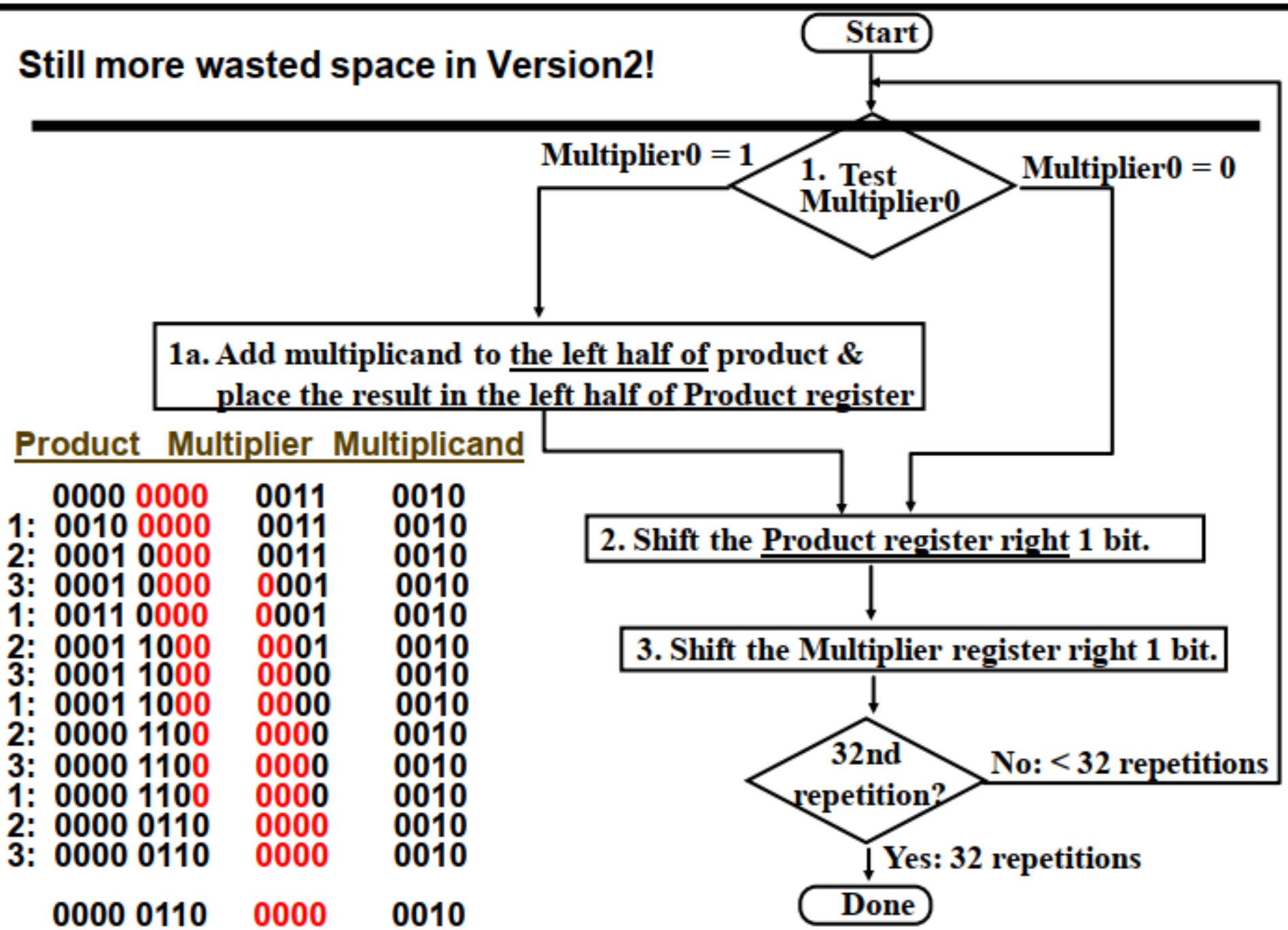

Observations on Multiply Version 2


- Product register **wastes space that exactly matches size of multiplier**
=> combine Multiplier register and Product register

Example (1 0 1) x (0 1 1) Again

- Reorganizing example to follow hardware algorithm:

	1	0	1									← Multiplicand (B)
x	0	1	1									← Multiplier (Q)
0	0	0	0									Clear C A (Carry and register A)
+	1	0	1									Multiplier ₀ = 1 => Add B
	<hr/>											Addition
0	1	0	1									Shift Right (Zero-fill C)
0	0	1	0	1								Multiplier ₁ = 1 => Add B
+	1	0	1									Addition
	<hr/>											Addition
0	1	1	1	1								Shift Right
0	0	1	1	1	1							Multiplier ₂ = 0 => No Add, Shift Right
0	0	0	1	1	1	1						Right

Multiplier Example: Block Diagram

 

Multiplexer Example: Operation

1. The multiplicand is loaded into register B.
2. The multiplier is loaded into register Q.
3. When G becomes 1, register C|| A is initialized to 0.
4. Down Counter P is initialized to $n - 1$ (n = number of bits in multiplier)
5. The partial products are formed in register C||A||Q.
6. Each multiplier (Q) bit, beginning with the LSB, is processed (if bit is 1, B is added to partial product of A; if bit is 0, do nothing)
7. C||A||Q is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
8. Steps 6 and 7 are repeated until $P = 0$ as detected by Zero detect.

University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

ASM Based Datapath and Control Design

Dr. Yasir Al-Zubaidi


Third stage

2021

Overview

- Datapath and control
- Microoperations
- **Sequencing and control**
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

Multiplier Example: ASM Chart

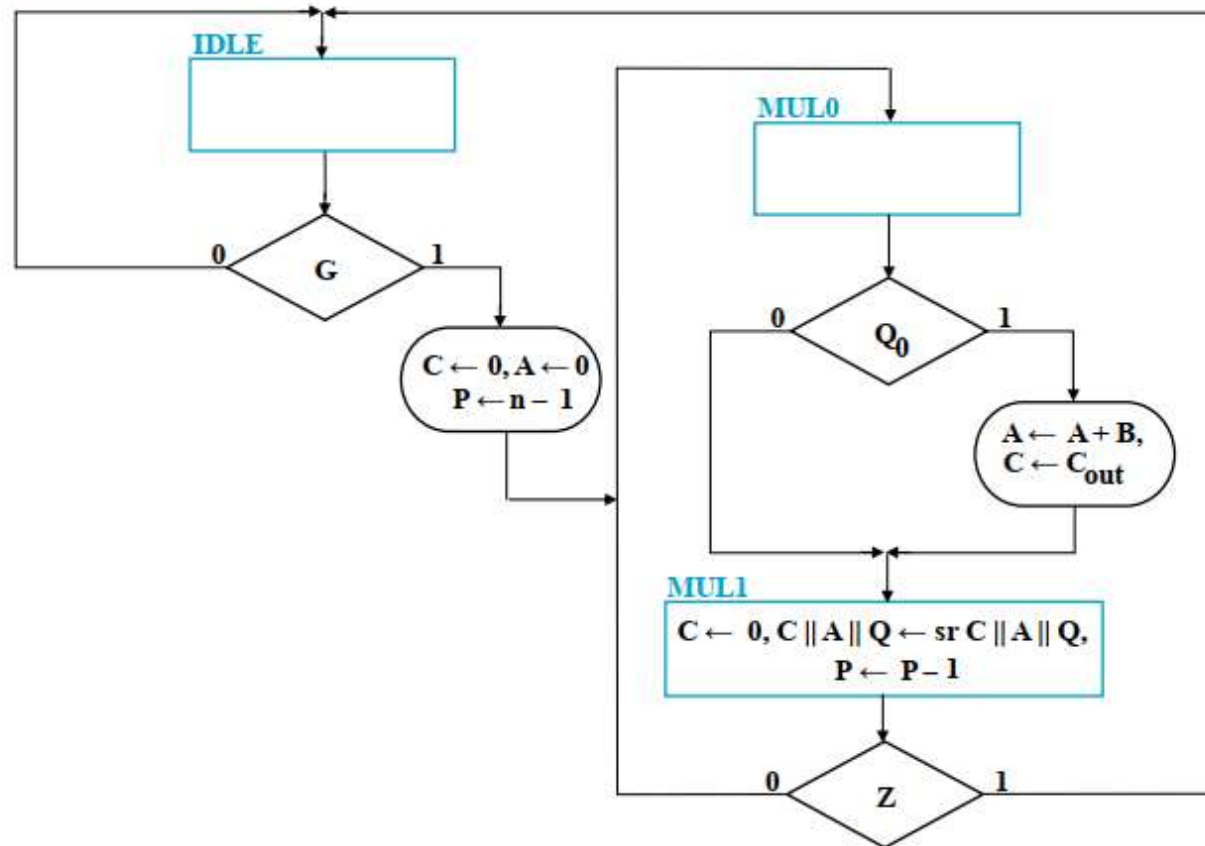

Multiplier Example: ASM Chart (Contd.)

- Three states employed here:
 - IDLE state:
 - input G is used as the condition for starting the multiplication
 - C, A, and P are initialized
 - MUL0 state: conditional addition is performed based on the value of Q_0 .
 - MUL1 state:
 - right shift is performed to capture the partial product and position the next bit of the multiplier in Q_0
 - Down counter $P = P - 1$
 - $P=0$ is used to sense completion or continuation of the multiplication.

Multiplier Example: Control Signal Table

Control Signals for Binary Multiplier


Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register <i>A</i> :	$A \leftarrow 0$ $A \leftarrow A + B$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Initialize Load Shift_dec	IDLE · <i>G</i> MUL0 · Q_0 MUL1
Register <i>B</i> :	$B \leftarrow IN$	<i>Load_B</i>	LOADB
Flip-Flop <i>C</i> :	$C \leftarrow 0$ $C \leftarrow C_{out}$	Clear_C Load	IDLE · <i>G</i> + MUL1 —
Register <i>Q</i> :	$Q \leftarrow IN$ $C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	<i>Load_Q</i> Shift_dec	LOADQ —
Counter <i>P</i> :	$P \leftarrow n - 1$ $P \leftarrow P - 1$	Initialize Shift_dec	— —


Multiplier Example: Control Signal Table (Contd.)

- Signals are defined on a register basis
- LOADQ and LOADB: external signals controlled from the system using the multiplier and will not be considered a part of this design
- Many control signals are “reused” for different registers.
 - These 4 control signals are the “outputs” of the control unit: initialize, load, shift_dec, clear_c

Multiplier Example - Sequencing Part of ASM

- With the outputs represented by the table, they can be removed from the ASM making the ASM to represent only the sequencing (next state) behavior

Similar to FSM 

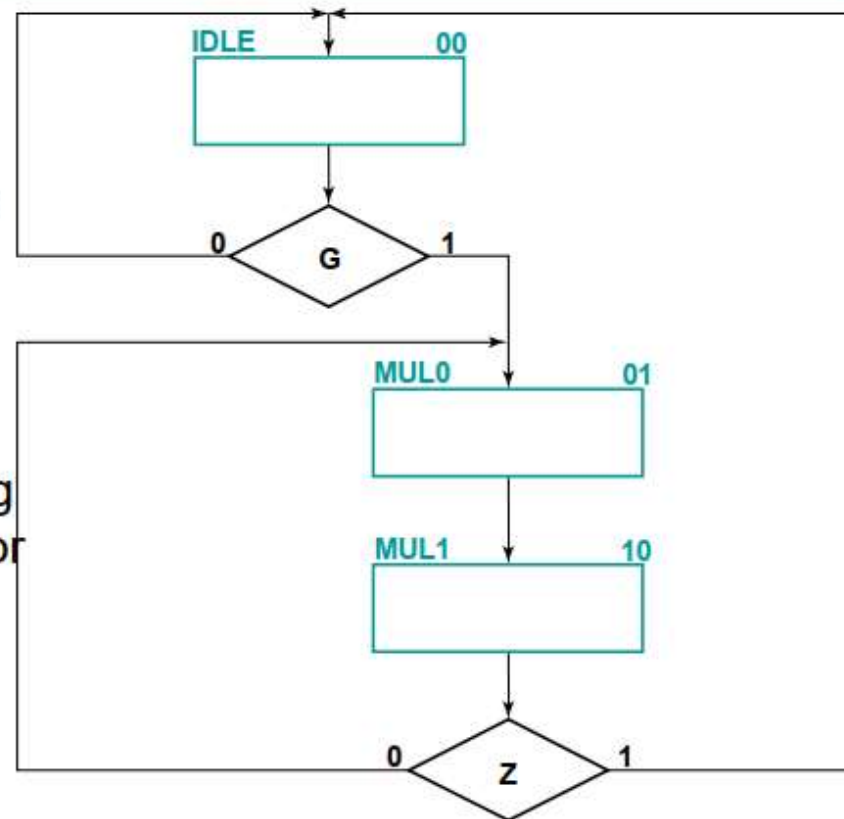

Hardwired Control

- Control Design Methods
 - Procedure specializations that use a single signal to represent each state
 - Sequence Register and Decoder
 - Sequence register with encoded states, e.g., 00, 01, 10, 11.
 - Decoder outputs produce “state” signals, e.g., 0001, 0010, 0100, 1000.
 - One Flip-flop per State
 - Flip-flop outputs as “state” signals, e. g., 0001, 0010, 0100, 1000.

Multiplier Example: Sequencer and Decoder Design - Specification

- Initially, use sequential circuit design techniques
- First, define:
 - States: IDLE, MUL0, MUL1
 - Input Signals: G, Z, Q_0 (Q_0 affects outputs, not next state)
 - Output Signals: Initialize, LOAD, Shift_Dec, Clear_C
 - State Transition Diagram (Use Sequencing ASM)
 - Output Function: Use Control Signal Table
- Second, find
 - State Assignments
 - Use two state bits to encode the three states IDLE, MUL0, and MUL1.



State	M1	M0
IDLE	0	0
MUL0	0	1
MUL1	1	0
Unused	1	1

Multiplier Example: Sequencer and Decoder Design - Formulation

- Assuming that state variables M1 and M0 are decoded into states, the next state part of the state table is:


Current State	Input G Z	Next State M1 M0
IDLE	0 0	0 0
IDLE	0 1	0 0
IDLE	1 0	0 1
IDLE	1 1	0 1
MUL0	0 0	1 0
MUL0	0 1	1 0
MUL0	1 0	1 0
MUL0	1 1	1 0

Current State M1 M0	Input G Z	Next State M1 M0
MUL1	0 0	0 1
MUL1	0 1	0 0
MUL1	1 0	0 1
MUL1	1 1	0 0
Unused	0 0	d d
Unused	0 1	d d
Unused	1 0	d d
Unused	1 1	d d

Multiplier Example: Sequencer and Decoder Design –Equations Derivation/Optimization

- Finding the equations for M1 and M0 using decoded states:
 $M1 = MUL0$
 $M0 = IDLE \cdot G + MUL1 \cdot \bar{Z}$
- The output equations using the decoded states:
Initialize = $IDLE \cdot G$
Load = $MUL0 \cdot Q_0$
Clear_C = $IDLE \cdot G + MUL1$
Shift_dec = $MUL1$
- Doing multiple level optimization, extract $IDLE \cdot G$:
 $START = IDLE \cdot G$
 $M1 = MUL0$
 $M0 = START + MUL1 \cdot \bar{Z}$
Initialize = $START$
Load = $MUL0 \cdot Q_0$
Clear_C = $START + MUL1$
Shift_dec = $MUL1$
- The resulting circuit using flip-flops, a decoder, and the above equations is given on the next slide.

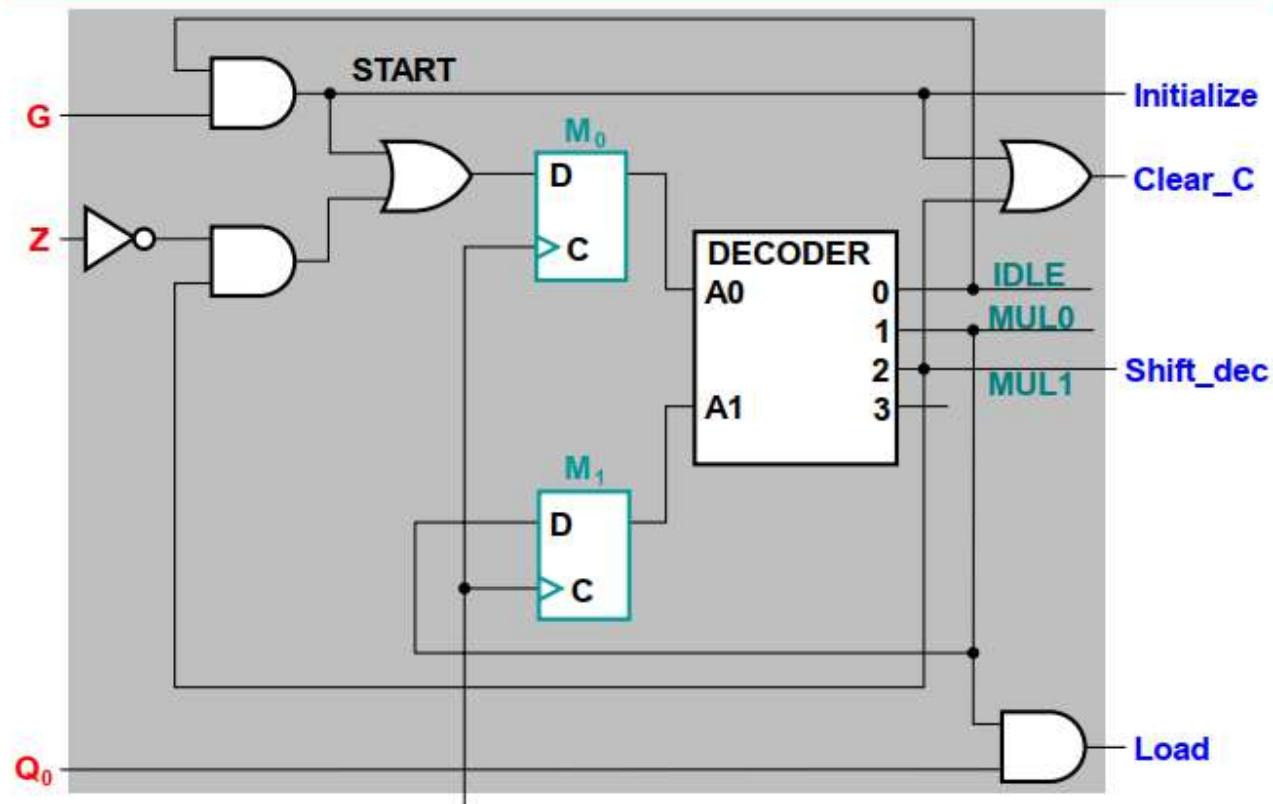Multiplier Example: Sequencer and Decoder Design - Implementation




```

--Binary multiplier with n=4
library ieee;
use ieee.std_logic_unsigned.all;
entity binary_multiplier is
    port(CLK, RESET, G, LOADB, LOADQ: in std_logic;
         MULT_IN : in std_logic_vector (3 downto 0);
         MULT_OUT : out std_logic_vector (7 downto 0));
end binary_multiplier;

```

```

architecture behavior_4 of binary_multiplier is
    type state_type is (IDLE, MUL0, MUL1);
    variable P:=3;
    signal state, next_state : state_type;
    signal A, B, Q:std_logic_vector(3 downto 0);
    signal C, Z:std_logic;

```

```

begin
    Z<= P(1) NOR P(0);
    MULT_OUT <= A & Q;

    state_register : process (CLK, RESET)
    begin
        if (RESET = '1') then
            state <= IDLE;
        elsif (CLK'event and CLK='1') then
            state <= next_state;
        endif;
    end process;

    next_state_func : process (G, Z, state)
    begin
        case state is
            when IDLE =>
                if G='1' then next_state <= MUL0;
                else next_state <= IDLE;
                end if;
            when MUL0 =>
                next_state <= MUL1;
            when MUL1 =>
                if Z='1' then next_state <= IDLE;
                else next_state <= MUL0;
                end if;
        end case;
    end process;

```

```

datapath_func : process (CLK)
variable CA: std_logic_vector (4 downto 0);
begin
    if (CLK'event and CLK='1') then
        if LOADB='1' then
            B <= MULT_IN;
        end if;
        if LOADQ = '1' then
            Q <= MULT_IN;
        end if;
        case state is
            when IDLE =>
                if G = '1' then
                    C <= '0';
                    A <= "0000";
                    P <= "11";
                end if;
            when MUL0 =>
                if Q(0)='1' then
                    CA := ('0' & A) + ('0' & B);
                else
                    CA := C & A;
                end if;
                C <= CA(4);
                A <= CA(3 downto 0);
            when MUL1 =>
                C <= '0';
                A <= C & A(3 downto 1);
                Q <= A(0) & Q(3 downto 1);
                P <= P - "01";
            end case;
        end if;
    end process;

end behavior_4;

```

Speeding Up the Multiplier

- In processing each bit of the multiplier, the circuit visits states MUL0 and MUL1 in sequence.
- By redesigning the multiplier, is it possible to visit only a single state per bit processed?

Speeding Up Multiply (Contd.)


- The operations in MUL0 and MUL1:
 - In MUL0, a conditional add of B
 - In MUL1, a right shift of $C \parallel A \parallel Q$ in a shift register, the decrementing of P, and a test for $P = 0$ (on the old value of P)
- Any solution that uses one state must combine all of the operations listed into one state
 - The operations involving P are already done in a single state, so not a problem.
 - The right shift, however, depends on the result of the conditional addition. So these two operations must be combined!

Speeding Up Multiply (Contd.)

- By replacing the shift register with a combinational shifter and combining the adder and shifter, the states can be merged.


- The C-bit is no longer needed.

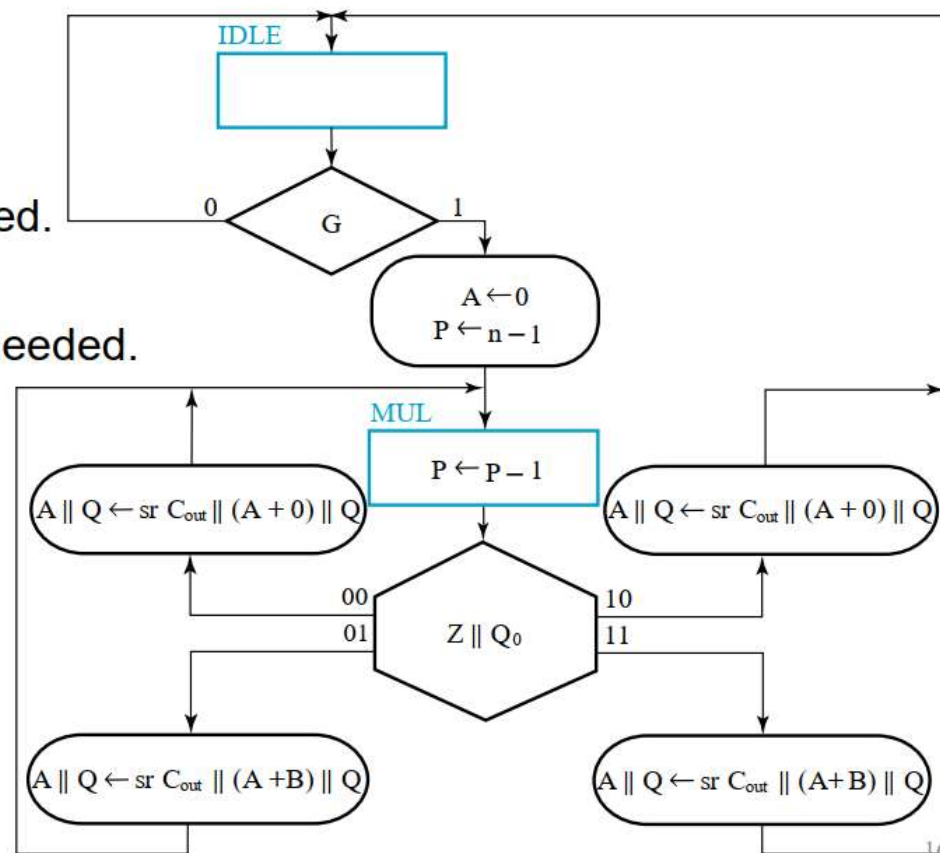- In this case, Z and Q_0 have been made into a vector.



Microprogrammed Control

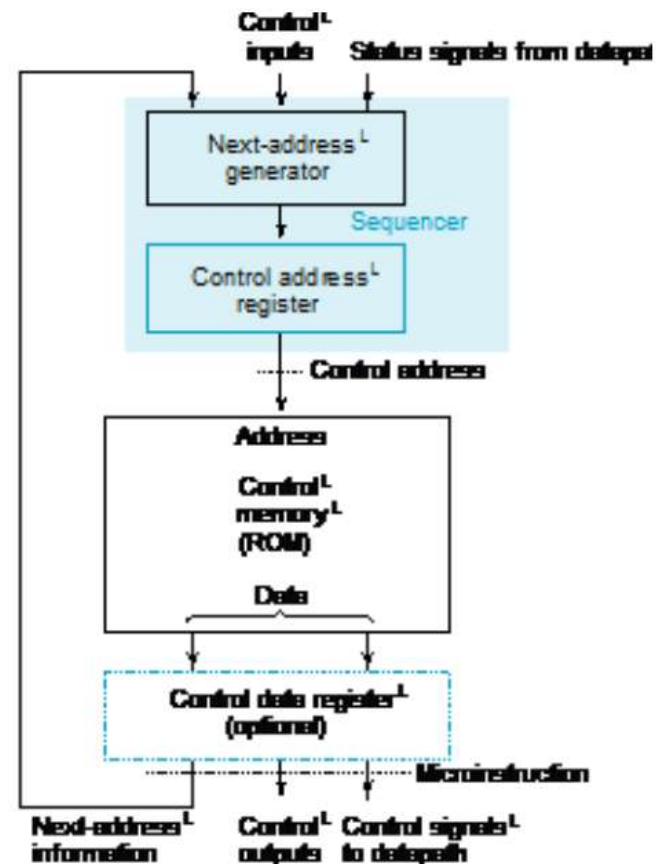- *Microprogrammed Control* — a control unit with binary control values stored as words in memory.
- *Microinstructions* — words in the control memory.
- *Microprogram* — a sequence of microinstructions.
- *Control Memory* — RAM or ROM memory holding the microinstructions.
 - *Writeable Control Memory* — RAM Memory into which microinstructions may be written



University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

Memories Overview

Dr. Yasir Al-Zubaidi

Third stage

2021

Memories


Read-Write Memory			Read-Only Memory
Volatile Memory		Non-volatile Memory	Mask-Programmed ROM (PROM) (nonvolatile)
Random Access	Sequential Access	EPROM	
DRAM SRAM	FIFO LIFO Shift Register CAM	EEPROM FLASH	

- **Volatile:** need electrical power
- **Nonvolatile:** magnetic disk, retains its stored information after the removal of power
- **Random access:** memory locations can be read or written in a random order
- **EPROM:** erasable programmable read-only memory
- **EEPROM:** electrically erasable programmable read-only memory
- **FLASH:** memory stick, USB disk
- **Access pattern:** sequential access: (video memory streaming) first-in-first-out (buffer), last-in-first-out (stack), shift register, content-addressable memory

Memories


- k address lines are decoded to address 2^k words of memory.
- Each word is n bits.
- Read and Write are single control lines defining the simplest memory operations.

A basic memory system:

 


Memory Operation Timing - Reading

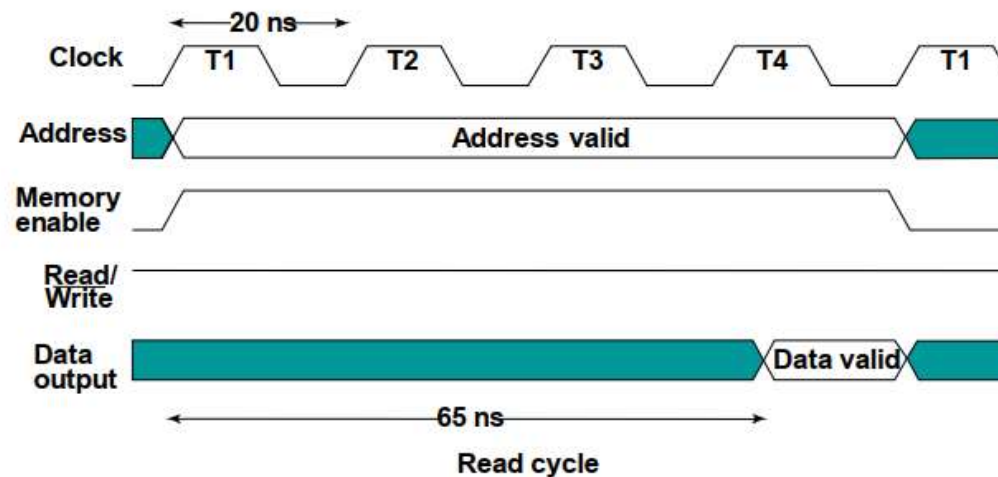- Most basic memories are asynchronous
 - Storage in latches or storage of electrical charge
 - **No clock**
 - Controlled by control inputs and address, which are controlled by CPU and **synchronized** by its own clock
- Timing of signal changes/data observation is critical to the operation



- Read cycle: the access time, the maximum time from the application of the address to the appearance of the data at the Data output.

Memory Operation Timing - Writing

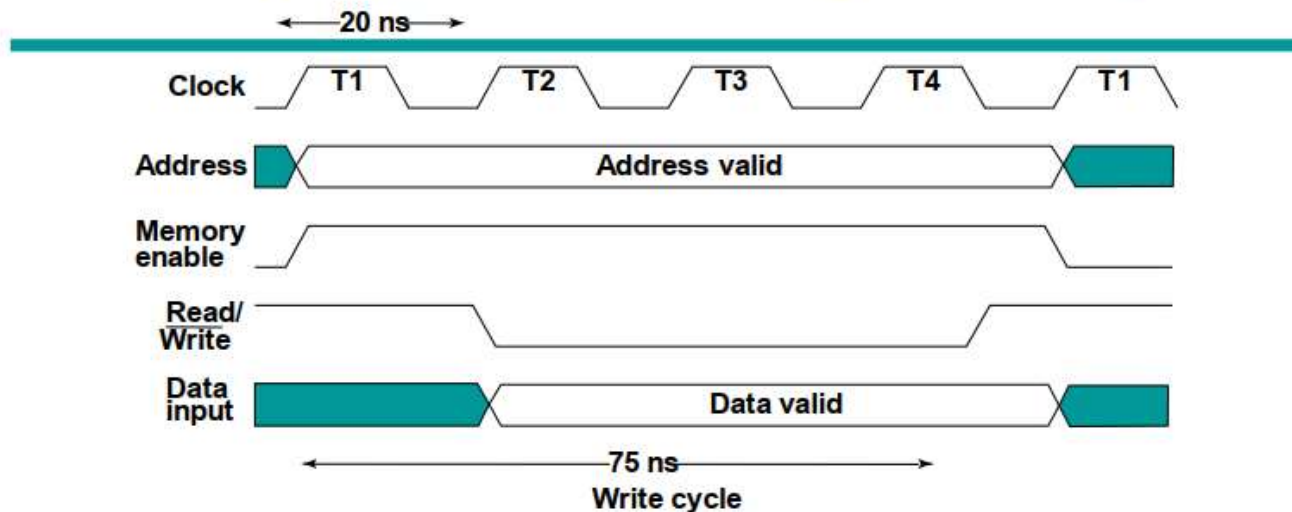

- Write cycle: the maximum time from the application of the address to the completion of all internal operations required to store a word
- Critical times measured with respect to edges of write pulse (1-0-1):
 - Address must be established at least a specified time before 1-0 and held for at least a specified time after 0-1 to avoid disturbing stored contents of other addresses
 - Data must be established at least a specified time before 0-1 and held for at least a specified time after 0-1 to write correctly

VHDL code for ROM

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
ENTITY rom8x4 IS  
PORT (  
  addr: in std_logic_vector(2 downto 0);  
  q: out std_logic_vector(3 downto 0));  
END rom8x4;
```

```
ARCHITECTURE behav OF rom8x4 IS  
BEGIN
```


```
PROCESS(addr)  
BEGIN  
  CASE addr IS  
    when "000" => q <= "0001";  
    when "001" => q <= "0000";  
    when "010" => q <= "0111";  
    when "011" => q <= "1101";  
    when "100" => q <= "1000";  
    when "101" => q <= "1100";  
    when "110" => q <= "0110";  
    when "111" => q <= "1011";  
    when others => NULL;  
  END case;  
END process;  
END behav;
```

Random Access Memories (RAMs)


- Read/Write memory
- Types:
 - Static RAM (SRAM):
 - Once a word is written at a location, it remains stored as long as power is applied to the chip, unless the same location is written again.
 - **Fast speed**, but **their cost per bit higher**.
 - Application: Caches memories in Microprocessor
 - Dynamic RAM (DRAM):
 - The data stored at each location must be periodically refreshed by reading it and then writing it back again, otherwise it disappears.
 - **Their density is greater and their cost per bit lower**, but the **speed is slower**.

SRAM Cell

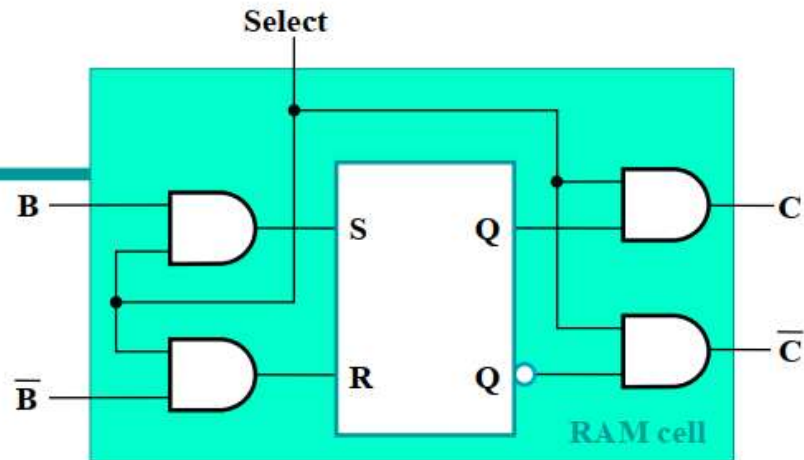- Array of storage cells used to implement static RAM




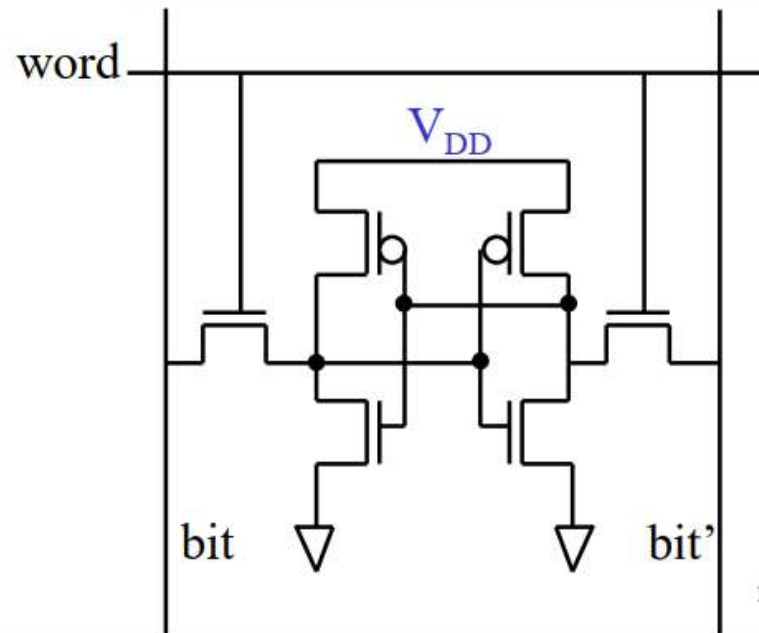- Storage Cell
 - SR Latch
 - Input "Select" for control
 - Dual Rail Data
 - Inputs B and \bar{B}
 - Outputs C and \bar{C}




SRAM Bit Slice

 - Represents all circuitry that is required for 2^n 1-bit words
 - Multiple RAM cells
 - Control Lines:
 - Word select i
– one for each word
 - $\text{Read}/\overline{\text{Write}}$
 - Bit Select
 - Data Lines:
 - Data in
 - Data out



2ⁿ-Word by 1-Bit RAM IC

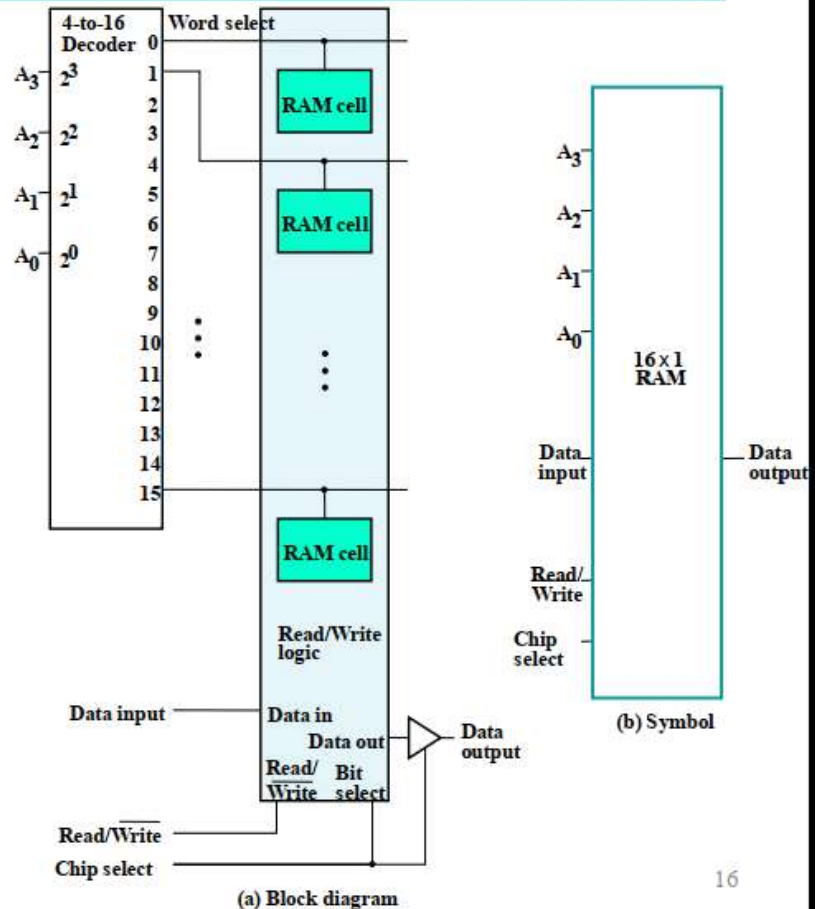- To build a RAM IC from a RAM slice:
 - Decoder decodes the n address lines to 2ⁿ word select lines
 - A 3-state buffer on the data output permits RAM ICs to be combined into a RAM with $c \times 2^n$ words




Cell Arrays and Coincident Selection

- Memory arrays can be very large =>
 - Large decoders
 - Large fanouts for the input bit lines
 - The decoder size and fanouts can be reduced by approximately \sqrt{n} using a coincident selection in a 2-D array: uses two decoders, one for words and one for bits:
 - Word select becomes Row select
 - Bit select becomes Column select


- See next slide for example

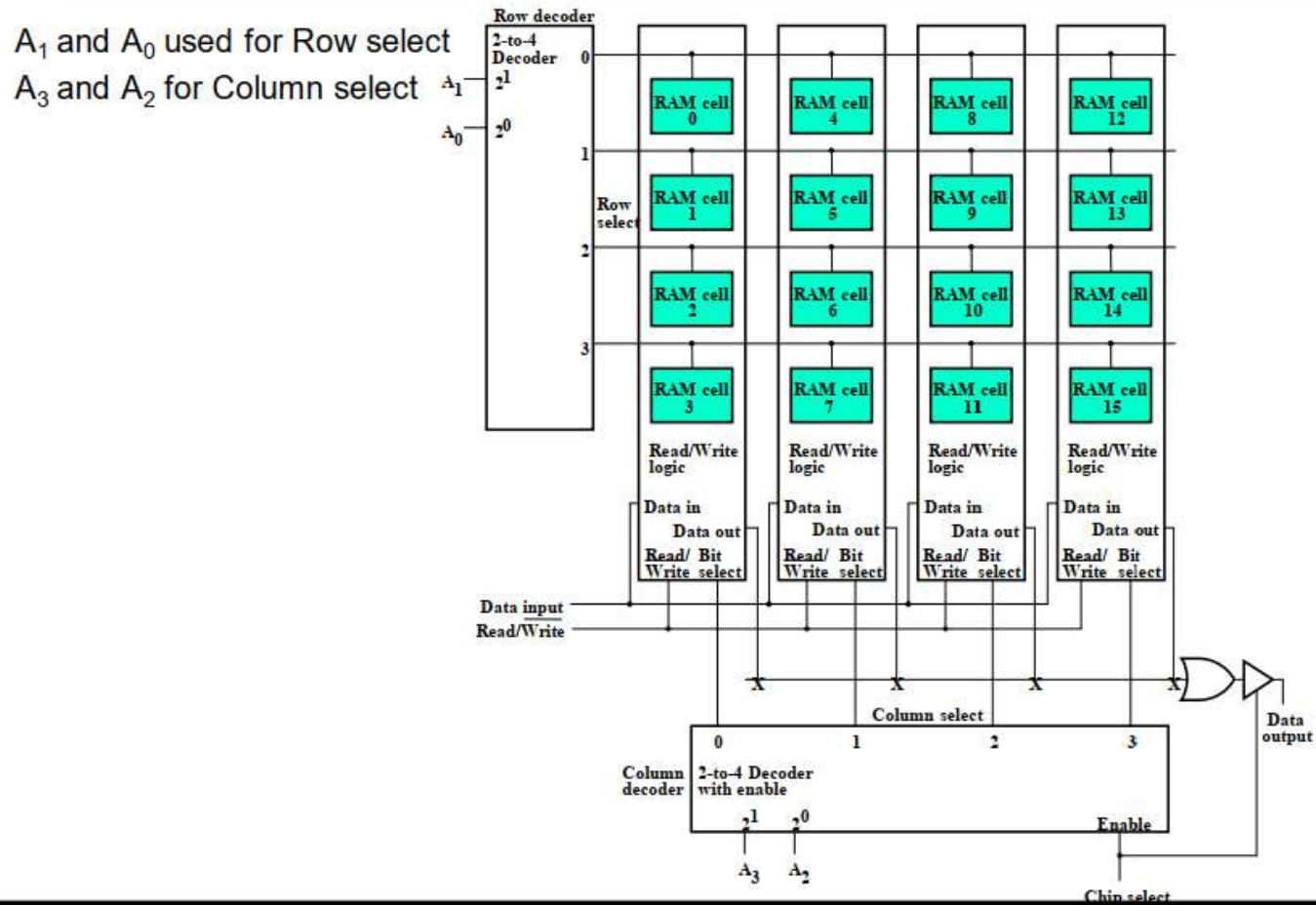Cell Arrays and Coincident Selection (Contd.)




Making Larger Memories

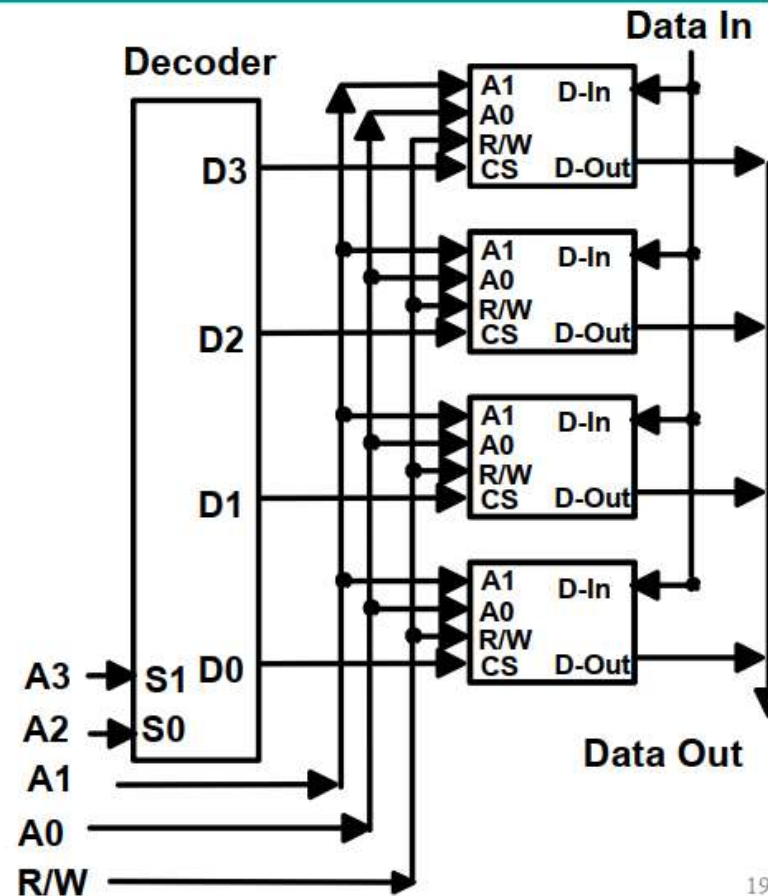- We can make larger memories from smaller ones by using the decoded higher order address bits to control CS (chip select) lines, tying all address, data, and R/W lines in parallel.
- A 16-Word by 1-Bit memory constructed using 4-Word by 1-Bit memory.



Making Wider Memories

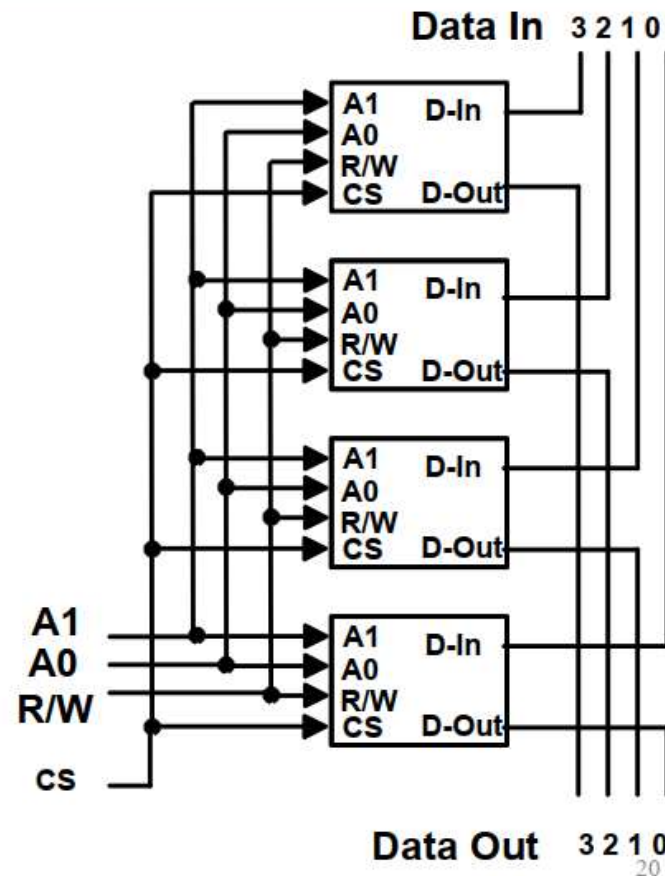- Tie the address and control lines in parallel and keep the data lines separate.
- Example: make a 4-word by 4-bit memory from 4, 4-word by 1-bit memories
- Note: Both 16x1 and 4x4 memories take 4-chips and hold 16 bits of data.




DRAM

- Basic Principle: Storage of information on capacitors.
- Charge and discharge of capacitor to change stored value
- Use of transistor as “switch” to:
 - Store charges
 - Charge or discharge


Dynamic RAM (Contd.)

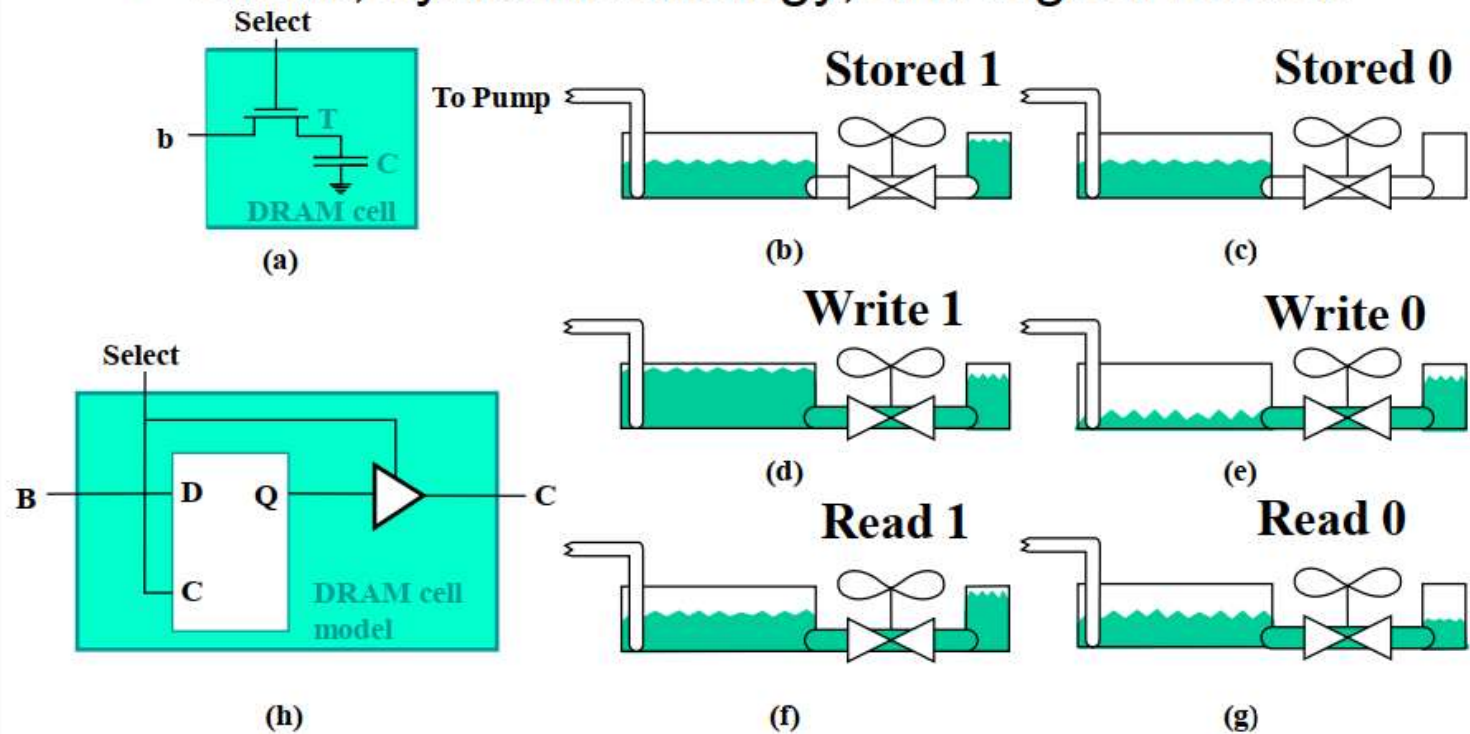- Circuit, hydraulic analogy, and logical model.



Dynamic RAM - Bit Slice

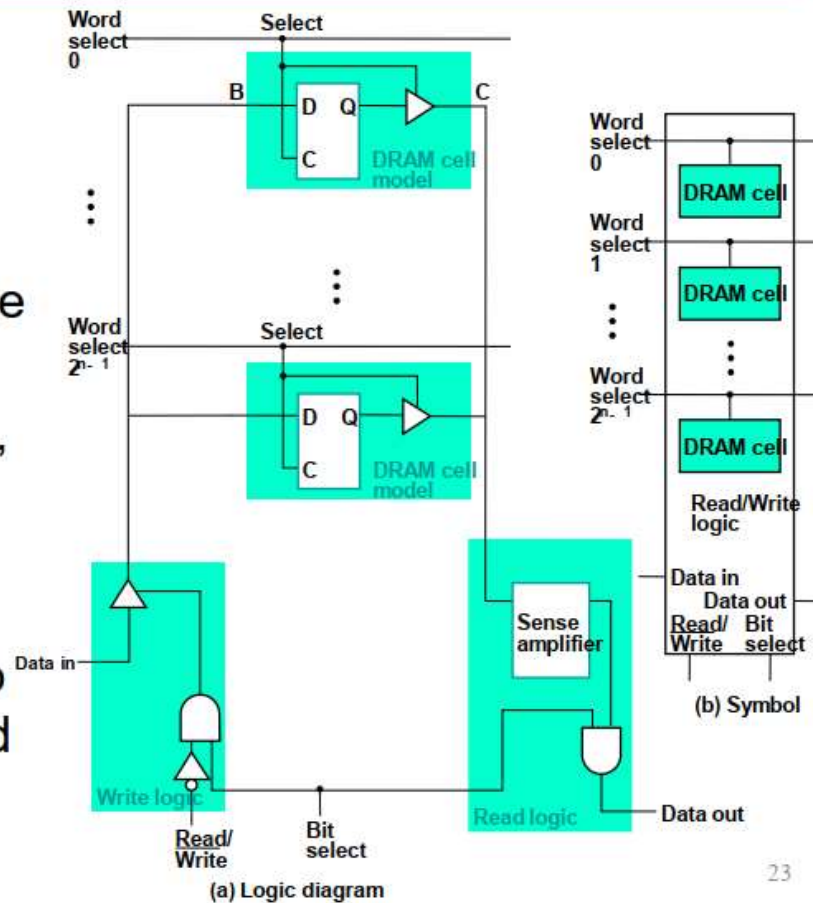- C driven by 3-state drivers
- Sense amplifier is used to change the small voltage change on C into H or L
- In the electronics, B, C, and the sense amplifier output are connected to make destructive read into non-destructive read



University Of Diyala
College Of Engineering
Department of Computer Engineering



Digital System Design II

Microprogramming

Dr. Yasir Al-Zubaidi

Third stage

2021

Microprogramming Overview


- **Part 1 – Datapaths**
 - Introduction
 - Datapath Example
 - Arithmetic Logic Unit (ALU)
 - Shifter
 - Datapath Representation and Control Word

- **Part 2 – A Simple Computer**
 - Instruction Set Architecture (ISA)
 - Single-Cycle Hardwired Control

 - **Part 3 – Multiple Cycle Hardwired Control**
 - Single Cycle Computer Issues
 - Sequential Control Design


Introduction

- Computer Specification
 - *Instruction Set Architecture (ISA)* - the specification of a computer's appearance to a programmer at its lowest level
 - *Computer Architecture* - a high-level description of the hardware implementing the computer derived from the ISA
 - The architecture usually includes additional specifications such as speed, cost, and reliability.




Introduction (Contd.)

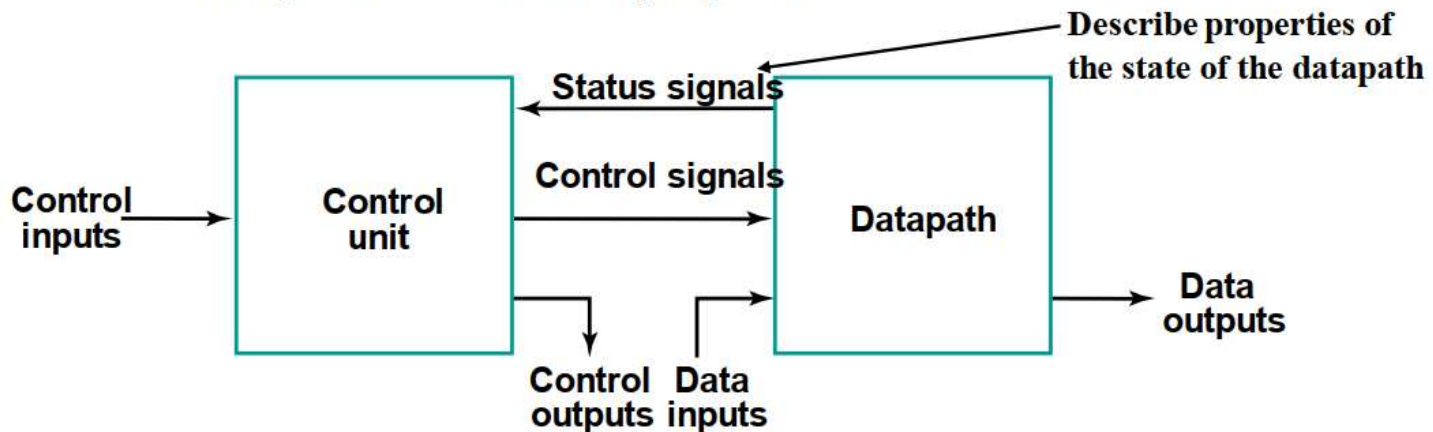- Simple computer architecture decomposed into:
 - Datapath: performing operations
 - A set of registers
 - Microoperations performed on the data stored in the registers
 - A control interface
 - Control unit: controlling datapath operations
 - Programmable & Non-programmable



Datapath Example

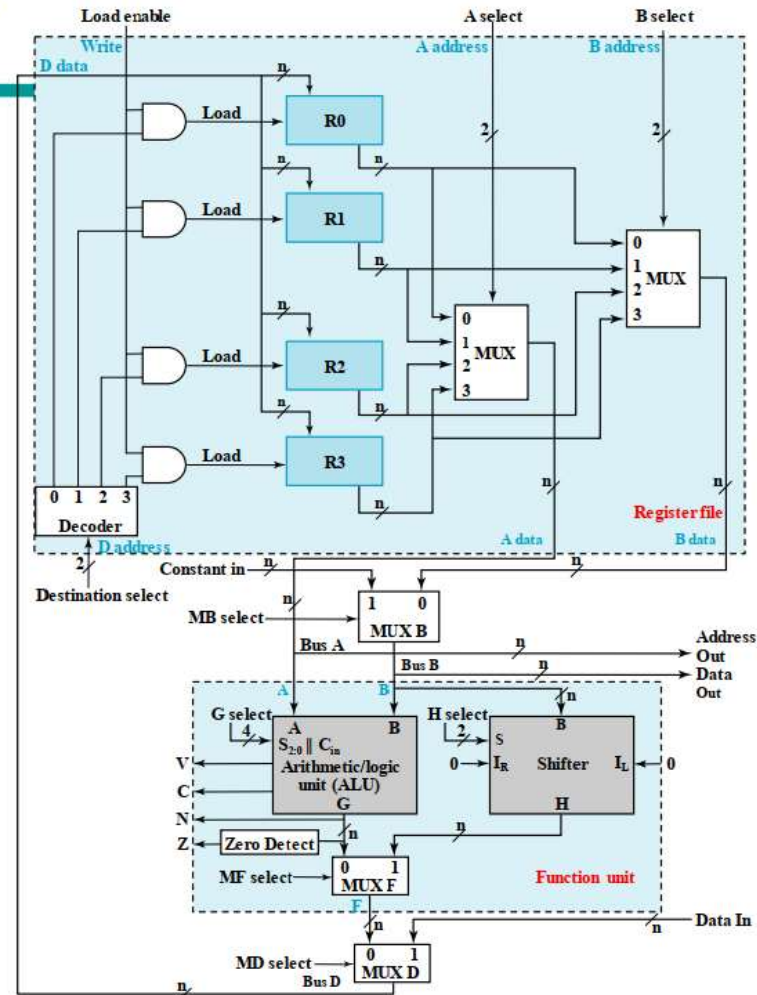
- Register file:
 - Four parallel-load regs
 - Two mux-based register selectors
 - Register destination decoder
- Microoperation Implementation
 - Mux B for external constant input
 - Buses A and B with external address and data outputs
 - Function Unit:
 - ALU and Shifter with Mux F for output select
 - Mux D for external data input
 - Logic for generating status bits V, C, N, Z



Datapath Example: Performing a Microoperation

Microoperation: $R0 \leftarrow R1 + R2$


- Apply 01 to A select to place contents of R1 onto Bus A
- Apply 10 to B select to place contents of R2 onto B data and apply 0 to MB select to place B data on Bus B
- Apply 0010 to G select to perform addition $G = \text{Bus A} + \text{Bus B}$
- Apply 0 to MF select and 0 to MD select to place the value of G onto BUS D
- Apply 00 to Destination select to enable the Load input to R0
- Apply 1 to Load Enable to force the Load input to R0 to 1 so that R0 is loaded on the clock pulse (not shown)
- The overall microoperation requires 1 clock cycle

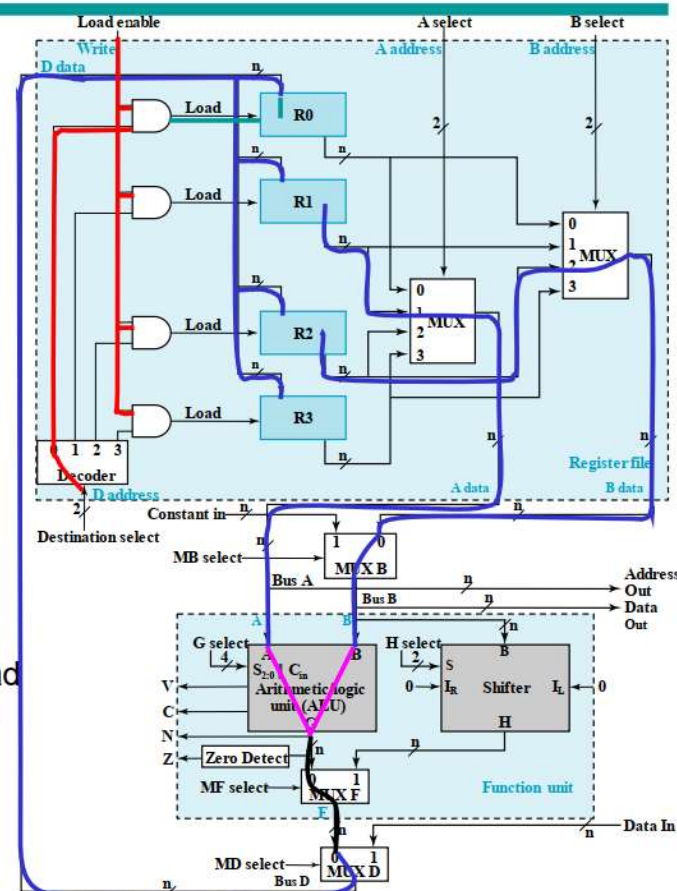

Datapath Example: Key Control Actions for Microoperation Alternatives


Various microoperations:

- Perform a shift microoperation: **apply 1 to MF select**
- Use a constant in a micro-operation using Bus B: apply 1 to MB select
- Provide an address and data for a memory or output write microoperation – apply 0 to Load enable to prevent register loading
- Provide an address and obtain data for a memory or output read microoperation – apply 1 to MD select
- For some of the above, other control signals become don't cares

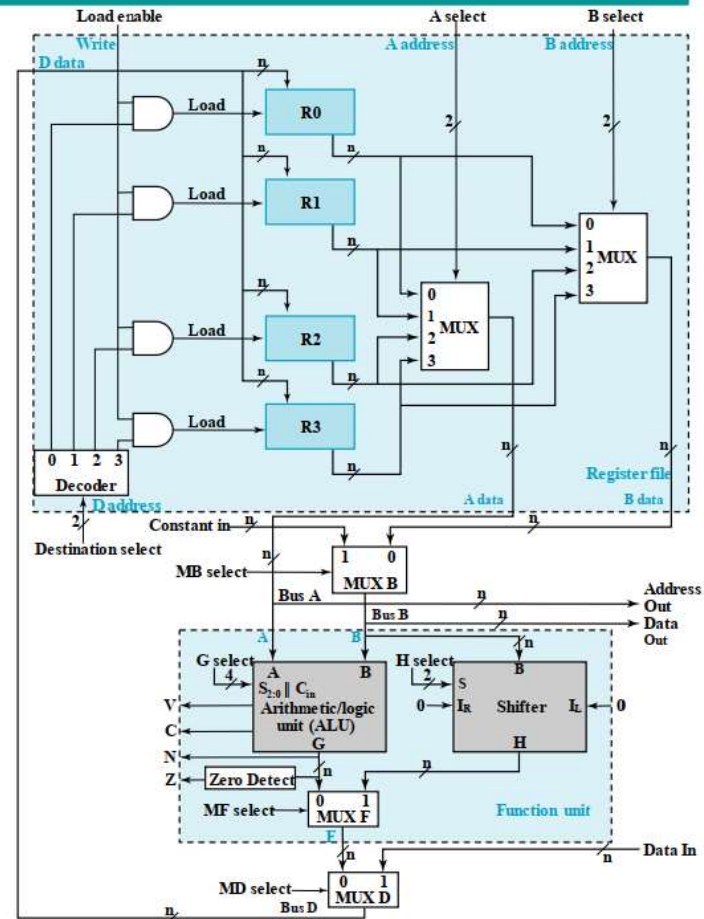

Arithmetic Logic Unit (ALU)

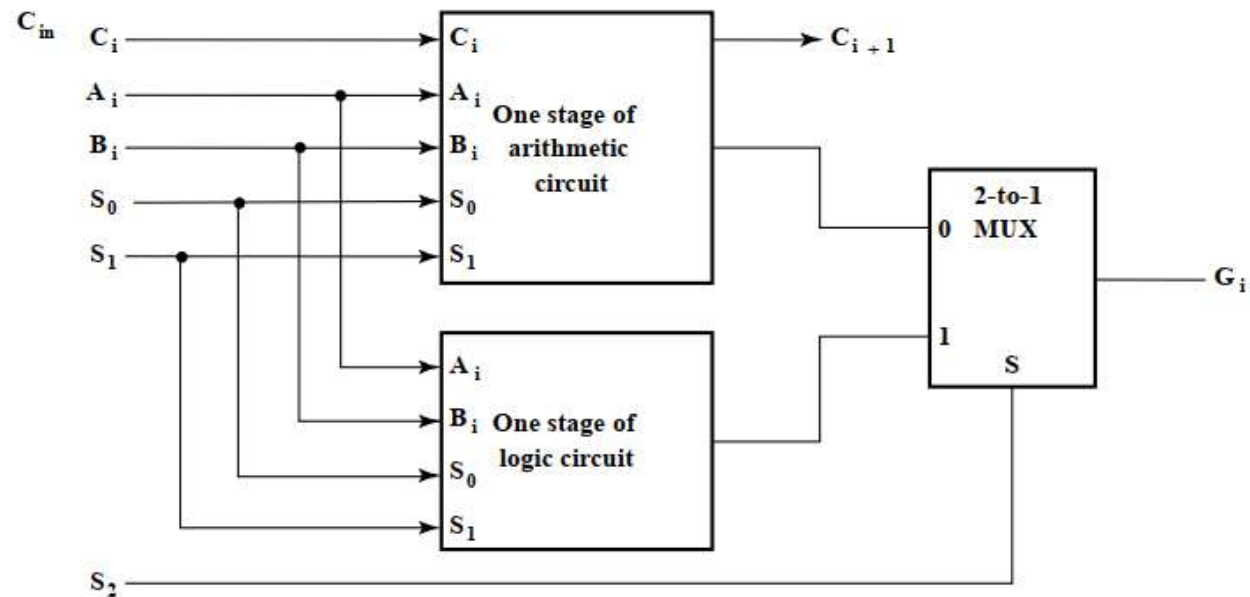- Decompose the ALU into:
 - An arithmetic circuit & A logic circuit
 - A selector to pick between the two circuits




Arithmetic Circuit Design

- Arithmetic circuit design


- Decompose the arithmetic circuit into:
 - An n-bit parallel adder
 - A block of logic that selects four choices for the B input to the adder

- There are only four functions of B to select as Y in $G = A + Y + C_{in}$:

	$C_{in} = 0$	$C_{in} = 1$
• 0	$G = A$	$G = A + 1$
• B	$G = A + B$	$G = A + B + 1$
• \overline{B}	$G = A + \overline{B}$	$G = A + \overline{B} + 1$
• 1	$G = A - 1$	$G = A$

 


4-Bit Basic Left/Right Shifter

 

- Serial Inputs:
 - I_R for right shift
 - I_L for left shift
- Shift Functions:
 - $(S_1, S_0) = 00$ Pass B unchanged
 - 01 Right shift
 - 10 Left shift
 - 11 Unused

Barrel Shifter

 


- A rotate is a shift in which the bits shifted out are inserted into the positions vacated
- The circuit rotates its contents left from 0 to 3 positions depending on S:


S = 00 position unchanged	S = 10 rotate left by 2 positions
S = 01 rotate left by 1 positions	S = 11 rotate left by 3 positions

Combinational Shifter from MUXes

Basic Building Block

 

8-bit right shifter

 

• - Example 8-bit:

- Layer 1 shifts by 0, 4
- Layer 2 shifts by 0, 2
- Layer 3 shifts by 0, 1

▪ Large barrel shifters can be constructed using:

- Layers of multiplexers
- 2 - dimensional array circuits designed at the electronic level