

University of Diyala

College of Engineering

Department of Power and Electrical Machines Engineering

Academic Year 2025-2026

Second Year – Bachelor (BSc) – EPE 203

Fall Semester

EPE 203 Electric Circuits Analysis I

Lecture 3

Assist. Lect. Ibrahim I. Ibrahim

Lecture 3

Power in a balanced system & Unbalanced three-phase systems.

Part 1:

Power in a balanced system

A balanced three-phase system means:

- 1) All phase voltages (or currents) have equal magnitudes.
- 2) They are separated by 120° from each other in phase.
- 3) The loads connected to each phase are identical in impedance.

The power in a balanced three-phase system either its Y-connection or Δ -connection means the power absorbed by the load.

The power components are:

- 1- Active (Real) Power : P (W) (Useful work)
- 2- Reactive Power : Q (VAR) (Energy for magnetic fields)
- 3- Apparent Power : S_{app} (VA) (The total power delivered)

Phase form

$$P = 3V_P I_P \cos \varphi$$

$$Q = 3V_P I_P \sin \varphi$$

$$S_{app} = 3V_P I_P$$

Complex Power is a vector sum of real power and reactive power

Apparent Power is the magnitude of the complex power, representing the total power demanded

The Power Factor $\cos \varphi$ can be calculated as: $\cos \varphi = \frac{P}{S}$

φ is the phase angle between **phase voltage** and **phase current**

Line form

$$P = \sqrt{3}V_L I_L \cos \varphi$$

$$Q = \sqrt{3}V_L I_L \sin \varphi$$

$$S_{app} = \sqrt{3}V_L I_L$$

$$S = P + jQ$$


$$|S| = \sqrt{P^2 + Q^2}$$

Ex1: Determine the total average power, reactive power, and complex power at the source and at the load.

$$Z_Y = Z_l + Z_L \Rightarrow Z_Y = (5 - j2) + (10 + j8) = 15 + j6 \Omega \quad 15 + j6 \Omega = 16.155 \angle 21.8^\circ \Omega$$

It is sufficient to consider one phase, as the system is balanced.
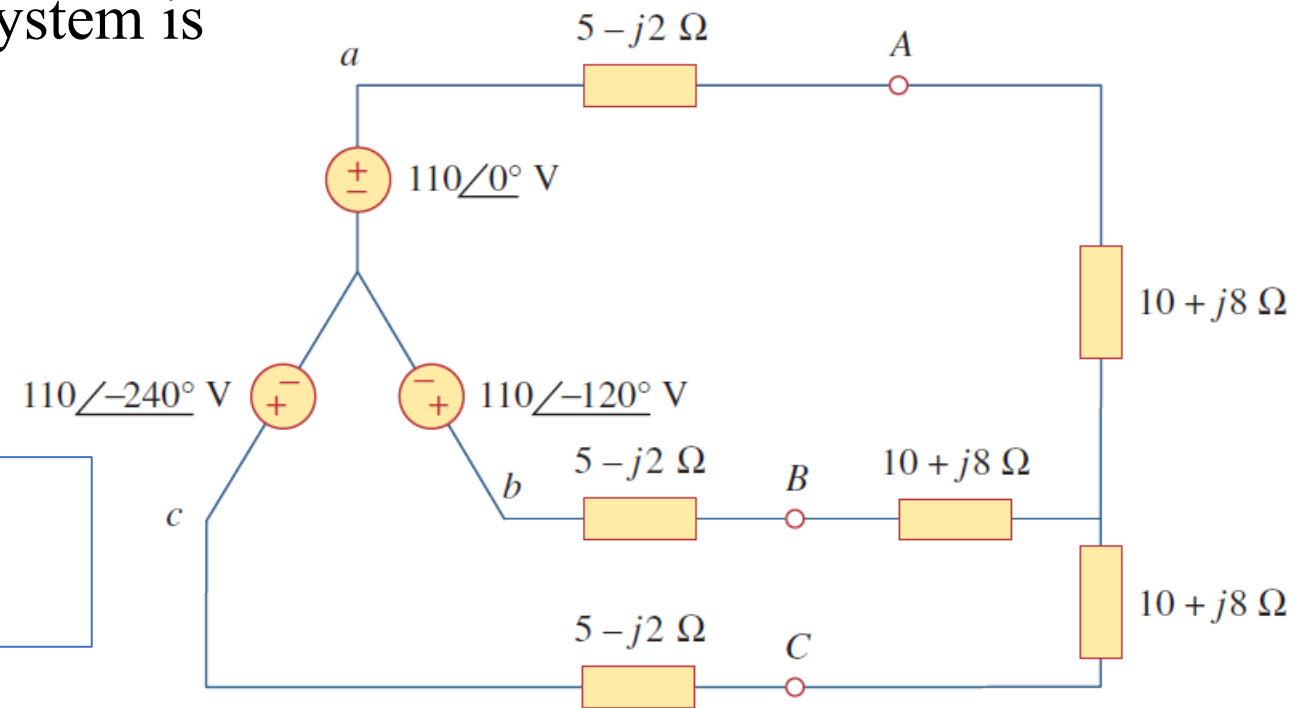
$$I_p = \frac{V_p}{Z_Y} = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$



Thus, at the source, the complex power absorbed is

$$\begin{aligned}\mathbf{S}_s &= -3\mathbf{V}_p\mathbf{I}_p^* = -3(110\angle 0^\circ)(6.81\angle 21.8^\circ) \\ &= -2247\angle 21.8^\circ = -(2087 + j834.6) \text{ VA}\end{aligned}$$

The real or average power absorbed is -2087 W and the reactive power is -834.6 VAR.

At the load, the complex power absorbed is

$$\mathbf{S}_L = 3|\mathbf{I}_p|^2\mathbf{Z}_p$$

where $\mathbf{Z}_p = 10 + j8 = 12.81\angle 38.66^\circ$ and $\mathbf{I}_p = \mathbf{I}_a = 6.81\angle -21.8^\circ$. Hence,

$$\begin{aligned}\mathbf{S}_L &= 3(6.81)^2 12.81\angle 38.66^\circ = 1782\angle 38.66^\circ \\ &= (1392 + j1113) \text{ VA}\end{aligned}$$

Ex2: A three-phase motor can be regarded as a balanced Y-load. A three-phase motor draws 5.6 kW when the line voltage is 220 V and the line current is 18.2 A. Determine the power factor of the motor.

The apparent power is

$$S = \sqrt{3}V_L I_L = \sqrt{3}(220)(18.2) = 6935.13 \text{ VA}$$

Since the real power is

$$P = S \cos \theta = 5600 \text{ W}$$

the power factor is

$$\text{pf} = \cos \theta = \frac{P}{S} = \frac{5600}{6935.13} = 0.8075$$

Part 2:

Unbalanced three-phase systems

An **unbalanced system** is due to *unbalanced voltage sources* or an *unbalanced load*.

An **unbalanced system** as shown in **Figure 1** is caused by two possible situations:

- (1) The source voltages are not equal in magnitude and/or differ in phase by angles that are unequal.
- (2) load impedances are unequal.

An example of an unbalanced three-phase system that consists of balanced source voltages (not shown in the **Figure 1**) and an unbalanced Y-connected load (shown in the **Figure 1**).

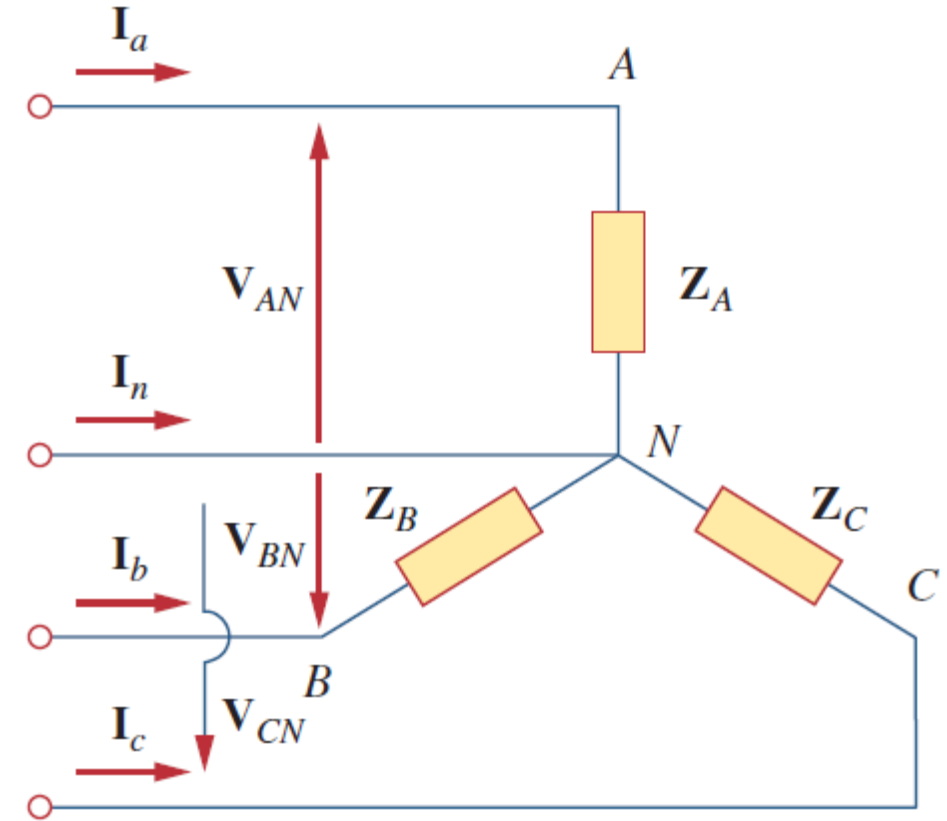


Figure 1: Unbalanced three-phase Y-connected load.

Since the load is unbalanced, Z_A , Z_B and Z_C are not equal. The line currents are determined by Ohm's law as

$$\mathbf{I}_a = \frac{\mathbf{V}_{AN}}{\mathbf{Z}_A}, \quad \mathbf{I}_b = \frac{\mathbf{V}_{BN}}{\mathbf{Z}_B}, \quad \mathbf{I}_c = \frac{\mathbf{V}_{CN}}{\mathbf{Z}_C}$$

This set of **unbalanced** line currents produces current in the neutral line, which is **not zero** as in a **balanced system**.

$$I_n = -(I_a + I_b + I_c) \neq 0$$

To calculate power in an **unbalanced** three-phase system requires that we find the power in **each phase**. The total power is not simply three times the power in one phase but the sum of the powers in the three phases.

Ex3: The **unbalanced** Y-load of **Figure 1** has balanced voltages of 100 V and the acb sequence. Calculate the line currents and the neutral current. Take $Z_A = 15\Omega$, $Z_B = 10 + j5\Omega$ and $Z_C = 6 - j8\Omega$.

$$\mathbf{I}_a = \frac{100\angle 0^\circ}{15} = 6.67\angle 0^\circ \text{ A}$$


$$\mathbf{I}_b = \frac{100\angle 120^\circ}{10 + j5} = \frac{100\angle 120^\circ}{11.18\angle 26.56^\circ} = 8.94\angle 93.44^\circ \text{ A}$$

$$\mathbf{I}_c = \frac{100\angle -120^\circ}{6 - j8} = \frac{100\angle -120^\circ}{10\angle -53.13^\circ} = 10\angle -66.87^\circ \text{ A}$$

The current in the neutral line is

$$\begin{aligned}\mathbf{I}_n &= -(\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c) = -(6.67 - 0.54 + j8.92 + 3.93 - j9.2) \\ &= -10.06 + j0.28 = 10.06\angle 178.4^\circ \text{ A}\end{aligned}$$

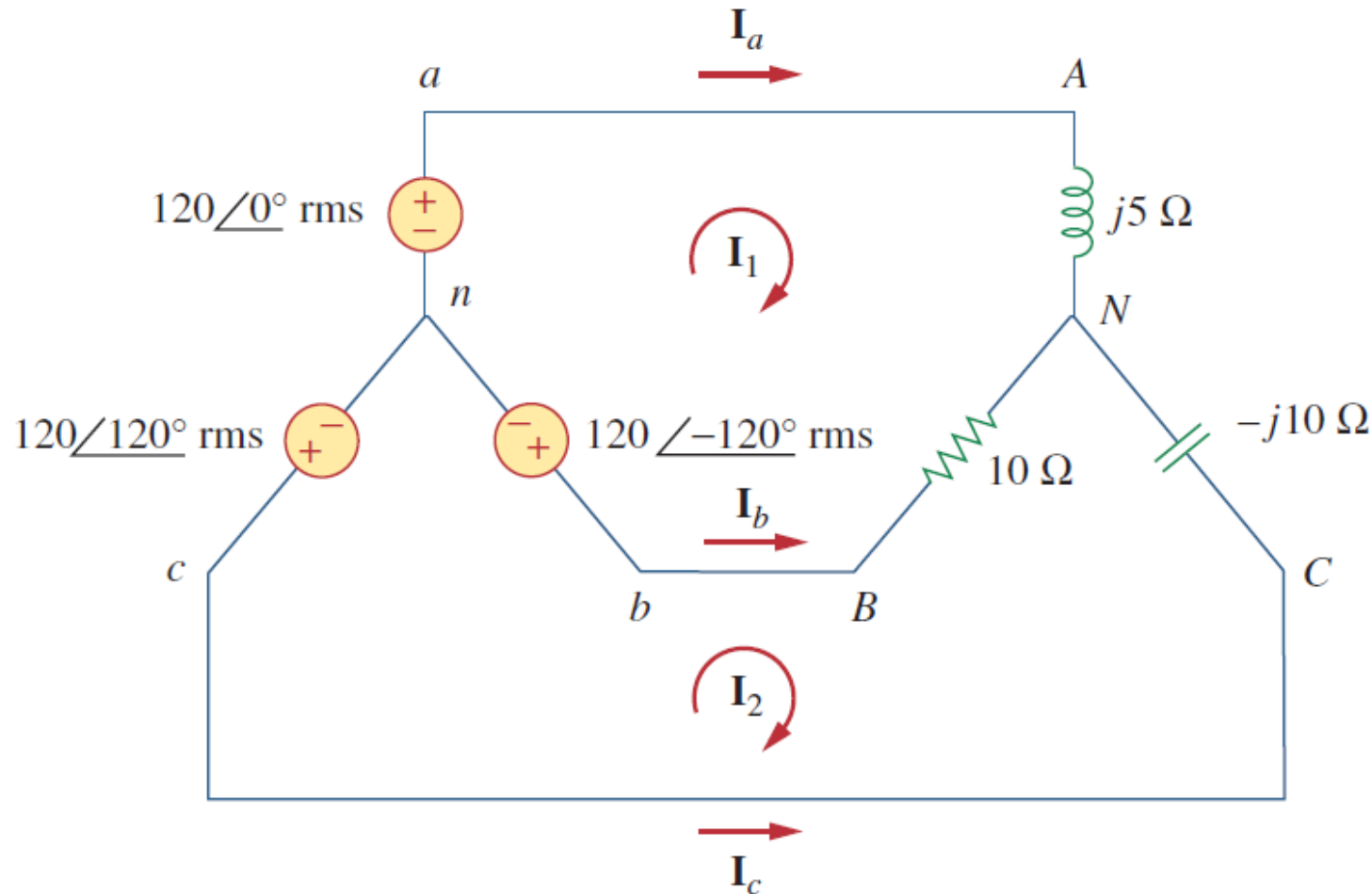Ex4: For the unbalanced system shown below, find: (a) the line currents, (b) the total complex power absorbed by the load, and (c) the total complex power absorbed by the source.



(a) We use mesh analysis to find the required currents.

For mesh 1, $(10 + j5)I_1 - 10I_2 = 120\sqrt{3}\angle 30^\circ$

For mesh 2, $-10I_1 + (10 - j10)I_2 = 120\sqrt{3}\angle -90^\circ$

$$\begin{bmatrix} 10 + j5 & -10 \\ -10 & 10 - j10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 120\sqrt{3}\angle 30^\circ \\ 120\sqrt{3}\angle -90^\circ \end{bmatrix}$$

Now, from the above mesh 1 and mesh 2 equations we obtained the matrix, then we have to calculate the determinants so as to find the I_1 and I_2 .

The determinants are

$$\Delta = \begin{bmatrix} 10 + j5 & -10 \\ -10 & 10 - j10 \end{bmatrix} = 70.71 \angle -45^\circ$$

$$\Delta_1 = \begin{bmatrix} 120\sqrt{3} \angle 30^\circ & -10 \\ 120\sqrt{3} \angle -90^\circ & 10 - j10 \end{bmatrix} = 4015 \angle -45^\circ$$

$$\Delta_2 = \begin{bmatrix} 10 + j5 & 120\sqrt{3} \angle 30^\circ \\ -10 & 120\sqrt{3} \angle -90^\circ \end{bmatrix} = 3023.4 \angle -20.1^\circ$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{4015 \angle -45^\circ}{70.71 \angle -45^\circ} = 56.78 \text{ A} \qquad I_2 = \frac{\Delta_2}{\Delta} = \frac{3023.4 \angle -20.1^\circ}{70.71 \angle -45^\circ} = 42.75 \angle 24.9^\circ \text{ A}$$

The line currents are

$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_1 = 56.78 \text{ A}, & \mathbf{I}_c &= -\mathbf{I}_2 = 42.75 \angle -155.1^\circ \text{ A} \\ \mathbf{I}_b &= \mathbf{I}_2 - \mathbf{I}_1 = 38.78 + j18 - 56.78 = 25.46 \angle 135^\circ \text{ A} \end{aligned}$$

(b) We can now calculate the complex power absorbed by the load.

For phase A,

$$\mathbf{S}_A = |\mathbf{I}_a|^2 \mathbf{Z}_A = (56.78)^2(j5) = j16,120 \text{ VA}$$

For phase B,

$$\mathbf{S}_B = |\mathbf{I}_b|^2 \mathbf{Z}_B = (25.46)^2(10) = 6480 \text{ VA}$$

For phase C,

$$\mathbf{S}_C = |\mathbf{I}_c|^2 \mathbf{Z}_C = (42.75)^2(-j10) = -j18,276 \text{ VA}$$

The total complex power absorbed by the load is

$$\mathbf{S}_L = \mathbf{S}_A + \mathbf{S}_B + \mathbf{S}_C = 6480 - j2156 \text{ VA}$$

(c) We check the result above by finding the power absorbed by the source. For the voltage source in phase a,

$$\mathbf{S}_a = -\mathbf{V}_{an}\mathbf{I}_a^* = -(120\angle 0^\circ)(56.78) = -6813.6 \text{ VA}$$

For the source in phase b,

$$\begin{aligned}\mathbf{S}_b &= -\mathbf{V}_{bn}\mathbf{I}_b^* = -(120\angle -120^\circ)(25.46\angle -135^\circ) \\ &= -3055.2\angle 105^\circ = 790 - j2951.1 \text{ VA}\end{aligned}$$

For the source in phase c,

$$\begin{aligned}\mathbf{S}_c &= -\mathbf{V}_{cn}\mathbf{I}_c^* = -(120\angle 120^\circ)(42.75\angle 155.1^\circ) \\ &= -5130\angle 275.1^\circ = -456.03 + j5109.7 \text{ VA}\end{aligned}$$

The total complex power absorbed by the three-phase source is

$$\mathbf{S}_s = \mathbf{S}_a + \mathbf{S}_b + \mathbf{S}_c = -6480 + j2156 \text{ VA}$$