

University of Diyala

College of Engineering

Department of Power and Electrical Machines Engineering

Academic Year 2025-2026

Second Year – Bachelor (BSc) – EPE 204

Spring Semester

EPE 204 Electric Circuits Analysis II

Lecture 3

Assist. Lect. Ibrahim I. Ibrahim

Lecture 3

Step Response of an RC and an RL Circuits

The Step Function

A **step input** is a sudden change in voltage or current from zero to a constant value.

Mathematically, the unit step function is:

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$

When the dc source of an RC/RL circuit is suddenly applied, the voltage or current source can be modelled as a step function, and the response is known as a *step response*.

The **step response** of a circuit is the behavior of it when the excitation is the step function, which may be a voltage or a current source.

Part 1

Step Response of an RC Circuits

Consider the RC circuit in Fig. (a) which can be replaced by the circuit in Fig. (b), where V_s is a constant dc voltage source. Again, select the capacitor voltage as the circuit response to be determined.


Assume an initial voltage on the capacitor V_0 , although this is not necessary for the step response. Since the voltage of a capacitor cannot change at once,

$$v(0^-) = v(0^+) = V_0$$


where $v(0^-)$ is the voltage across the capacitor just before switching and $v(0^+)$ is its voltage immediately after switching.

After applying KCL, we obtain:
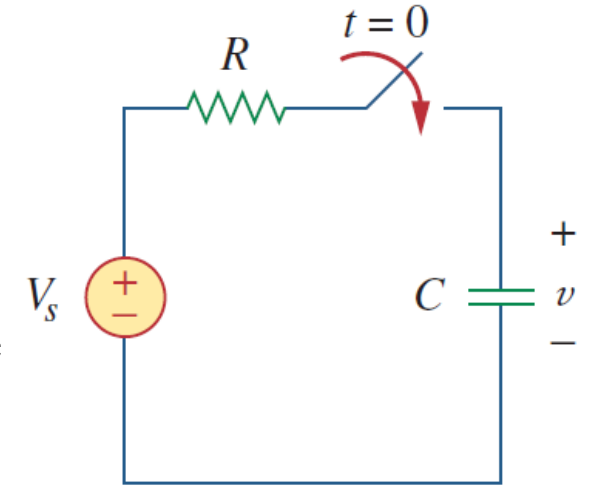
$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$



(a)

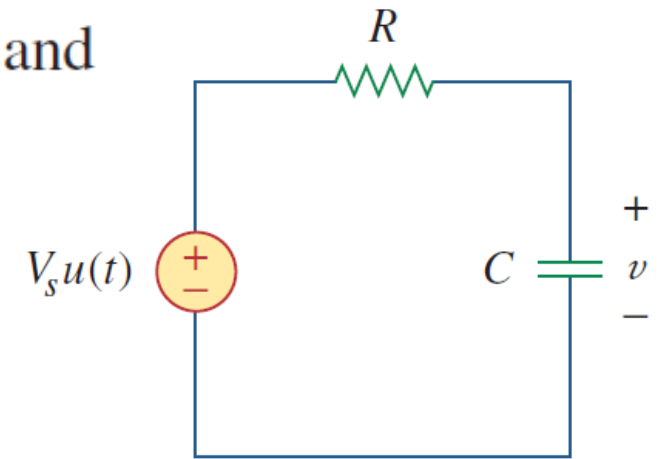

(b)

$$\text{Complete response} = \underset{\text{stored energy}}{\text{natural response}} + \underset{\text{independent source}}{\text{forced response}}$$
$$v = v_n + v_f$$
$$v_n = V_o e^{-t/\tau}$$
$$v_f = V_s(1 - e^{-t/\tau})$$

The second way to break the complete response into a “transient response” and a “steady-state

$$\text{Complete response} = \underset{\text{temporary part}}{\text{transient response}} + \underset{\text{permanent part}}{\text{steady-state response}}$$

or

$$v = v_t + v_{ss}$$

where

$$v_t = (V_o - V_s)e^{-t/\tau}$$

and

$$v_{ss} = V_s$$

The **transient response** is the circuit's temporary response that will die out with time.

The **steady-state response** is the behavior of the circuit a long time after an external excitation is applied.

The **first decomposition** of the complete response is in terms of **the source of the responses**, while the **second decomposition** is in terms of **the permanency of the responses**. Under certain conditions, the **natural response** and **transient response** are the same. The same can be said about the **forced response** and **steady-state response**.

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

Thus, to find the step response of an RC circuit requires three things:

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$.
3. The time constant τ .

Part 2

Step Response of an RL Circuits

EPE 204 Electric Circuits Analysis II

Lecture 3

Consider the RL circuit in Fig.(a), which may be replaced by the circuit in Fig.(b).

Again, our goal is to find the inductor current i as the circuit response. Let the response be the sum of the transient response and the steady-state response,


$$i = i_t + i_{ss}$$

We know that the transient response is always a decaying exponential, that is,


$$i_t = Ae^{-t/\tau}, \quad \tau = \frac{L}{R}$$

where A is a constant to be determined.

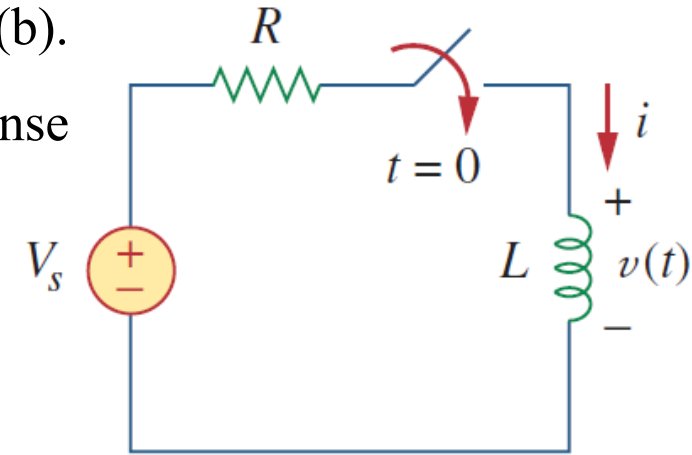The steady-state response is the value of the current a long time after the switch in Fig.(a) is closed.



(a)

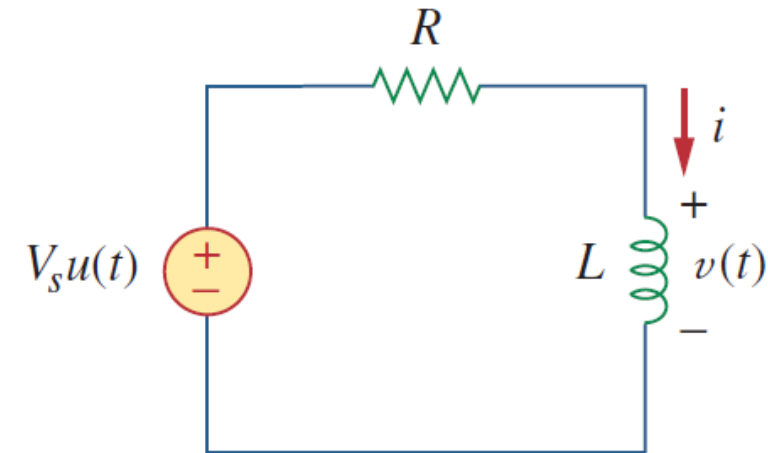

(b)

We know that the transient response essentially dies out after five-time constants. At that time, the inductor becomes a short circuit, and the voltage across it is zero. The entire source voltage V_s appears across R . Thus, the steady-state response is

$$i_{ss} = \frac{V_s}{R}$$

$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

We now determine the constant A from the initial value of i . Let I_0 be the initial current through the inductor, which may come from a source other than V_s . Since the current through the inductor cannot change instantaneously,

$$i(0^+) = i(0^-) = I_0$$

Thus, at $t = 0$,

$$I_0 = A + \frac{V_s}{R}$$

From this, we obtain A as

$$A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$

This is the complete response of the RL circuit.

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

Thus, to find the step response of an RL circuit requires three things:

1. The initial inductor current $i(0)$ at $t = 0$.
2. The final inductor current $i(\infty)$.
3. The time constant τ .