

University of Diyala

College of Engineering

Department of Power and Electrical Machines Engineering

Academic Year 2025-2026

Second Year – Bachelor (BSc) – EPE 204

Spring Semester

EPE 204 Electric Circuits Analysis II

Lecture 4

Assist. Lect. Ibrahim I. Ibrahim

Lecture 4

Initial and Final Values

A ***second-order circuit*** is characterized by a second-order differential equation. It consists of **resistors** and the equivalent of **two energy storage elements**.

Perhaps the major problem arise in handling second-order circuits is finding the initial and final conditions on circuit variables. It's always easy getting the initial and final values of v and i but often have difficulty finding the initial values of their derivatives: dv/dt and di/dt . So that, this lecture is explicitly devoted to the explanation of getting, $v(0)$, $i(0)$, $dv(0)/dt$, $di(0)/dt$, $i(\infty)$, and $v(\infty)$.

There are two key points to keep in mind in determining the initial conditions. **First**—as always in circuit analysis—we must carefully handle the polarity of voltage across the capacitor and the direction of the current through the inductor. Keep in mind that v and i are defined strictly according to the passive sign convention (See **Fig.1 & Fig.2**). One should carefully observe how these are defined and apply them accordingly. **Second**, keep in mind that the capacitor voltage is always continuous so that $v(0^+) = v(0^-)$ and the inductor current is always continuous so that $i(0^+) = i(0^-)$.

where $t = 0^-$ denotes the time just before a switching event and $t = 0^+$ is the time just after the switching event, assuming that the switching event takes place at $t = 0$.

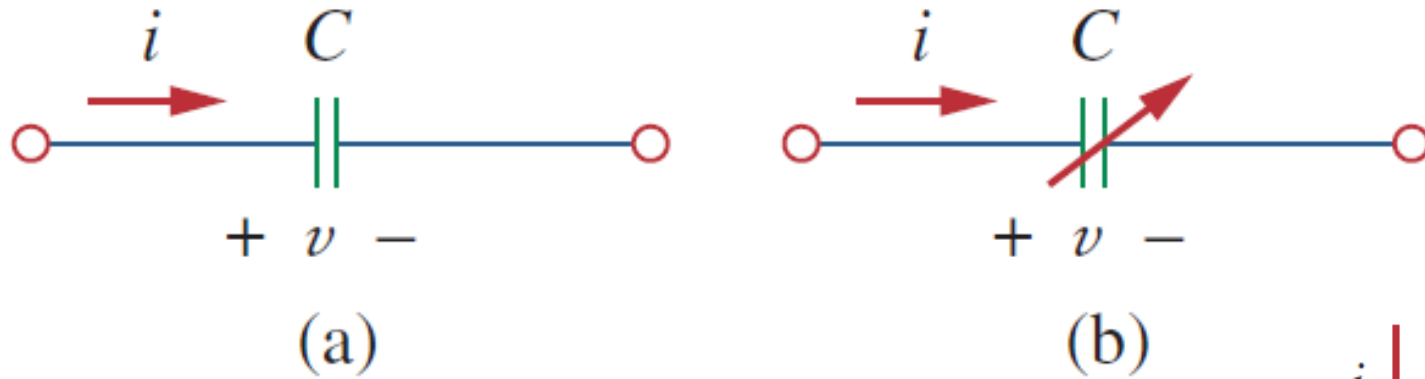


Fig.1 (a) Fixed capacitor, (b) variable capacitor.


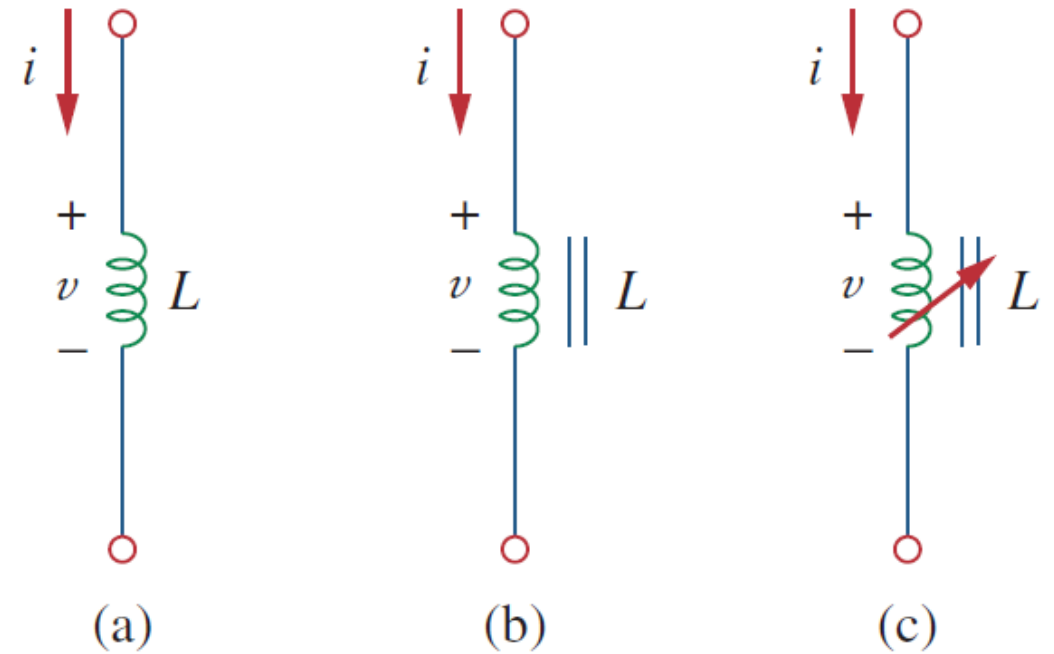


Fig.2 (a) air-core, (b) iron-core, (c) variable iron-core.

Ex:1/ The switch in the following figure has been closed for a long time and it is opened at $t=0$. Find:

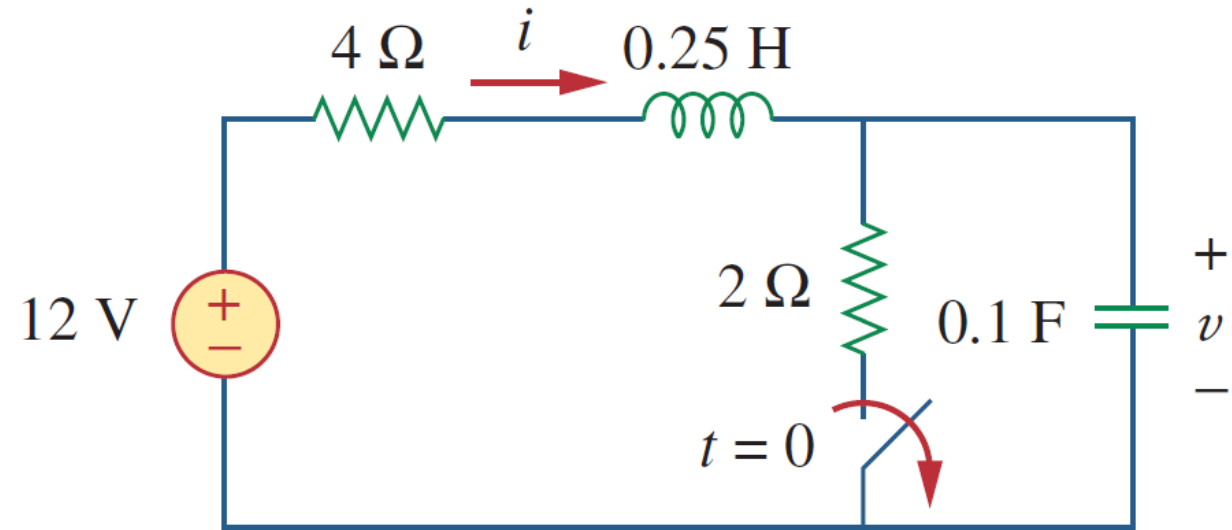- a) $i(0^+)$ and $v(0^+)$
- b) $\frac{di(0^+)}{dt}$ and $\frac{dv(0^+)}{dt}$
- c) $i(\infty)$ and $v(\infty)$



Let's study each scenario of these $t = 0^-$, $t = 0$ and $t = 0^+$ for the given circuit.

(a) If the switch is closed a long time before $t = 0$, it means that the circuit has reached dc steady state at $t = 0$. At dc steady state, the inductor acts like a short circuit, while the capacitor acts like an open circuit, so we have the circuit in the figure below at $t = 0^-$. So that we'll have:


$$i(0^-) = \frac{12}{4 + 2} = 2\text{A}$$

$$v(0^-) = 2i(0^-) = 4\text{V}$$

As the inductor current and the capacitor voltage cannot change abruptly, this leads to:

$$i(0^+) = i(0^-) = 2\text{A}$$

$$v(0^+) = v(0^-) = 4\text{V}$$

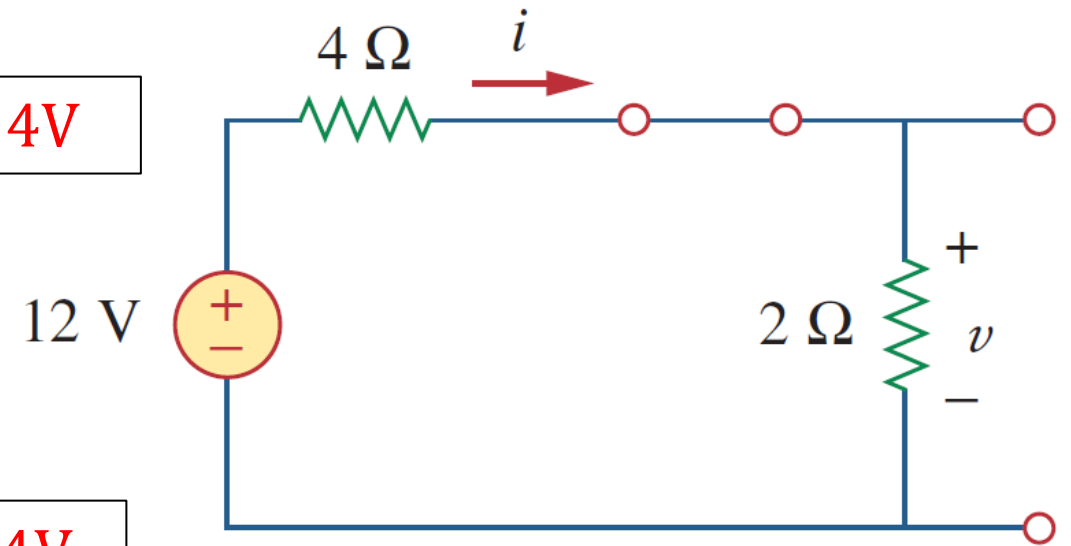

(b) At $t = 0^+$ the switch is open; the equivalent circuit is as shown in figure below. The same current flows through both the inductor and capacitor. Hence,

$$i(0^+) = i_c(0^+) = 2\text{A}$$

$$i_c = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{i_c}{C} \Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2}{0.1} = 20\text{V/s}$$

Similarly, since $L di/dt = v_L$, $di/dt = v_L/L$. We now obtain v_L by applying KVL to the loop


$$-12 + 4i(0^+) + v_L(0^+) + v(0^+) = 0$$

or

$$v_L(0^+) = 12 - 8 - 4 = 0$$


Thus,
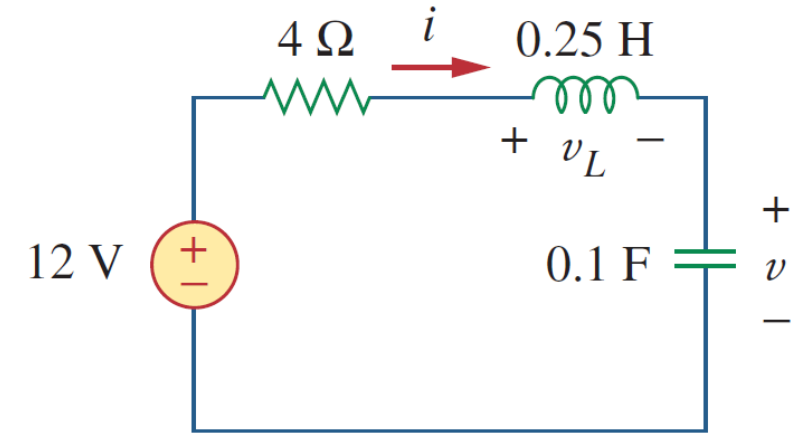
$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{0}{0.25} = 0\text{ A/s}$$



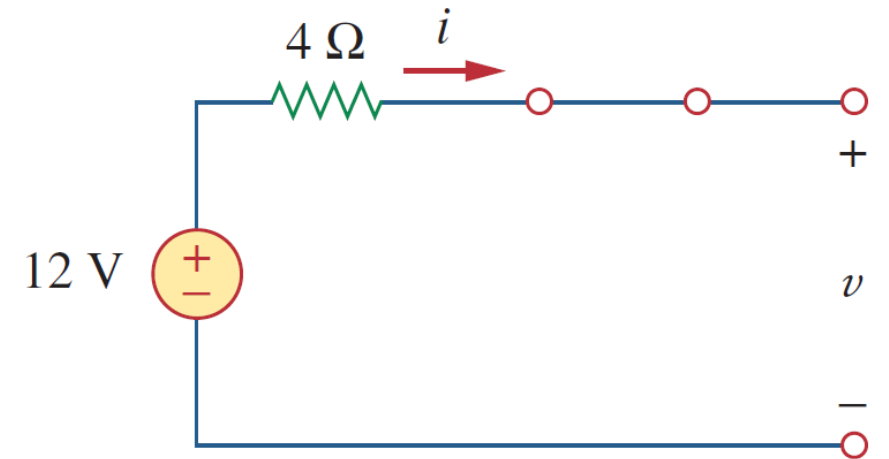(c) For $t > 0$ the circuit undergoes transience. But as $t \rightarrow \infty$ the circuit reaches steady state again. The inductor acts like a short circuit and the capacitor like an open circuit, so that the circuit becomes like that shown in figure below. from which we have

$$i(\infty) = 0 \text{ A}, \quad v(\infty) = 12 \text{ V}$$



HOMEWORK

1. Resolve Example 8.1: Page no. (315) with these parameters:

$$R = 6\Omega, L = 0.45H \text{ \& } C = 0.02F$$

2. Solve practice Problem 8.1: Page no.(316)

Report Assignment

Step Response of an RC and an RL Circuits