

University of Diyala

College of Engineering

Department of Power and Electrical Machines Engineering

Academic Year 2025-2026

Second Year – Bachelor (BSc) – EPE 204

Spring Semester

EPE 204 Electric Circuits Analysis II

Lecture 5

Assist. Lect. Ibrahim I. Ibrahim

Lecture 5

The Source-Free Series and Parallel RLC Circuit

A **source-free RLC circuit** is a circuit where:

- All **independent sources are removed (set to zero)**
- The response depends only on **initial stored energy**
 - Capacitor $\rightarrow$ stored electric energy 
 - Inductor $\rightarrow$ stored magnetic energy 

👉 This leads to a **natural response** (transient response only).

An understanding of the natural response of the series and parallel **RLC** circuit is a necessary background for future studies in filter design and communications networks.

Part 1

The Source-Free Series RLC Circuit

EPE 204 Electric Circuits Analysis II

Lecture 5

A series connection of RLC with initial energy in L and/or C.


Governing Equation $v_R + v_L + v_C = 0$ and substitute the following

$$v_R = iR \quad v_L = L \frac{di}{dt} \quad v_C = \frac{1}{C} \int i \, dt$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i \, dt = 0 \quad \text{Differentiate to eliminate the integral:}$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0 \quad \text{Thus, the standard form will be}$$
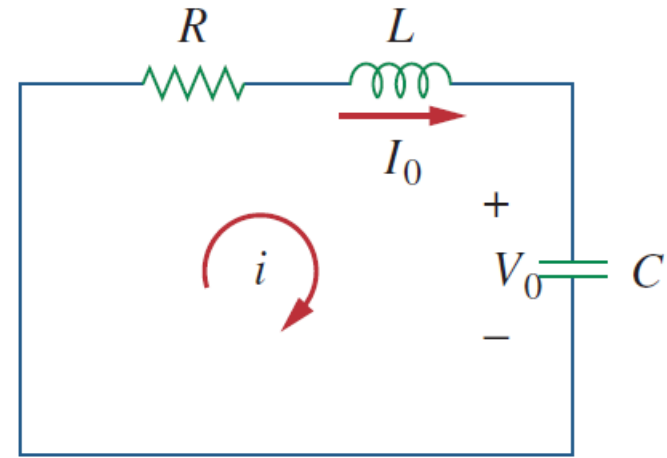
$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$



Now, define new parameters:

Damping factor /Neper frequency (Np/s)

$$\alpha = \frac{R}{2L}$$

Undamped Natural frequency (rad/s)

$$\omega_o = \frac{1}{\sqrt{LC}}$$

Characteristic Equation

$$s^2 + 2\alpha s + \omega_o^2$$

The roots s_1 and s_2 are called natural frequencies (Np/s)

Types of Responses

1. Overdamped ($\alpha > \omega_0$) $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

- Two real roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

2. Critically Damped ($\alpha = \omega_0$) $i(t) = (A_1 + A_2 t) e^{-\alpha t}$ $s_1 = s_2 = -\alpha$

- Repeated root




3. Underdamped ($\alpha < \omega_0$) $i(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$

- Complex roots

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = -\alpha + j\omega_d$$

$$s_2 = -\alpha - j\omega_d$$

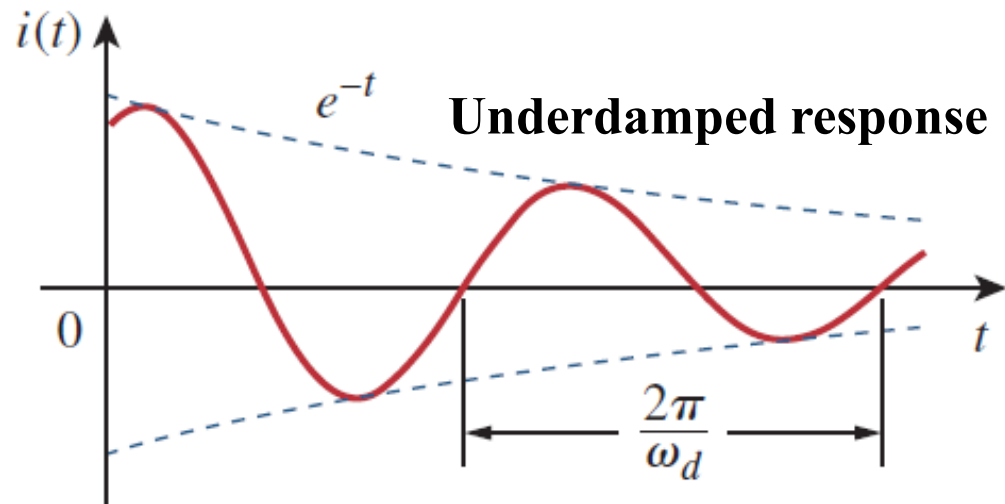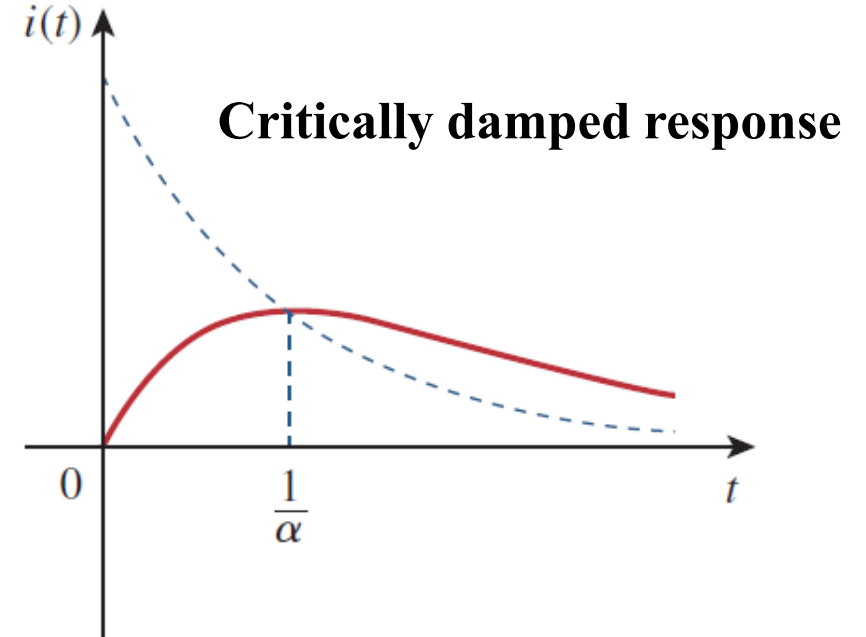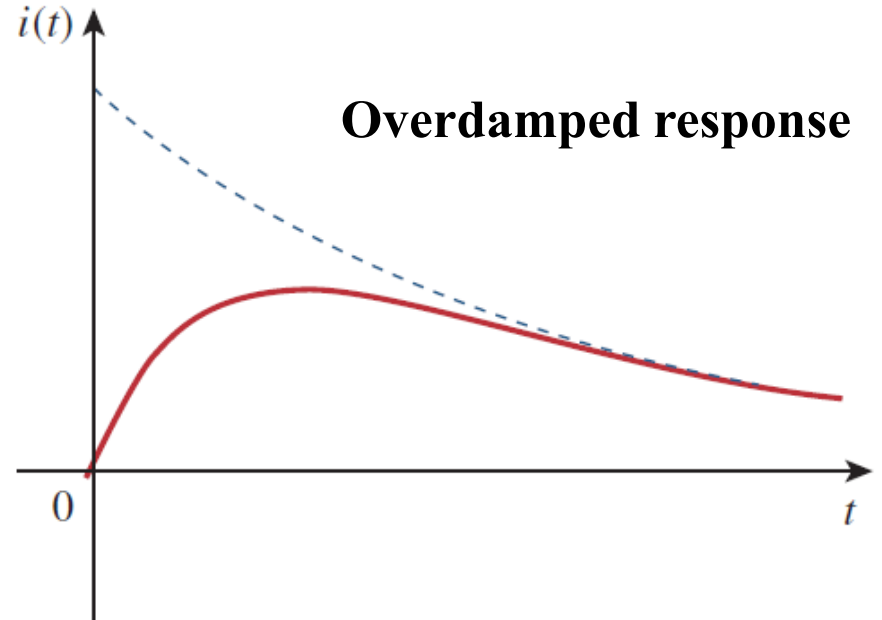

Example 1: Calculate the roots of the RLC series circuit knowing that $R = 40\Omega$, $L = 4\text{H}$ and $C = 0.25\text{F}$. Is the natural response overdamped, underdamped, or critically damped?

We first calculate

$$\alpha = \frac{R}{2L} = \frac{40}{2(4)} = 5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times \frac{1}{4}}} = 1$$

Since $\alpha > \omega_0$ this means the response is overdamped, and this leads to:

The roots are

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{25 - 1}$$

or

$$s_1 = -0.101, \quad s_2 = -9.899$$

This is also evident from the fact that the roots are real and negative.

Part 2

The Source-Free Parallel RLC Circuit

EPE 204 Electric Circuits Analysis II

Lecture 5

A parallel connection of RLC with initial energy in L and/or C.

Governing Equation $i_R + i_L + i_C = 0$ and substitute the following

$$i_R = \frac{v}{R}$$


$$i_L = \frac{1}{L} \int v \, dt$$

$$i_C = C \frac{dv}{dt}$$

$$\frac{v}{R} + \frac{1}{L} \int v \, dt + C \frac{dv}{dt} = 0$$
 Differentiate to eliminate the integral:

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$
 Thus, the standard form will be
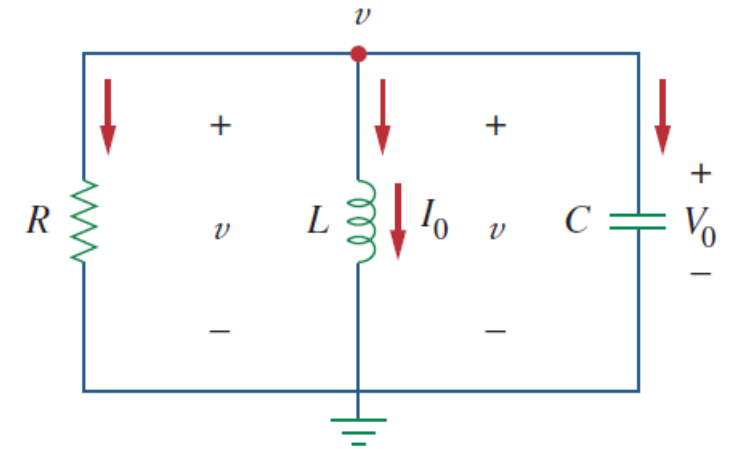
$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$



Now, define new parameters:

Damping factor /Neper frequency (Np/s)

$$\alpha = \frac{1}{2RC}$$

Undamped Natural frequency (rad/s)

$$\omega_o = \frac{1}{\sqrt{LC}}$$

Characteristic Equation

$$s^2 + 2\alpha s + \omega_o^2$$

The roots s_1 and s_2 are called natural frequencies (Np/s)

Types of Responses

1. Overdamped ($\alpha > \omega_0$) $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

- Two real roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

2. Critically Damped ($\alpha = \omega_0$) $v(t) = (A_1 + A_2 t) e^{-\alpha t}$ $s_1 = s_2 = -\alpha$

- Repeated root

3. Underdamped ($\alpha < \omega_0$) $v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$

- Complex roots

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = -\alpha + j\omega_d$$

$$s_2 = -\alpha - j\omega_d$$

Example 2: Calculate the roots of the RLC parallel circuit knowing that $R = 2\Omega$, $L = 1\text{H}$ and $C = 0.5\text{F}$. Is the natural response overdamped, underdamped, or critically damped?

We first calculate $\alpha = \frac{1}{2RC} = \frac{1}{2 \times 2 \times 0.5} = \frac{1}{2}$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1$$

Since $\alpha < \omega_0$ this means the response is underdamped, and this leads to:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{1 - 0.25} = 0.866$$

$$s_{1,2} = -0.5 \pm j\omega_d$$

Comparison: Series vs Parallel RLC

Feature	Series RLC	Parallel RLC
Variable	$i(t)$	$v(t)$
Damping factor	$\alpha = \frac{R}{2L}$	$\alpha = \frac{1}{2RC}$
Governing law	KVL	KCL
Energy loss	R	R