

University of Diyala

College of Engineering

Department of Power and Electrical Machines Engineering

Academic Year 2025-2026

Second Year – Bachelor (BSc) – EPE 204

Spring Semester

EPE 204 Electric Circuits Analysis II

Lecture 6

Assist. Lect. Ibrahim I. Ibrahim

Lecture 6

General Second-Order Circuits

A **second-order circuit** is any circuit that contains: Two energy storage elements: Inductor L and Capacitor C such as RLC series and parallel circuits. These circuits are described by a **second-order differential equation**.

General Differential Equation

The standard form:

$$\frac{d^2x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0x(t) = f(t)$$

$x(t)$: Voltage or Current.

a_1, a_0 : Constants depending on R, L, C

$f(t)$: Forcing function (source)

Characteristic Equation

From the homogeneous equation:

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

α : Damping factor (Np/s)


ω_o : Natural frequency (rad/s)

These roots s_1 and s_2 determine the type of response.

In the second-order circuit, we determine its step response $x(t)$ (which may be voltage or current) by taking the following procedure:

- 1) Determine the initial conditions $x(0)$ and $\frac{dx(0)}{dt}$ and the final value $x(\infty)$.
- 2) Remove the independent sources and find the form of the transient response $x_t(t)$ by applying KCL and KVL. Once a second-order differential equation is obtained, we determine its characteristic roots. Depending on whether the response is overdamped, critically damped, or underdamped, we obtain $x_t(t)$ with two unknown constants.
- 3) Find the steady-state response as: $x_{ss}(t) = x(\infty)$. Where $x(\infty)$ is the final value of x , obtained in the first step.
- 4) Here, the total response is now found as the sum of the transient response and steady-state response: $x(t) = x_t(t) + x_{ss}(t)$
- 5) Finally determine the constants associated with the transient response by imposing the initial conditions $x(0)$ and $\frac{dx(0)}{dt}$ determined in the first step.

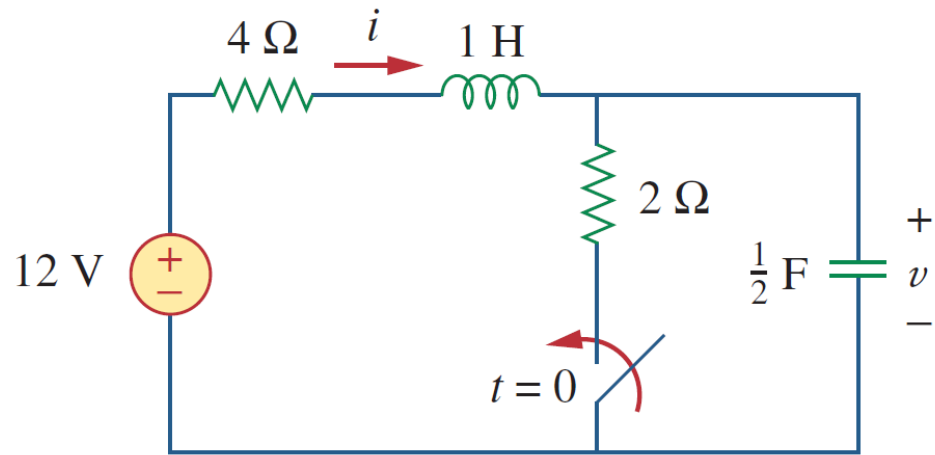
Example 1: Find the complete response for v and i when $t > 0$ in the circuit shown below.



For $t = 0^-$ the switch is open and the circuit is at steady-state, so that the equivalent circuit that used to calculate the initial values is shown in **Fig1**.

$$v(0^-) = 12V$$

$$i(0^-) = 0A$$

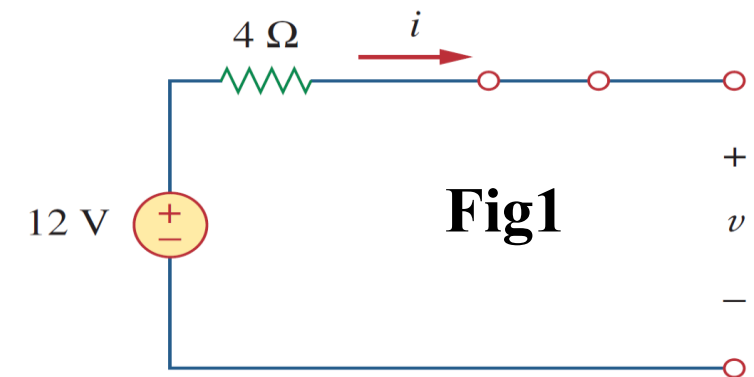

For $t = 0^+$ the switch is close and the equivalent circuit that used to calculate the initial values is shown in **Fig2**. Thus, by the continuity of capacitor voltage and inductor current:

$$v(0^+) = v(0^-) = 12V \quad i(0^+) = i(0^-) = 0A$$


$$i_C = C \frac{dv}{dt} \Rightarrow \frac{i_C}{C} = \frac{dv}{dt} \quad \text{Applying KCL at node a in Fig2}$$

$$i(0^+) = i_C(0^+) + \frac{v(0^+)}{2} \Rightarrow 0 = i_C(0^+) + \frac{12}{2}$$

$$i_C(0^+) = -6A \Rightarrow \frac{dv}{dt} = \frac{-6}{0.5} = -12V/s \rightarrow (1)$$

Now, replace the L with a short circuit and C by an open circuit in **Fig2** to obtain the final values of $i(\infty)$ and $v(\infty)$
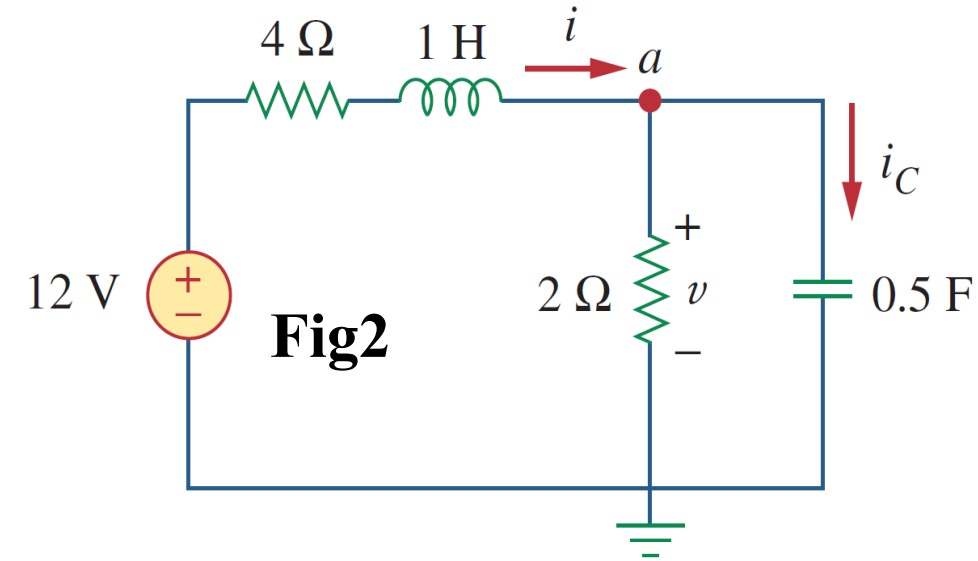
$$i(\infty) = \frac{12}{4+2} = 2A \quad v(\infty) = Ri(\infty) = 2 \times 2 = 4V$$



Remove the independent sources and find the form of the transient response for $t > 0$, thus we have the circuit of **Fig3**.

Applying KCL at node a in **Fig3**. $i = \frac{v}{2} + \frac{1}{2} \frac{dv}{dt} \rightarrow (2)$

Applying KVL to the left mesh in **Fig3**. $4i + 1 \frac{di}{dt} + v = 0 \rightarrow (3)$

Now, substitute (2) into (3).


$$2v + 2 \frac{dv}{dt} + \frac{1}{2} \frac{dv}{dt} + \frac{1}{2} \frac{d^2v}{dt^2} + v = 0 \Rightarrow \frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 0 \rightarrow (4)$$

From (4), we obtain the characteristic equation as: $s^2 + 5s + 6 = 0 \Rightarrow s_1 = -2$ & $s_2 = -3$

Thus, the natural response is: $v_n(t) = Ae^{-2t} + Be^{-3t}$

The steady-state response is $v_{ss}(t) = v(\infty) = 4$

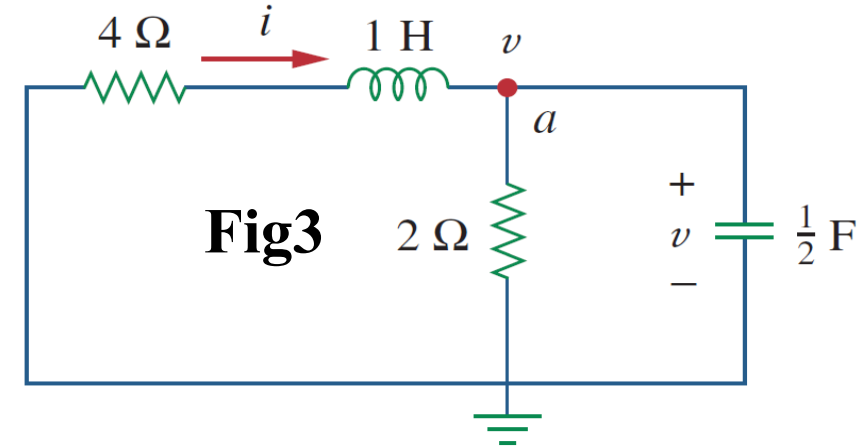The complete response is: $v(t) = v_t(t) + v_{ss}(t) = 4 + Ae^{-2t} + Be^{-3t}$



The complete response is: $v(t) = v_t(t) + v_{ss}(t) = 4 + Ae^{-2t} + Be^{-3t} \rightarrow (5)$

Now, determine A and B at $t = 0$ using the initial values $v(0^+) = v(0^-) = 12V$

$$12 = 4 + A + B \Rightarrow A + B = 8 \rightarrow (6)$$

Taking the derivative of v for (5) $\Rightarrow \frac{dv}{dt} = -2Ae^{-2t} - 3Be^{-3t} \rightarrow (7)$

Now, substitute (1) into (7) at $t = 0 \Rightarrow -12 = -2A - 3B \Rightarrow 2A + 3B = 12 \rightarrow (8)$

From (6) and (8): $A = 12$ and $B = -4$


The complete response is: $v(t) = v_t(t) + v_{ss}(t) = 4 + 12e^{-2t} - 4e^{-3t} \text{ V } t > 0$

From (2)

$$i = \frac{v}{2} + \frac{1}{2} \frac{dv}{dt} = 2 + 6e^{-2t} - 2e^{-3t} - 12e^{-2t} + 6e^{-3t}$$

$$i = 2 - 6e^{-2t} + 4e^{-3t} \text{ A } \quad t > 0$$

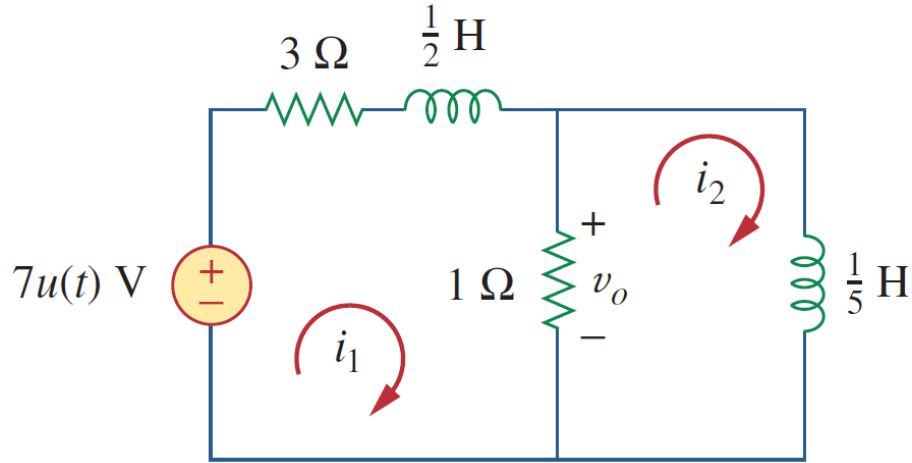Example 2: Find $v_o(t)$ when $t > 0$ in the circuit shown below.



This is a second-order circuit that have two inductors. The first step is to obtain the mesh currents i_1 and i_2 which happen to be the currents through the inductors. Then, obtain the initial and final values of these currents

For $t < 0$, $7u(t) = 0$ and this leads to $i_1(0^-) = i_2(0^-) = 0$


For $t > 0$, $7u(t) = 7$ and the circuit will be as shown in **Fig1**

Because of the continuity of inductor current,

$$i_1(0^-) = i_1(0^+) = 0 \quad i_2(0^-) = i_2(0^+) = 0 \quad v_o(0^+) = v_{L_2}(0^+) = 1[i_1(0^+) - i_2(0^+)] = 0 \rightarrow (1)$$

Applying KVL to the left loop in **Fig1** at $t = 0^+$
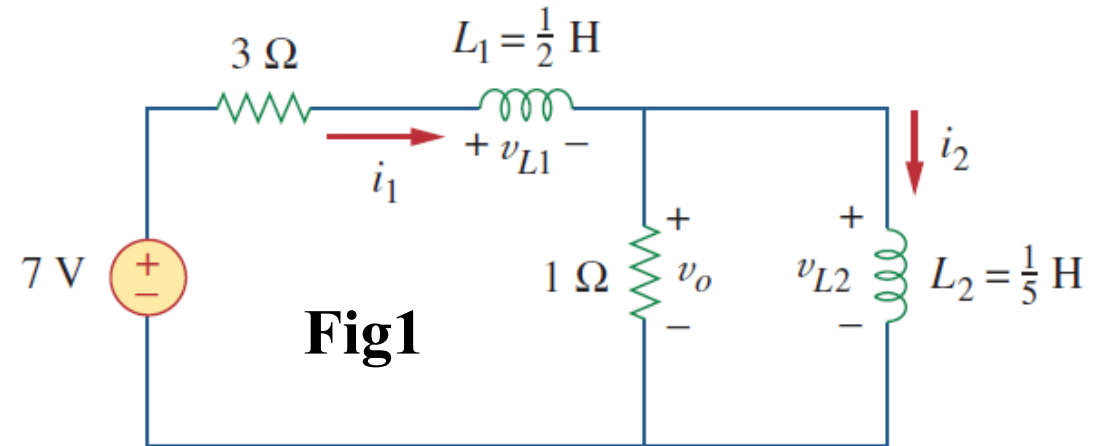
$$7 = 3i_1(0^+) + v_{L_1}(0^+) + v_o(0^+) \Rightarrow v_{L_1}(0^+) = 7$$



$$v_{L_1}(0^+) = L_1 \frac{di_1(0^+)}{dt} \Rightarrow \frac{di_1(0^+)}{dt} = \frac{v_{L_1}(0^+)}{L_1} = \frac{7}{0.5} = 14 \text{ V/s} \quad v_{L_2}(0^+) = L_2 \frac{di_2(0^+)}{dt} \Rightarrow \frac{di_2(0^+)}{dt} = \frac{v_{L_2}(0^+)}{L_2} = 0 \text{ V/s}$$

When $t \rightarrow \infty$ the circuit reaches steady state, and the inductors become short circuits, as shown in **Fig2**

$$i_1(\infty) = i_2(\infty) = \frac{7}{3} \text{ A}$$

Now, we obtain the form of the transient responses by removing the voltage source, as shown in **Fig3**. Applying KVL to the two meshes:



$$4i_1 - i_2 + 0.5 \frac{di_1}{dt} = 0 \Rightarrow i_2 = 4i_1 + 0.5 \frac{di_1}{dt} \rightarrow (2)$$

$$i_2 + 0.2 \frac{di_2}{dt} - i_1 = 0 \rightarrow (3)$$

$$4i_1 + 0.5 \frac{di_1}{dt} + 0.8 \frac{di_1}{dt} + 0.1 \frac{d^2 i_1}{dt^2} - i_1 = 0$$

$$\frac{d^2 i_1}{dt^2} + 13 \frac{di_1}{dt} + 30i_1 = 0 \Rightarrow s^2 + 13s + 30 = 0$$

$$s_1 = -3 \text{ \& } s_2 = -10$$

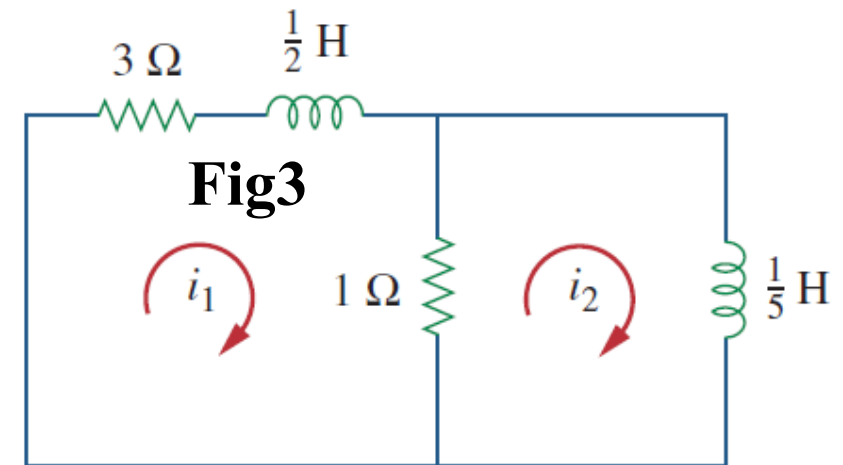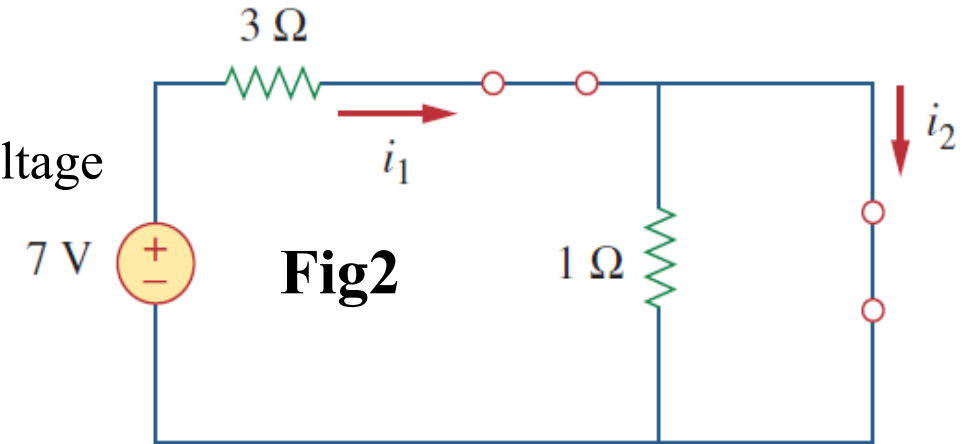

The form of the transient response is $i_{1n}(t) = Ae^{-3t} + Be^{-10t} \rightarrow (4)$

The steady-state response is $i_{1ss} = i_1(\infty) = \frac{7}{3} \rightarrow (5)$

From Eqs. (4) and (5), we obtain the complete response as $i_1(t) = \frac{7}{3} + Ae^{-3t} + Be^{-10t} \rightarrow (6)$

$$\frac{7}{3} + A + B = 0 \rightarrow (7)$$

Taking the derivative of Eq. (6) and setting $t = 0$ in the derivative and use the Eq. (*)

$$14 = -3A - 10B \rightarrow (8) \quad \text{From Eqs. (7) and (8), } A = -\frac{4}{3} \text{ and } B = -1$$

$$i_1(t) = \frac{7}{3} - \frac{4}{3}e^{-3t} - e^{-10t} \rightarrow (9) \quad i_2 = 4i_1 + 0.5 \frac{di_1}{dt} \rightarrow (2) \Rightarrow i_2 = \frac{7}{3} - \frac{10}{3}e^{-3t} + e^{-10t} A$$

$$v_0(0^+) = v_{L_2}(0^+) = 1[i_1(0^+) - i_2(0^+)] = 0 \rightarrow (1)$$

$$v_0(0^+) = 2(e^{-3t} - e^{-10t})V$$