



UNIVERSITY OF DIYALA
COLLEGE OF ENGINEERING
DEPARTMENT OF THE
ELECTRICAL POWER AND
MACHINES ENGINEERING




Second Stage

ELECTRICAL MACHINES

Lecture: 7

Lecturer
Mayyadah Sahib

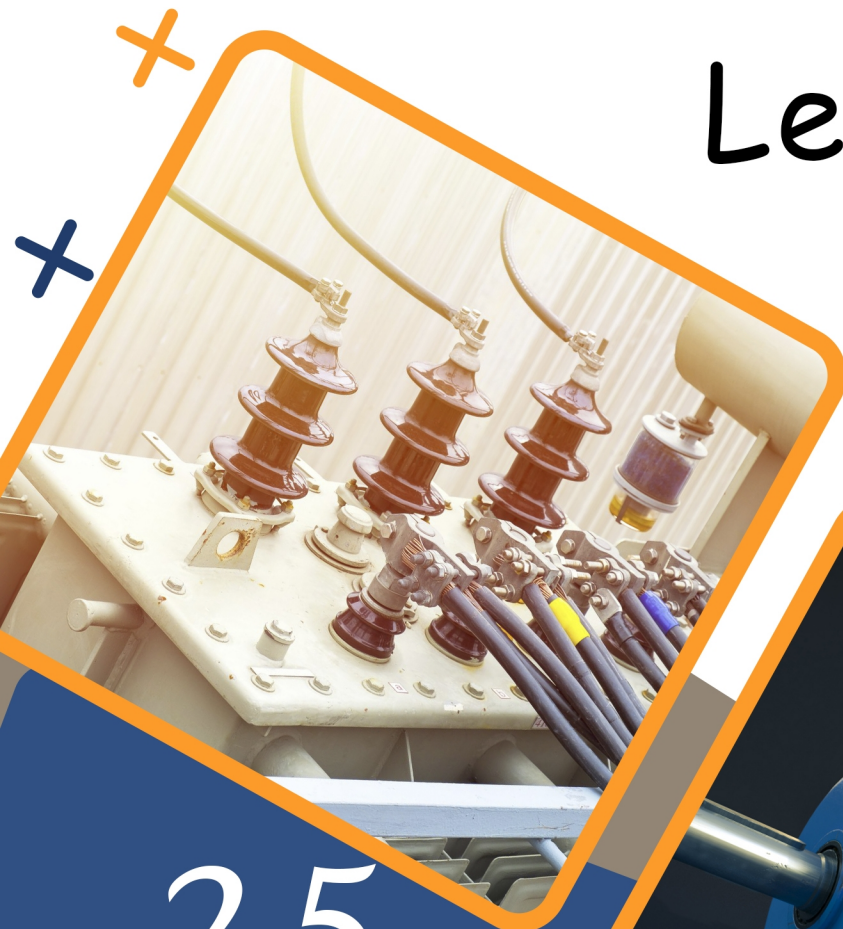

25
26

Transformer on Load:

When the transformer is loaded, the current I_2 flows through the secondary winding. The magnitude and phase of I_2 is determined by the load.

There exists a secondary m.m.f. $N_2 I_2$ due to which secondary current sets up its own flux Φ_2 . This flux opposes the main flux Φ produced in the core due to magnetising component of no-load current. Hence the m.m.f. $N_2 I_2$ is called demagnetizing ampere-turns.

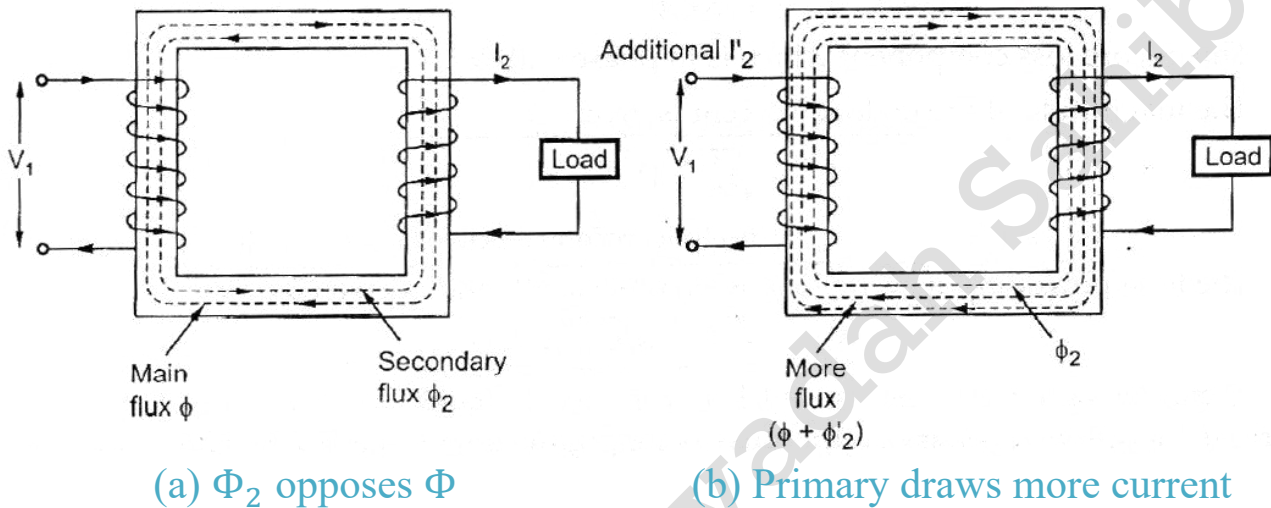


Figure (1)

The flux Φ_2 momentarily reduces the main flux Φ , due to which the primary induced e.m.f. E_1 also reduces. Hence the vector difference $V_1 - E_1$ increases due to which primary draws more current from the supply. This additional current drawn by primary is due to the load hence called load component of primary current denoted as I'_2 .

This current I'_2 is antiphase with I_2 . The current I'_2 sets up its own flux Φ'_2 which opposes the flux Φ_2 and helps the main flux Φ . This flux Φ'_2 neutralises the flux Φ_2 produced by I_2 . The m.m.f. ampere turns $N_1 I'_2$ balanced the ampere turns $N_2 I_2$. Hence the net flux in the core is again maintained at constant level.

As the ampere turns are balanced we can write,

$$N_2 I_2 = N_1 I'_2$$

$$I'_2 = \frac{N_2}{N_1} I_2$$

$$I'_2 = K I_2$$

When transformer is loaded, the primary current I_1 has two components:

1. The no load current I_0 which lags V_1 by angle Φ_0 . It has two components I_m and I_c .
2. The load components I'_2 which antiphase with I_2 . And phase of I_2 decided by the load.

Hence primary current I_1 is vector sum of I_0 and I_2' .

$$\therefore I_1 = I_0 + I_2'$$

Assume inductive load, I_2 lags E_2 by Φ_2 , the phasor diagram is shown in the Figure (2-a).

Assume purely resistive load, I_2 in phase with E_2 , the phasor diagram is shown in the Figure (2-b).

Assume capacitive load, I_2 leads E_2 by Φ_2 , the phasor diagram is shown in the Figure (2-c).

Note: that I_2' is always in antiphase with I_2 .

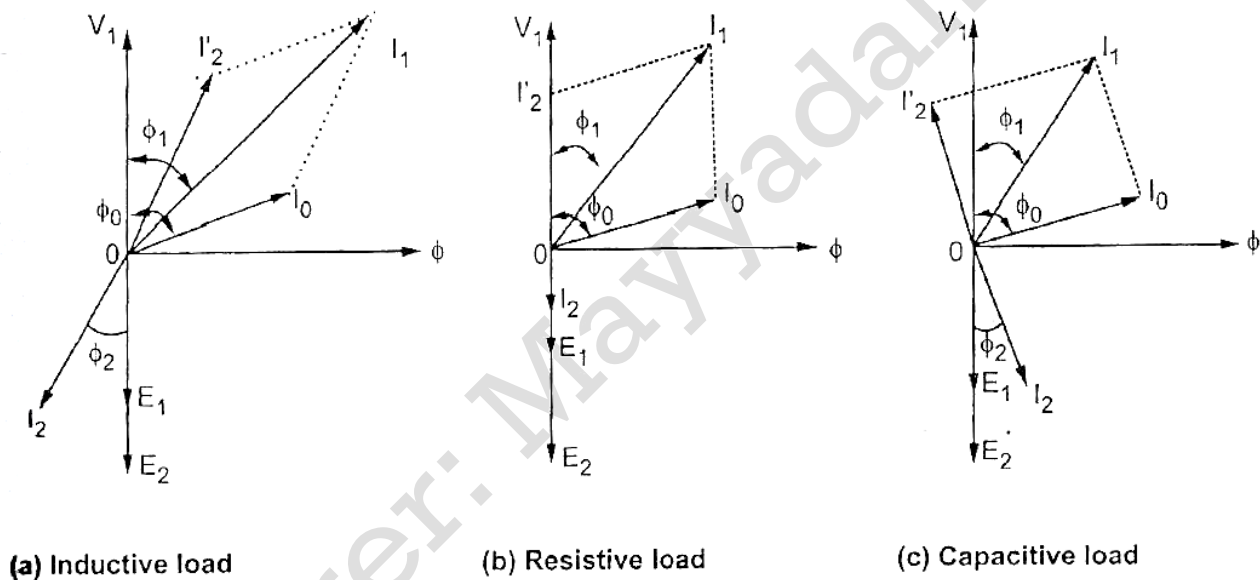


Figure (2)

But if we neglect I_0 as compared to I_2'

$$N_1 I_2' = N_1 I_1 = N_2 I_2$$

$$\therefore \frac{I_2'}{I_2} = \frac{I_1}{I_2} = \frac{N_2}{N_1} = K$$

Example 1: A single-phase transformer with a ratio of 440/110 V takes a no-load current of 5A at 0.2 power factor lagging. If the secondary supplies a current of 120A at a p.f. of 0.8 lagging, estimate the current taken by the primary.

Solution:

$$\cos \Phi_2 = 0.8, \Phi_2 = \cos^{-1} 0.8 \cong 36.87^\circ$$

$$\cos \Phi_0 = 0.2, \Phi_0 = \cos^{-1} 0.2 = 78.46^\circ$$

$$\text{Now, } K = \frac{V_2}{V_1} = \frac{110}{440} = 1/4$$

$$\therefore I'_2 = KI_2 = 120 \times 1/4 = 30\text{A}$$

$$I_0 = 5\text{A}$$

$$\begin{aligned} \text{Angle between } I_0 \text{ and } I'_2 \\ = 78.46^\circ - 36.87^\circ = 41.59^\circ \end{aligned}$$

Using parallelogram law of vectors **Figure (3)** we get

$$\begin{aligned} I_1 &= \sqrt{(5^2 + [2 \times 5 \times 30 \times \cos 41.59^\circ] + 30^2)} \\ &= \mathbf{33.9\text{A}} \end{aligned}$$

The resultant current could also have been found by Resolving I'_2 and I_0 into their X and Y-components.

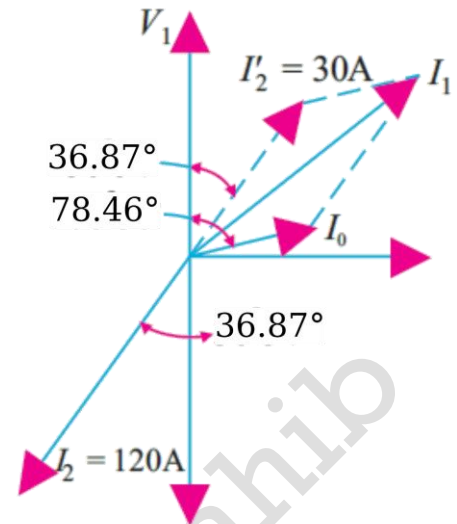


Figure (3)

Note: vectors can be solved by any one of these methods,

1. Parallelogram method (as in **Example 1**).
2. Vector components analysis.
3. Complex number methods.

Example 2: A transformer has a primary winding of 800 turns and a secondary winding of 200 turns. When the load current on the secondary is 80A at 0.8 power factor lagging, the primary current is 25A at 0.707 power factor lagging. Determine graphically or otherwise the no-load current of the transformer and its phase with respect to the voltage.

Solution:

$$\begin{aligned} \text{Here, } K &= 200/800 = 1/4; I'_2 = 80 \times 1/4 = 20\text{A}; \Phi_2 = \cos^{-1} 0.8 \cong 36.9^\circ; \\ \Phi_1 &= \cos^{-1} 0.707 \cong 45^\circ \end{aligned}$$

As seen from **Figure (4)**, I_1 is the vector sum of I_0 and I'_2 . Let I_0 lag behind V_1 by an angle Φ_0 .

$$I_0 \cos \Phi_0 + 20 \cos 36.9^\circ = 25 \cos 45^\circ$$

$$\therefore I_0 \cos \Phi_0 = 25 \times 0.707 - 20 \times 0.8$$

$$I_0 \cos \Phi_0 = 1.675\text{A}$$

$$I_0 \sin \Phi_0 + 20 \sin 36.9^\circ = 25 \sin 45^\circ$$

$$\therefore I_0 \sin \Phi_0 = 25 \times 0.707 - 20 \times 0.6$$

$$I_0 \sin \Phi_0 = 5.675\text{A}$$

$$\therefore \tan \Phi_0 = \frac{5.675}{1.675} = 3.388$$

$$\therefore \Phi_0 \cong 73.6^\circ$$

$$\text{Now, } I_0 \sin \Phi_0 = 5.675$$

$$\therefore I_0 = \frac{5.675}{\sin 73.6^\circ} \cong \mathbf{5.92\text{A}}$$

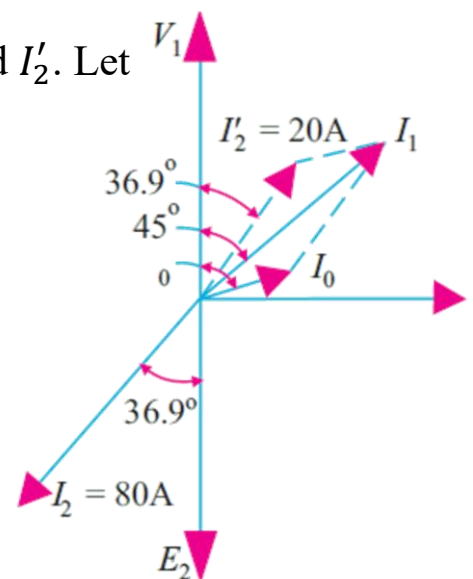


Figure (4)

Example 3: A single phase transformer takes 10A on no load at p.f. of 0.2 lagging. The turns ratio is 4: 1 (step down). If the load on the secondary is 200A at a p.f. of 0.85 lagging. Find the primary current and power factor. Neglect the voltage-drop in the winding.

Solution:

Secondary load of 200A, 0.85 lag is reflected as 50A, 0.85 lag in terms of the primary equivalent current.

$$I_0 = 10 \angle -\Phi_0, \text{ where } \Phi_0 = \cos^{-1} 0.20 = 78.5^\circ \text{ lagging}$$

$$I_0 \cong 2 - j9.8A$$

$$I'_2 = 50 \angle -\Phi_L, \text{ where } \Phi_L = \cos^{-1} 0.85 = 31.8^\circ \text{ lagging}$$

$$I'_2 \cong 42.5 - j26.34$$

Hence primary current I_1

$$I_1 = I_0 + I'_2$$

$$I_1 = 2 - j9.8 + 42.5 - j26.34$$

$$I_1 = 44.5 - j36.14$$

$$|I_1| \cong 57.33A ; \cos \Phi = 0.776 \text{ lagging}$$

$$\Phi = \cos^{-1} \frac{44.5}{57.33} \cong 39.09^\circ \text{ lagging}$$

The phasor diagram is shown in Figure (5).

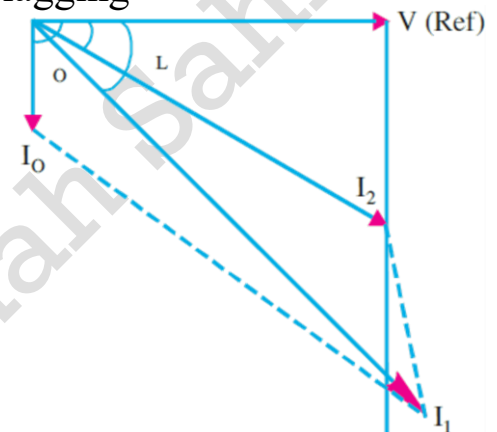


Figure (5)

Transformer with Winding Resistance but No Magnetic Leakage:

An ideal transformer was supposed to possess no resistance, but in an actual transformer, there is always present some resistance of the primary and secondary windings. Due to this resistance, there is some voltage drop in the two windings. The result is that:

(i) The secondary terminal voltage V_2 is vectorially less than the secondary induced e.m.f. E_2 by an amount $I_2 R_2$ where R_2 is the resistance of the secondary winding. Hence, V_2 is equal to the vector difference of E_2 and resistive voltage drop $I_2 R_2$.

$$\therefore V_2 = E_2 - I_2 R_2 \quad \dots \text{vector difference}$$

(ii) Similarly, primary induced e.m.f. E_1 is equal to the vector difference of V_1 and $I_1 R_1$ where R_1 is the resistance of the primary winding.

$$E_1 = V_1 - I_1 R_1 \quad \dots \text{vector difference}$$

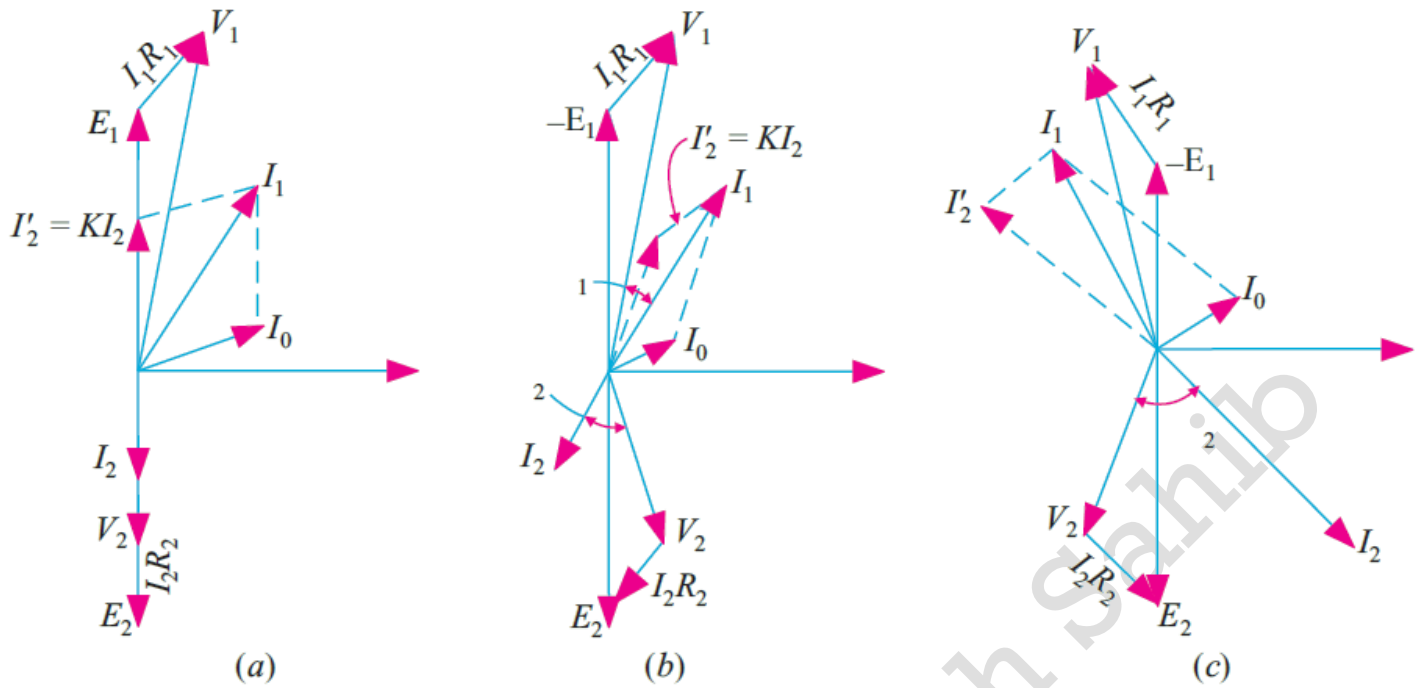


Figure (6)

The vector diagrams for non-inductive, inductive and capacitive loads are shown in Figure (6) (a), (b) and (c) respectively.

Equivalent Resistance:

In Figure (7) a transformer is shown whose primary and secondary windings have resistances of R_1 and R_2 respectively. It would now be shown that the resistances of the two windings can be transferred to any one of the two windings. The advantage of concentrating both the resistances in one winding is that it makes calculations very simple and easy because one has then to work in one winding only.

It is to be noted that

1. a resistance of R_1 in primary is equivalent to $K^2 R_1$ in secondary. Hence, it is called **equivalent primary resistance as referred to secondary** i. e. R'_1 (as shown in Figure (8)).
2. a resistance of R_2 in secondary is equivalent to R_2/K^2 in primary. Hence, it is called the **equivalent secondary resistance as referred to primary** i. e. R'_2 (as shown in Figure (7)).
3. **Total or effective resistance of the transformer as referred to primary** is,
 $R_{01} = \text{primary resistance} + \text{equivalent secondary resistance as referred to primary}$

$$R_{01} = R_1 + R'_2 = R_1 + R_2/K^2$$

4. Similarly, total **transformer resistance as referred to secondary** is,

R_{02} = secondary resistance + equivalent primary resistance as referred to secondary

$$R_{02} = R_2 + R'_1 = R_2 + K^2 R_1$$

5. The copper loss in secondary is $(I_2)^2 R_2$. This loss is supplied by primary which takes a current of I_1 . Hence if R'_2 is the **equivalent resistance in primary which would have caused the same loss** as R_2 in secondary, then,

$$I_1^2 R'_2 = I_2^2 R_2 \quad \text{or} \quad R'_2 = \left(\frac{I_2}{I_1}\right)^2 R_2$$

Now, if we neglect no-load current I_0 , then $I_2/I_1 = 1/K$. Hence, $R'_2 = R_2/K^2$. Similarly, equivalent primary resistance as referred to secondary is $R'_1 = K^2 R_1$

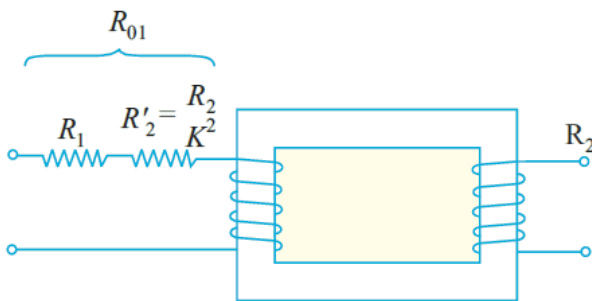


Figure (7)

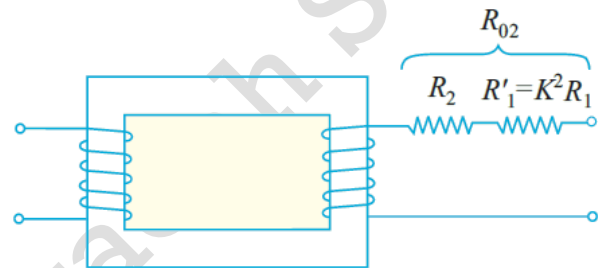


Figure (8)

6. When shifting any **voltage** from one winding to another only K is used,

$$E'_1 = K E_1 \quad \& \quad E'_2 = E_2 / K$$


7. When shifting any **current** from one winding to another only K is used but inverse to the transformation of resistances and currents,

$$I'_1 = I_1 / K \quad \& \quad I'_2 = K I_2$$

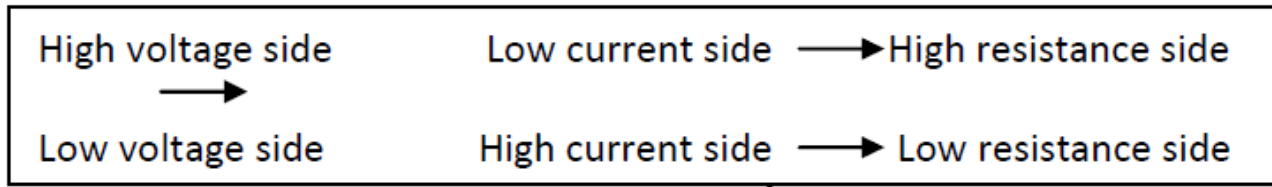8. It is important to remember that,

When shifting any primary resistance to the secondary, *multiply* it by K^2 i.e. (transformation ratio)². When shifting secondary resistance to the primary, *divide* it by K^2 .

The result can be cross-checked by another approach. The high voltage winding is always low current winding and hence the resistance of high voltage side is high. The low voltage side is high current side and hence resistance of low voltage side is low. So, while transferring resistance from low voltage side to high voltage side, its value must increase while transferring resistance from high voltage side to low voltage side, its value must decrease.



Transformer with Resistance and Leakage Reactance:

In Figure (9) the primary and secondary windings of a transformer with reactance's taken out of the windings are shown. The primary impedance is given by

$$Z_1 = \sqrt{(R_1^2 + X_1^2)}$$

Similarly, secondary impedance is given by

$$Z_2 = \sqrt{(R_2^2 + X_2^2)}$$

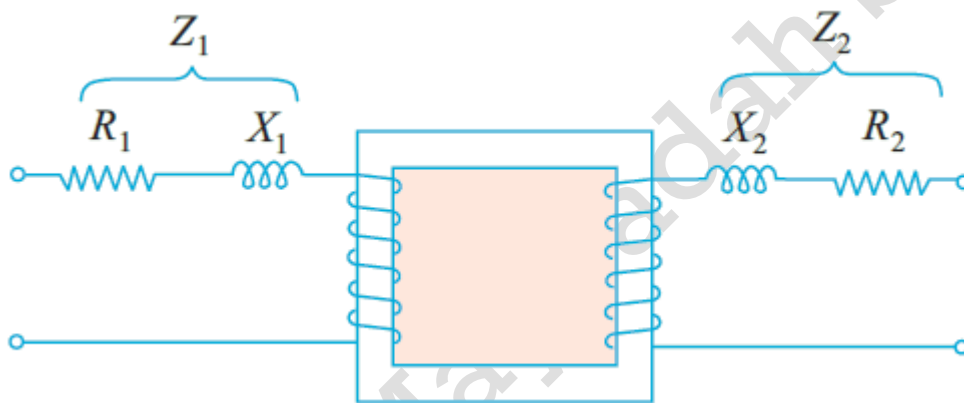


Figure (9)

The resistance and leakage reactance of each winding is responsible for some voltage drop in each winding. In primary, the leakage reactance drop is $I_1 X_1$ (usually 1 or 2% of V_1). Hence

$$V_1 = E_1 + I_1(R_1 + jX_1) = E_1 + I_1 Z_1$$

Similarly, there are $I_2 R_2$ and $I_2 X_2$ drops in secondary which combine with V_2 to give E_2 .

$$E_2 = V_2 + I_2(R_2 + jX_2) = V_2 + I_2 Z_2$$

The vector diagram for such a transformer for different kinds of loads is shown in Figure (10). In these diagrams, vectors for resistive drops are drawn parallel to current vectors whereas reactive drops are perpendicular to the current vectors. The angle Φ_1 between V_1 and I_1 gives the power factor angle of the transformer.

It may be noted that leakage reactance's can also be transferred from one winding to the other in the same way as resistance.

$$\therefore X'_2 = X_2/K^2 \quad \text{and} \quad X'_1 = K^2 X_1$$

And $X_{01} = X_1 + X'_2 = X_1 + X_2/K^2$

And $X_{02} = X_2 + X'_1 = X_2 + K^2 X_1$

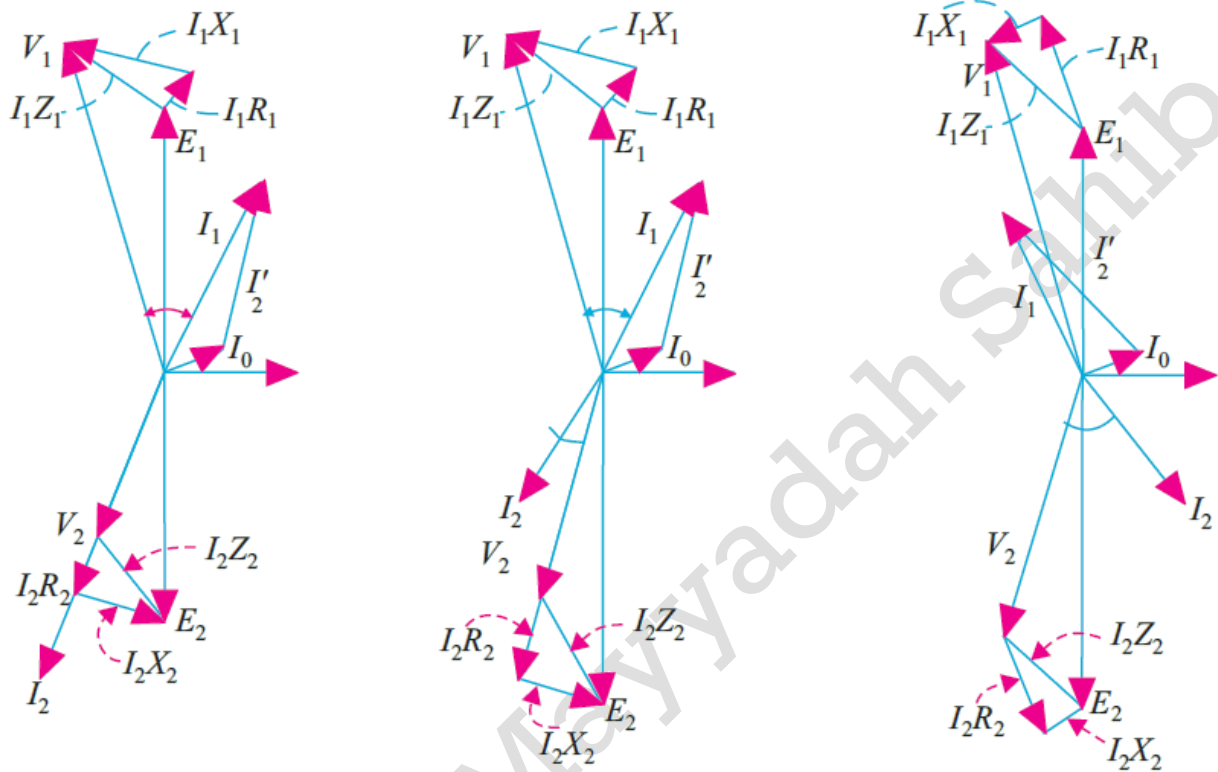


Figure (10)


It is obvious that total impedance of the transformer as referred to primary is given by

$$Z_{01} = \sqrt{(R_{01}^2 + X_{01}^2)}$$


$$Z_{02} = \sqrt{(R_{02}^2 + X_{02}^2)}$$

Figure (11-a)

Figure (11-b)

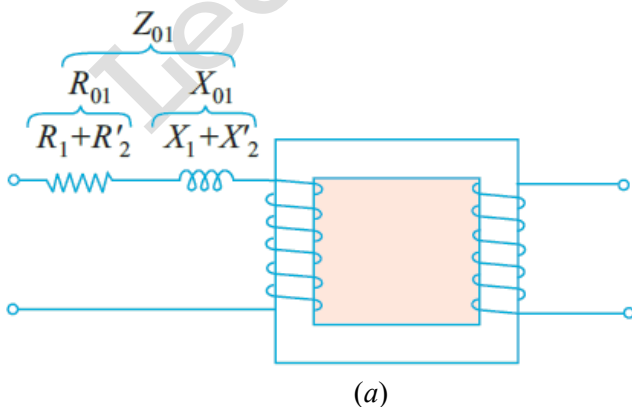

(a)

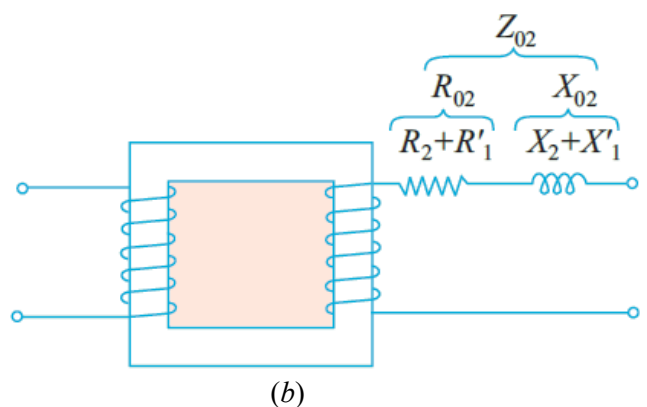

(b)

Figure (11)

Example 4: A 30kVA, 2,400/120 V, 50Hz transformer has a high voltage winding resistance of 0.1Ω and a leakage reactance of 0.22Ω . The low voltage winding resistance 0.035Ω and the leakage reactance is 0.012Ω . Find the equivalent winding resistance, reactance and impedance referred to the (i) high voltage side and (ii) the low-voltage side.

Solution:

$$K = 120/2,400 = 1/20 ; R_1 = 0.1\Omega ; X_1 = 0.22\Omega ; R_2 = 0.035\Omega ; X_2 = 0.012\Omega$$

(i) Here, high-voltage side is, obviously, the primary side. Hence, values as referred to primary side are

$$R_{01} = R_1 + R'_2 = R_1 + R_2/K^2 = 0.1 + \frac{0.035}{(1/20)^2} = 14.1\Omega$$

$$X_{01} = X_1 + X'_2 = X_1 + X_2/K^2 = 0.22 + \frac{0.012}{(1/20)^2} = 5.02\Omega$$

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{14.1^2 + 5.02^2} \cong 15\Omega$$

$$(ii) R_{02} = R_2 + R'_1 = R_2 + K^2 R_1 = 0.035 + (1/20)^2 \times 0.1 = 0.03525\Omega$$

$$X_{02} = X_2 + X'_1 = X_2 + K^2 X_1 = 0.012 + (1/20)^2 \times 0.22 = 0.01255\Omega$$

$$Z_{02} = \sqrt{R_{02}^2 + X_{02}^2} = \sqrt{0.03525^2 + 0.01255^2} = 0.0374\Omega$$

$$\text{Or } Z_{02} = K^2 Z_{01} = (1/20)^2 \times 15 = 0.0375\Omega$$

Example 5: A 50kVA, 4,400/220 V transformer has $R_1 = 3.45\Omega$, $R_2 = 0.009\Omega$. The values of reactance's are $X_1 = 5.2\Omega$ and $X_2 = 0.015\Omega$. Calculate for the transformer (i) equivalent resistance as referred to primary (ii) equivalent resistance as referred to secondary (iii) equivalent reactance as referred to both primary and secondary (iv) equivalent impedance as referred to both primary and secondary (v) total Cu loss, first using individual resistances of the two windings and secondly, using equivalent resistances as referred to each side.

Solution:

$$\text{Full-load } I_1 = \frac{50,000}{4,400} = 11.36\text{A (assuming 100\% efficiency)}$$

$$\text{Full-load } I_2 = \frac{50,000}{220} \cong 227\text{A} ; K = \frac{220}{4,400} = \frac{1}{20} = 0.05$$

$$(i) R_{01} = R_1 + R'_2 = R_1 + R_2/K^2 = 3.45 + \frac{0.009}{(1/20)^2} = 3.45 + 3.6 = 7.05\Omega$$

$$(ii) R_{02} = R_2 + R'_1 = R_2 + K^2 R_1$$

$$R_{02} = 0.009 + (1/20)^2 \times 3.45 = 0.009 + 0.0086 = 0.0176\Omega$$

$$\text{Also, } R_{02} = K^2 R_{01} = (1/20)^2 \times 7.05 = 0.0176\Omega$$

$$(iii) X_{01} = X_1 + X'_2 = X_1 + X_2/K^2 = 5.2 + \frac{0.015}{(1/20)^2} = 11.2\Omega$$

$$X_{02} = X_2 + X'_1 = X_2 + K^2 X_1 = 0.015 + 5.2 \times (1/20)^2 = 0.028\Omega$$

$$\text{Also, } X_{02} = K^2 X_{01} = \frac{11.2}{400} = 0.028\Omega$$

$$(iv) Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{(7.05^2 + 11.2^2)} = 13.23\Omega$$

$$Z_{02} = \sqrt{R_{02}^2 + X_{02}^2} = \sqrt{(0.0176^2 + 0.028^2)} \cong 0.0331\Omega$$

$$\text{Also, } Z_{02} = K^2 Z_{01} = \frac{13.23}{400} \cong 0.0331\Omega$$

$$(v) \text{ Cu loss} = I_1^2 R_2 + I_2^2 R_2 = 11.36^2 \times 3.45 + 227^2 \times 0.009 \cong 910W$$

$$\text{Also, Cu loss} = I_1^2 R_{01} = 11.36^2 \times 7.05 \cong 910W$$

$$\text{Also, Cu loss} = I_2^2 R_{02} = 227^2 \times 0.0176 \cong 910W$$

Example 6: A 100kVA, 1,100/220 V, 50Hz, single-phase transformer has a leakage impedance of $(0.1 + 0.4)\Omega$ for the H.V. winding and $(0.006 + 0.015)\Omega$ for the L.V. winding. Find the equivalent winding resistance, reactance and impedance referred to the H.V. and L.V. sides.

Solution:

$$K = \frac{V_2}{V_1} = \frac{220}{1,100} = 0.2 \Rightarrow K^2 = 0.04$$

$$R_{1eq} = R_1 + R'_2 = R_1 + R_2/K^2 = 0.1 + \frac{0.006}{0.04} = 0.1 + 0.15 = 0.25\Omega$$

$$X_{1eq} = X_1 + X'_2 = R_1 + X_2/K^2 = 0.4 + \frac{0.015}{0.04} = 0.4 + 0.375 = 0.775\Omega$$

$$Z_{1eq} = \sqrt{(R_{1eq})^2 + (X_{1eq})^2} = \sqrt{(0.25)^2 + (0.775)^2} = 0.814\Omega$$

$$R_{2eq} = R_2 + R'_1 = R_2 + R_1 \times K^2 = 0.006 + (0.1 \times 0.04) = 0.01\Omega$$

$$X_{2eq} = X_2 + X'_1 = X_2 + X_1 \times K^2 = 0.015 + (0.4 \times 0.04) = 0.031\Omega$$

$$Z_{2eq} = \sqrt{(R_{2eq})^2 + (X_{2eq})^2} = \sqrt{(0.01)^2 + (0.031)^2} \cong 0.0326\Omega$$

Approximate Voltage Drop:

When the transformer is on *no-load*, then V_1 is approximately equal to E_1 . Hence $E_2 = KE_1 = KV_1$. Also, $E_2 = {}_0V_2$ where ${}_0V_2$ is secondary terminal voltage on *no-load*, hence no-load secondary terminal voltage is KV_1 . The secondary voltage on load is V_2 . The difference between the two is $I_2 Z_{02}$ as shown in Figure (16). The approximate voltage drop of the transformer *as referred to secondary* is found thus:

$$E_2 = V_2 + I_2 R_{02} + I_2 X_{02} = V_2 + I_2 (R_{02} + jX_{02}) = V_2 + I_2 Z_{02}$$

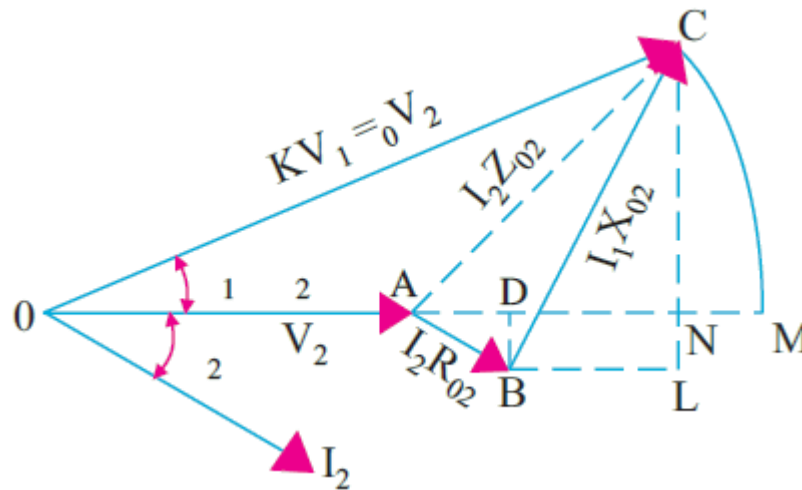


Figure (16)

With O as the centre and radius OC draw an arc cutting OA produced at M . The total voltage drop $I_2Z_{02} = AC = AM$ which is approximately equal to AN . From B draw BD perpendicular on OA produced. Draw CN perpendicular to OM and draw BL parallel to OM .

Approximate voltage drop

$$= AN = AD + DN$$

$$= I_2R_{02} \cos \Phi + I_2X_{02} \sin \Phi$$

Where, $\Phi_1 = \Phi_2 = \Phi$ (approx).

This is the value of approximate voltage drop for a *lagging* power factor.

The different figures for unity and leading power factors are shown in Figure (17) (a) and (b) respectively.

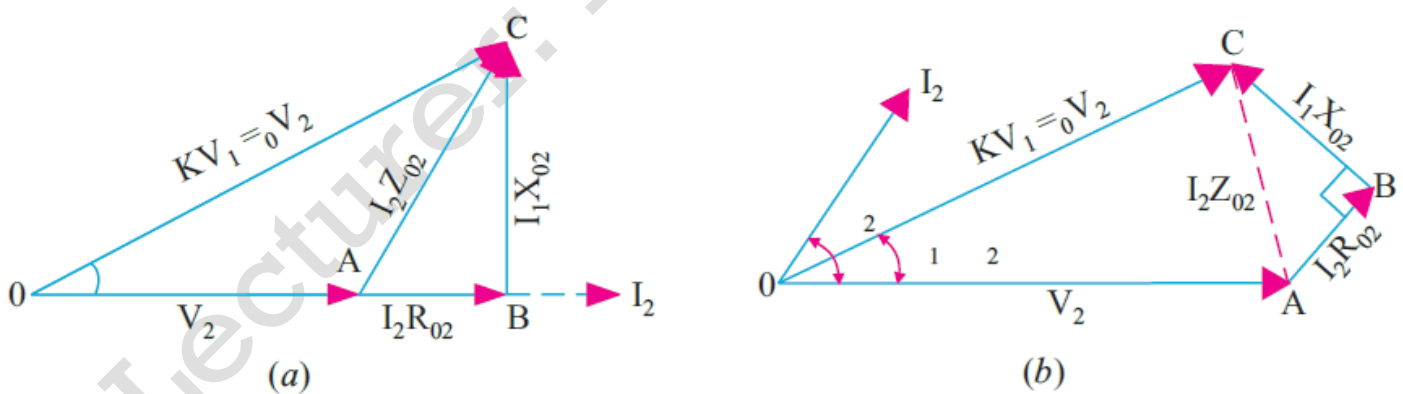


Figure (17)

The approximate voltage drop for *leading* power factor becomes

$$I_2R_{02} \cos \Phi \pm I_2X_{02} \sin \Phi$$

In general, approximate voltage drop is

$$I_2R_{02} \cos \Phi \pm I_2X_{02} \sin \Phi$$

It may be noted that approximate voltage drop as referred to primary is

$$I_1R_{01} \cos \Phi \pm I_1X_{01} \sin \Phi$$

$$\begin{aligned} \% \text{ voltage drop in secondary is} &= \frac{I_2 R_{02} \cos \Phi \pm I_2 X_{02} \sin \Phi}{{}_0V_2} \times 100 \\ &= \frac{100 \times I_2 R_{02}}{{}_0V_2} \cos \Phi \pm \frac{100 \times I_2 X_{02}}{{}_0V_2} \sin \Phi \\ &= v_r \cos \Phi \pm v_x \sin \Phi \end{aligned}$$

Where, $v_r = \frac{100 I_2 R_{02}}{{}_0V_2}$ = percentage resistive drop = $\frac{100 I_1 R_{01}}{V_1}$

Where, $v_x = \frac{100 I_2 X_{02}}{{}_0V_2}$ = percentage reactive drop = $\frac{100 I_1 X_{01}}{V_1}$

Voltage Regulation:

The voltage regulation of a transformer is the arithmetic difference (not phasor difference) between the no-load secondary voltage (${}_0V_2$) and the secondary voltage V_2 on load expressed as percentage of no-load voltage *i. e.*

$$\% \text{ age voltage regulation} = \frac{{}_0V_2 - V_2}{{}_0V_2} \times 100$$

Where, ${}_0V_2$ = No-load secondary voltage = KV_1

Where, V_2 = Secondary voltage on load

$${}_0V_2 - V_2 = I_2 R_{02} \cos \Phi_2 \pm I_2 X_{02} \sin \Phi_2$$

The + ve sign is for lagging p.f. and – ve sign for leading p.f.

Transformer Tests:

The circuit constants, efficiency and voltage regulation of a transformer can be determined by two simple tests:

(i) Open-Circuit Test ; (ii) Short-Circuit Test

(i) Open-Circuit or No-Load Test:

This test is conducted to determine:

- ♦ The iron losses (or core losses).
- ♦ Parameters R_0 and X_0 of the transformer

In this test (in [Figure \(18\)](#)), the rated voltage is applied to the primary (usually low-voltage winding) while the secondary is left open-circuited. As the normal rated voltage is applied to the primary, therefore, normal iron losses will occur in the transformer core. Cu losses in the primary under no-load condition are negligible as compared with iron losses.

- ♦ Iron losses, P_i = Wattmeter reading = W_0

- ♦ No load current = Ammeter reading = I_0
- ♦ Applied voltage = Voltmeter reading = V_1
- ♦ Input power, $W_0 = V_1 I_0 \cos \Phi_0$

No-load p.f. $\cos \Phi_0 = \frac{W_0}{V_1 I_0}$

$$I_w = I_0 \cos \Phi_0$$

$$I_m = I_0 \sin \Phi_0$$

$$R_o = \frac{V_1}{I_w}$$

$$X_0 = \frac{V_1}{I_m}$$

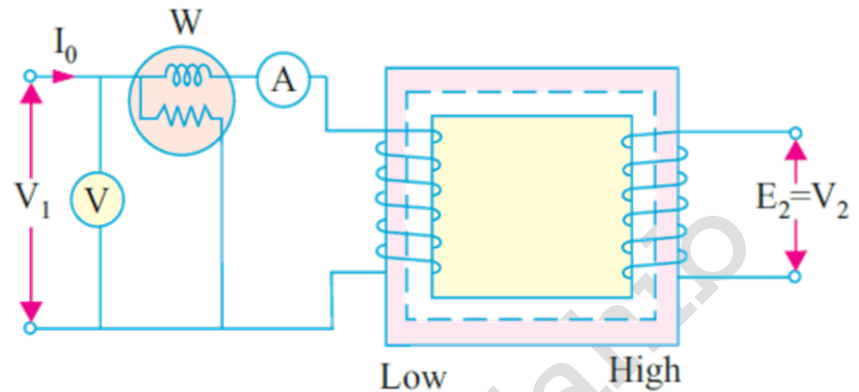


Figure (18)

(ii) Short-Circuit or Impedance Test:

This test is conducted to determine:

- ♦ Full-load copper losses of the transformer
- ♦ R_{01} (or R_{02}) ; X_{01} (or X_{02})

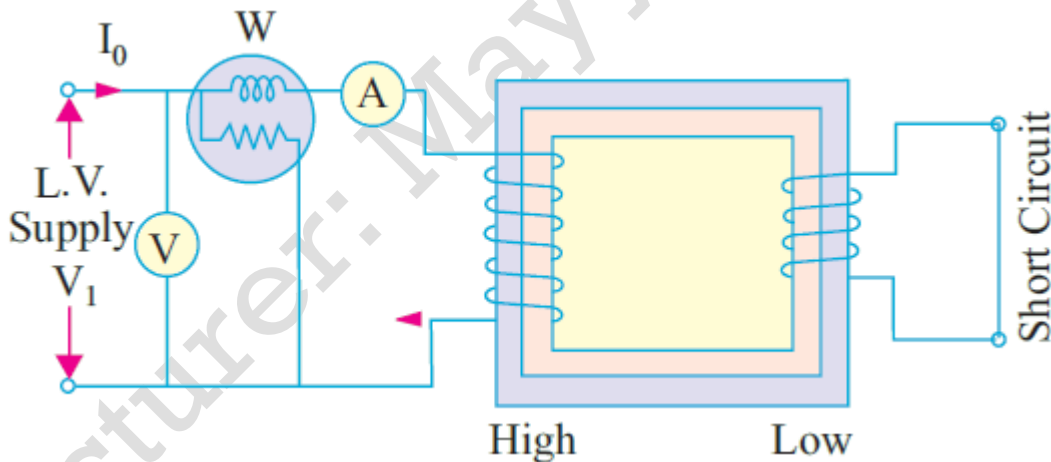


Figure (19)

In this test (in Figure (19)), the secondary (usually low-voltage winding) is short-circuited by a thick conductor and variable low voltage is applied to the primary. The low input voltage is gradually raised till at voltage V_{SC} , full-load current I_1 flows in the primary. Then I_2 in the secondary also has full-load value since $(I_1/I_2 = N_2/N_1)$. Under such conditions, the copper loss in the windings is the same as that on full load.

For the Figure (19):

- Full load Cu loss, $P_C = \text{Wattmeter reading} = W_S$
- Applied voltage = Voltmeter reading = V_{SC}
- F.L. primary current = Ammeter reading = I_1

$$P_C = I_1^2 R_1 + I_1^2 R'_2 = I_1^2 R_{01}$$

$$\therefore R_{01} = \frac{P_C}{I_1^2}$$

Where, R_{01} is the total resistance of transformer referred to primary.

$$\text{Total impedance referred to primary, } Z_{01} = \frac{V_{SC}}{I_1}$$

$$\text{Total leakage reactance referred to primary, } X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

$$\text{Short-circuit p.f., } \cos \Phi_2 = \frac{P_C}{V_{SC} I_1}$$

Example 7: Obtain the equivalent circuit of a 200/400 V, 50Hz, 1-phase transformer from the following test data:

O.C. test: 200V ; 0.7A ; 70W – on L.V. side

S.C. test: 15V ; 10A ; 85W – on H.V. side

Calculate the secondary voltage when delivering 5kW at 0.8 p.f. lagging, the primary voltage being 200V.

Solution:

From O.C. Test:

$$V_1 I_0 \cos \Phi_0 = W_0$$

$$\therefore 200 \times 0.7 \times \cos \Phi_0 = 70$$

$$\cos \Phi_0 = 0.5 \quad \text{and} \quad \sin \Phi_0 = \frac{\sqrt{3}}{2} = 0.866$$

$$I_w = I_0 \cos \Phi_0 = 0.7 \times 0.5 = 0.35\text{A}$$

$$I_\mu = I_0 \sin \Phi_0 = 0.7 \times 0.866 = 0.606\text{A}$$

$$R_0 = V_1 / I_w = \frac{200}{0.35} = 571.4\Omega$$

$$X_0 = V_1 / I_\mu = \frac{200}{0.606} \cong 330\Omega$$

As shown in Figure (20), these values refer to primary *i.e.* low-voltage side.

From S.C. Test:

It may be noted that in this test, instruments have been placed in the secondary *i.e.* high-voltage winding whereas the low-voltage winding *i.e.* primary has been short-circuited.

$$Z_{02} = V_{SC} / I_2 = \frac{15}{10} = 1.5\Omega \quad ; \quad K = \frac{400}{200} = 2$$

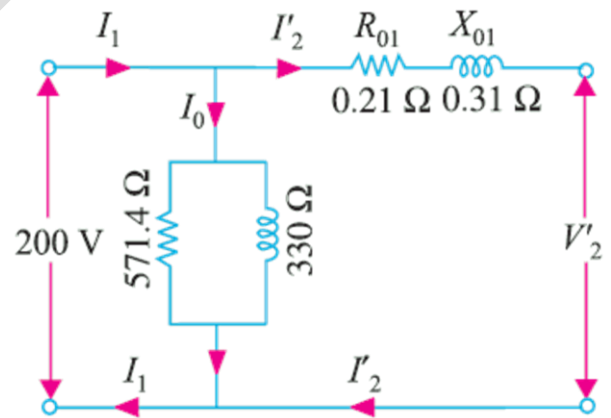


Figure (20)

$$Z_{01} = Z_{02}/K^2 = \frac{1.5}{4} = 0.375\Omega$$

Also, $I_2^2 R_{02} = W$; $R_{02} = \frac{85}{100} = 0.85\Omega$

$$R_{01} = R_{02}/K^2 = \frac{0.85}{4} \cong 0.21\Omega$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{0.375^2 - 0.21^2} = 0.31\Omega$$

Output kVA = $\frac{5}{0.8}$; Output current $I_2 = \frac{5,000}{0.8 \times 400} = 15.625\text{A}$

This value of I_2 is approximate because V_2 (which is to be calculated as yet) has been taken equal to 400V (which, in fact, is equal to E_2 or $0V_2$).

Now, $Z_{02} = 1.5\Omega$; $R_{02} = 0.85\Omega \Rightarrow \therefore X_{02} = \sqrt{1.5^2 - 0.85^2} \cong 1.24\Omega$

Total transformer drop as referred to secondary

$$= I_2(R_{02} \cos \Phi_2 + X_{02} \sin \Phi_2) = 15.6(0.85 \times 0.8 + 1.24 \times 0.6) = 22.2\text{V}$$

$\therefore V_2 = 400 - 22.2 = 377.8\text{V}$

Example 8: A 1-phase, 10kVA, 500/250 V, 50Hz transformer has the following constants:

Reactance: primary 0.2Ω ; secondary 0.5Ω

Resistance: primary 0.4Ω ; secondary 0.1Ω

Resistance of equivalent exciting circuit referred to primary, $R_0 = 1,500\Omega$

Reactance of equivalent exciting circuit referred to primary, $X_0 = 750\Omega$

What would be the reading of the instruments when the transformer is connected for the open-circuit and short-circuit tests?

Solution:

O.C. Test:

$$I_\mu = V_1/X_0 = \frac{500}{750} = \frac{2}{3}\text{A} ; I_w = V_1/R_0 = \frac{500}{1,500} = \frac{1}{3}\text{A}$$

$$\therefore I_0 = \sqrt{\left[\left(\frac{1}{3}\right)^2 + \left(\frac{2}{3}\right)^2\right]} = 0.745\text{A}$$

No-load primary input = $V_1 I_w = 500 \times \frac{1}{3} \cong 167\text{W}$

Instruments used in primary circuit are: voltmeter, ammeter and wattmeter, their readings being **500V** ; **0.745A** and **167W** respectively.

S.C. Test:

Suppose S.C. test is performed by short-circuiting the l.v. winding i.e. the secondary so that all instruments are in primary.

$$R_{01} = R_1 + (R_2/K^2)$$

Here, $K = \frac{1}{2}$, $K^2 = 0.25$

$$\therefore R_{01} = 0.4 + (0.1/0.25) = 0.4 + 0.4 = 0.8\Omega$$

Similarly, $X_{01} = X_1 + (X_2/K^2)$

$$X_{01} = 0.2 + (0.5/0.25) = 0.2 + 2 = 2.2\Omega$$

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2}$$

$$Z_{01} = \sqrt{(0.8^2 + 2.2^2)} \cong 2.341\Omega$$

Full-load primary current

$$I_1 = \frac{10,000}{500} = 20A$$

$$\therefore V_{SC} = I_1 Z_{01} = 20 \times 2.341 = 46.82V$$

$$\text{Power absorbed} = I_1^2 R_{01} = 20^2 \times 2.2 = 880W$$

Primary instruments will read: **46.82V ; 20A ; 880W**

Example 9: Consider a 20kVA, 2,200/220 V, 50Hz transformer. The *O.C./S.C.* test results are as follows:

O.C. test: 220V ; 4.2A ; 148W (*l.v.* side)

S.C. test : 86V ; 10.5A ; 360W (*h.v.* side)

Determine the regulation at 0.8 p.f. lagging and at full load. What is the p.f. on short-circuit?

Solution: It may be noted that *O.C.* data is not required in this question for finding the regulation. Since during *S.C.* test instruments have been placed on the h.v. side *i.e.* primary side.

$$\therefore Z_{01} = \frac{86}{10.5} = 8.19\Omega ; R_{01} = \frac{360}{10.5^2} \cong 3.27\Omega ; X_{01} = \sqrt{8.19^2 - 3.26^2} = 7.51\Omega$$

$$\text{F.L. primary current, } I_1 = \frac{20,000}{2,200} = 9.09A$$

$$\text{Total voltage drop as referred to primary} = I_1 (R_{01} \cos \Phi + X_{01} \sin \Phi)$$

$$= 9.09 \times (3.26 \times 0.8 + 7.51 \times 0.6) \cong 64.67V$$

$$\% \text{ age regn.} = \frac{64.67}{2,200} \times 100 \cong \mathbf{2.94\%} ; \text{ p.f. on short-circuit} = R_{01}/Z_{01} = \frac{3.26}{8.19} \cong \mathbf{0.4 \text{ lag}}$$

Losses in a Transformer:

(i) Core or Iron Loss:

$$\text{Hysteresis loss, } W_h = \eta B_{max}^{1.6} f V \text{ watt}$$

$$\text{Eddy current loss, } W_e = P B_{max}^2 f^2 t^2 \text{ watt}$$

(ii) Copper loss:

$$\text{Total Cu loss} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} = I_2^2 R_{02} \text{ watt}$$

Efficiency of a Transformer:

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Output+losses}} = \frac{\text{Output}}{\text{Output+Cu loss+Cu loss}}$$

$$\text{Or } \eta = \frac{\text{Input-Losses}}{\text{Input}} = 1 - \frac{\text{losses}}{\text{Input}}$$

Condition for Maximum Efficiency:

$$\text{Cu loss} = I_1^2 R_{01} \quad \text{or} \quad I_2^2 R_{02} = W_{cu}$$

$$\text{Iron loss} = \text{Hysteresis loss} + \text{Eddy current loss} = W_h + W_e = W_i$$

Considering primary side,

$$\text{Primary input} = V_1 I_1 \cos \Phi_1$$

$$\eta = \frac{V_1 I_1 \cos \Phi_1 - \text{losses}}{V_1 I_1 \cos \Phi_1} = \frac{V_1 I_1 \cos \Phi_1 - I_1^2 R_{01} - W_i}{V_1 I_1 \cos \Phi_1} = 1 - \frac{I_1 R_{01}}{V_1 \cos \Phi_1} - \frac{W_i}{V_1 I_1 \cos \Phi_1}$$

Differentiating both sides with respect to I_1 , we get

$$\frac{d\eta}{dI_1} = 0 - \frac{R_{01}}{V_1 \cos \Phi_1} + \frac{W_i}{V_1 I_1^2 \cos \Phi_1}$$

For η to be maximum, $\frac{d\eta}{dI_1} = 0$. Hence, the above equation becomes

$$\frac{R_{01}}{V_1 \cos \Phi_1} = \frac{W_i}{V_1 I_1^2 \cos \Phi_1} \quad \text{or} \quad W_i = I_1^2 R_{01} \quad \text{or} \quad W_i = I_2^2 R_{02}$$

Or Cu loss = Iron loss

The output current corresponding to maximum efficiency is $I_2 = \sqrt{(W_i / R_{02})}$

Load kVA corresponding to maximum efficiency, = Full load $\times \sqrt{\left(\frac{\text{Iron loss}}{\text{F.L. Cu loss}} \right)}$

The efficiency at any load is given by $\eta = \frac{x \times \text{full-load kVA} \times \text{p.f.}}{(x \times \text{full-load kVA} \times \text{p.f.}) + W_{cu} x^2 + W_i} \times 100$

Where:

x = ratio of actual to full-load in kVA

W_i = iron loss in kW

W_{cu} = Cu loss in kW

Why Transformer Rating in kVA?

As seen, Cu loss of a transformer depends on current and iron loss on voltage. Hence, total transformer loss depends on volt-ampere (VA) and not on phase angle between voltage and current *i. e.* it is independent of load power factor. That is why rating of transformers is in kVA and not in kW.

Example 10: A 600kVA, 1-phase transformer has an efficiency of 92% both at full-load and half-load at unity power factor. Determine its efficiency at 60% of full-load at 0.8 power factor lag.

Solution:

$$\eta = \frac{x \times \text{full-load kVA} \times \text{p.f.}}{(x \times \text{full-load kVA} \times \text{p.f.}) + W_{cu} + W_i} \times 100 = \frac{x \times \text{kVA} \times \cos \Phi}{(x \times \text{kVA}) \times \cos \Phi + W_i + x^2 W_{cu}} \times 100$$

Where:

x = represents percentage of full-load in kVA

W_i = iron loss in kW ; W_{cu} = Cu loss in kW

At F.L. u.p.f.: Here $x = 1$

$$\therefore 92 = \frac{1 \times 600 \times 1}{1 \times 600 \times 1 + W_i + W_{cu}} \times 100, W_i + W_{cu} \cong 52.174 \text{ kW} \quad \dots (i)$$

At half F.L. UPF: Here $x = \frac{1}{2}$

$$92 = \frac{(1/2) \times 600 \times 1}{(1/2) \times 600 \times 1 + W_i + (1/2)^2 W_{cu}} \times 100 ; W_i + 0.25 W_{cu} \cong 26.087 \text{ kW}$$

... (ii)

From (i) and (ii), we get, $W_i = 17.39 \text{ kW}$; $W_{cu} = 34.78 \text{ kW}$

60% F.L. 0.8 p.f. (lag) Here, $x = 0.6$

$$\eta = \frac{0.6 \times 600 \times 0.8}{(0.6 \times 600 \times 0.8) + 17.39 + (0.6)^2 \times 34.78} \times 100 = 90.59\%$$

Example 11: A 11,000/230 V, 150kVA, 1-phase, 50Hz transformer has core loss of 1.4kW and F.L. Cu loss of 1.6kW. Determine:

(i) The kVA load for max. efficiency and value of max. efficiency at unity p.f.

(ii) The efficiency at half F.L. 0.8 p.f. leading

Solution:

(i) Load kVA corresponding to maximum efficiency is

$$= \text{F.L kVA} \times \sqrt{\left(\frac{\text{Iron loss}}{\text{F.L. Cu loss}} \right)} = 150 \times \sqrt{\frac{1.4}{1.6}} \cong 140 \text{ kVA}$$

Since Cu loss equals iron loss at maximum efficiency,

Total loss = 1.4 + 1.4 = 2.8kW, Output = 140 × 1 = 140kW

$$\eta_{max} = \frac{140}{142.8} \cong 0.9804 \quad \text{or} \quad 98.04\%$$

(ii) Cu loss at half full-load = $1.6 \times \left(\frac{1}{2} \right)^2 = 0.4 \text{ kW}$,

Total loss = 1.4 + 0.4 = 1.8kW

Half F.L. output at 0.8 p.f. = $\left(\frac{150}{2} \right) \times 0.8 = 60 \text{ kW}$

$$\therefore \text{Efficiency} = \frac{60}{60 + 1.8} = 0.97 \quad \text{or} \quad 97.08\%$$